


To do:

- Complete HW 7 due today
- No Pre-Lab #5

Last Time: • Definition of current

$$I = \frac{dQ}{dt} \quad [I] = \frac{C}{s} = A$$


• Capacitors in Parallel

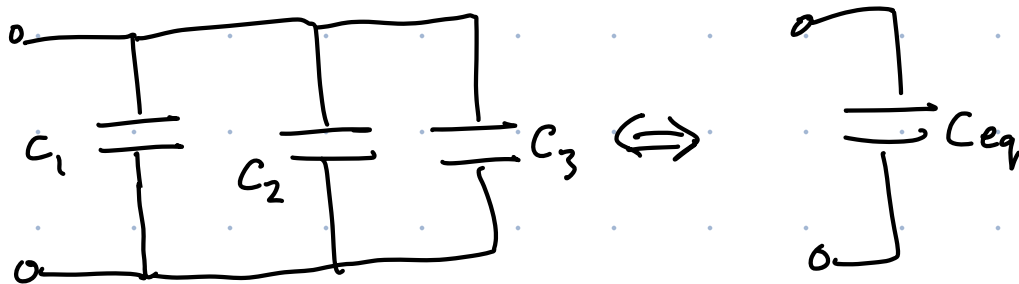

$$C_{eq} = C_1 + C_2 + C_3$$

For the parallel case, $C_{eq} > C_i \quad \forall i = 1..n$

Today: Capacitors in Series

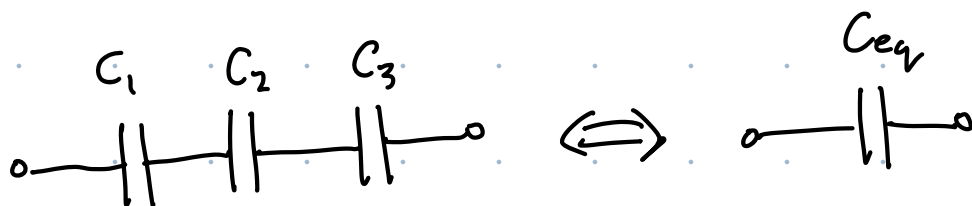


Will show that

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

For the series case, $C_{eq} < C_i \quad \forall i=1..n$

Along the way, we will also derive Kirchoff's laws for circuit analysis.

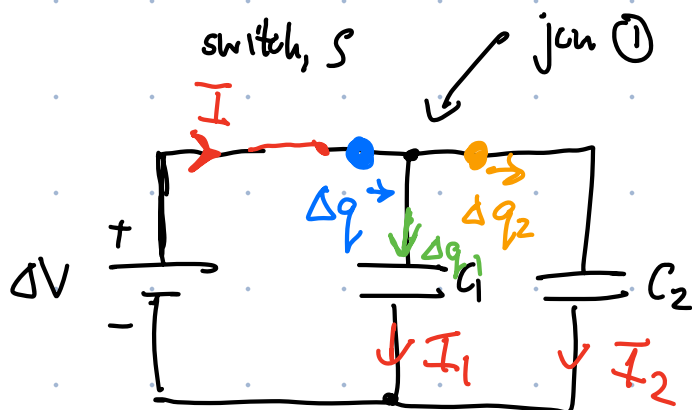Imagine a simple parallel combination of two cap. & a battery w/ a switch:



When we close the switch, get a flow of charge or a current that transports pos. charge from the btm plates to the top plates.

Suppose we close the switch and watch the charge flow into & out of the junction ① in the circuit.

In a time Δt , a packet of charge Δq approaches junction ①.

At the junction, some charge Δq_1 takes the path to C_1 & some takes the path to C_2 .

Require $\Delta q = \Delta q_1 + \Delta q_2$ because charge is neither created nor destroyed at the junction.
If these observations are made in a time Δt , then \Rightarrow Conservation of charge.

$$\frac{\Delta q}{\Delta t} = \frac{\Delta q_1}{\Delta t} + \frac{\Delta q_2}{\Delta t}$$

\Downarrow


$$I = I_1 + I_2 \quad \text{Kirchhoff's Junction Rule}$$

In general, Kirchhoff's Junction Rule:

current into a junction = current out of a junction

Second Kirchhoff Rule:

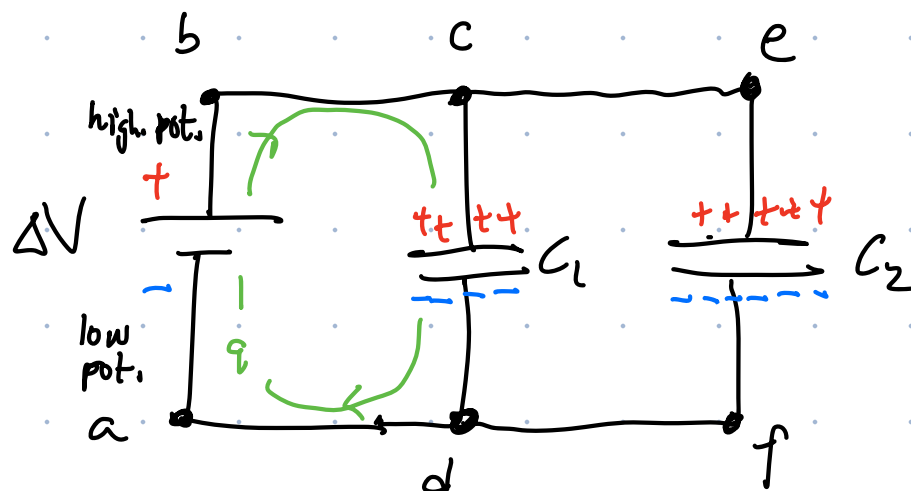Let's now imagine that our capacitors are fully charged.



Imagine taking a charge q around any closed loop in the circuit.

Consider the loop $a \rightarrow b \rightarrow c \rightarrow d \rightarrow a$

Keep track of changes in P.E.

Reminders: (1) $C = \frac{Q}{\Delta V}$ $\Delta V = \frac{Q}{C}$ (2) $\Delta U = q\Delta V$

$a \rightarrow b$, gain volt. ΔV of battery,
gain P.E. $\Delta U = +q\Delta V$

$b \rightarrow c$, here $\Delta V = 0 \therefore \Delta U = 0$

$c \rightarrow d$, cross C_1 from pos. plate to neg. plate

loss voltage $\Delta V = -\frac{Q}{C_1}$, loss P.E. $\Delta U = -q\Delta V$

$d \rightarrow a$ $\Delta V = 0$, $\Delta U = 0$

\therefore total change in P.E. around the loop is:

$$\Delta U_{\text{net}} = +q\Delta V + 0 - q\frac{Q}{C_1} + 0$$

$$= q\left(\Delta V - \frac{Q}{C_1}\right)$$


zero

$$\therefore \Delta U_{\text{net}} = 0.$$

For any closed loop in a circuit, the change in P.E. of charge q is zero.

$$\Delta U_{\text{net}} = q \Delta V_{\text{net}} = 0$$


$$\Rightarrow \Delta V_{\text{net}} = 0$$

Kirchoff Loop Rule:

Net change in voltage around any closed loop in a circuit is zero.

$$\sum_i \Delta V_i = 0$$

Capacitors in series

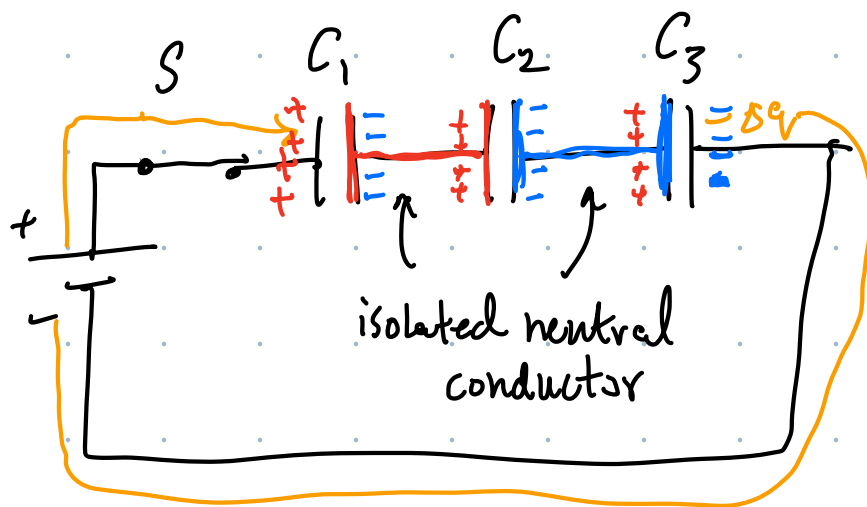

Start w/ switch open & capacitors uncharged.


The red & blue conductors always remain neutral.
Charge cannot pass through the gaps of the capacitors.

When the switch is closed battery causes charge to transfer from right plate of C_3 to left plate of C_1 .

- The neutral conductors (red & blue) become polarized (separation of of charge).

\Rightarrow Each of the series capacitors carry the same charge

$$Q_1 = Q_2 = Q_3 \equiv Q$$

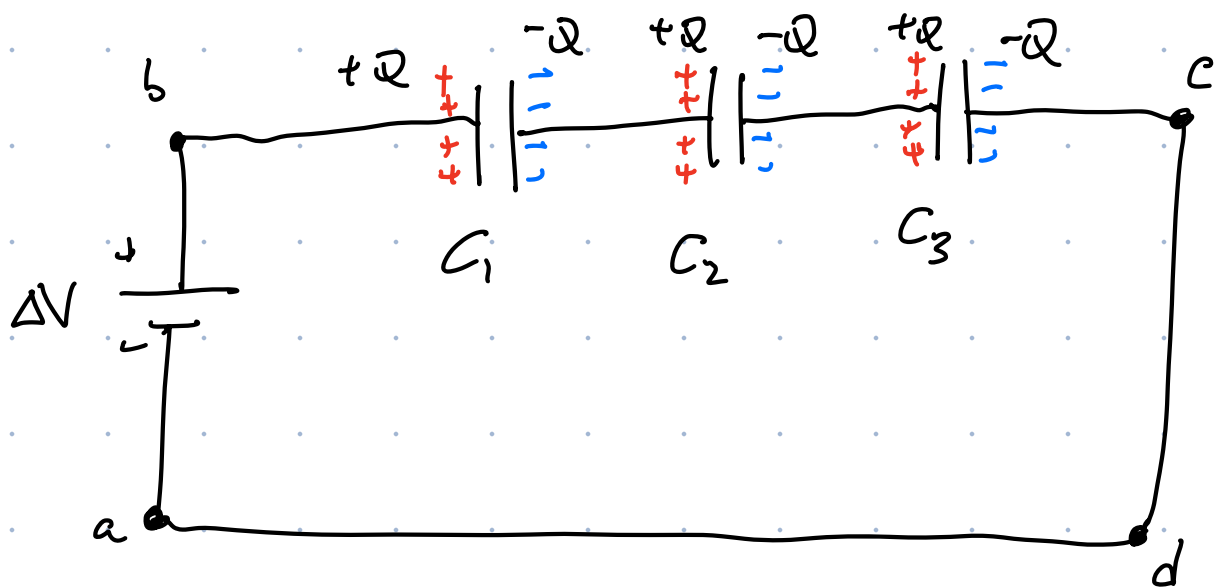

Apply the Kirchoff loop rule. $a \rightarrow b \rightarrow c \rightarrow d \rightarrow a$

$a \rightarrow b$: $+\Delta V$ (voltage of battery)

$b \rightarrow c$: $-\Delta V_{C_1} - \Delta V_{C_2} - \Delta V_{C_3}$

$c \rightarrow d$: 0


$d \rightarrow a$: 0

$$\Delta V_{\text{net}} = 0 = \Delta V - \Delta V_{C_1} - \Delta V_{C_2} - \Delta V_{C_3}$$

$$\therefore 0 = \Delta V - \frac{Q}{C_1} - \frac{Q}{C_2} - \frac{Q}{C_3}$$

$$\Delta V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \quad \textcircled{1}$$

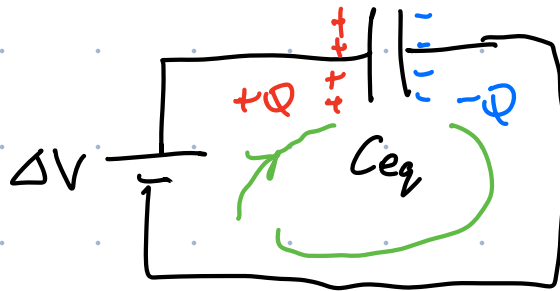Finally, want to represent the series combination as a single equiv. capacitor C_{eq} :



$$\text{loop rule: } +\Delta V - \underbrace{\Delta V_{C_{eq}}}_{\frac{Q}{C_{eq}}} = 0$$

$$\therefore \Delta V = \frac{Q}{C_{eq}} \quad (2)$$

Set (1) = (2)

$$\frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} = \frac{Q}{C_{eq}}$$

\Downarrow

$$\therefore \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

In general, for N caps. in series

$$\frac{1}{C_{eq}} = \sum_{i=1}^N \frac{1}{C_i}$$