
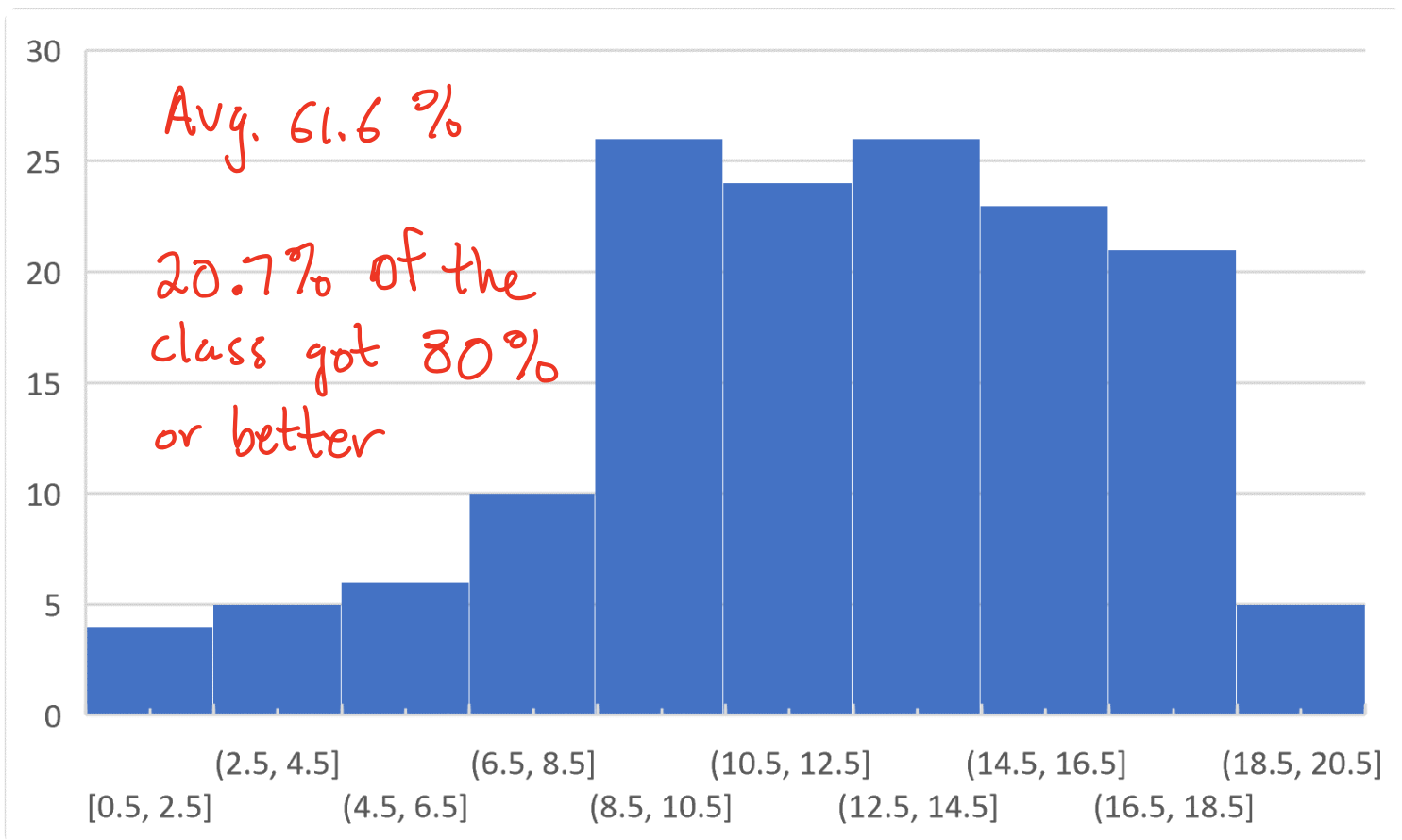


- Complete Prairie Learn HW by Friday @ 23:59
- No Pre-Lab #5
- Tutorials resume this week.

Midterm dist'n

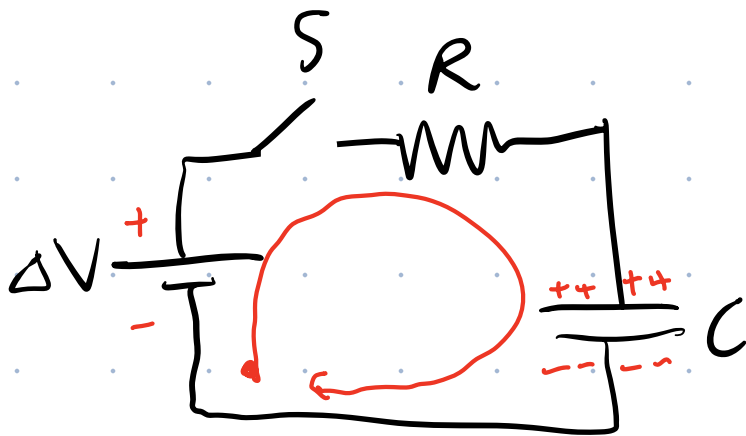

Today: Charging a capacitor using an RC circuit.



$$C = \frac{Q}{\Delta V_C}$$

$$\Delta V_C = \frac{Q}{C}$$

Loop Rule: Change in voltage around a closed loop is zero.

$$\Delta V_{\text{net}} = 0 = \underset{\substack{\uparrow \\ \text{battery}}}{\Delta V} - \underset{\substack{\uparrow \\ \text{resistor}}}{\Delta V_R} - \underset{\substack{\uparrow \\ \text{capacitor}}}{\Delta V_C}$$

$$0 = \Delta V - IR - \frac{Q}{C} \quad \textcircled{0}$$

Solve $\textcircled{0}$ for current I

$$I = \frac{\Delta V}{R} - \frac{Q}{RC}$$

define some constants: $I_0 = \frac{\Delta V}{R}$ $\left. \begin{array}{l} \text{current @ } t=0 \\ \text{when cap is uncharged} \end{array} \right\}$

tan: $\tau = RC$ } time constant.

$\therefore$ Current at any time in our RC circuit is given by:

$$I = I_0 - \frac{Q}{\tau} \quad (1)$$

Since $I = \frac{\Delta Q}{\Delta t}$, we calc how much charge

is added to cap. in time Δt using:

$$\Delta Q = I \Delta t \quad (2)$$

After finding ΔQ , know that the new charge on the cap is the original value of Q plus ΔQ .

$$Q \rightarrow Q + \Delta Q$$

Likewise:

$$t \rightarrow t + \Delta t$$

Strategy:

- Start w/ known values of ΔV , R , $C \Rightarrow$ const.
- Pick a value for the time interval Δt .
- Calc. $I_0 = \frac{\Delta V}{R}$ $\tau = RC$

Start w/ $Q = 0$ @ $t = 0$

1. Use Eq. ① to find I
2. Use Eq. ② to find ΔQ
3. Update value of $Q \Rightarrow Q + \Delta Q$
4. Update value of $t \Rightarrow t + \Delta t$
5. Return to step 1 & iterate until Q reaches a stable value (equilibrium).

See course website for an example implementation.

For fun, let's see how to calc. Q & I exactly (won't test).

Start w/ Eq. ①

$$I = I_0 - \frac{Q}{\tau} \quad \text{①}$$

$$I = \frac{dQ}{dt} \quad (\text{instantaneous current})$$

$$\therefore \frac{dQ}{dt} = I_0 - \frac{Q}{\tau}$$

differential equation
for the charge Q .
Want to solve for
 $Q(t)$.

- Multiply by dt .

$$dQ = \left(I_0 - \frac{Q}{\tau} \right) dt$$

- Divide by $\left(I_0 - \frac{Q}{\tau} \right)$

$$\frac{dQ}{I_0 - \frac{Q}{\tau}} = dt$$

- Integrate both sides

$$\int_{Q=0}^Q \frac{dQ}{I_0 - \frac{Q}{\tau}} = \int_{t=0}^t dt$$

- make the substitution $u = I_0 - \frac{Q}{\tau}$

$$du = -\frac{dQ}{\tau} \Rightarrow dQ = \underline{-\tau du}$$

when $Q=0$, $u = I_0$

$Q=Q$, $u = I_0 - \frac{Q}{\tau}$

$$\int_{u=I_0}^{I_0 - \frac{Q}{\tau}} \frac{-\tau du}{u} = t \Big|_0^t = t$$

$$\therefore -\tau \int_{u=I_0}^{I_0 - Q/\tau} \frac{du}{u} = t$$

$\ln u$

divide
by $-\tau$

$$-\tau \ln u \Big|_{I_0}^{I_0 - \frac{Q}{\tau}} = t$$

$$\ln u \Big|_{I_0}^{I_0 - \frac{Q}{\tau}} = -\frac{t}{\tau}$$

$$\therefore \ln \left(I_0 - \frac{Q}{\tau} \right) - \ln I_0 = -\frac{t}{\tau}$$

use $\ln A - \ln B = \ln \left(\frac{A}{B} \right)$

$$\ln \left(\frac{I_0 - Q/\tau}{I_0} \right) = -\frac{t}{\tau}$$

Take exponential of both sides & solve for Q .

$$\frac{I_0 - \frac{Q}{\tau}}{I_0} = e^{-t/\tau}$$

$$\frac{1 - \frac{Q}{I_0 \tau}}{1} = e^{-t/\tau}$$

$$\frac{Q}{I_0 \tau} = 1 - e^{-t/\tau}$$

$$\therefore Q = I_0 \tau (1 - e^{-t/\tau})$$


$$\text{sub in } I_0 = \frac{\Delta V}{R}, \tau = RC$$

$$\therefore I_0 \tau = C \Delta V$$

$$Q = C \Delta V (1 - e^{-t/\tau})$$

Charge on Cap
vs t , when switch
is closed @ $t=0$.

3

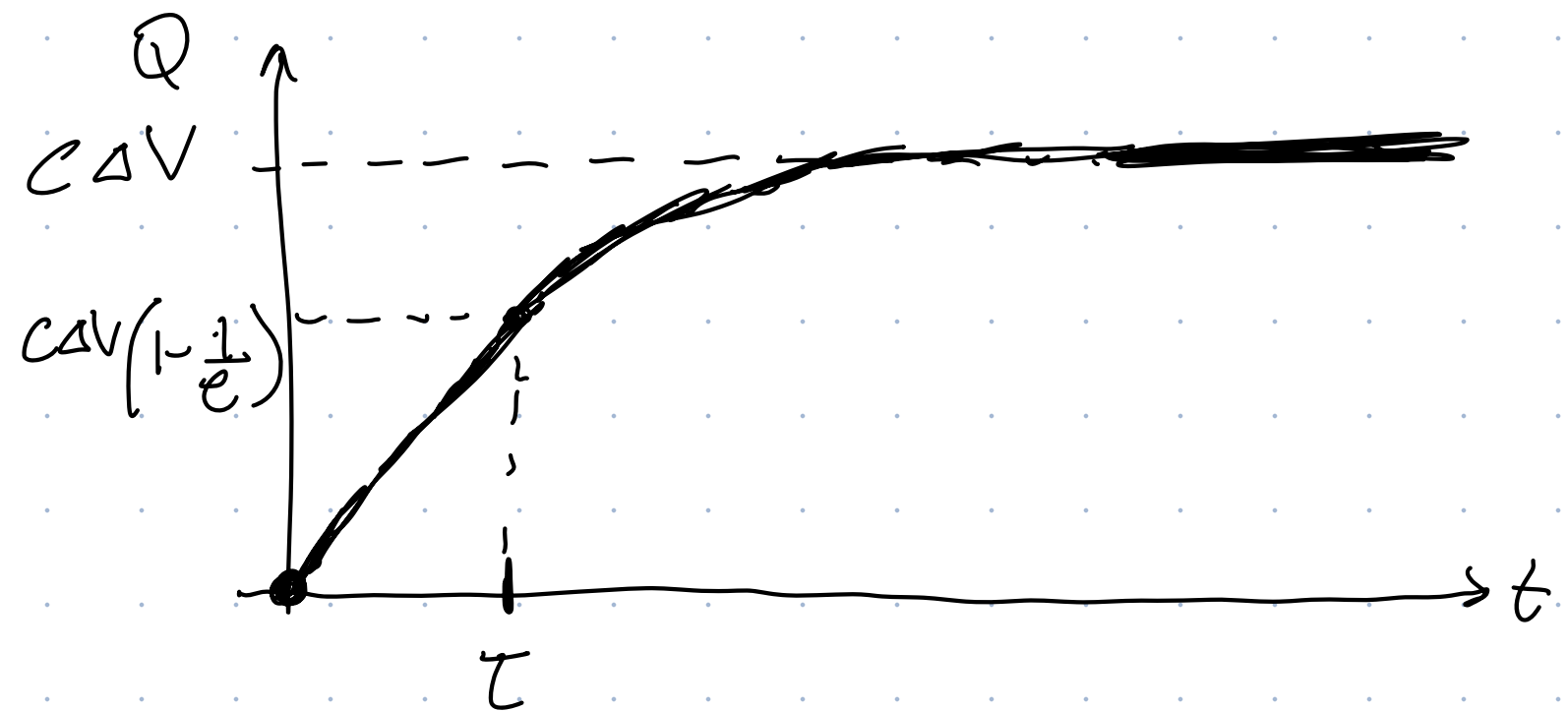

Can use Eq. (3) to calc. the current:

$$I = \frac{dQ}{dt} = \frac{d}{dt} \left[C\Delta V (1 - e^{-t/\tau}) \right]$$

$$= C\Delta V \left[\cancel{\frac{d}{dt}(1)} - \frac{d}{dt}(e^{-t/\tau}) \right]$$

$$= C\Delta V \left[-(-\frac{1}{\tau}) e^{-t/\tau} \right]$$

$$= C \frac{\Delta V}{\tau} e^{-t/\tau} \quad \text{but } \tau = RC$$

$$\therefore I(t) = \frac{\Delta V}{R} e^{-t/\tau}$$

