

- Complete Prairie Learn HW by 23:59 today
- Complete Pre-Lab #6 before the start of your lab.

Last Time: $I = env_d A$
 $J = \frac{I}{A} = env_d$

Ohmic materials obey: $J = \sigma E$
 $\Downarrow$
 $\Delta V = IR$


where $R = \rho \frac{l}{A} = \frac{1}{\sigma} \frac{l}{A}$

Today: When is ΔV across a resistor positive & when is it negative?

Rule of Thumb: - If you cross a resistor in the dir'n of the current I , the voltage change is negative.

- If you cross a resistor in opp dir'n of current I , the voltage change is positive.

CASE 1

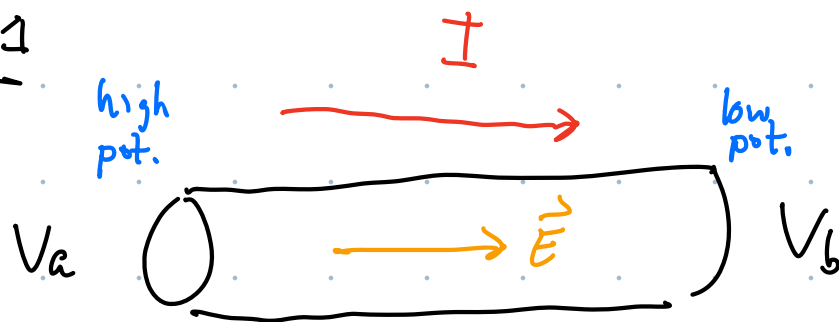

cross resistor in dir'n of $I \rightarrow$

Track changes in voltage.

$$V_a + \underbrace{\Delta V_R}_{\text{change in voltage across resistor}} = V_b$$

change in
voltage across
resistor

$$\therefore \Delta V_R = \overset{\text{low pot.}}{V_b} - \overset{\text{high pot.}}{V_a} < 0$$

$\therefore$ when cross R
in dir'n of I

$$\Delta V_R = -IR$$

CASE 2 Cross R antiparallel to I



cross R in opp. dir'n of $I \rightarrow$

$$V_a + \Delta V_R = V_b$$

$$\therefore \Delta V_R = \overset{\text{high pot.}}{V_b} - \overset{\text{low pot.}}{V_a} < 0$$

When cross R
antiparallel to I
 $\Delta V_R = +IR$


Power Dissipated by a Resistor (OSUP v2 sec. 9.5)

Recall that power is defined as:

$$P = \frac{\text{change in energy}}{\text{time interval}}$$

$$[P] = \frac{\text{J}}{\text{s}} \equiv \text{W} \quad (1 \text{ Watt})$$

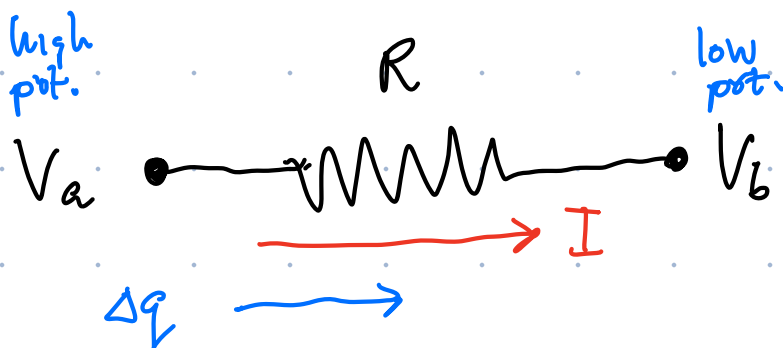Consider an amount of charge $\Delta q > 0$ that crosses a resistor R in time Δt .



The charge Δq loses pot./voltage ΔV_R when it crosses the resistor.

The corresponding loss of P.E. of the charge is

$$\Delta U = \Delta q \Delta V_R$$

If time to cross R is Δt , then the dissipated power is:

$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta q \Delta V_R}{\Delta t} = \underbrace{\left(\frac{\Delta q}{\Delta t} \right)}_I \Delta V_R$$

$\therefore$ Power dissipated by a resistor is:

$$P = I \Delta V_R$$

know $\Delta V_R = \underline{IR}$ $\Rightarrow P = I^2 R$


alternatively, $I = \frac{\Delta V_R}{R} \Rightarrow P = \frac{(\Delta V_R)^2}{R}$

The power dissipated by a resistor is given by:

$$P = I \Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

The dissipated power is converted to heat/
thermal energy.

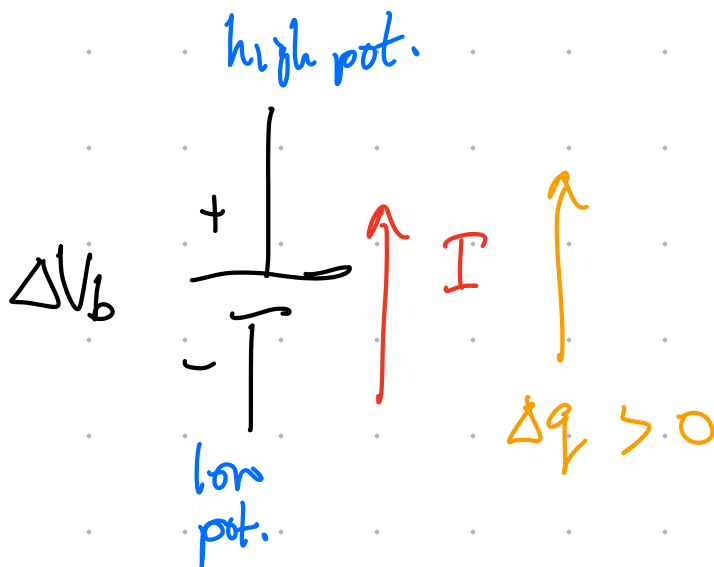In a similar way, we can determine the
power supplied by a voltage source, such as
a battery.



If $\Delta q > 0$ crosses
battery from the
neg. to pos. terminal
in time Δt ,

Change in energy is: $\Delta U = \Delta q \Delta V_b$


Power supplied is: $P = \frac{\Delta U}{\Delta t} = \left(\frac{\Delta q}{\Delta t} \right) \Delta V_b$

$$P = I \Delta V_b$$

In a circuit consisting of only batteries and resistors, the total power supplied by all batteries exactly balances the total power dissipated by all resistors.

Eg. The nichrome wire in a toaster has a resistance of 24Ω . If the outlet in the wall supplies $120V$, find:

(a) current in the toaster.

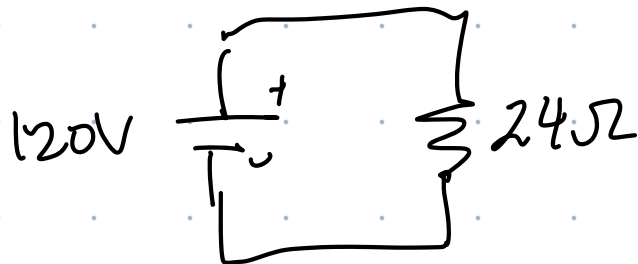

$$I = \frac{120V}{24\Omega} = 5A.$$

(b) Power dissipated by resistor (nichrome wire)

$$P = I^2 R = (5A)^2 24\Omega = 600W$$


(c) Power supplied by outlet

same.
conservation
of energy.


$$P = I \Delta V = (5A)(120V) = 600W$$

Combinations of Resistors (OSUP, 2 sec. 10.2)

Series

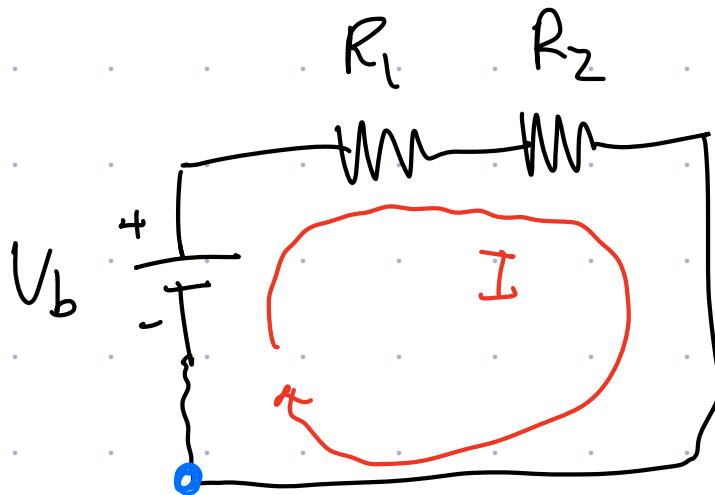

(A)

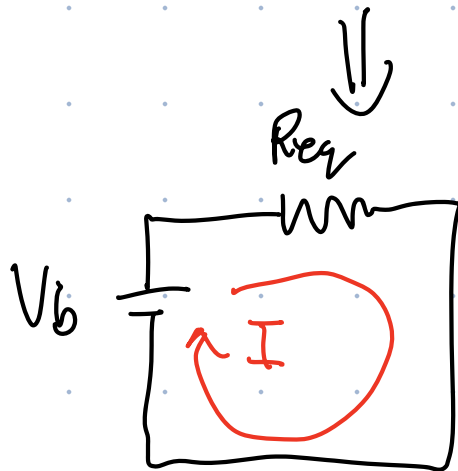

(B)

require current in both circuits to be the same when driven by the same battery

Do Kirchhoff loop rule for both circuits

$$\sum_{\text{closed loop}} \Delta V_i = 0$$

$$\textcircled{A} \quad +V_b - IR_1 - IR_2 = 0$$

$$\therefore V_b = I(R_1 + R_2) \quad \textcircled{i}$$

$$\textcircled{B} \quad +V_b - IR_{eq} = 0$$

$$\therefore V_b = IR_{eq} \quad \textcircled{ii}$$

$$\textcircled{i} = \textcircled{ii}$$



$$\Rightarrow \cancel{I(R_1 + R_2)} = \cancel{IR_{eq}}$$

$$\therefore R_{eq} = R_1 + R_2$$

In general, for N resistors in series

$$R_{eq} = \sum_{i=1}^N R_i$$

Resistors in Parallel

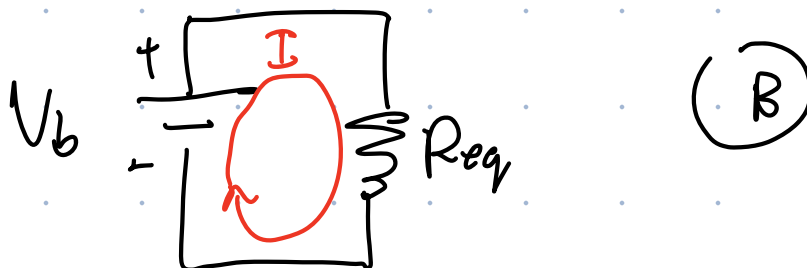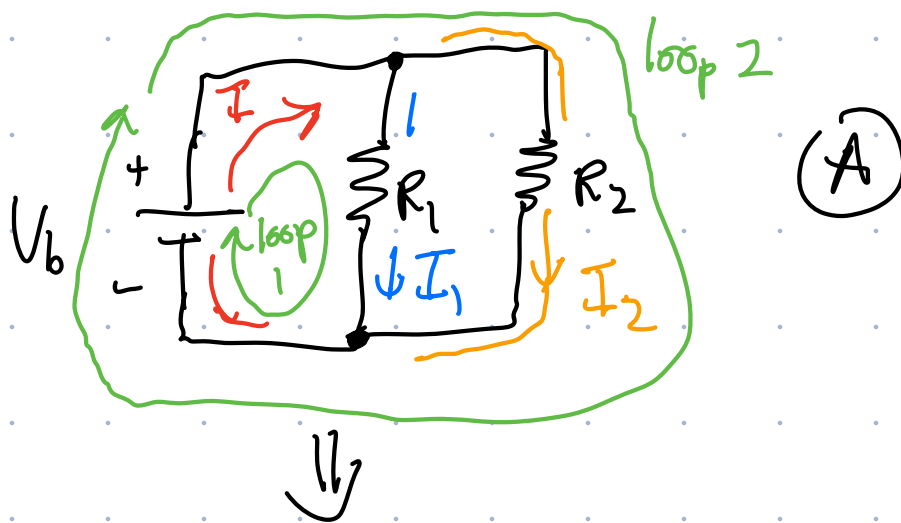

Analysis of (A)

By the gen rule (current in = current out)

$$I = I_1 + I_2$$

loop 1: Track changes in voltage.

$$+V_b - \Delta V_{R_1} = 0 \Rightarrow \Delta V_{R_1} = V_b$$

loop 2: $+V_b - \Delta V_{R_2} = 0 \Rightarrow \Delta V_{R_2} = V_b$

$\therefore$ Battery, R_1 , R_2 all have the same voltage difference V_b .

$$\begin{aligned} I &= I_1 + I_2 \\ &= \frac{\Delta V_{R_1}}{R_1} + \frac{\Delta V_{R_2}}{R_2} = \frac{V_b}{R_1} + \frac{V_b}{R_2} \end{aligned}$$

$$\therefore I = V_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \quad (i')$$

Analysis of (B) $I = \frac{V_b}{R_{eq}}$ (ii')

Require (i') = (ii')

$$\therefore \cancel{V_b} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \cancel{V_b} \frac{1}{R_{eq}}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

In general, for N resistors in parallel,

$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i}$$