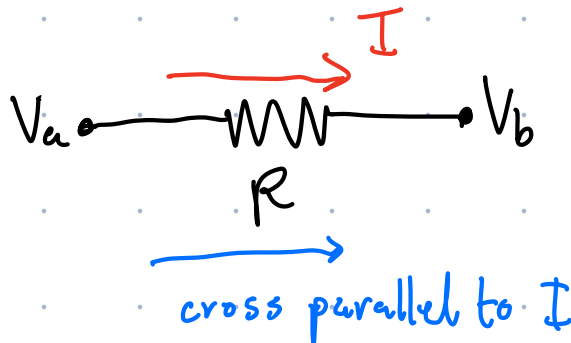



- Complete Prairie Learn Hw by 23:59 on March 14.
- Complete Pre-Lab #6 before the start of your lab.
- Quiz #2 will be March 19. See the course website for details / formula sheet.

Cut off for Quiz #2 : Up to § including the material from the March 7 class.

Last Time:




$$\Delta V_R = V_b - V_a = -IR$$

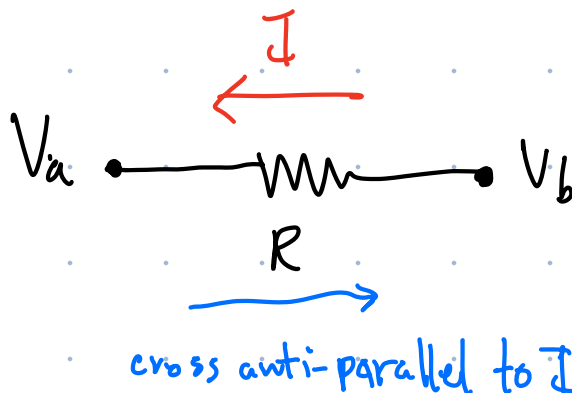

$$\Delta V_R = V_b - V_a = +IR$$

Previously : Kirchhoff Laws


1. Junction Rule

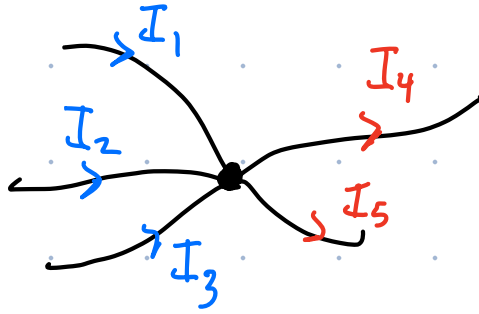

Conservation of charge :

current into jcn
= current out of jcn

2. Loop Rule

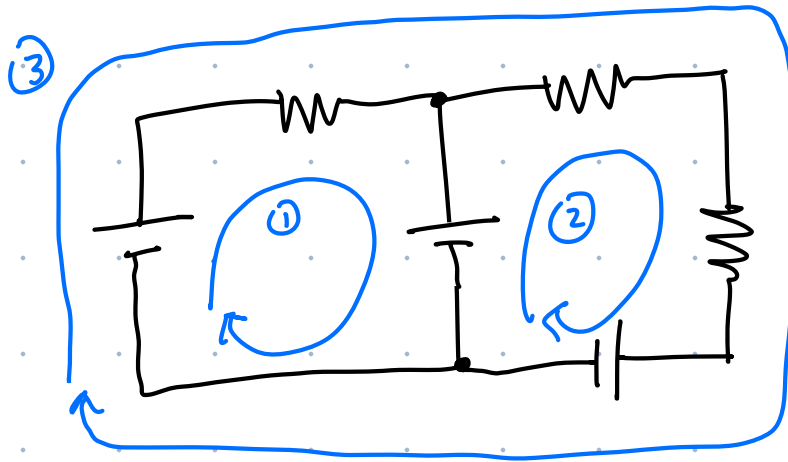


Conservation of energy:

Net change in voltage around any closed loop in a circuit is zero.

$$\sum_{\text{loop}} \Delta V_i = 0$$

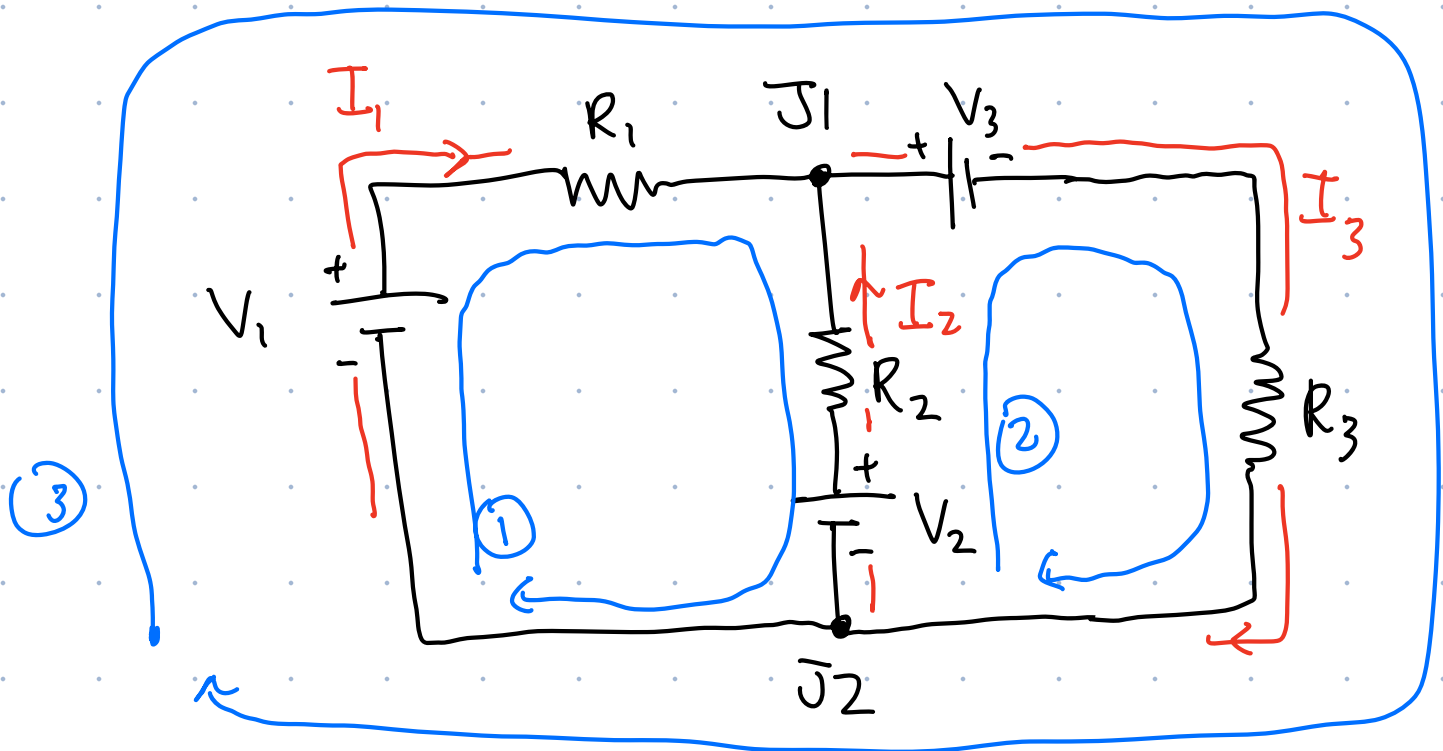Ex. Consider the following circuit consisting of batteries and resistors



Typically in a circuit like this, we will have some unknowns to solve for (currents, battery voltages, resistor values).

Step up a system of N eqns to solve for N unknowns.

Ex. In the circuit above find the current in each branch of the circuit (current in each resistor).

Step 1: Assign a current to each branch of the circuit. Label the currents & pick a dir'n.

If at the end of the calc. we find a negative value for a current, it just means that we chose the wrong dir'n. The value of the current (assuming no mistakes) will be correct.

Step 2: Identify the unknowns.

In this example, assume battery voltages & resistor values are given.

Unknowns are: I_1, I_2, I_3 .

To solve for the 3 unknowns, need to construct a system of 3 indep. equations involving the 3 unknowns.

Step 3: Apply the junction to start building our system of eq'ns.

Eg. J1: $I_{in} = I_{out}$

$$I_1 + I_2 = I_3$$

(a)

J2: $I_3 = I_1 + I_2$ } same expression obtained from J1.

→ no new info.

Step 4: Use the loop rule to find the other two required eq'ns.

Loop ①: $0 = +V_1 - \underbrace{I_1 R_1}_{\text{neg-to-pos}} + \underbrace{I_2 R_2}_{\substack{\text{anti-parallel} \\ \text{to } I_2}} - V_2$ parallel to I_1

Loop ②: $0 = +V_2 - I_2 R_2 - V_3 - I_3 R_3$

Loop ③: $0 = +V_1 - I_1 R_1 - V_3 - I_3 R_3$

3 loop Eqns. Notice that there are only 2 indep. eq'ns.

Consider (loop ①) + (loop 2)

$$= (V_1 - I_1 R_1 + \cancel{I_2 R_2} - \cancel{V_2}) \\ + (\cancel{V_2} - \cancel{I_2 R_2} - V_3 - I_3 R_3)$$

$$= V_1 - I_1 R_1 - V_3 - I_3 R_3 = \text{loop } \textcircled{3}$$

Since we can construct the 3rd eqn using the first two, only have two indep. loop eqns.

Step 5: Finalize system of 3 eqns

→ use one jcn rule

→ any two of the loop rules.

For our current example:

$$I_1 + I_2 = I_3 \quad \textcircled{a}$$

$$V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0 \quad \textcircled{b} \rightarrow \text{loop } \textcircled{1}$$

$$V_2 - I_2 R_2 - V_3 - I_3 R_3 = 0 \quad \textcircled{c} \rightarrow \text{loop } \textcircled{2}$$

Step 6: Solve the system of 3 eqns for the 3 unknowns (just a math problem)

Eg. Take the circuit drawn above and assume

$$\begin{array}{ll} V_1 = V_0 & R_1 = R_0 \\ V_2 = 2V_0 & R_2 = 2R_0 \\ V_3 = 3V_0 & R_3 = R_0 \end{array}$$

System of 3 eqns becomes:

$$I_1 + I_2 = I_3 \quad (a)$$

$$V_0 - I_1 R_0 + 2I_2 R_0 - 2V_0 = 0$$

$$-V_0 - I_1 R_0 + 2I_2 R_0 = 0$$

$$\therefore -\frac{V_0}{R_0} - I_1 + 2I_2 = 0 \quad (b)$$

$$V_2 - I_2 R_2 - V_3 - I_3 R_3 = 0$$

$$2V_0 - 2I_2 R_0 - 3V_0 - I_3 R_0 = 0$$

$$-V_0 - 2I_2 R_0 - I_3 R_0 = 0$$

$$\therefore -\frac{V_0}{R_0} - 2I_2 - I_3 = 0 \quad (c)$$

To solve for the unknowns, start by using two of the eq'ns to eliminate one of the unknowns.

Sub (a) into (c) to eliminate I_3

$$-\frac{V_0}{R_0} - 2I_2 - (I_1 + I_2) = 0$$

$$\therefore -\frac{V_0}{R_0} - I_1 - 3I_2 = 0 \quad \text{(d)}$$

Now, eq'ns (b) & (d) form a system of two eq'ns & two unknowns.

Take (b) - (d) to eliminate I_1

$$\left(-\cancel{\frac{V_0}{R_0}} - \cancel{I_1} + 2I_2 \right) - \left(-\cancel{\frac{V_0}{R_0}} - \cancel{I_1} - 3I_2 \right) = 0$$

$$\therefore 2I_2 + 3I_2 = 0$$

$$\therefore 5I_2 = 0 \Rightarrow I_2 = 0$$

Sub known value of I_2 into (b) or (d)
to find I_1

(b)
$$-\frac{V_0}{R_0} - I_1 + \cancel{2(0)} = 0$$



$$\therefore I_1 = -\frac{V_0}{R_0}$$

neg., so in opp dir'n
as drawn.

Sub known values of I_1 & I_2 into (a)
to find I_3

$$I_1 + I_2 = I_3$$

$$-\frac{V_0}{R_0} + 0 = I_3$$

$$\therefore I_3 = -\frac{V_0}{R_0}$$

in dir'n opp. to
what was drawn.