PHYSICS		121	
March	10,	2020	

Tutorial #7 – quiz

Name:	
Student Number:	

(2^{pts}) 1.

Rank in order, from largest to smallest, the three currents I_1 to I_3 .

_		-			
0	r	а	A	r	٠
$\mathbf{\circ}$	T	u	·	1	

+	$I_1 \downarrow R_1 = 3R$
<u>-</u> =	$R_2 = R $