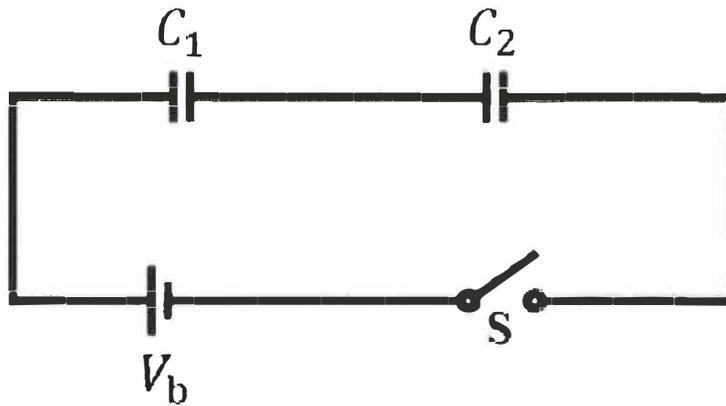


Series Capacitors

A pair of capacitors $C_1 = 38.0 \mu\text{F}$ and $C_2 = 28.0 \mu\text{F}$ are connected to a battery $V_b = 60.0 \text{ V}$ and a switch. The capacitors are initially uncharged. After the switch has been closed and the capacitors are fully charged, what is the ratio Q_2/Q_1 of the charges on the capacitors, where Q_1 is the charge on C_1 and Q_2 is the charge on C_2 ?




- (a) 0.543
- (b) 1.36
- (c) 0.737
- (d) 1.84
- (e) 1

For capacitors in series $Q_1 = Q_2$.

$$\frac{Q_2}{Q_1} = 1$$

Series Capacitors Voltage

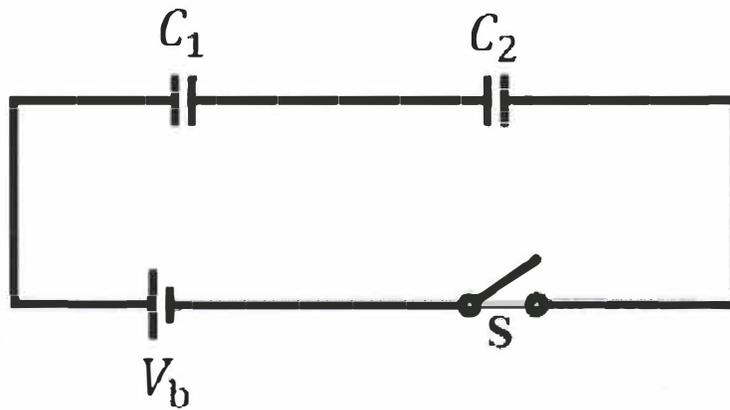A pair of capacitors $C_1 = 20.0 \mu\text{F}$ and $C_2 = 15.0 \mu\text{F}$ are connected to a battery $V_b = 60.0 \text{ V}$ and a switch S . The capacitors are initially uncharged. After the switch has been closed and the capacitors are fully charged, what is the ratio V_2/V_1 of the voltages across the capacitors, where V_1 is the voltage across C_1 and V_2 is the voltage across C_2 ?



- (a) 1.33
- (b) 1
- (c) 0.562
- (d) 0.75
- (e) 1.78


$$C = \frac{Q}{V} \quad \therefore \quad V = \frac{Q}{C}$$

$$\frac{V_2}{V_1} = \frac{Q_2/C_2}{Q_1/C_1} \quad \text{since } Q_2 = Q_1$$


$$\frac{V_2}{V_1} = \frac{C_1}{C_2} = \frac{20}{15} = \frac{4}{3} = 1.33$$

Resistor Circuit

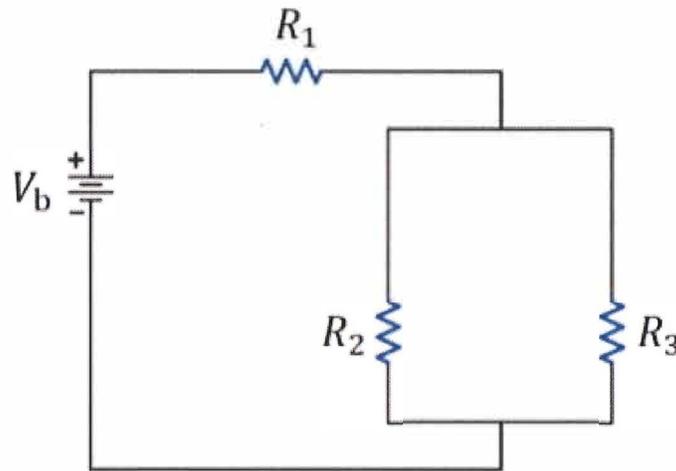Consider the circuit below with $V_b = 5.40 \text{ V}$, $R_1 = 150 \Omega$, $R_2 = 185 \Omega$ and $R_3 = 230 \Omega$. Find the voltage across R_2 .



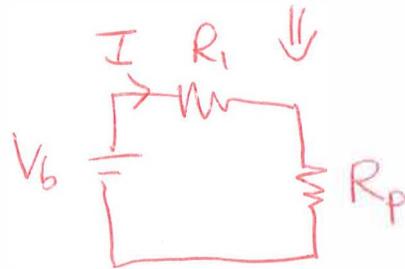- (a) 3.96 V
- (b) 4.92 V
- (c) 3.21 V
- (d) 2.19 V
- (e) 5.4 V



$$R_p = \frac{R_2 R_3}{R_2 + R_3} = 102.5 \Omega$$


$$I = \frac{V_b}{R_1 + R_p} = \frac{5.4 \text{ V}}{150 \Omega + 102.5 \Omega} = 0.0214 \text{ A}$$

$$V_2 = V_b - IR_1 = \boxed{2.19 \text{ V}}$$

$$\underline{\underline{2.19}} \quad V_2 = IR_p = \boxed{2.19 \text{ V}}$$


Wire Loop

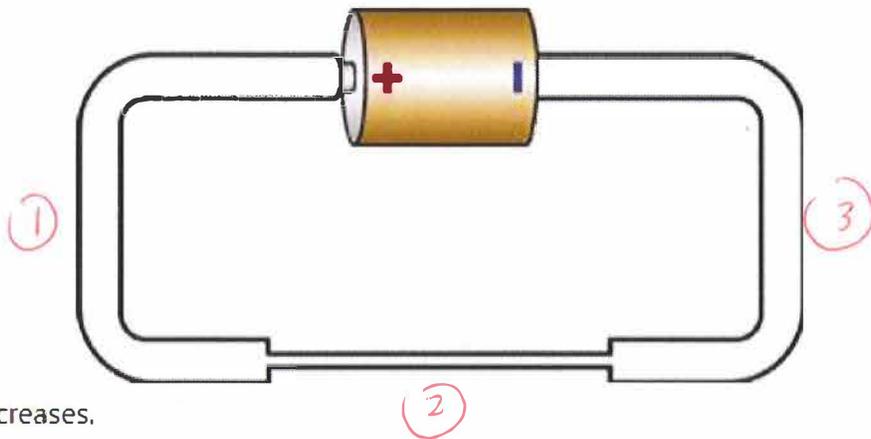The circuit below consists of a battery and a tungsten wire. As shown in the figure, the tungsten wire has a thin (small radius) section in the middle. What happens to the current as it moves from the thick section of the wire to the thin section?



- (a) The current decreases.
- (b) The current is zero.
- (c) The current increases.
- (d) The current is unchanged.
- (e) More information is needed.


like series resistors

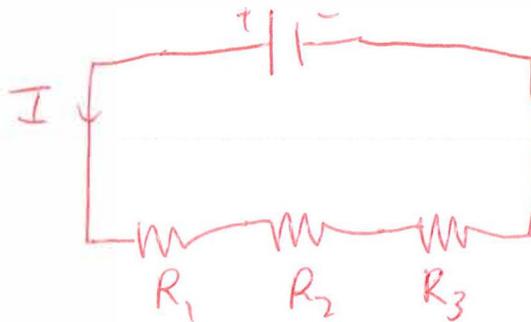

*current I is same
in all resistors.*

Drift velocity

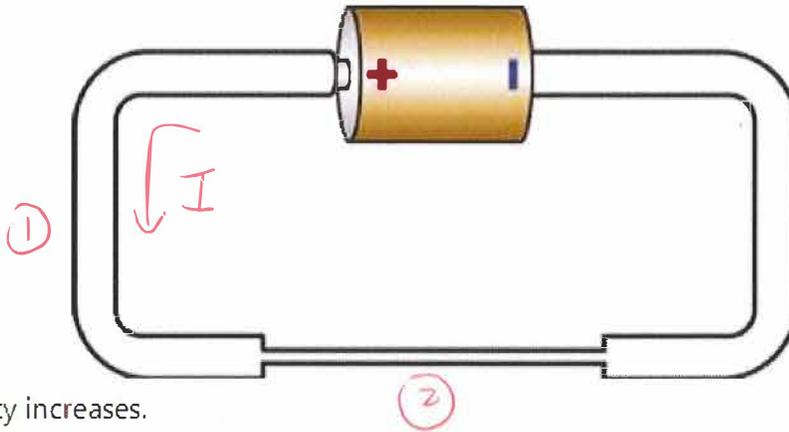The circuit below consists of a battery and a tungsten wire. As shown in the figure, the tungsten wire has a thin (small radius) section in the middle. As charges move from the thick section of wire to the thin section, what happens to the drift velocity?



- (a) The drift velocity increases.
- (b) The drift velocity decreases.
- (c) The drift velocity is unchanged.
- (d) The drift velocity is zero.
- (e) More information is needed.

$$\text{know } I_1 = I_2$$

$$I = qnvdA$$

$$\therefore \frac{I_1}{I_2} = \frac{qn_1 v_{d1} A_1}{qn_2 v_{d2} A_2}$$

$$\text{but } I_1 = I_2$$

$$\therefore \frac{v_{d2}}{v_{d1}} = \frac{A_1}{A_2}$$


$$A_2 < A_1$$

$$\therefore v_{d2} > v_{d1}$$

The drift speed increases as I goes from thick to thin section of wire.

Equivalent capacitance

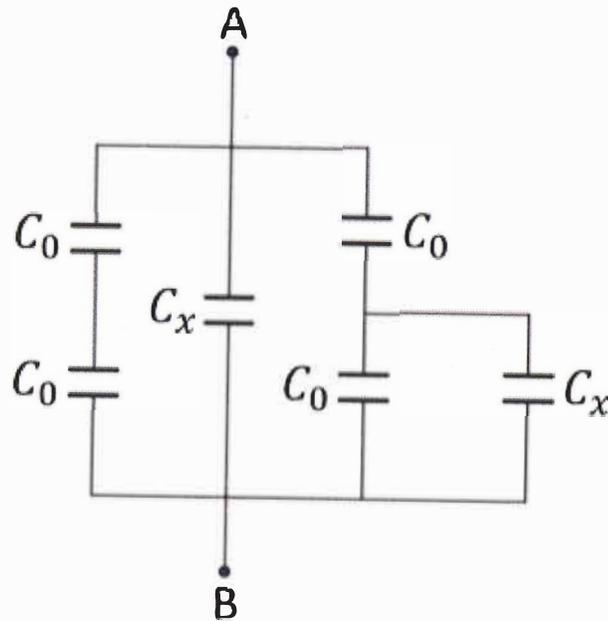If $C_x = 1.6C_0$, find the equivalent capacitance between the circuit nodes A and B.




- (a) $1.6C_0$
- (b) $2.6C_0$
- (c) $0.5C_0$
- (d) $2.82C_0$
- (e) $0.722C_0$


$$\frac{1}{C_{eq1}} = \frac{1}{C_0} + \frac{1}{C_0}$$

$$= \frac{2}{C_0}$$

$$\therefore C_{eq1} = \frac{C_0}{2}$$

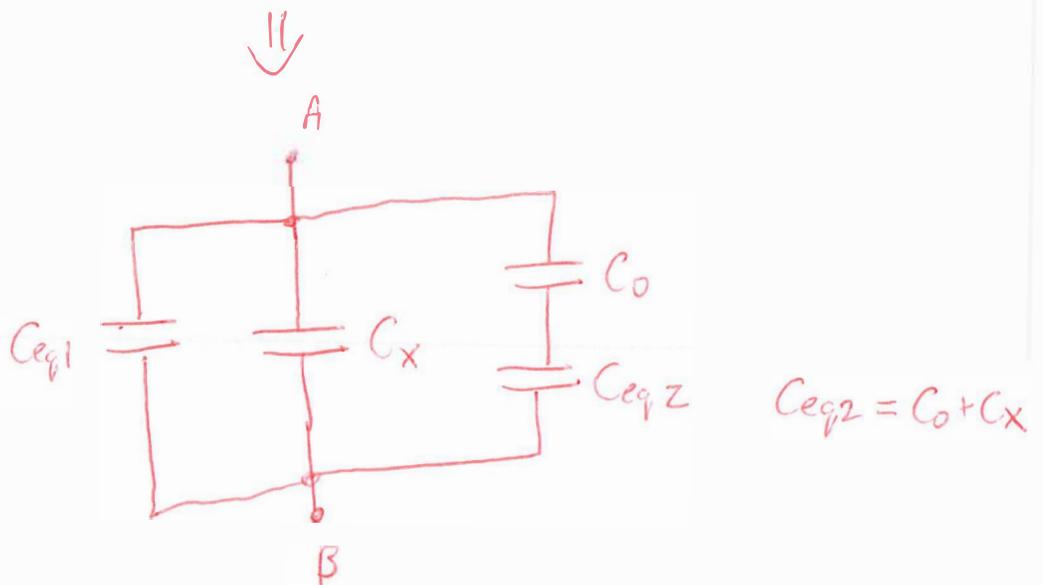

$$C_{eq2} = C_0 + C_x$$

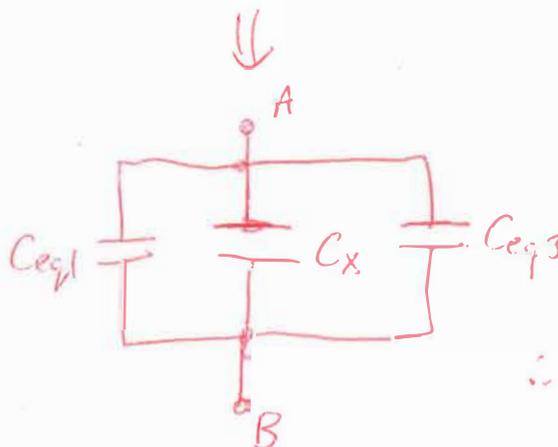

$$\frac{1}{C_{eq3}} = \frac{1}{C_0 + C_x} + \frac{1}{C_0}$$

$$= \frac{C_0 + C_0 + C_x}{C_0(C_0 + C_x)}$$

$$\therefore C_{eq3} = \frac{C_0(C_0 + C_x)}{2C_0 + C_x}$$

$$\therefore C_{eq} = C_{eq1} + C_x + C_{eq3} = \frac{C_0}{2} + C_x + \frac{C_0(C_0 + C_x)}{2C_0 + C_x} = \boxed{2.82C_0}$$

Stored energy

A parallel plate capacitor with plate separation d_0 is charged by connecting it to a battery. The energy stored by the capacitor is U_0 . The battery is then disconnected and the plate separation is changed to $d_1 = 2.4d_0$. If U_1 is the energy stored by the capacitor when the plate separation is d_1 , what is the ratio U_1/U_0 ?

- (a) 0.645
- (b) 0.417
- (c) 5.76
- (d) 1.55
- (e) 2.4
- (f) 0.174

$$U_0 = \frac{Q^2}{2C_0}$$

$$U_1 = \frac{Q^2}{2C_1}$$

} after battery disconnected, charge on plates cannot change.

$$\therefore \frac{U_1}{U_0} = \frac{Q^2/2C_1}{Q^2/2C_0} = \frac{C_0}{C_1}$$

$$C = \epsilon_0 \frac{A}{d}$$

$$\therefore \frac{U_1}{U_0} = \frac{\epsilon_0 A / d_0}{\epsilon_0 A / d_1} = \frac{d_1}{d_0} = \boxed{2.4}$$

Dissipated power

The power rating of a $2.20 \text{ k}\Omega$ resistor is 1.00 W . What is the maximum voltage that can be applied across this resistor?

- (a) $2.2 \times 10^3 \text{ V}$
- (b) 1.48 V
- (c) 0.0213 V
- (d) 2.2 V
- (e) 46.9 V

$$P = \frac{V^2}{R}$$

$$\begin{aligned} \therefore V_{\max} &= \sqrt{PR} = \sqrt{(2200 \text{ }\Omega)(1 \text{ W})} \\ &= 46.9 \text{ V} \end{aligned}$$

Kirchhoff laws

The Kirchhoff loop rule is a statement of which conservation principle?

- (a) conservation of charge
- (b) conservation of entropy
- (c) conservation of momentum
- (d) conservation of energy
- (e) conservation of angular momentum

Net change in P.E. of a charge around a closed loop in a circuit is zero.

Instantaneous current

A charge crossing a surface due to a proton beam is given by $Q = 5.0t^3 + 4.0t^2 + 6.0$ where Q is measured in Coulombs and the time t is measured in seconds. What is the current due to the proton beam when $t = 1.0$ s.

$$I = \frac{dQ}{dt} = (3)(5)t^2 + (2)(4)t \\ = 23 \text{ A}$$

- (a) 23 A
- (b) 14 A
- (c) 23 A
- (d) 14 A
- (e) 15 A