


# PHYS 231 - Intro to Electronics.

Jake Bobowski

SCI 266

jake.bobowski@ubc.ca

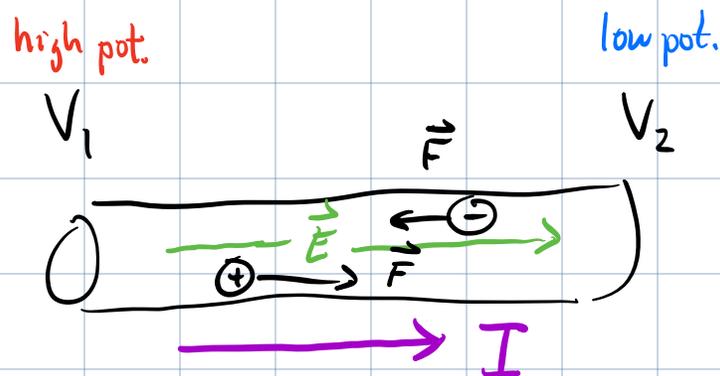Consider a conductor w/ a pot. diff. across it



Recall that  $\vec{E}$  point from high to low pot.

Cross conductor from left to right.

$$V_2 - V_1 < 0 \quad (\text{negative}).$$

Get a negative change in voltage when cross

a resistor/conductor in the dir'n of current  $I$ .

$$V_2 - V_1 = \Delta V = -IR$$

↙ resistance.

Cross conductor from right to left

$$V_1 - V_2 > 0 \text{ (positive).}$$

Get a pos. change in voltage when cross a resistor/conductor in the opp. dir'n of the current.

$$V_1 - V_2 = \Delta V = +IR$$

Relationship between electric field  $\vec{E}$  & voltage differences.

$$\Delta V = -\int \vec{E} \cdot d\vec{l}$$

mult. by pt. charge  $q$ .

$$\underbrace{q \Delta V}_{\Delta U} = - \int \underbrace{q \vec{E}}_{\vec{F}} \cdot d\vec{\ell}$$

$$\Delta U = - \int \underbrace{\vec{F}}_{\text{work } W} \cdot d\vec{\ell}$$

$$\underbrace{\Delta U}_{-\Delta K} = -W \quad \left. \vphantom{\Delta U} \right\} \boxed{W = \Delta K}$$