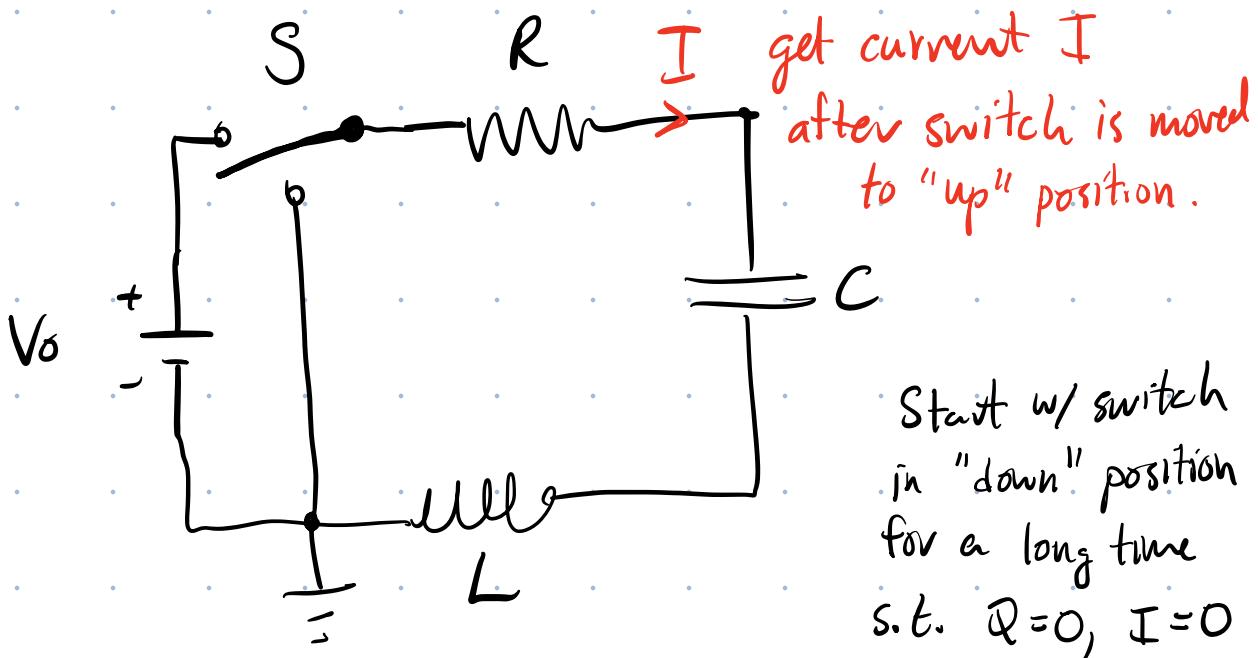


Last time

$$|\Delta V_C| = \frac{Q}{C}, |\Delta V_R| = IR = R \frac{dQ}{dt}, |\Delta V_L| = L \frac{dI}{dt} = L \frac{d^2Q}{dt^2}$$

LRC circuit

Kirchhoff Loop Rule

$$V_0 - \frac{1}{C}Q - R \frac{dQ}{dt} - L \frac{d^2Q}{dt^2} = 0$$

2nd order differential eq'n.

Math 225
Phys 216

Solve for $Q(t)$. \rightarrow Called time-domain
or a transient analysis.


Rewrite diff. eq'n as:

$$\boxed{\frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{1}{LC} Q = \frac{V_0}{L}} \quad @$$


If you like, see full sol'n to @ on PHYS 231
website (optional)

We will demonstrate that the LRC circuit
has a mechanical analogy that we already
understand intuitively.

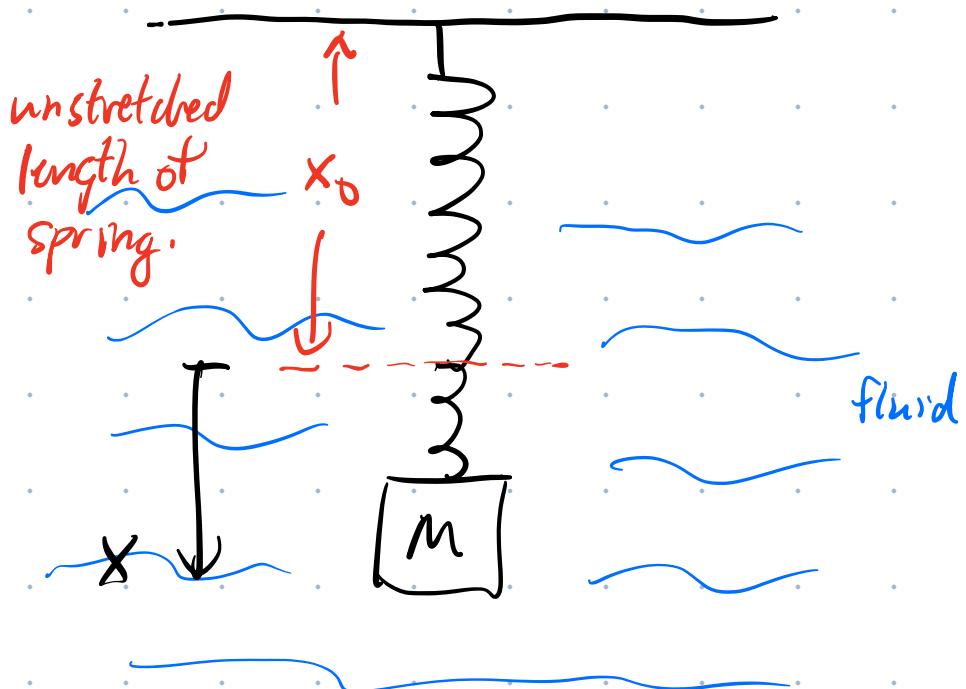
Consider a mass hanging from ceiling by a spring. Mass is also submerged in a viscous fluid.



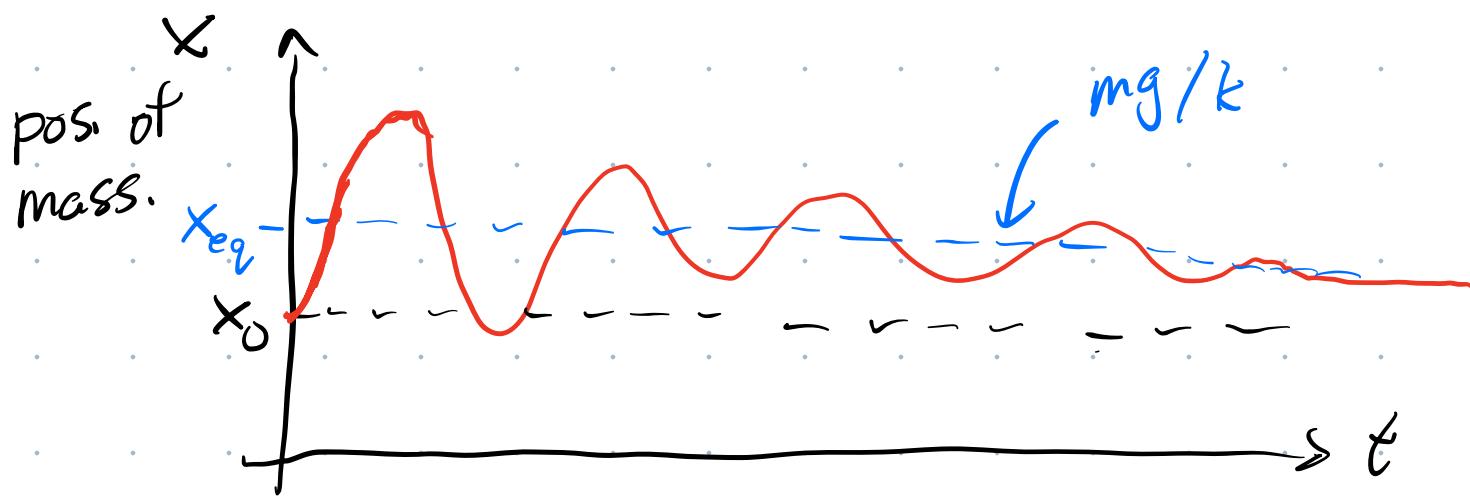If we stretch & release the mass, it will begin to oscillate about an equil. position. The drag force on the mass due to fluid converts some of the system's mechanical energy into heat. This dissipation, causes the amplitude of the osc. to decrease w/ time (damping).



FBD of mass on spring:

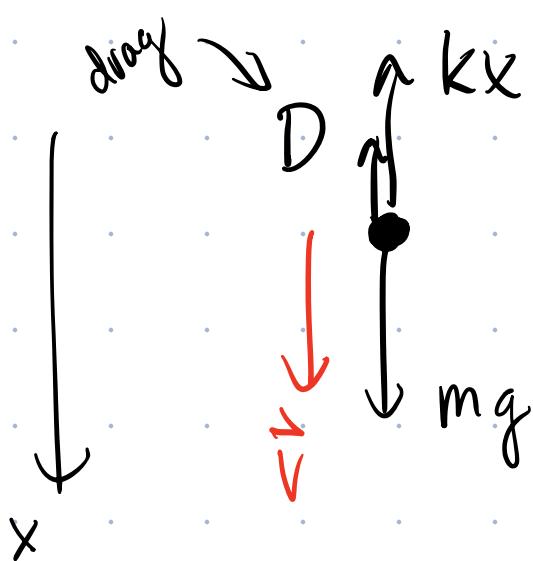

Assume that
the drag force D
is given by $D = bV$

drag
coefficient.

Newton's 2nd Law

$$ma = mg - kx - bv$$

net force.

rewrite $V = \frac{dx}{dt}$, $a = \frac{d^2x}{dt^2}$, then:

$$m \frac{d^2x}{dt^2} = mg - kx - b \frac{dx}{dt}$$

$$\therefore \frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m} x = g$$

⑥

Mathematically, Eqns ⑤ & ⑥ are identical.

\therefore Sol'n for $Q(t)$ in ⑤ is of the same form as the sol'n for $x(t)$ in ⑥.


For the mass on a spring we can find the final equilib. position by setting $\frac{dx}{dt} = 0$

$\frac{d^2x}{dt^2} = 0$ to be equal to zero.


$$\frac{k}{m} x_{eq} = g \Rightarrow x_{eq} = \frac{mg}{k}$$

For LRC circuit, can find final equil. charge
on cap. by setting $\dot{I} = \frac{dQ}{dt}$ ↗ $\frac{dI}{dt} = \frac{d^2Q}{dt^2}$
to zero in ①

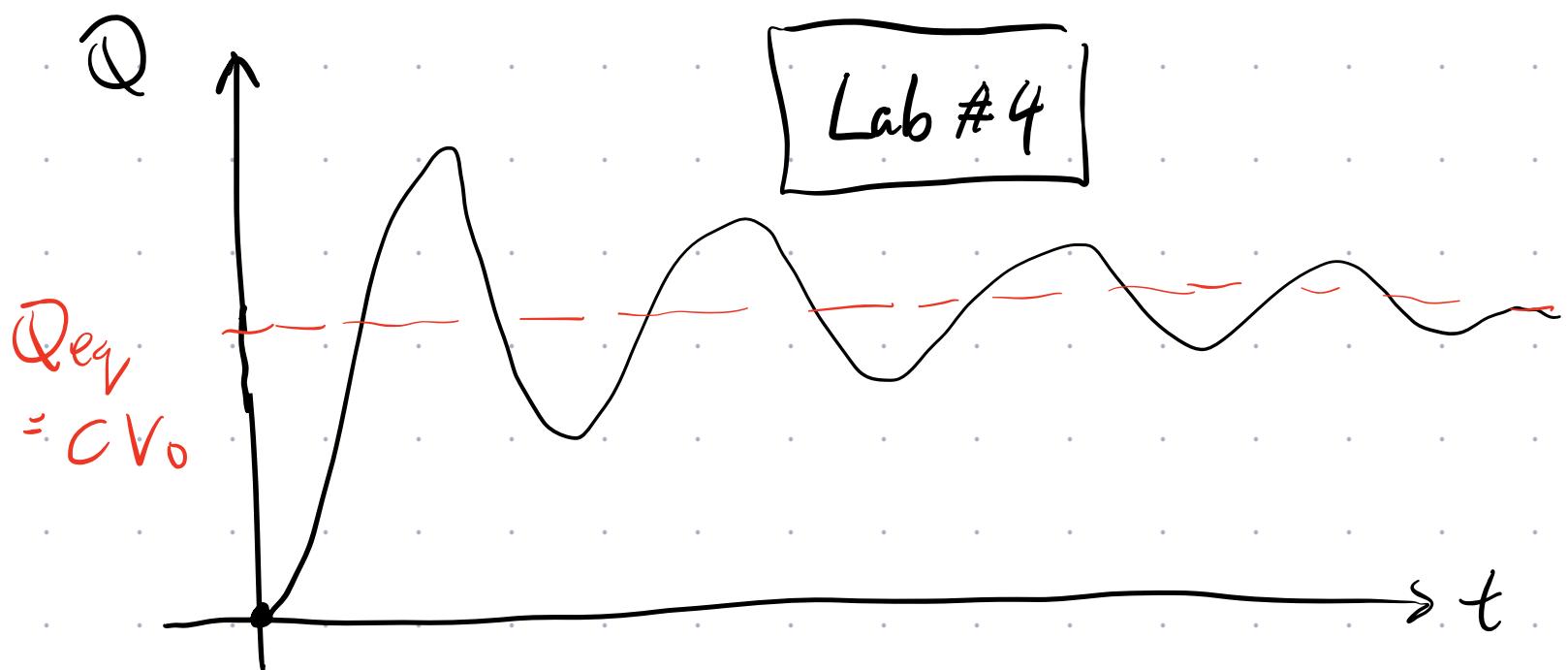
$$\cancel{\frac{1}{LC}} Q_{eq} = \frac{V_0}{\cancel{L}} \quad \boxed{\therefore Q_{eq} = CV_0}$$



Mass on a spring submerged in honey.

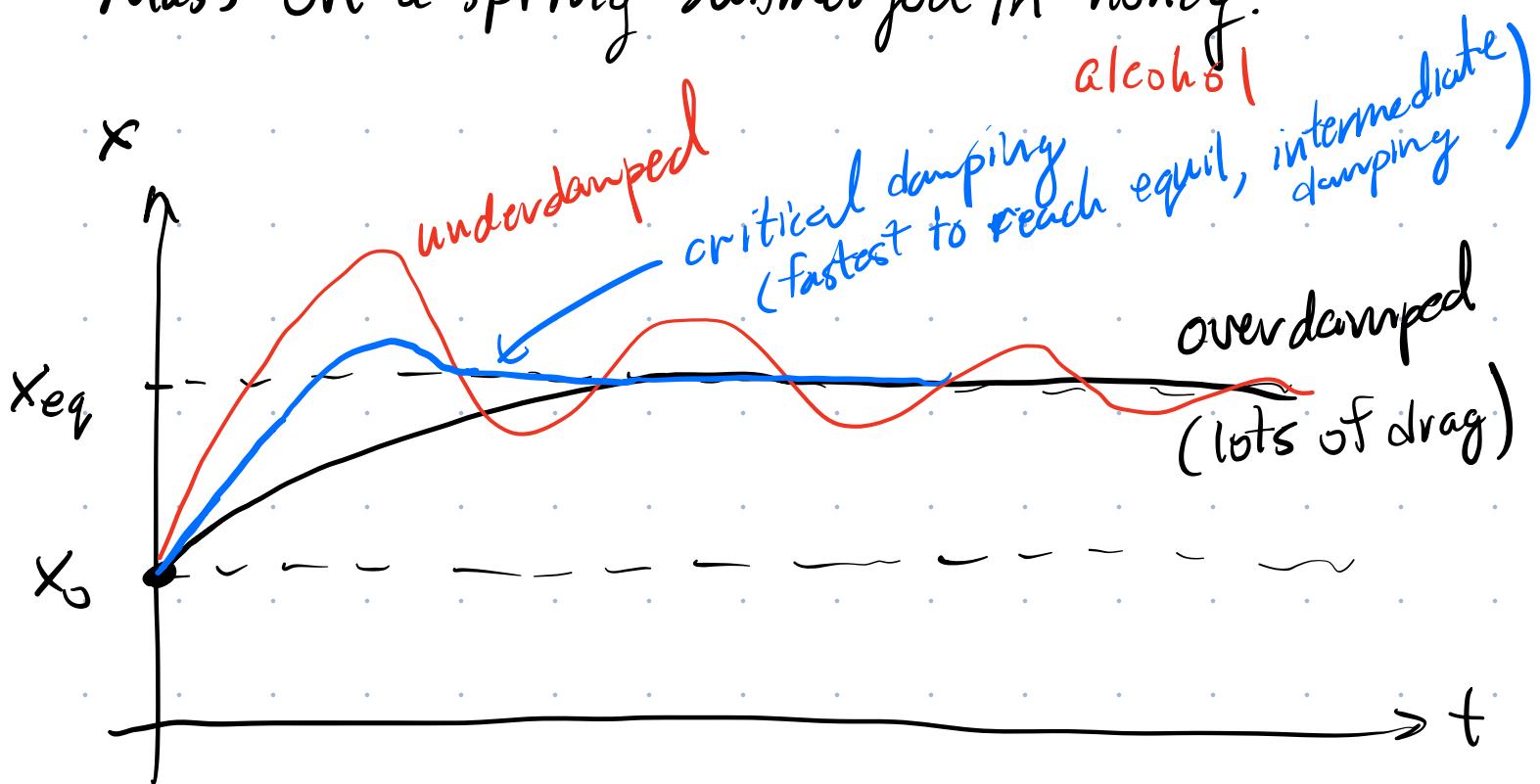

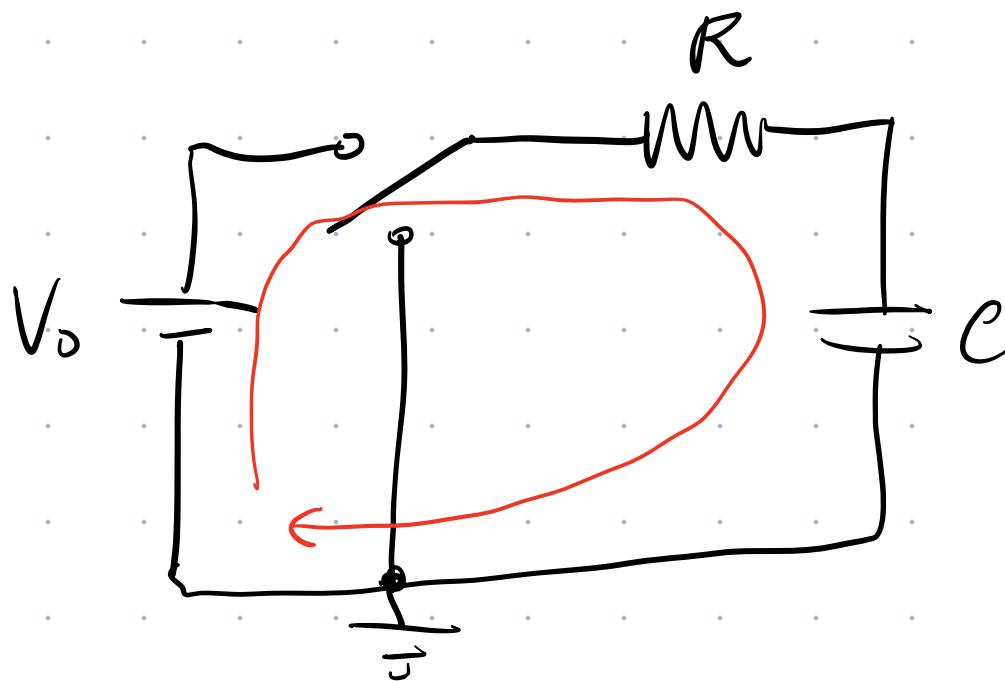Next time, we'll analyze the RC series circuit.



Start w/
switch down
s.t.
 $Q=0$
 $I=0$

At $t=0$, flip switch up. Find $Q(t)$ as system approaches new equil.

KLR w/ switch up.

$$V_0 - R \frac{dQ}{dt} - \frac{1}{C} Q = 0$$

$$\therefore \frac{dQ}{dt} + \frac{1}{RC} Q = \frac{V_0}{R}$$

First order
diff. eq'n.
want to solve
for $Q(t)$.

Long time after switch up, $\frac{dQ}{dt} = 0$

$$\therefore \cancel{\frac{1}{RC}} Q_{\text{eq}} = \frac{V_0}{R} \Rightarrow Q_{\text{eq}} = CV_0$$

Q



Q_{eq}
 $= CV_0$

O

t