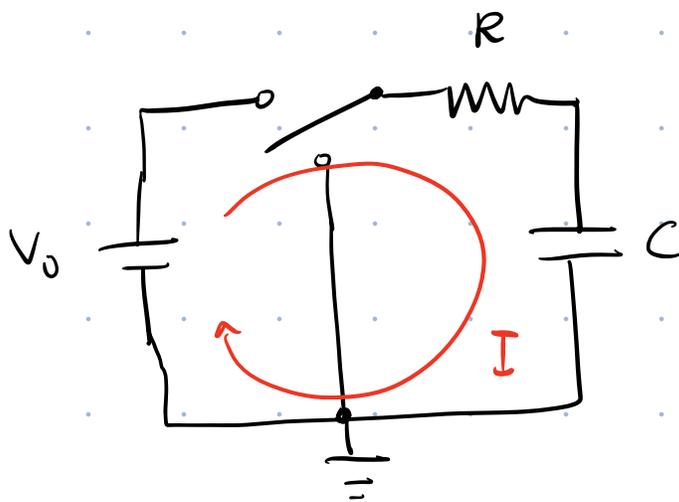


Last Time: Series RC Circuit



Start w/ switch
down $\Rightarrow Q=0,$

$$I = \frac{dQ}{dt} = 0$$

@ $t=0$, flip switch
up, $I \neq 0$.

KLR:


$$\frac{dQ}{dt} + \frac{1}{RC} Q = \frac{V_0}{R} \quad \text{⊗}$$

Solve for $Q(t)$ subject to initial condition
 $Q(0) = 0$.

After switch has been up for a long time,
system reaches a new equil. s.t.

$$Q = Q_{eq} \text{ (const)} \quad \left\{ \begin{array}{l} I = \frac{dQ}{dt} = 0 \end{array} \right.$$
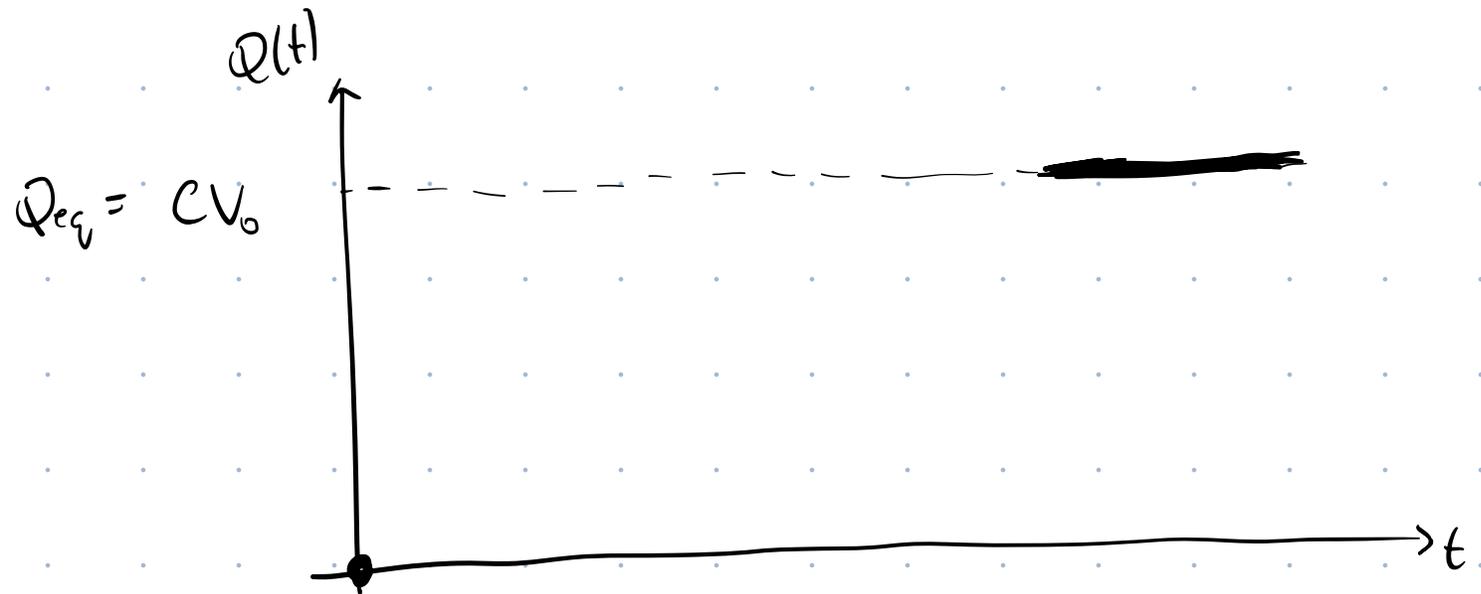
$$\therefore \frac{1}{RC} Q_{eq} = \frac{V_0}{R} \Rightarrow \boxed{Q_{eq} = CV_0}$$



Express $Q(t) = Q_h(t) + \underbrace{Q_{eq}}_{\text{const.}} = CV_0$

$$Q(t) = Q_h(t) + CV_0$$

sub into \textcircled{A} s.t.

$$\frac{V_0}{R} = \frac{d}{dt} (Q_h(t) + CV_0) + \frac{1}{RC} (Q_h(t) + CV_0)$$

$$\frac{dQ_h(t)}{dt}$$

since CV_0 is const.

$$\therefore \cancel{\frac{V_0}{R}} = \frac{dQ_h(t)}{dt} + \frac{1}{RC} Q_h(t) + \cancel{\frac{V_0}{R}}$$

⊕ $0 = \frac{dQ_h(t)}{dt} + \frac{1}{RC} Q_h(t)$ Homogeneous 1st order diff. eq'n.

→ LHS is zero.

→ $Q_h(t)$ called the homogeneous sol'n.

Goal is to solve ⊕ for $Q_h(t)$. Then, we will know the capacitor charge at all times since

$$Q(t) = Q_h(t) + CV_0.$$

Start by defining $\tau = RC$ (time const.)

$$0 = \frac{dQ_h(t)}{dt} + \frac{1}{\tau} Q_h(t).$$

$$\therefore -\frac{1}{\tau} Q_h(t) = \frac{dQ_h(t)}{dt} \quad \left(\begin{array}{l} \text{mult. by} \\ dt \end{array} \right)$$

$$\therefore -\frac{dt}{\tau} Q_h(t) = dQ_h(t) \quad \left(\begin{array}{l} \text{divide by} \\ Q_h(t) \end{array} \right)$$

$$\therefore -\frac{dt}{\tau} = \frac{dQ_n(t)}{Q_n(t)} \quad \left(\begin{array}{l} \text{integrate} \\ \text{both sides} \end{array} \right)$$

$$\therefore \int \left(-\frac{dt}{\tau} \right) = \int \frac{dQ_n(t)}{Q_n(t)}$$

$$\therefore -\frac{1}{\tau} \int dt = \int \frac{dQ_n(t)}{Q_n(t)}$$

$$\therefore -\frac{t}{\tau} = \ln Q_n(t) + B$$

integration constant.

$$\therefore \ln Q_n(t) = -\left(\frac{t}{\tau} + B \right) \quad \left(\text{exponentiate} \right)$$

$$Q_n(t) = e^{-\left(\frac{t}{\tau} + B \right)} = e^{-t/\tau} \underbrace{e^{-B}}_{\equiv B'} \quad \left(\text{const.} \right)$$

$$\therefore Q_n(t) = B' e^{-t/\tau}$$

use our initial condition $Q(t) = Q_n(t) + CV_0$

Require $Q(0) = 0$

$$\therefore 0 = Q_h(0) + CV_0$$

$$\text{But } Q_h(0) = B'e^{-0/\tau} = B'$$


$$\therefore 0 = B' + CV_0 \Rightarrow B' = -CV_0$$

$$\therefore Q_h(t) = -CV_0 e^{-t/\tau}$$

$$\begin{aligned} \therefore Q(t) &= Q_h(t) + CV_0 \\ &= -CV_0 e^{-t/\tau} + CV_0 \end{aligned}$$

$$\therefore Q(t) = CV_0 (1 - e^{-t/\tau})$$

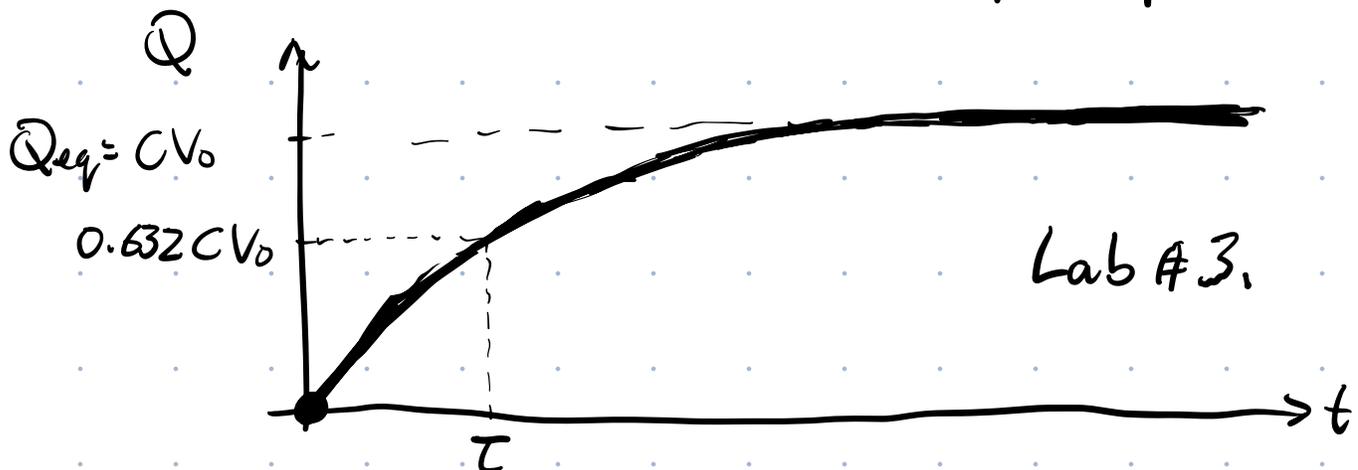Charge on cap. at all times
after switch flipped up.



Consider the time $t = \tau$ ($\tau = RC$)

$$\begin{aligned} Q(t=\tau) &= CV_0 \left(1 - e^{-\tau/\tau} \right) \\ &= CV_0 \left(1 - \frac{1}{e} \right) \\ &\quad \underbrace{\hspace{1.5cm}} \\ &\quad 0.632 \end{aligned}$$

The capacitor reaches 63% of its final charge after one time const.

aside

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$e^{-t/\tau} = 1 - \frac{t}{\tau} + \frac{1}{2!} \left(\frac{t}{\tau} \right)^2 - \frac{1}{3!} \left(\frac{t}{\tau} \right)^3 + \dots$$


small c.t. t/τ , linear

To find the time dependence of the current,
evaluate

$$\begin{aligned} I(t) &= \frac{dQ}{dt} = \frac{d}{dt} \left[CV_0 (1 - e^{-t/\tau}) \right] \\ &= 0 - CV_0 \frac{d}{dt} (e^{-t/\tau}) \\ &= -CV_0 \left(-\frac{1}{\tau} e^{-t/\tau} \right) \end{aligned}$$

$$\therefore I(t) = \frac{CV_0}{RC} e^{-t/\tau}$$

$$I(t) = \frac{V_0}{R} e^{-t/\tau}$$

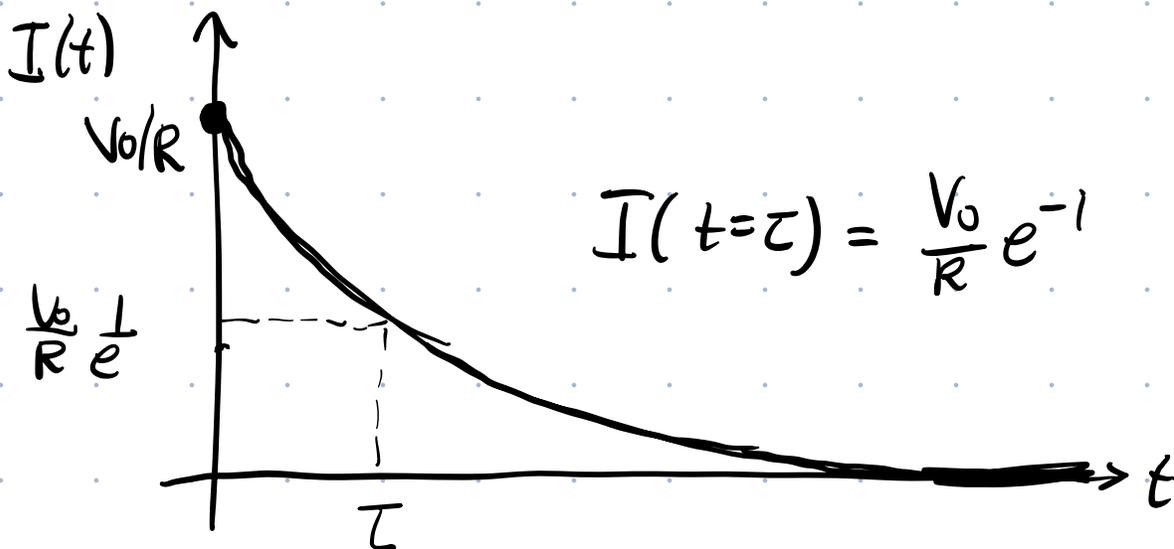

Uncertainties & Propagation of Errors

Every quantity that is measured has an associated uncertainty.

Experiment: Drop a penny from a tall building & meas. time for it to reach the ground. Make a table of repeated trials.

trial #	time (s)
1	148.25
2	151.36
3	146.20
4	153.67
⋮	⋮
N	149.71

$$\mu = \frac{1}{N} \sum_{i=1}^N t_i$$

Plot a histogram of the N trials.

