
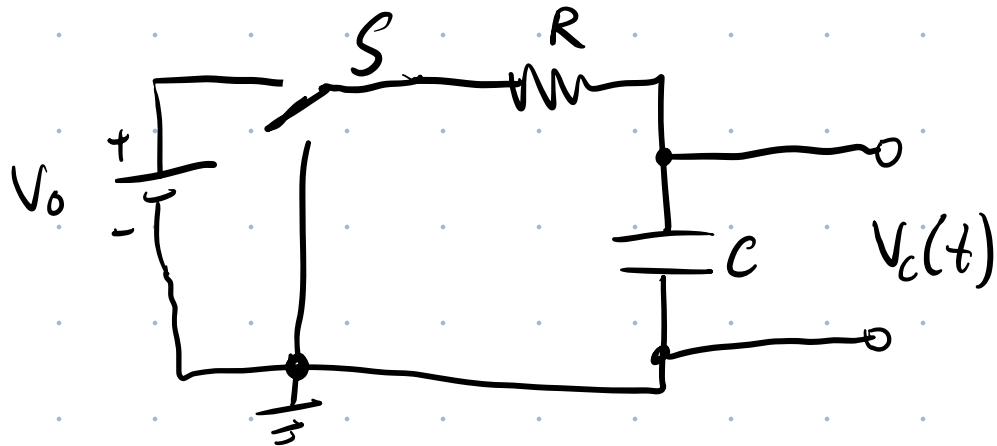


Lab #3 Preview

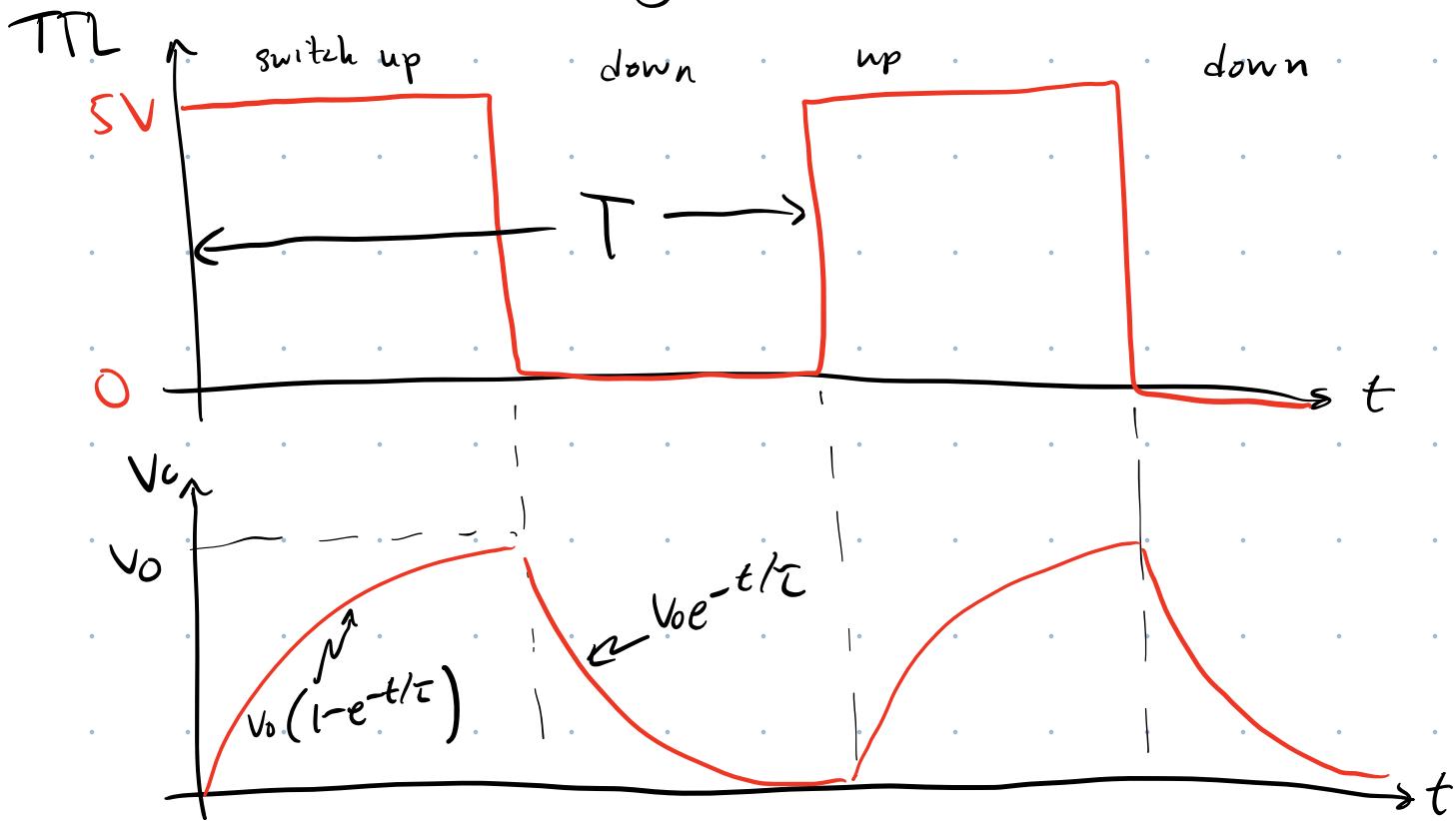


Use square wave TTL output of fcn generator to simulate opening & closing of switch.



In Lab #3, we focus on discharge of cap

$$V_c(t) = V_0 e^{-t/\tau}$$

Goal: Make a quick est. of τ .

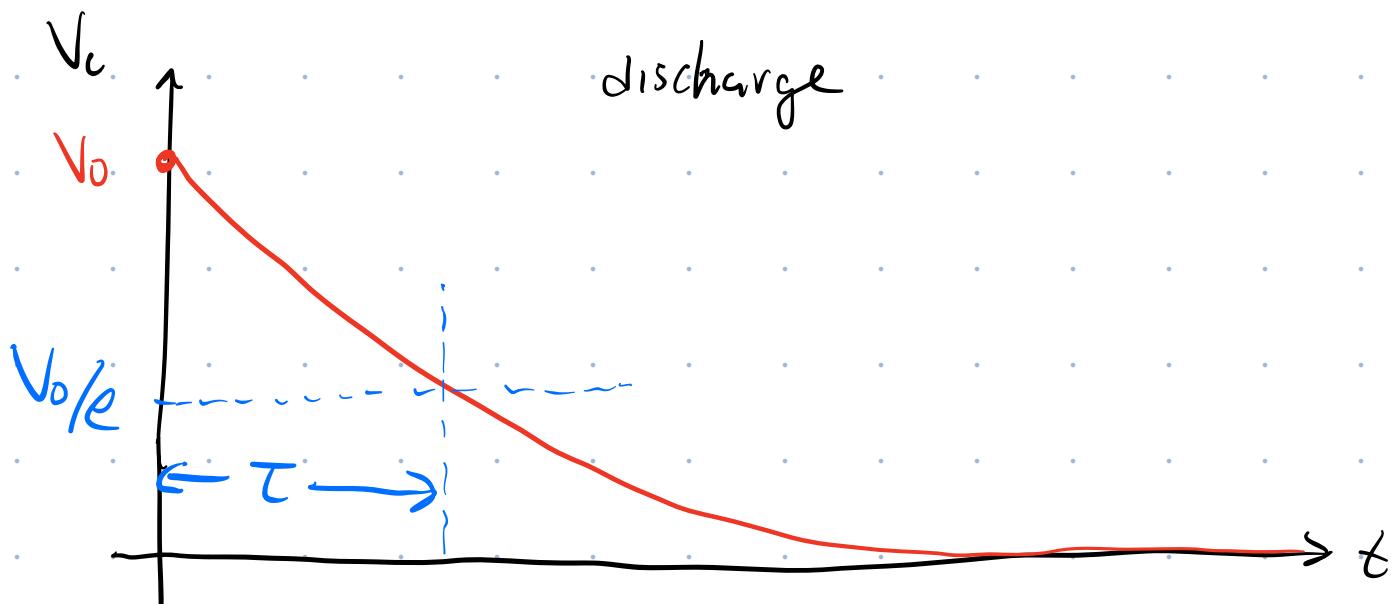


At time $t = \tau$ $V_c(t=\tau) = V_0 e^{-\tau/\tau}$

$$= \frac{V_0}{e} = 0.368 V_0$$

- ① Set up scope to observe discharge of cap.
- ② Meas. V_0 , the max voltage across cap.
- ③ Calc. and then find $V_0/e = 0.368 V_0$
- ④ Est. $\tau \pm \Delta\tau$ by finding the time required

for cap to discharge from V_0 to V_0/e .

$$\tau = RC$$

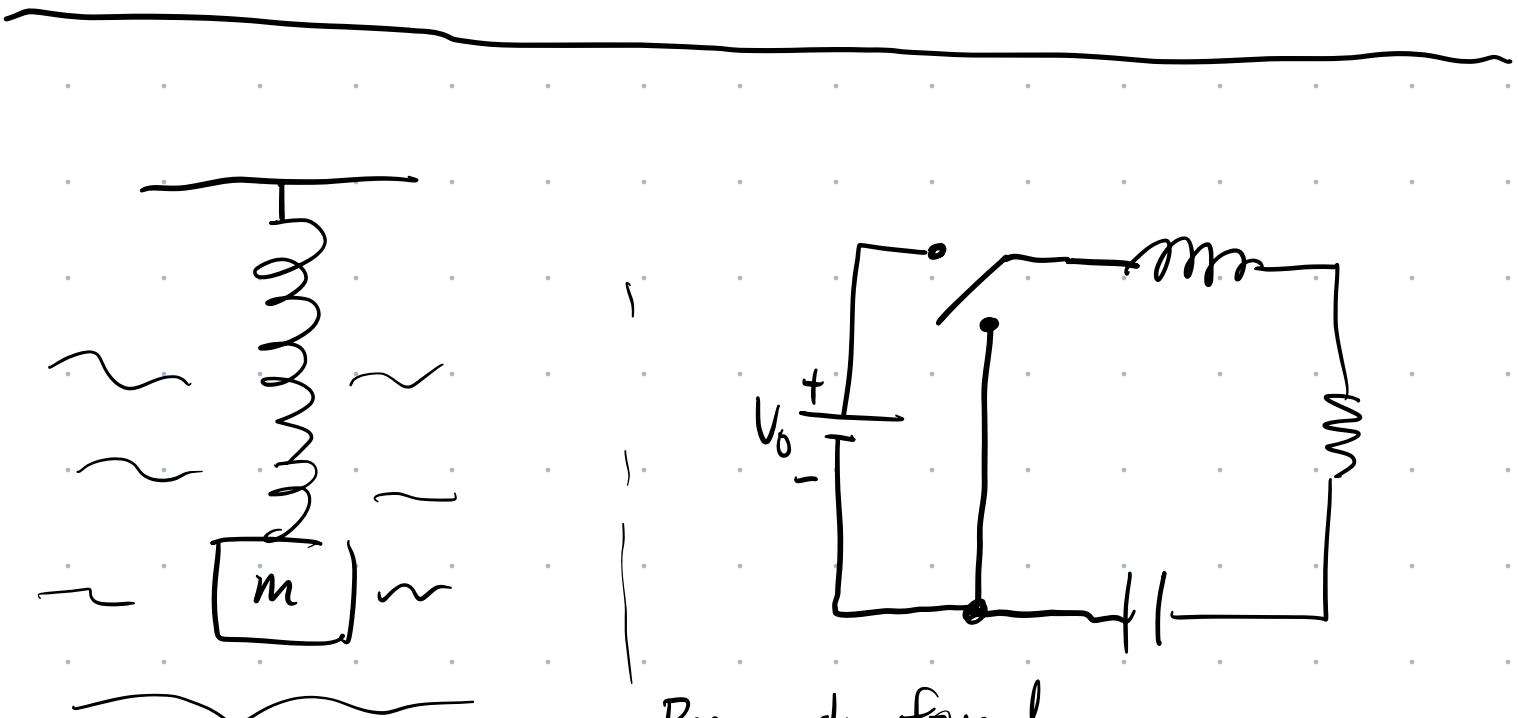


Previously found

$$q = \frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m} x$$

$$\frac{V_0}{L} = \frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{q}{LC}$$

$$x_{eq} = \frac{mg}{k}$$

$$q_{eq} = CV_0$$

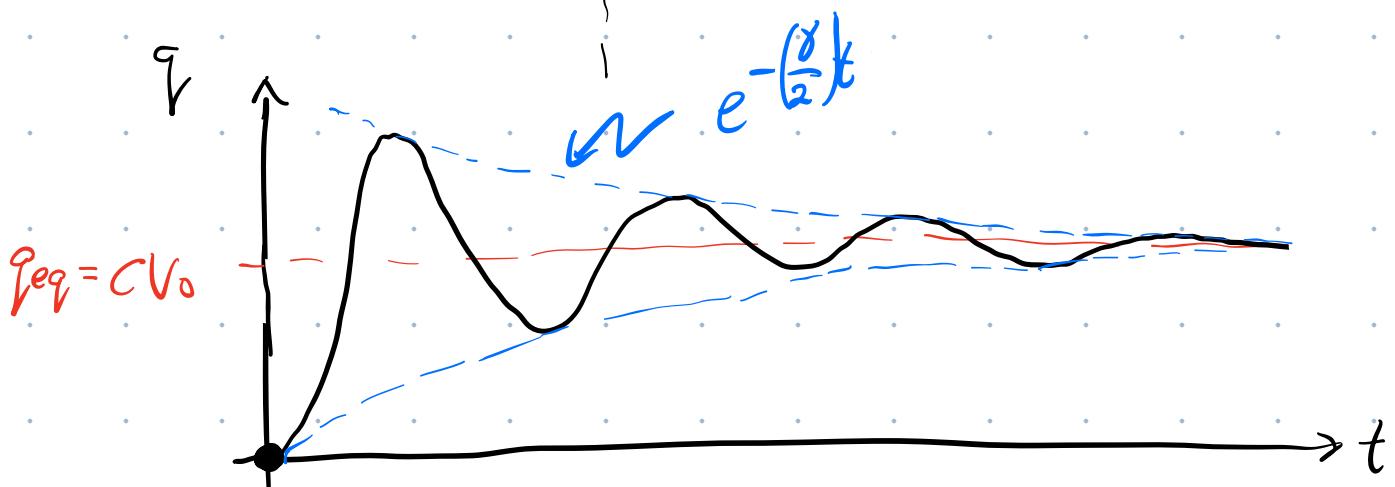

If $q=0$ @ $t=0$ (initial condition), then for an underdamped LRC circuit (R small), the sol'n for charge on the cap. as a fn of time is:

$$q(t) = CV_0 \left[1 - e^{-\left(\frac{\gamma}{2}\right)t} \cos(\omega_1 t) \right]$$

where $\gamma = \frac{R}{L}$ $\omega_1 = \sqrt{\omega_0^2 - \left(\frac{\gamma}{2}\right)^2}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

In Lab #4, you will meas. the volt. across the resistor which is $V_R = IR$

Need to evaluate $I = \frac{dq}{dt}$

$$\begin{aligned} \therefore I &= +\frac{\gamma}{2} e^{-\left(\frac{\gamma}{2}\right)t} \cos(\omega_1 t) \\ &\quad + \omega_1 e^{-\left(\frac{\gamma}{2}\right)t} \sin(\omega_1 t) \end{aligned} \quad \left. \right\} \text{complicated!}$$

For very underdamped circuits, R is small $\Rightarrow \gamma$ is small. \therefore can ignore the first term in I compared to the second term. Notice also that

$$\omega_1 = \sqrt{\omega_0^2 - \left(\frac{\gamma}{2}\right)^2} \approx \omega_0 \text{ when } R, \gamma \text{ small.}$$


$$I \approx \omega_0 C V_0 e^{-\left(\frac{\gamma}{2}\right)t} \sin(\omega_0 t)$$

$$\text{where } \gamma = \frac{R}{L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

\therefore The voltage across the resistor is

$$V_R = IR = \omega_0 R C V_0 e^{-\left(\frac{\gamma}{2}\right)t} \sin(\omega_0 t)$$


Lab #4 - day 1.

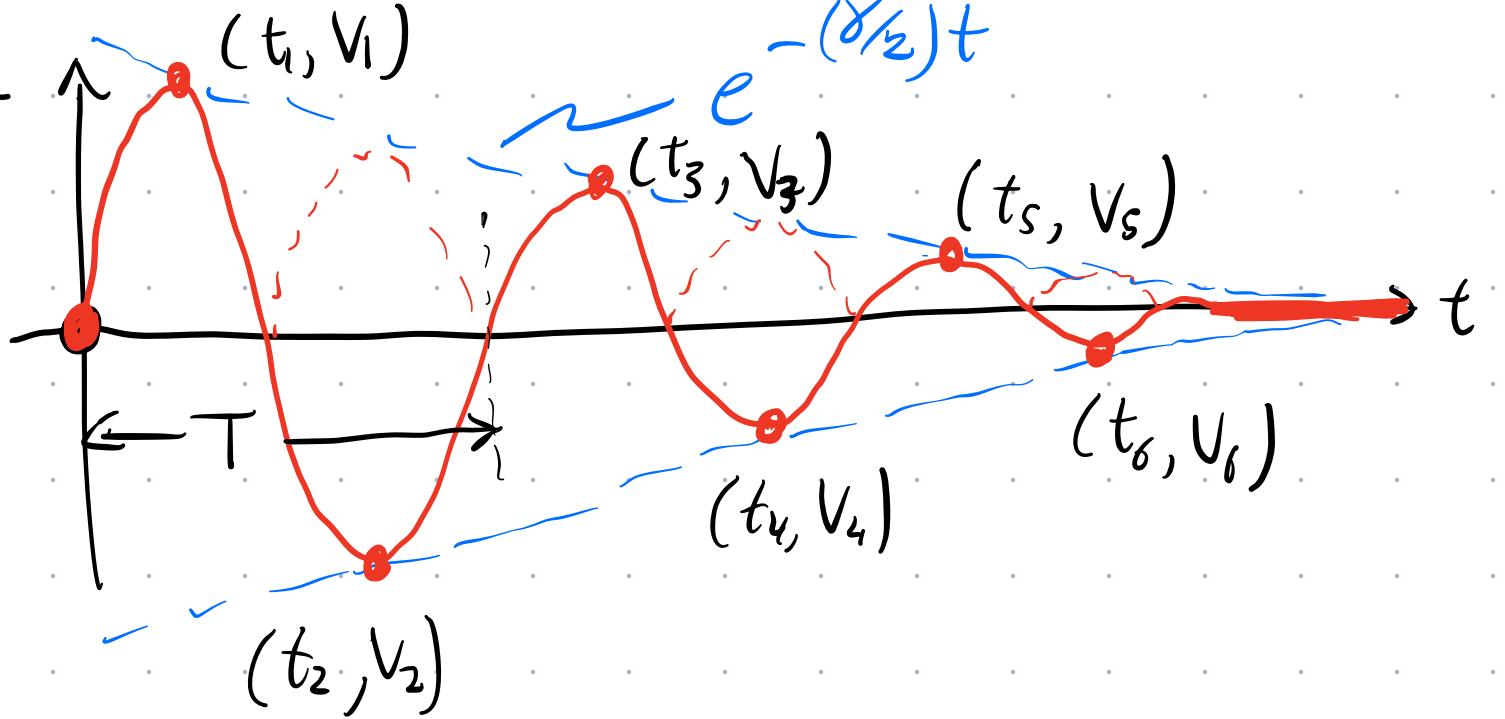



Plot of $|V_j|$ vs t_i \rightarrow use the data to meas. γ

Meas. the period T
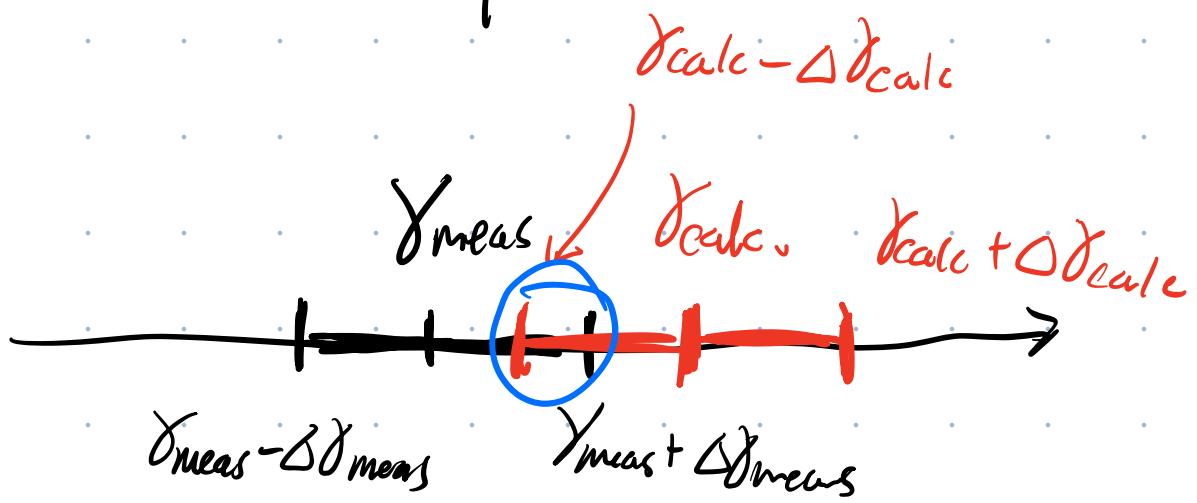
$$\omega_0 = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{\omega_0} = 2\pi\sqrt{LC}$$



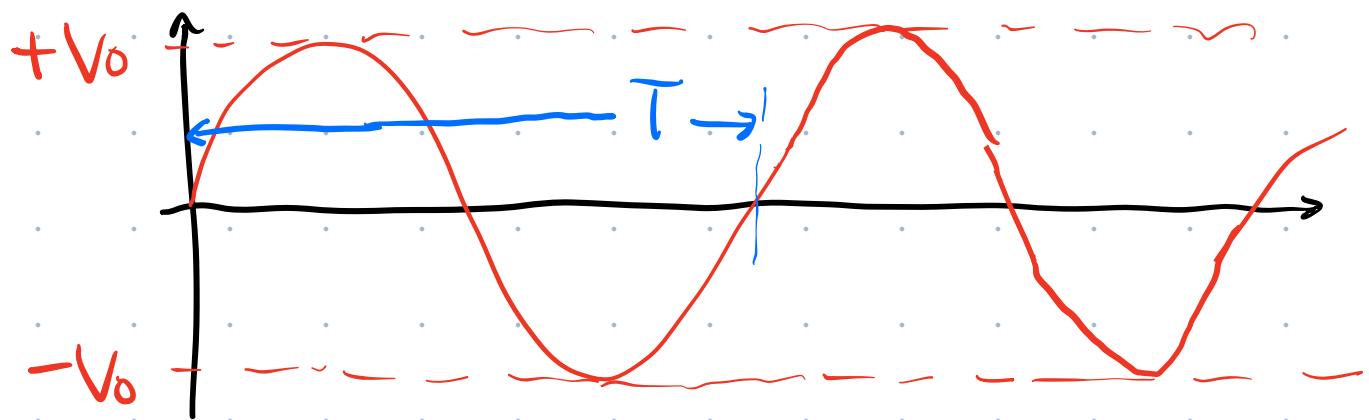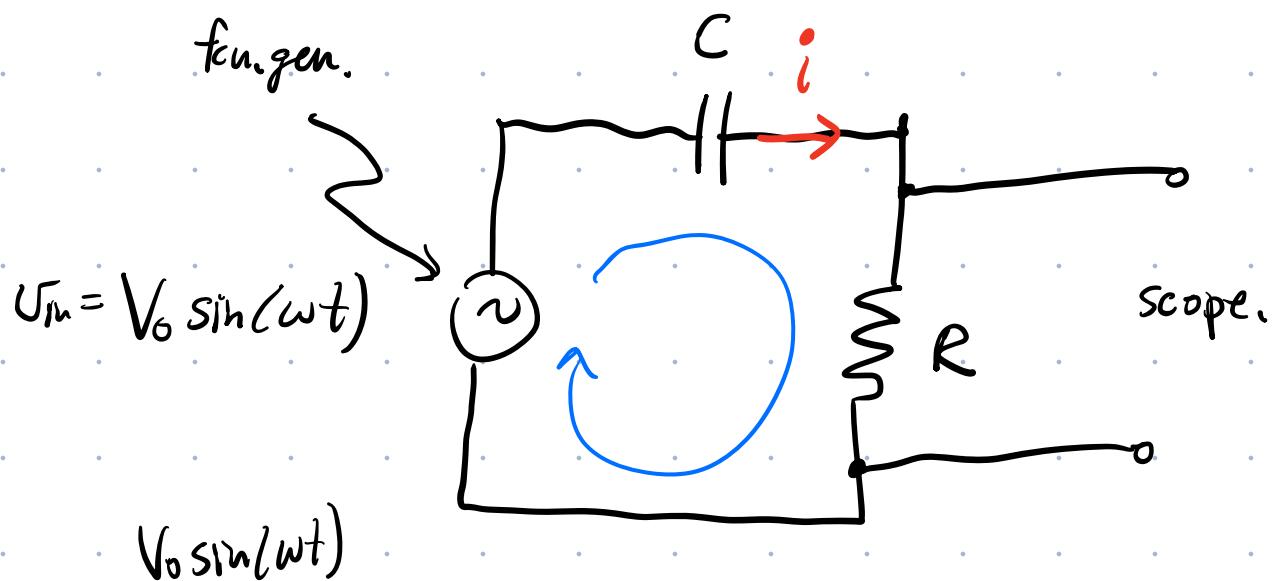Next topic: Analysis of the freq. response of an RC circuit. i.e. how does i vary w/ freq.?



V_0 : amplitude

tune
w/
fcn.gen. { T : period / time to complete one full cycle.
 f : $f = \frac{1}{T}$ freq. (freq.)

$$\omega : 2\pi f = \frac{2\pi}{T} \quad (\text{angular freq.})$$

Observations from Part 4 of Lab #2.

- current osc. sinusoidally at same freq. as V_{in}
- current was out of phase w/ V_{in}
- the amplitude of current depends on ω .

Assume that the current in RC circuit is of the form:

$$i = I_0(\omega) \sin [\omega t + \phi(\omega)]$$

↑ ↑
freq. dependent amp. freq. dep. phase.

Goal is to find expressions for $I_0(\omega)$ & $\phi(\omega)$

KLR of series RC circuit:

$$V_{in} - \frac{q}{C} - iR = 0 \quad \textcircled{*}$$

To make a diff. eq. in i , take deriv. of \textcircled{A}

$$\frac{dV_m}{dt} - \frac{1}{C} i - R \frac{di}{dt} = 0$$

Solve for $i(t)$