

Last Time:

Can represent any complex number in two ways:

$$z = x + jy = |z| e^{j\phi}$$

$$x = \operatorname{Re}[z] \quad \text{"real part of } z \text{"}$$

$$y = \operatorname{Im}[z] \quad \text{"imaginary part of } z \text{"}$$

$$\text{Euler's Eq'n: } e^{j\phi} = \cos \phi + j \sin \phi$$

$$x = |z| \cos \phi$$


$$y = |z| \sin \phi$$

$$|z| = \sqrt{x^2 + y^2}$$

$$\tan \phi = \frac{y}{x}$$

Today: Use complex nos. as a mathematical tool to help us analyze circuits driven by sinusoidal signals.

Series LRC circuit (Lab #4)

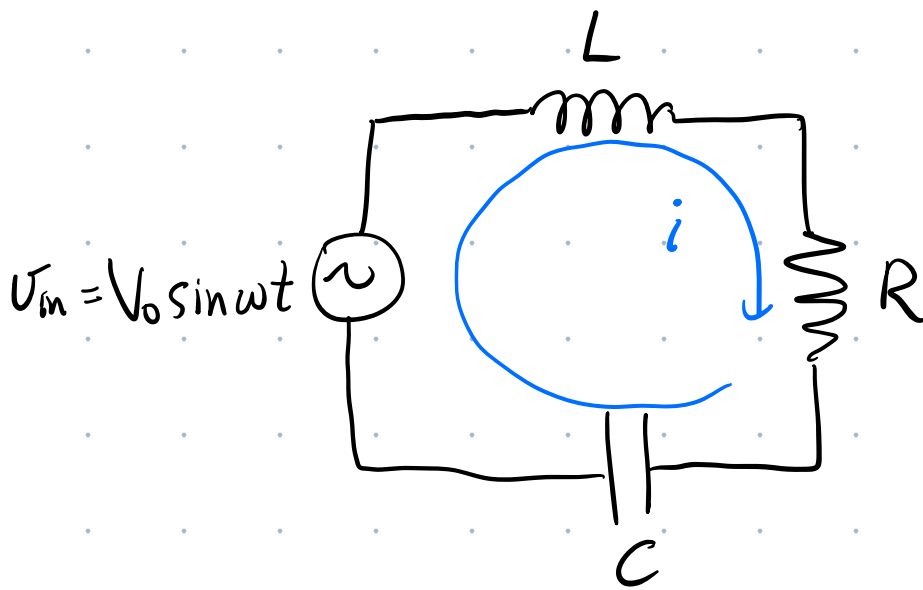

Assume that current is of the form

$$i = I_0 \sin(\omega t - \phi)$$

Find I_0 & ϕ .

KLR: $V_m - V_L - V_R - V_C = 0$

$$\therefore V_m = L \frac{di}{dt} + R i + \frac{1}{C} q$$

take time derivative.

$$\frac{dV_m}{dt} = L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i$$

Represent in input voltage $V_m = V_0 \sin \omega t$

as $V_m = V_0 e^{j\omega t} = V_0 [\cos(\omega t) + j \sin(\omega t)]$

$$\text{Im}[V_m] = V_0 \sin \omega t$$

We will do calculations using complex exponential representation of v_{in} & i . Then in the end, take imaginary part which corresponds to our original v_{in} & yields desired current.

Also represent the current $i = I_0 \sin(\omega t - \phi)$
as $i = I_0 e^{j(\omega t - \phi)}$

$$\text{Need: } \frac{d v_{in}}{dt} = \frac{d}{dt} (V_0 e^{j\omega t}) = j\omega \underbrace{V_0 e^{j\omega t}}_{v_{in}} = j\omega v_{in}$$

$$\frac{d i}{dt} = \frac{d}{dt} (I_0 e^{j(\omega t - \phi)}) = j\omega \underbrace{I_0 e^{j(\omega t - \phi)}}_i = j\omega i$$

$$\frac{d^2 i}{dt^2} = \frac{d}{dt} (j\omega i) = j\omega \frac{d i}{dt} = j\omega (j\omega i) = -\omega^2 i$$

$$\frac{dU_{in}}{dt} = L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i$$

$$j\omega U_{in} = -\omega^2 L i + j\omega R i + \frac{1}{C} i$$

divide by $j\omega$

$$\therefore U_{in} = \frac{-j\omega^2 L i}{j j\omega} + R i + \frac{1}{j\omega C} i$$

$$\therefore U_{in} = \underbrace{j\omega L i}_{U_L} + \underbrace{R i}_{U_R} + \underbrace{\frac{1}{j\omega C} i}_{U_C}$$

input voltage.

$$Z_R = R$$

Resistor $U_R = i R$

Inductor $U_L = i \underbrace{(j\omega L)}_{Z_L}$

Z_L : impedance of inductor.

Capacitor $U_C = i \underbrace{\left(\frac{1}{j\omega C}\right)}_{Z_C}$

Z_C : impedance of capacitor.

$$V_{in} = (Z_L + R + Z_C) i$$



Series combination of impedances:

Net series
equivalent
impedance.

$$Z = Z_L + R + Z_C$$

$$i = \frac{V_{in}}{Z}$$

write $i = I_0 e^{j(\omega t - \phi)}$

$$V_{in} = V_0 e^{j\omega t}$$

$$I_0 \underbrace{e^{j(\omega t - \phi)}}_{e^{j\omega t} e^{-j\phi}} = \frac{V_0 e^{j\omega t}}{Z}$$

$$I_0 \cancel{e^{j\omega t}} e^{-j\phi} = \frac{V_0 \cancel{e^{j\omega t}}}{Z}$$

$$I_0 e^{-j\phi} = \frac{V_0}{Z} \quad (\#)$$

work on Z .

$$Z = j\omega L + R + \frac{j}{j\omega C}$$

want to express Z as $|Z|e^{j\phi_z}$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$= x + jy \Rightarrow x = R \quad \begin{array}{l} \text{real part} \\ \text{of imped.} \end{array}$$

$$y = \omega L - \frac{1}{\omega C} \quad \begin{array}{l} \text{imaginary} \\ \text{part of} \\ \text{imped.} \end{array}$$

$$|Z| = \sqrt{x^2 + y^2}$$

$$= \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

factor out R^2
from $\sqrt{\quad}$.

$$|Z| = R \sqrt{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2}$$

$$\tan \phi_z = \frac{y}{x} = \omega \frac{L}{R} - \frac{1}{\omega RC}$$

$$\phi_z = \tan^{-1} \left(\frac{\omega L}{R} - \frac{1}{\omega RC} \right)$$

$$z = x + jy = |z| e^{j\phi_z}$$

sub $z = |z| e^{j\phi_z}$ into (7)

$$I_0 e^{-j\phi} = \frac{V_0}{|z| e^{j\phi_z}} = \frac{V_0}{|z|} e^{-j\phi_z}$$

This is valid only if $\phi = \phi_z$

\therefore phase of our current in LRC circuit is :

$$\tan \phi = \omega \frac{L}{R} - \frac{1}{\omega RC}$$

and

$$I_0 = \frac{V_0}{|Z|} = \frac{V_0/R}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

Return to (8)

$$I_0 e^{-j\phi} = \frac{V_0}{|Z|} \quad \text{multi. by } e^{j\omega t}$$

$$I_0 \underbrace{e^{j\omega t} e^{-j\phi}}_{e^{j(\omega t - \phi)}} = \frac{V_0 e^{j\omega t}}{|Z|}$$

write $e^{j\omega t} = \cos \omega t + j \sin \omega t$

$$e^{j(\omega t - \phi)} = \cos(\omega t - \phi) + j \sin(\omega t - \phi)$$

} Euler's eq'n.

$$\begin{aligned} I_0 & \left[\cos(\omega t - \phi) + j \sin(\omega t - \phi) \right] \\ & = \frac{V_0}{|Z|} \left[\cos(\omega t) + j \sin(\omega t) \right] \end{aligned}$$

We said that at the end of our manipulations, we would find our sol'n by taking the imaginary component of our result.

$$\Rightarrow \underbrace{I_0 \sin(\omega t - \phi)}_i = \frac{1}{|Z|} \underbrace{V_0 \sin \omega t}_{V_{in}}$$

$$\text{know } I_0 = \frac{V_0 / R}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

$$\tan \phi = \frac{\omega L}{R} - \frac{1}{\omega RC}$$