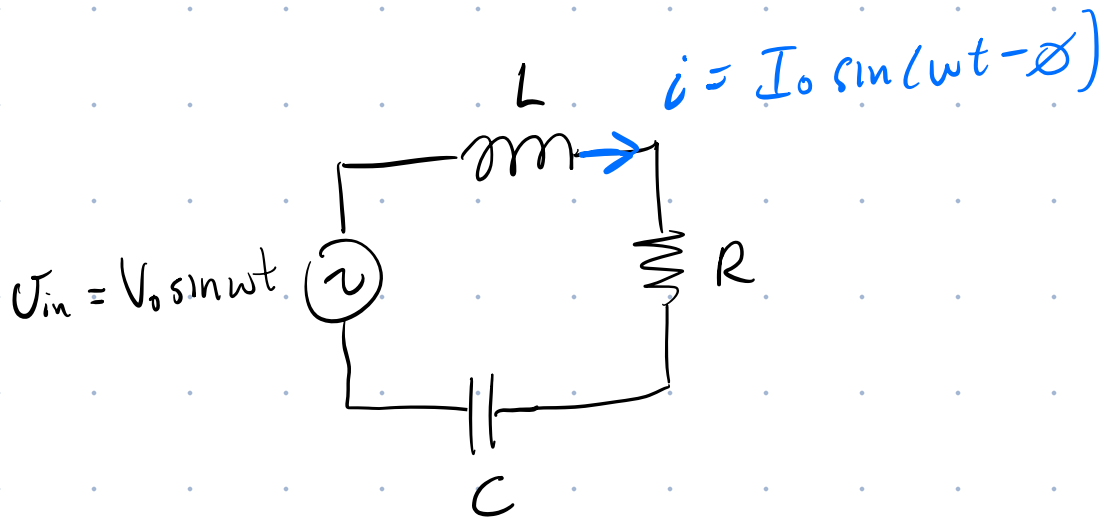


Last Time: LRC circuit driven by sinusoidal input



Goal: Find I_0 & ϕ of current.

1. Write $V_{in} = V_0 e^{j\omega t}$
 $i = I_0 e^{j(\omega t - \phi)}$


where $e^{jx} = \cos x + j \sin x$

2. Define impedance of L , R , & C .

$$Z_L = j\omega L, \quad Z_R = R, \quad Z_C = \frac{1}{j\omega C}$$

Impedances combine in series & parallel in the same way as resistors.

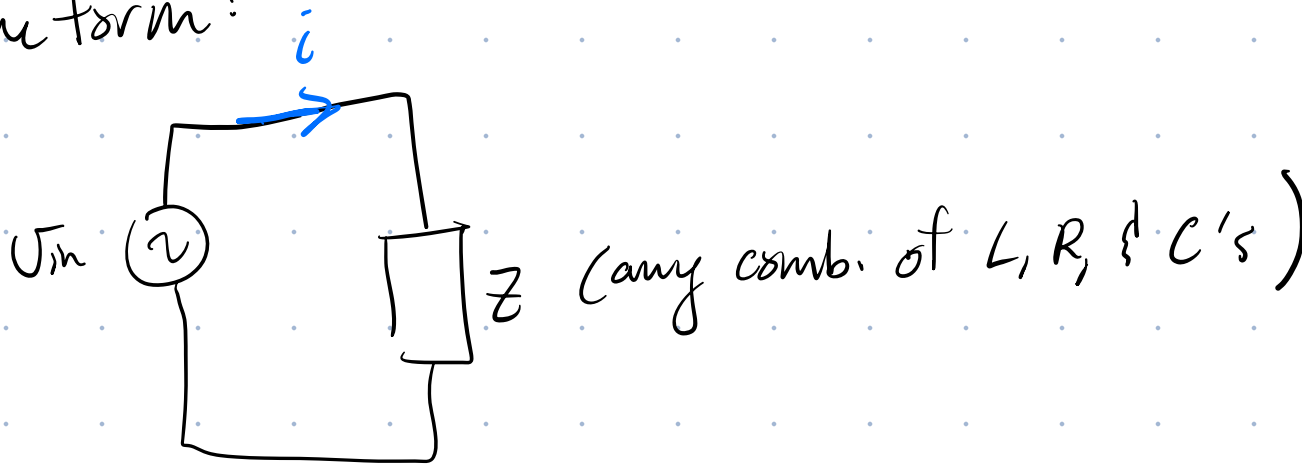For any circuit that can be drawn in the form:



$$I_0 = \frac{V_0}{|Z|} \quad \tan \phi = \frac{\text{Im}[Z]}{\text{Re}[Z]}$$

For series LRC circuit

$$Z = R + j\omega L + \frac{j}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$x = \text{Re}[Z]$ $y = \text{Im}[Z]$

$$Z = x + jy = |Z|e^{j\phi}$$

$$|Z| = \sqrt{x^2 + y^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = R \sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}$$

$$\therefore I_0 = \frac{V_0}{|Z|} = \frac{V_0/R}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

The current amp. & phase in LRC circuit.

$$\tan \phi = \frac{Y}{X} = \frac{\omega L}{R} - \frac{1}{\omega RC}$$

$$V_R = iR \Rightarrow V_R = I_0 R$$

resistor volt. amp.


signal gen. amp.

$$\frac{V_R}{V_0} = \frac{I_0 R}{V_0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

You will meas. this in Lab 4(b).



Examine freq. dependence of $\frac{V_R}{V_0}$ & ϕ .

$\omega \rightarrow 0$ case

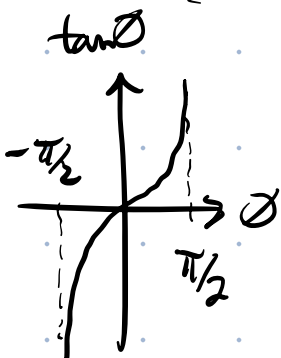

$$\tan \phi = \frac{\omega L}{R} - \frac{1}{\omega RC} \approx -\frac{1}{\omega RC}$$
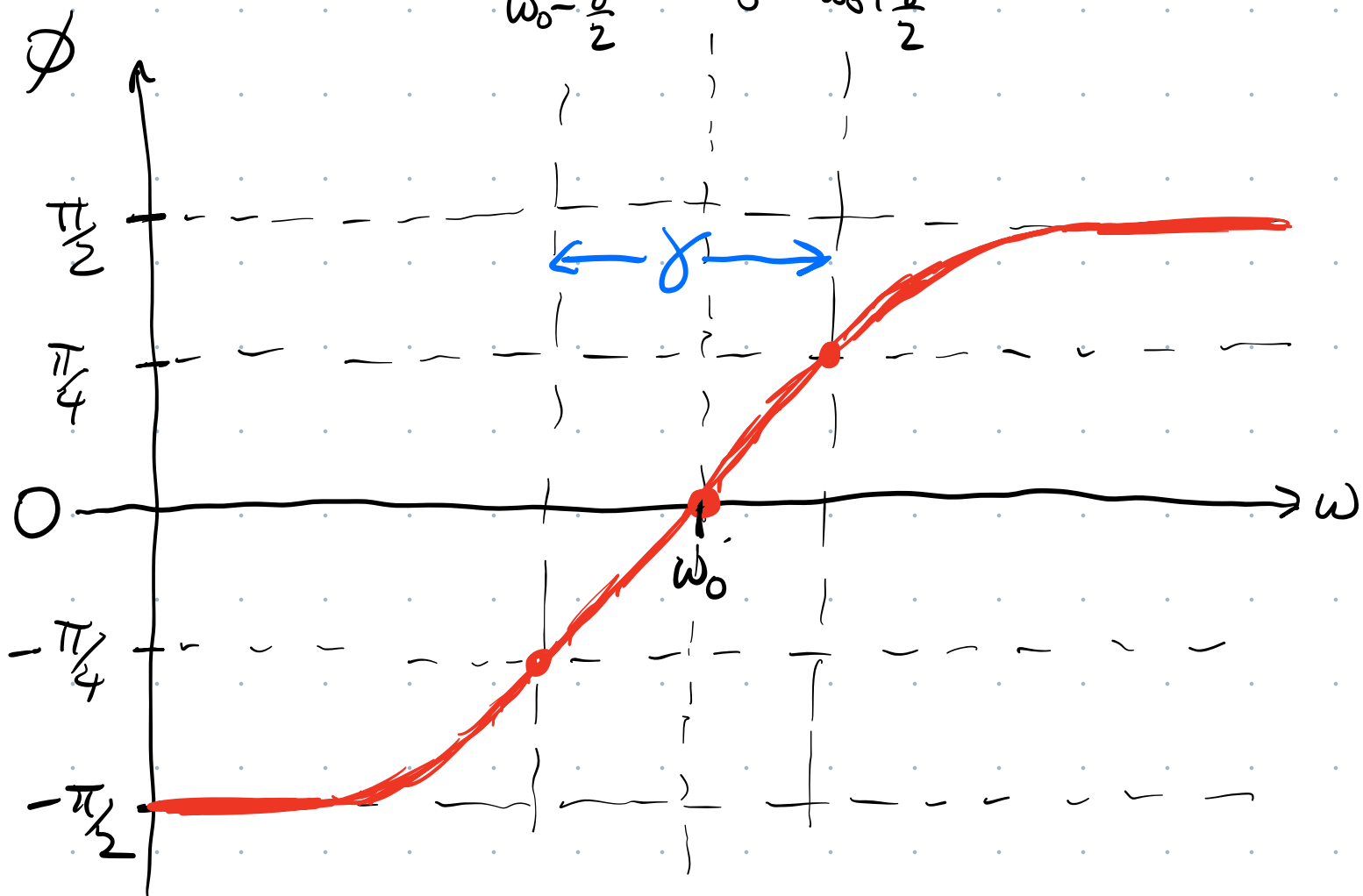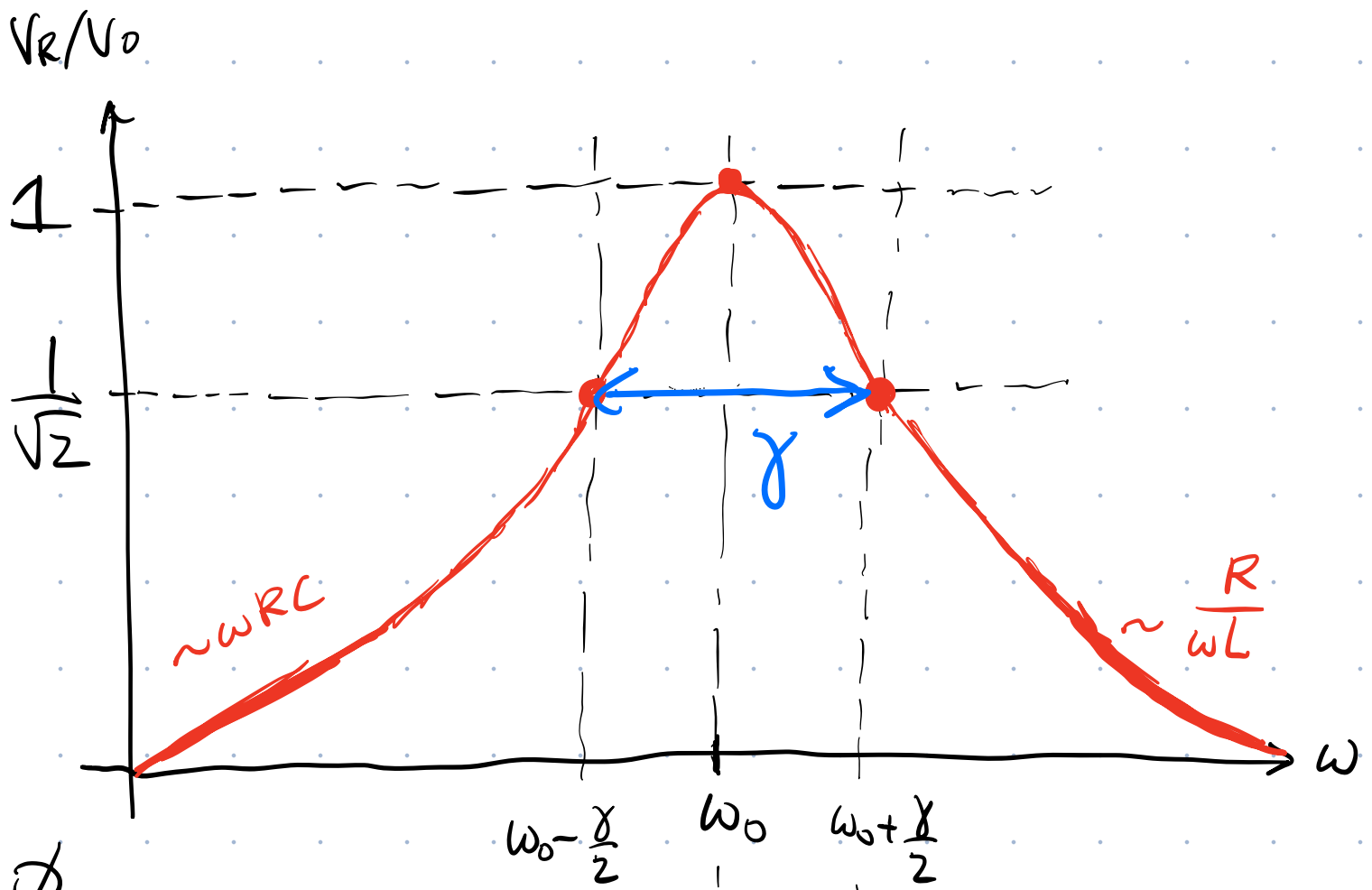
$$\Rightarrow \phi \rightarrow -\frac{\pi}{2}$$



$\omega \rightarrow 0$ case

$$\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}} \approx \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

$$\approx \frac{1}{\frac{1}{\omega RC}} = \omega RC \quad (\text{linear})$$

$\omega \rightarrow \infty$ case

$$\tan \phi = \frac{\omega L}{R} - \frac{1}{\omega RC} \approx \frac{\omega L}{R}$$

$$\Rightarrow \phi = +\frac{\pi}{2}$$

$$\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}} \approx \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \approx \frac{R}{\omega L}$$

Resonance condition

Start w/
$$\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$

The ratio $\frac{V_R}{V_0}$ is a maximum when $\left(\frac{\omega_0 L}{R} - \frac{1}{\omega_0 RC}\right) = 0$

The maximum occurs when $\omega = \omega_0$, where $\omega_0 = 2\pi f_0$ is the resonance freq.

$$\omega_0 \frac{L}{R} - \frac{1}{\omega_0 RC} = 0 \quad \text{solve for } \omega_0:$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

At $\omega = \omega_0$

$$\frac{V_R}{V_0} = \frac{1}{\sqrt{1 + (0)^2}} = 1$$

$$\tan \phi = \left(\frac{\omega_0 L}{R} - \frac{1}{\omega_0 RC}\right) = 0 \Rightarrow \phi = 0 \quad \text{when } \omega = \omega_0$$

Last case: $\omega = \omega_0 \pm \frac{\gamma}{2}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

when $\omega_0 \gg \gamma$ (underdamped case)


$$\gamma = \frac{R}{L}$$

Challenge for the student.

Show that when $\omega = \omega_0 \pm \frac{\gamma}{2}$

$$\frac{V_R}{V_0} = \frac{1}{\sqrt{2}} \quad \tan \varnothing = \pm 1 \Rightarrow \varnothing = \pm \frac{\pi}{4}$$

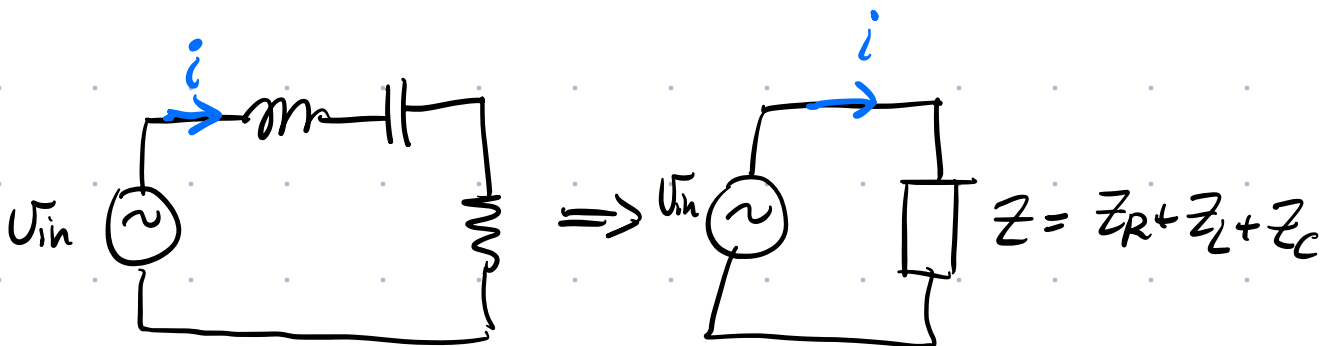- Why does $\frac{V_R}{V_0} \sim \omega RC$ at low freq? ✓
- Why does $\frac{V_R}{V_0} \sim \frac{R}{\omega L}$ at high freq? ✓
- Why is $\varnothing = 0$ when $\omega = \omega_0$?



$$i = \frac{V_m}{Z}$$

$$V_R = iR = V_m \frac{R}{Z}$$

$$\therefore \frac{V_R}{V_m} = \frac{R}{Z} = \frac{R}{Z_R + Z_L + Z_C} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

$\omega \rightarrow 0$ case. In this case $\frac{1}{j\omega C}$ dominates (large)

$$\therefore \frac{V_R}{V_m} \approx \frac{R}{\frac{1}{j\omega C}} = j\omega RC$$

Look at Euler's eq'n:

$$e^{j\phi} = \cos \phi + j \sin \phi$$

consider $\phi = \pi$

$$e^{j\pi} = \underbrace{\cos \pi}_{-1} + j \underbrace{\sin \pi}_0 \Rightarrow e^{j\pi} = -1$$

consider $\phi = \frac{\pi}{2}$

$$e^{j\frac{\pi}{2}} = \cancel{\cos \frac{\pi}{2}} + j \underbrace{\sin \frac{\pi}{2}}_1$$

$$e^{j\frac{\pi}{2}} = j$$

$$\therefore \frac{V_R}{V_{in}} = j\omega RC \quad \text{at low freq.}$$

$$\therefore \frac{V_R}{V_{in}} = \omega RC e^{j\pi/2}$$

$$\frac{iR}{V_{in}} = \omega RC e^{j\pi/2}$$

$$\frac{I_0 R e^{j\omega t} e^{-j\phi}}{V_0 e^{j\omega t}} = \omega RC e^{j\pi/2}$$

$$\frac{V_R}{V_0} e^{-j\phi} = \omega RC e^{j\pi/2}$$

High Freq case $\omega \rightarrow \infty$

$$\frac{V_R}{V_{in}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \approx \frac{R}{j\omega L} = \frac{R}{\omega L} e^{-j\pi/2}$$
$$= \frac{R}{\omega L} e^{-j\pi/2}$$

$\frac{V_R}{V_o} = \frac{R}{\omega L} \quad \phi = \pi/2$

 ω large.

When $\omega = \omega_0$

$$j(\omega_0 L - \frac{1}{\omega_0 C}) = 0$$

resonance condition.

$$\frac{V_R}{V_{in}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R} = 1 (e^{j0})$$

$= 0$ when $\omega = \omega_0$

$$\frac{V_R}{V_o} e^{-j\phi} = 1 e^{j0} \Rightarrow \frac{V_R}{V_o} = 1 \quad \phi = 0$$