

Assignment #3 on course website

Complex Numbers.


$$z = x + jy = |z|e^{j\phi}$$

$$x = |z| \cos \phi$$

$$y = |z| \sin \phi$$

$$|z| = \sqrt{x^2 + y^2}$$

$$\tan \phi = \frac{y}{x}$$

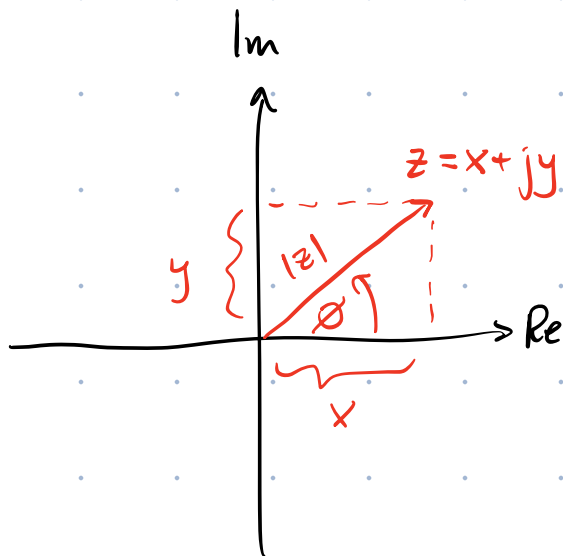

One more definition: The complex conjugate z^*

$$\text{If } z = x + jy = |z|e^{j\phi}$$

$$\text{then } z^* = x - jy = |z|e^{-j\phi} \quad (\text{replace all } j\text{'s w/ } -j)$$

\Rightarrow reverse sign in front of all j 's when taking complex conjugate.

$$\begin{aligned}
 \text{Consider } z z^* &= (x + jy)(x - jy) \\
 &= x^2 - \cancel{jxy} + \cancel{jxy} - \underbrace{j^2 y^2}_{+1} \\
 &= x^2 + y^2 = |z|^2
 \end{aligned}$$

$\therefore z z^* = |z|^2$ square of the mag.
or length of z .

Analogous to finding length of

$$\vec{V} = V_x \hat{i} + V_y \hat{j}$$

$$|\vec{V}|^2 = \vec{V} \cdot \vec{V} = V_x^2 + V_y^2$$

$$\begin{aligned}
 \text{What } z z^* &= \underbrace{(|z| e^{j\theta})}_z \underbrace{(|z| e^{-j\theta})}_{z^*} \\
 &= |z|^2
 \end{aligned}$$

Another use for the complex conjugate.

→ remove j 's from denominator of a fraction.

Take $z = \frac{z_1}{z_2}$

want to find
 $z = x + jy$

given that

$$z_1 = s + jt$$

$$z_2 = u + jv$$

$$\therefore z = \frac{s + jt}{u + jv}$$

want to find x & y
for $z = x + jy$.

Want to remove j from denominator.

$$z_2 = u + jv, \quad z_2^* = u - jv$$

Mult. top & btm of our fraction by z_2^*


$$z = \frac{(s+jt)(u-jv)}{(u+jv)(u-jv)} = \frac{(su - \overset{+1}{j^2}tv) + jtu - jsv}{u^2 + v^2}$$

$$z = x + jy = \frac{(su + tv) + j(tu - sv)}{u^2 + v^2}$$

$$x = \frac{su + tv}{u^2 + v^2}$$

$$y = \frac{tu - sv}{u^2 + v^2}$$

Operational Amplifier (Op Amps)

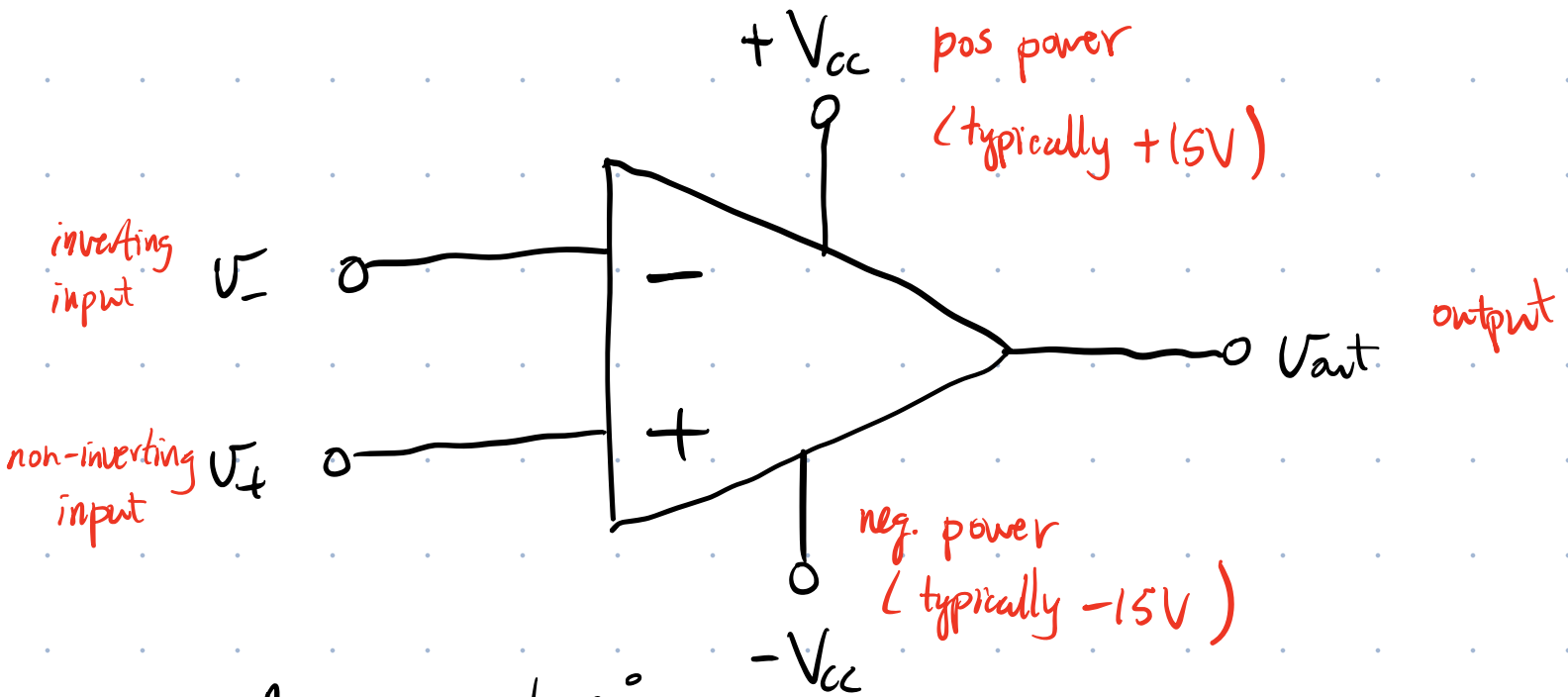

An op amp has:

- two inputs (U_- , U_+)
- one output (U_{out})
- two power terminals

The two inputs U_- & U_+ can each be pos. or neg. voltages.


Treat the op amp as a black-box device that performs the following fun:

$$V_{out} = A_{OL} (V_+ - V_-)$$

↑
"open-loop" gain.

We will use the LM741 op amp in the lab
& it is designed to have an open-loop gain of
about: $A_{OL} \approx 2 \times 10^5$

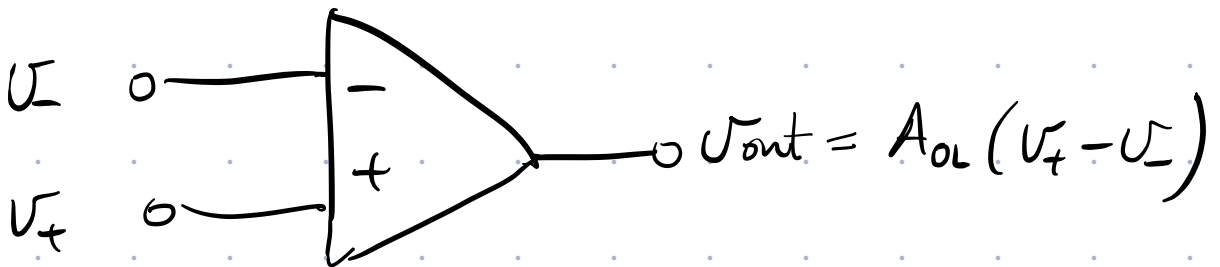In circuit diagrams, the power terminals
 $\pm V_{CC}$ are often omitted from diagrams.
However, the op amp always needs to be
powered to function properly.




Limitations:

saturation voltage

$$(1) \quad |U_{out}| \leq V_{sat} \approx V_{cc} - 1$$

$$\text{If } V_{cc} = 15 \text{ V, } V_{sat} \approx 14 \text{ V.}$$

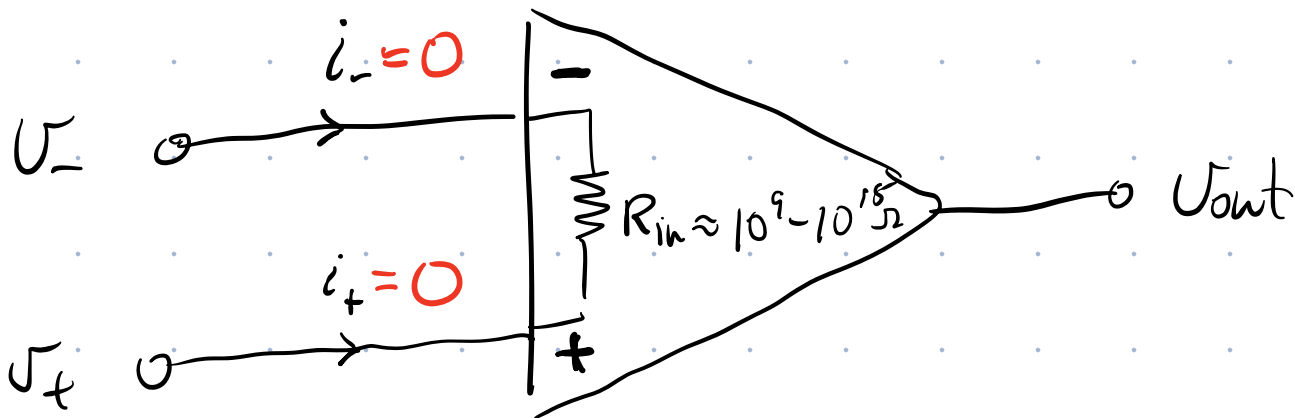(2) The input impedance/resistance of the op amp is very large ($10^9 - 10^{15} \Omega$)



Assume $R_{in} \rightarrow \infty$ s.t. $i_- = i_+ = 0$

No current flows into or out of the op amp inputs.


Note: Output can have non-zero current.

Op Amp Golden Rules

1. Op Amp input impedance $\rightarrow \infty$

$$i_- = i_+ = 0$$

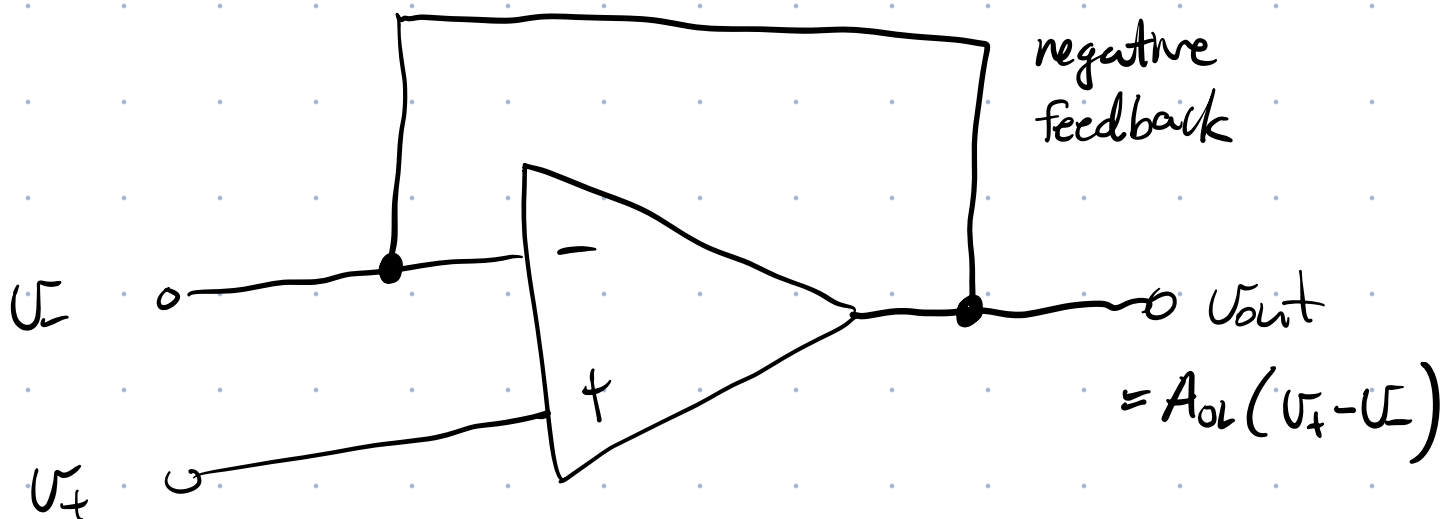2. The second op amp Golden rule applies to op amp circuits using negative feedback



Know $V_{out} = A_{OL} (V_+ - V_-)$

w/ negative feedback, we require:

$$V_{out} = V_-$$

$$V_- = A_{OL} (V_+ - V_-) \quad \text{solve for } V_-$$

$$\therefore V_- + V_- A_{OL} = V_+ A_{OL}$$

$$\therefore V_- (A_{OL} + 1) = A_{OL} V_+$$

$$\therefore V_- = \left(\frac{A_{OL}}{A_{OL} + 1} \right) V_+$$

If $A_{OL} \gg 1$ (always the case)

then

$$V_- = V_+$$

2nd Golden Rule

only true when using negative feedback!

First Op Amp Application: (Lab # 5)

Inverting Amplifier.

