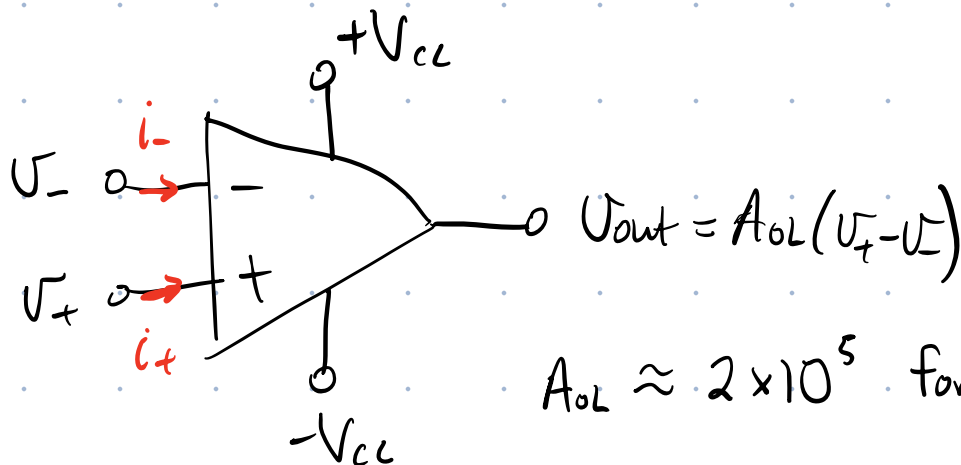


Last Time:

Op Amps:



$$A_{OL} \approx 2 \times 10^5 \text{ for LM741}$$

Op Amp Golden Rules:


$$\textcircled{1} \quad i_- = i_+ = 0$$

No current into or out of op amp inputs

$$\textcircled{2} \quad \text{When using negative feedback,}$$

$$V_- = V_+$$

Inverting Amplifier

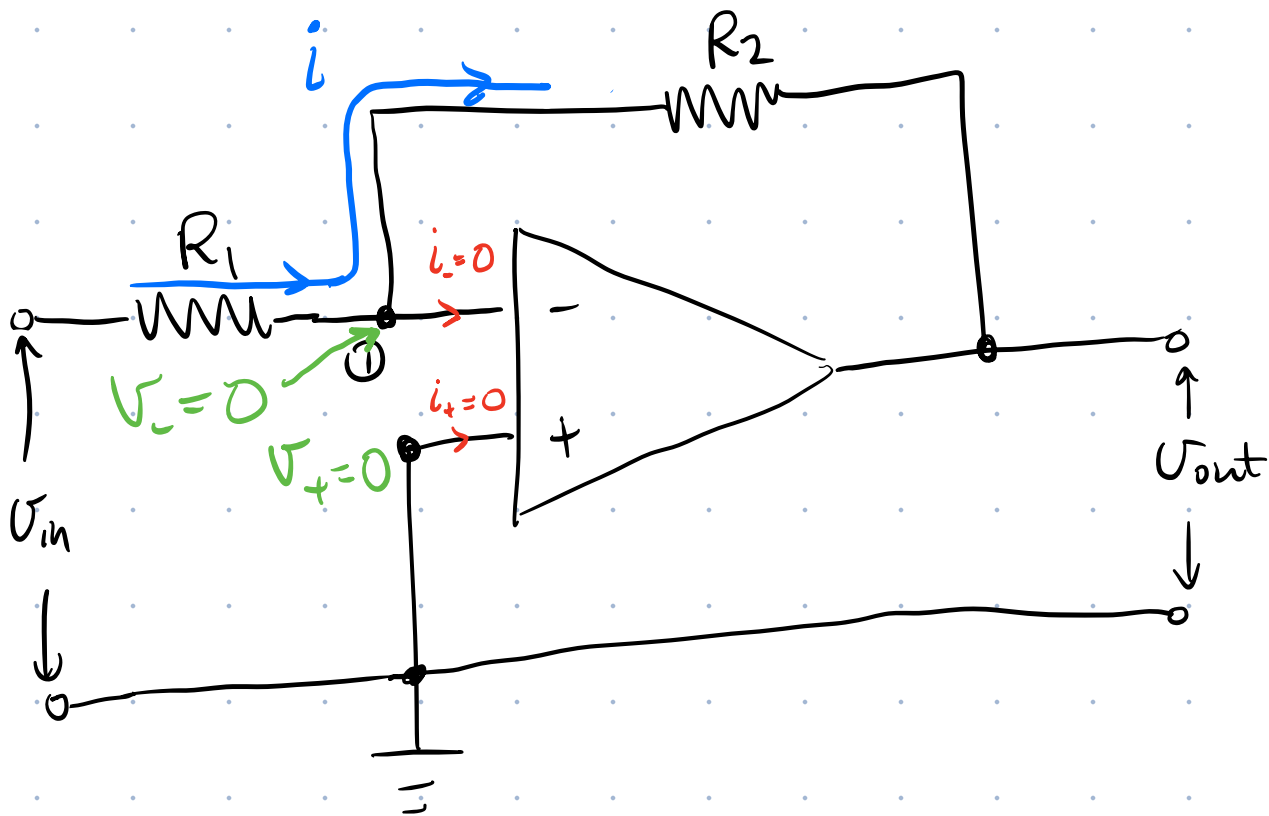

G.R. #1: $i_- = i_+ = 0$

Jan Rule @ ①.

$$i_1 = \cancel{i_-} + i_2 = i_1 = i_2 = i$$

G.R. #2: $V_- = V_+$

B/c V_+ has a direct connect to grid,

$V_+ = 0$. \therefore By G.R. #2 $V_- = 0$

① Track changes in volt. from V_{in} to V_-

$$V_{in} - iR_1 = \cancel{V_-}^0$$

Solve for $i = \frac{V_{in}}{R_1}$

② Track changes in voltage from V_- to V_{out}

$$\cancel{V_-}^0 - iR_2 = V_{out}$$

$$V_{out} = -iR_2 = -\frac{V_{in}}{R_1} R_2$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

"inverting"

$$\therefore \frac{V_{out}}{V_{in}} = G = -\frac{R_2}{R_1}$$

gain

In Lab # 5, you will use $R_2 = 100 \text{ k}\Omega$
 $R_1 = 1 \text{ k}\Omega$

$$\Rightarrow \underline{G = -100}$$


Recall that the opamp can output a maximum of $\pm V_{\text{sat}} \approx \pm 14 \text{ V}$ if $V_{\text{cc}} = \pm 15 \text{ V}$.

$$V_{\text{out, max}} = \pm V_{\text{sat}}$$

$$V_{\text{out}} = -G V_{\text{in}}$$

$$\therefore \text{require } G V_{\text{in}} \leq V_{\text{sat}}$$

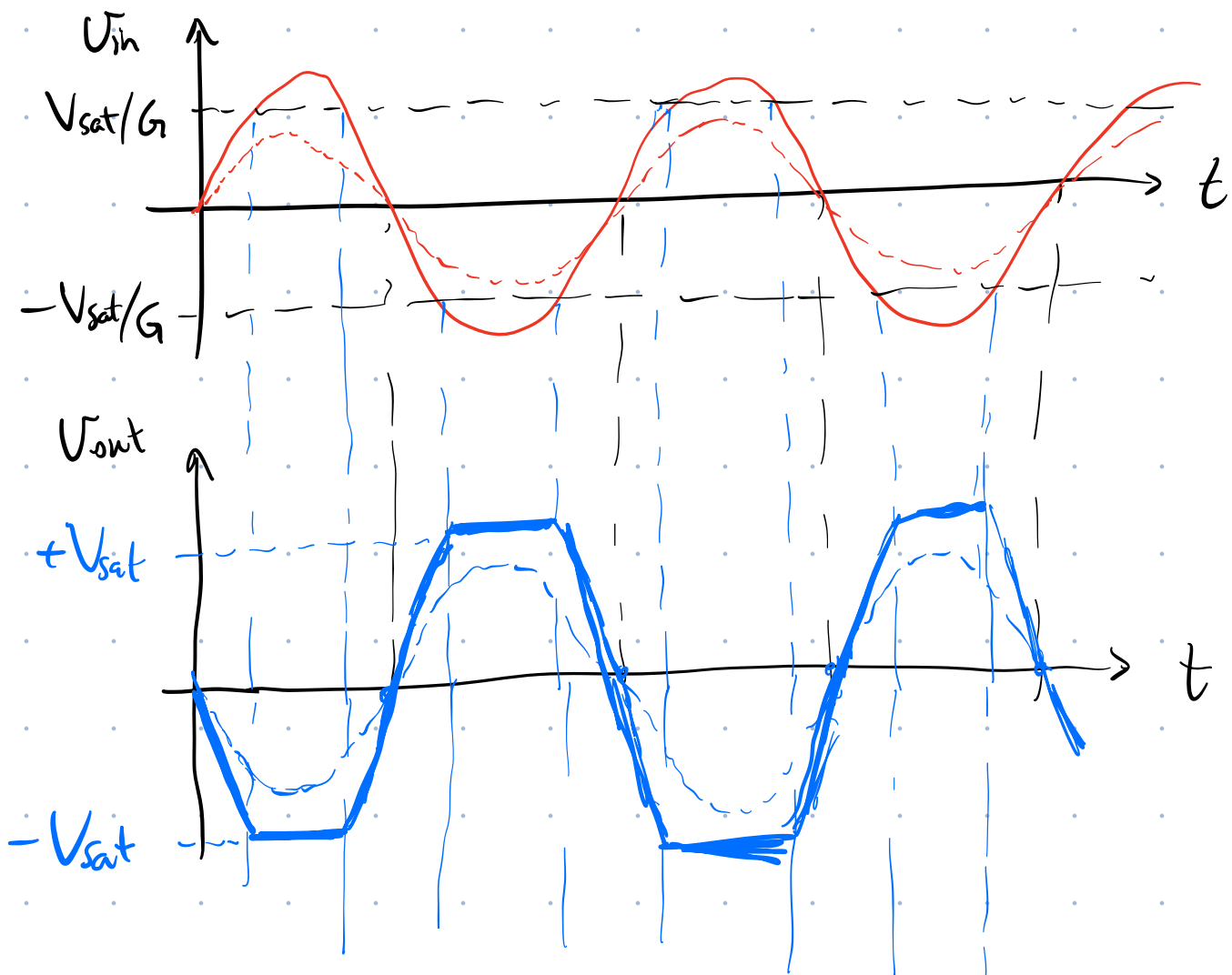
$$V_{\text{in}} \leq \frac{V_{\text{sat}}}{G}$$



saturation of op amp output
"clipping".


Op Amps come packaged as a chip.

Pins 1, 5, 8
we will not use.

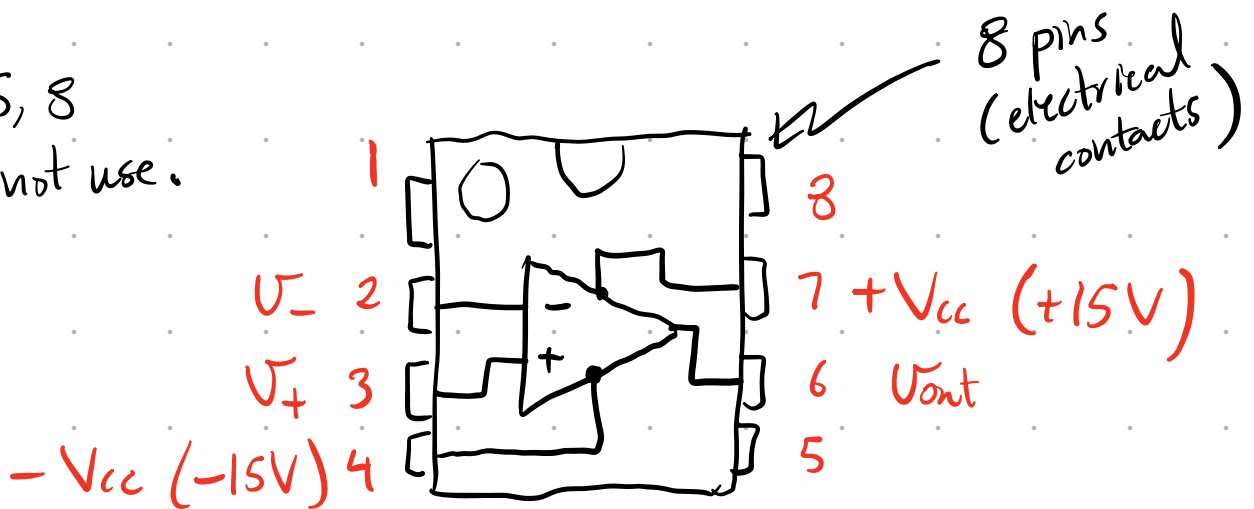


In Lab # 5, we will use a fun gen. to provide $V_{in} = V_{in} \sin(\omega t)$.

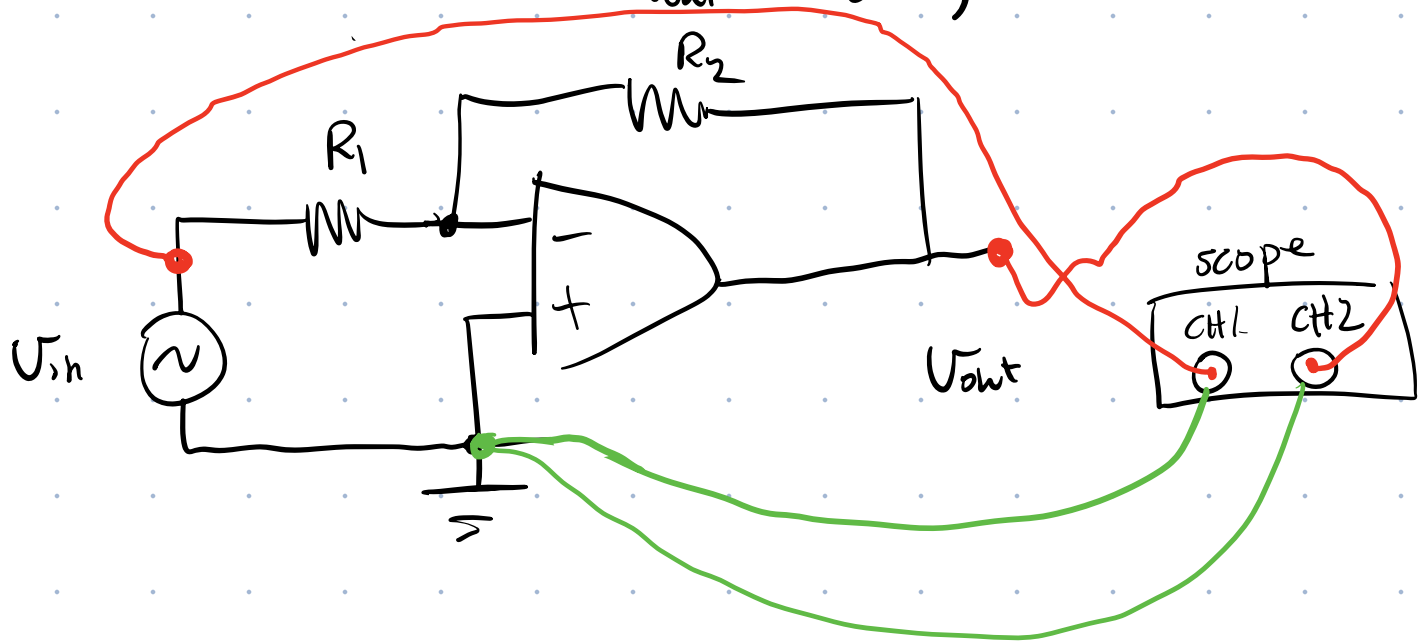Meas. V_{in} & $V_{out} = -V_{out} \sin(\omega t)$



Meas. amplitude of V_{in} (V_{in}) and amp. of V_{out} (V_{out}) as a fun of frequency f .

$$(f = \frac{\omega}{2\pi})$$

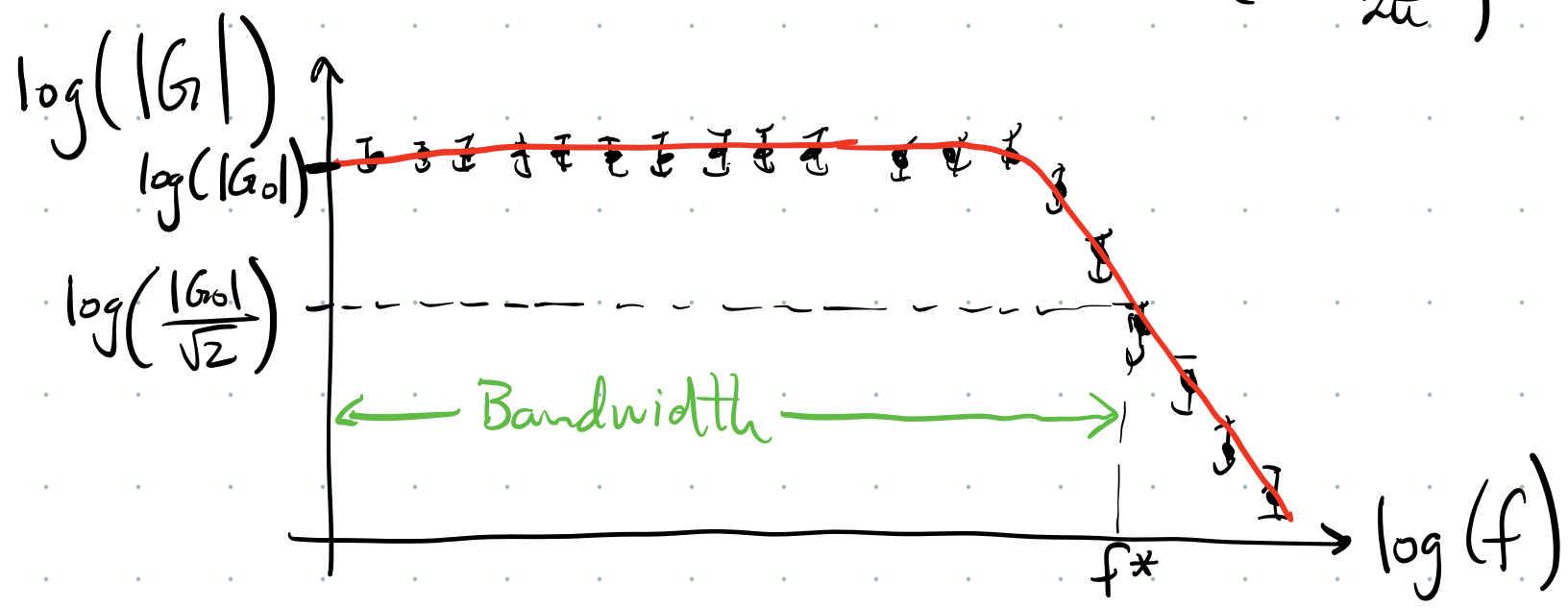


At low enough freq. the $|G| = \frac{V_{out}}{V_{in}}$ is const. (indep. of f).

However, as freq. is increased, eventually reach a point at which the gain decreases.

We define the "bandwidth" of the amplifier as the freq. f^* at which the gain falls to $\frac{1}{\sqrt{2}}$ of the low-freq. value.

The bandwidth (BW) $0 < BW < f^*$ defines the useful freq. range over which the amplifier behaves well.

Another Op amp Application

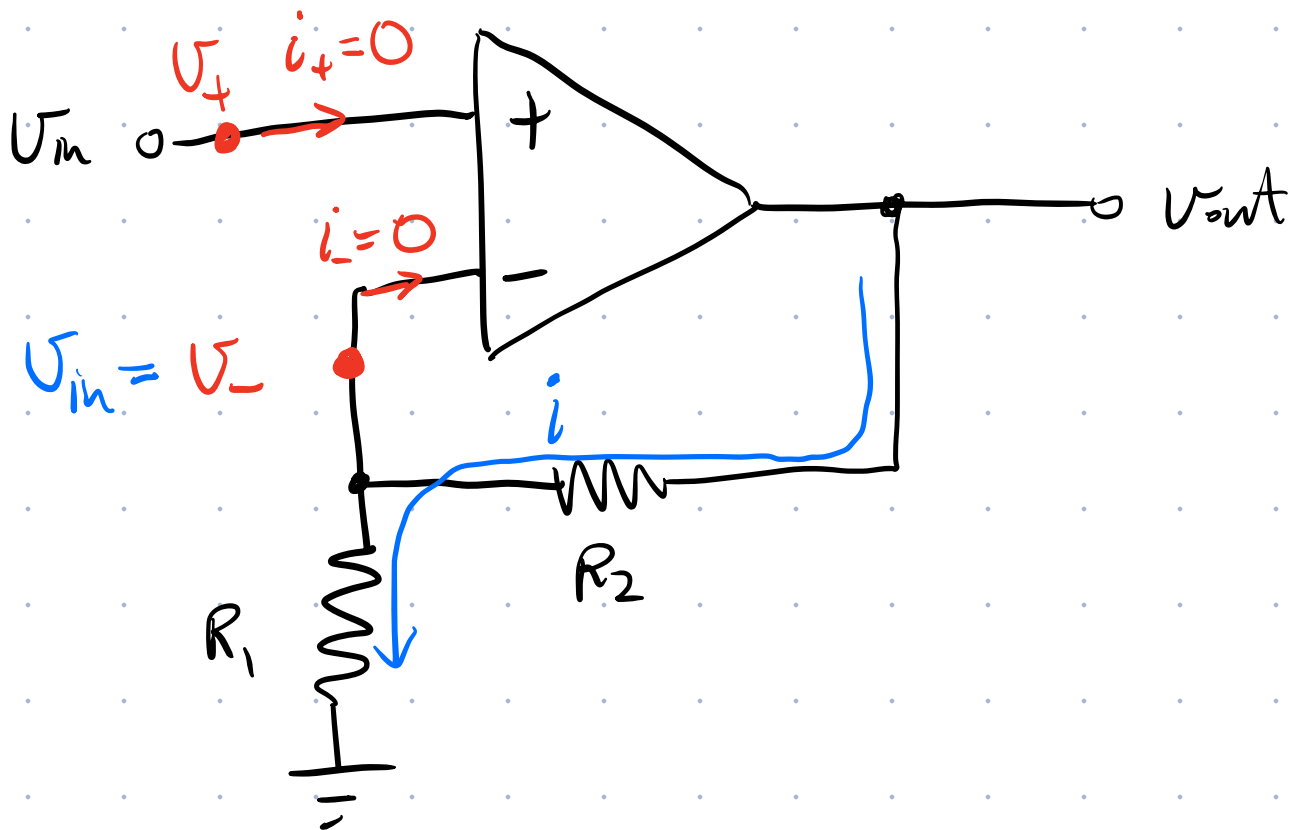

GR #1. $i_- = i_+ = 0 \Rightarrow R_1 \text{ \& } R_2$ have same current i .

GR #2. $U_- = U_+$

$$\boxed{U_+ = U_{in}} \quad \therefore \quad \boxed{U_- = U_{in}}$$

Track volt. changes from V_{in} to gnd.

$$V_{in} - iR_1 = 0 \Rightarrow i = \frac{V_{in}}{R_1}$$

Track volt. changes from V_{out} to gnd.

$$V_{out} - iR_1 - iR_2 = 0$$

$$\therefore V_{out} = i(R_1 + R_2)$$

$$\therefore V_{out} = \frac{V_{in}}{R_1} (R_1 + R_2)$$

$$\therefore V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

Another
amplifier
w/ gain

$$G = 1 + \frac{R_2}{R_1}$$

b/c V_{out} & V_{in} have the same sign,
this is a non-inverting amplifier.

Min. possible gain of ν inverting amp. is $+1$.
non