


Last Time:

Op Amp Golden Rules:

① $i_- = i_+ = 0$
 No current into or out of op amp inputs


② When using negative feedback,
 $V_- = V_+$

Inverting amplifier

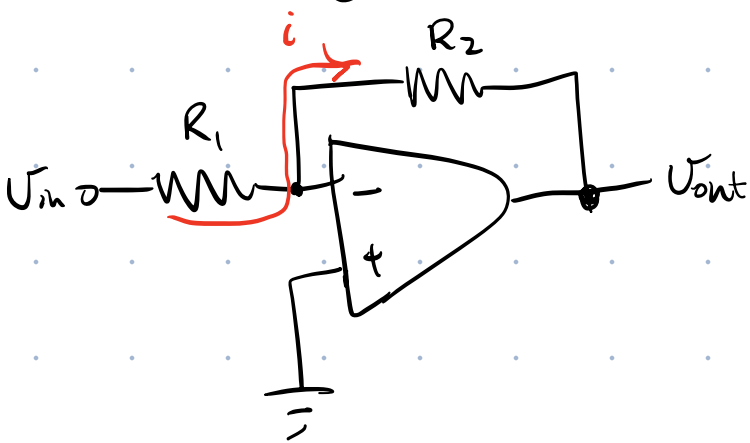


$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Non-inverting amplifier

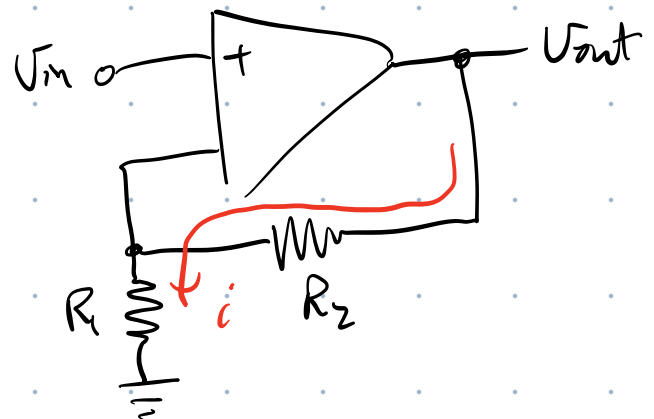

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

Today: Summing Circuit

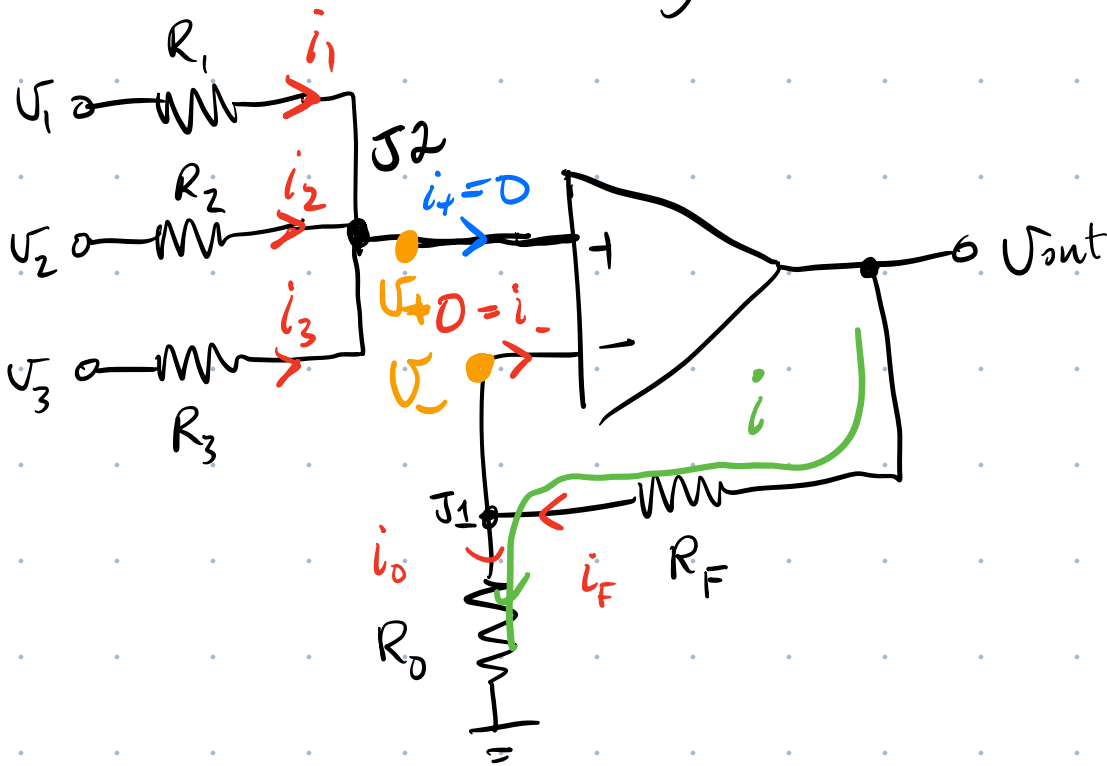

Ken rule @ J1

$$i_F = i_0 + \cancel{i_-} \Rightarrow i_F = i_0 = i$$

$$\text{GR \#1} \quad i_- = i_+ = 0$$

Track changes in volt. from V_{out} to gnd.

$$V_{out} - iR_F - iR_0 = 0$$

$$\Rightarrow i = \frac{V_{out}}{R_F + R_0}$$

At junction J2, KIR:

$$i_1 + i_2 + i_3 = \cancel{i_4} = 0$$

$$i_1 + i_2 + i_3 = 0$$

GR#2 requires when using neg. feedback,

$$V_- = V_+$$

Note that voltage at inverting input is equal to

$$V_- = i R_0 = V_{out} \frac{R_0}{R_0 + R_F}$$

$$\therefore V_+ = V_{out} \frac{R_0}{R_0 + R_F}$$

Finally, track voltage from V_1 to V_+ .

$$V_1 - i_1 R_1 = V_+ \Rightarrow i_1 = \frac{V_1 - V_+}{R_1}$$

Likewise, find $i_2 = \frac{U_2 - U_+}{R_2}$

$$i_3 = \frac{U_3 - U_+}{R_3}$$

Require $i_1 + i_2 + i_3 = 0$

$$\left(\frac{U_1}{R_1} - \frac{U_+}{R_1} \right) + \left(\frac{U_2}{R_2} - \frac{U_+}{R_2} \right) + \left(\frac{U_3}{R_3} - \frac{U_+}{R_3} \right) = 0$$

$$\therefore \left(\frac{U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_3}{R_3} \right) - U_+ \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = 0$$

$$\therefore U_{\text{out}} \frac{R_0}{R_0 + R_F} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \left(\frac{U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_3}{R_3} \right)$$

Solve for U_{out} :

$$U_{\text{out}} = \left(1 + \frac{R_F}{R_0} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \left(\frac{U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_3}{R_3} \right)$$

Here, U_{out} is a "weighted" sum of the input voltages U_1 , U_2 & U_3 .

If we choose $R_1 = R_2 = R_3 = R$

then

$$V_{out} = \left(1 + \frac{R_F}{R_0}\right) \underbrace{\left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R}\right)^{-1}}_{\left(\frac{3}{R}\right)^{-1} = \frac{R}{3}} \frac{1}{R} (V_1 + V_2 + V_3)$$

$$V_{out} = \frac{1}{3} \left(1 + \frac{R_F}{R_0}\right) (V_1 + V_2 + V_3)$$


Now, in this case, V_{out} is proportional to a "direct" sum of inputs V_1 , V_2 & V_3 .

If we not select $\frac{R_F}{R_0} = 2$,

then

$$V_{out} = V_1 + V_2 + V_3$$

Another Example:

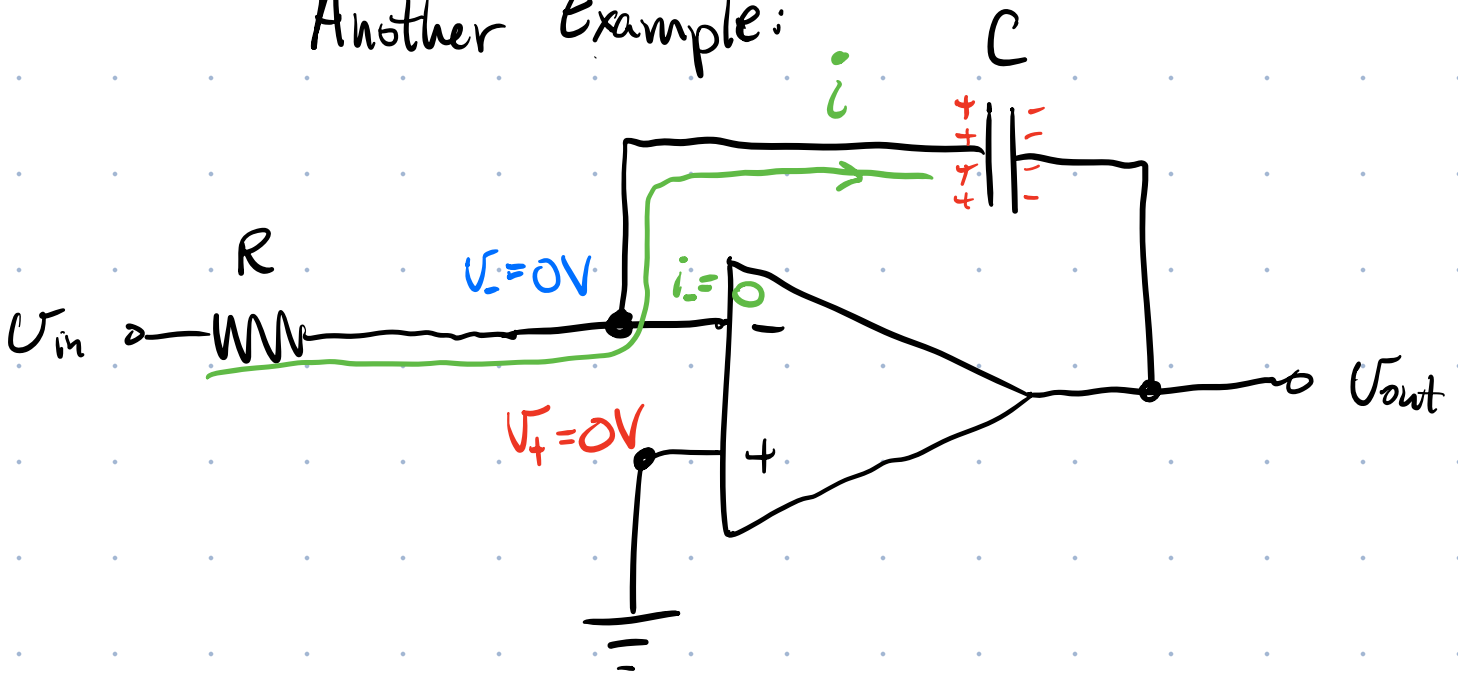

Track volt. changes from U_{in} to U_- .

$$U_{in} - iR = U_- = 0 \Rightarrow i = \frac{U_{in}}{R}$$

Track volt. changes from U_- to U_{out}

~~$$U_- - U_C = U_{out}$$~~

$$U_{out} = -U_C$$

$$= -\frac{q}{C}$$

$$= -\frac{1}{C} \int i dt$$


$$C = \frac{q}{U_C}$$

$$\Rightarrow U_C = \frac{q}{C}$$


$$i = \frac{dq}{dt} \Rightarrow q = \int i dt$$

$$\therefore V_{out} = -\frac{1}{C} \int \frac{V_{in}}{R} dt = -\frac{1}{RC} \int V_{in} dt = V_{out}$$

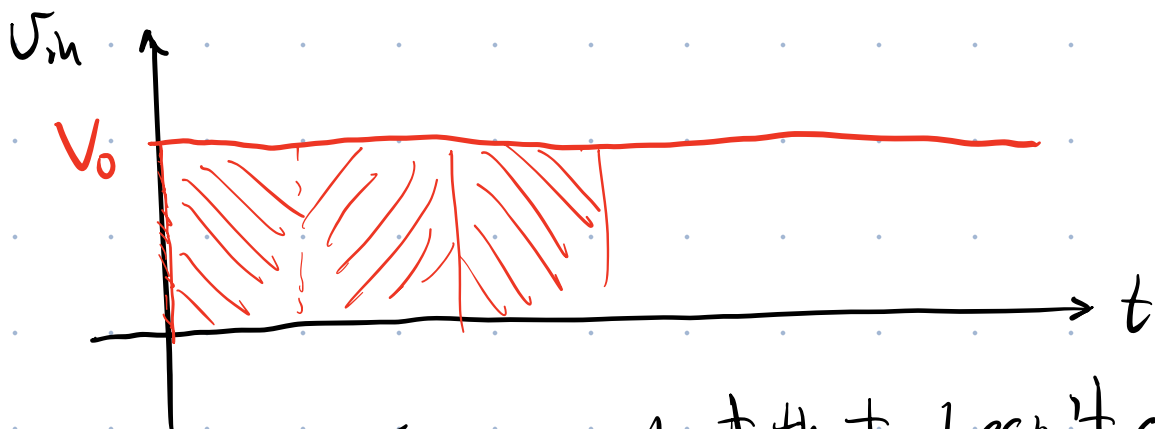Here, V_{out} is prop. to the integral of V_{in} !



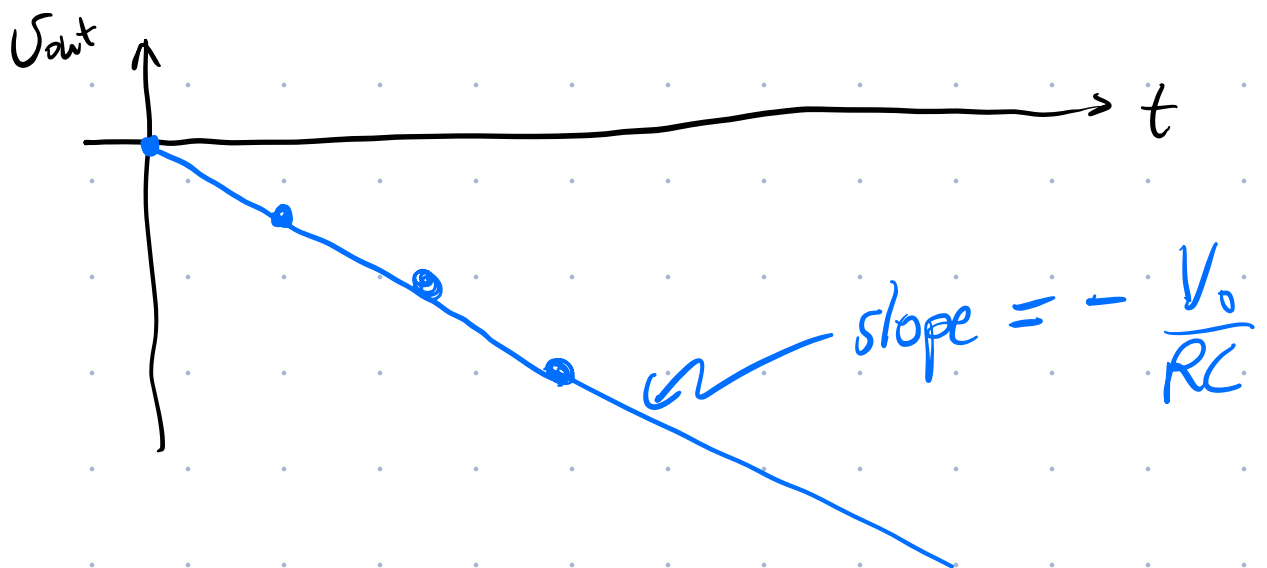V_{in} is a constant that doesn't change with time.




We will use an integrator circuit w/ a const. input voltage as part of your final PHYS 231 project.

$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$$

If $V_{in} = V_0$ (const)

$$\begin{aligned} V_{out} &= -\frac{1}{RC} \int_0^t V_0 dt = -\frac{V_0}{RC} \int_0^t dt \\ &= -\frac{V_0}{RC} t \end{aligned}$$

Change position of R & C.

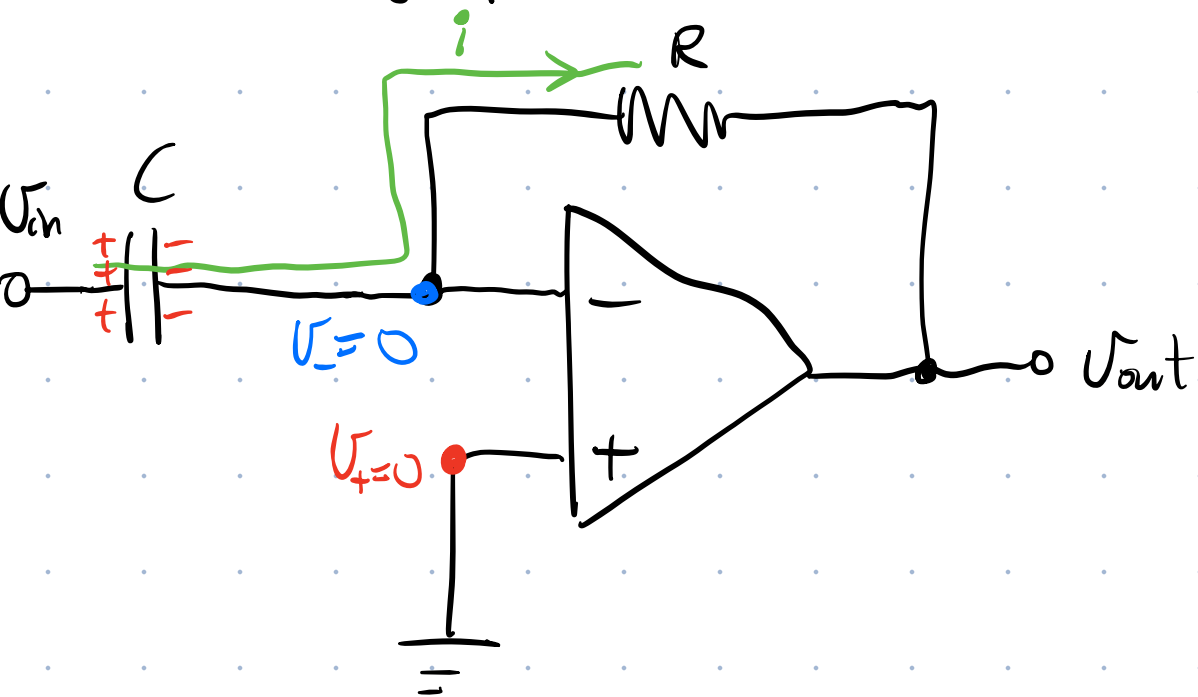

From V_{in} to V_-

$$V_{in} - V_C = V_- = 0$$

$$\therefore V_{in} = V_C = \frac{q}{C}$$

Take the derivative of V_{in} w.r.t. time.

$$\frac{dV_{in}}{dt} = + \frac{1}{C} \frac{dq}{dt} = \frac{i}{C}$$

solve for i :

$$i = C \frac{dV_{in}}{dt}$$

From U to U_{out}

$$\cancel{U} - iR = U_{out}$$

$$\therefore U_{out} = -iR$$

$$\therefore U_{out} = -RC \frac{dU_{in}}{dt}$$

$$U_{out} \propto \frac{dU_{in}}{dt}$$