


Assignment #4 on course website

Due: Nov. 18 @ 13:00


Today: Diodes & Rectifier Circuits

The diode is a semiconductor device that acts as a one-way valve \Rightarrow It passes current in one dir'n, but not the other.

Fluid analogy:

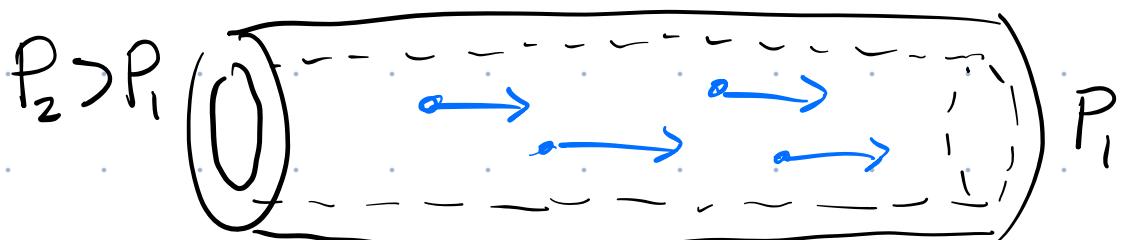

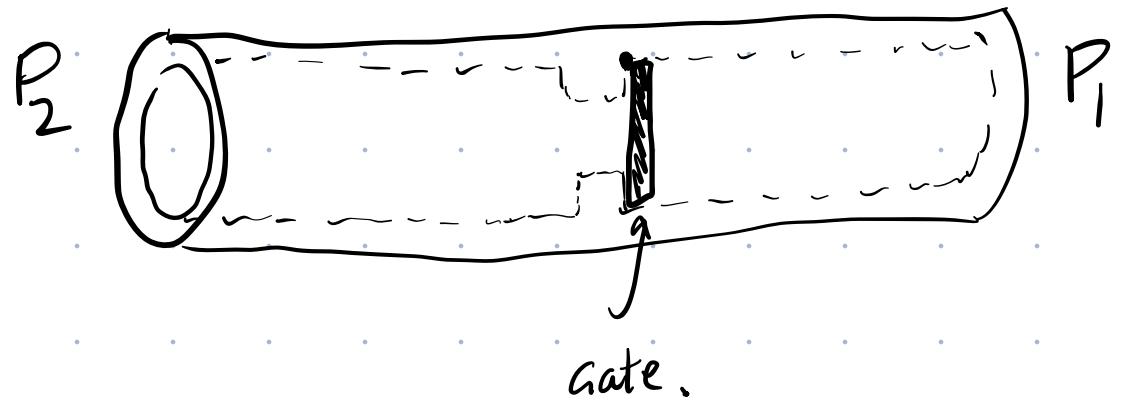To flow fluid through a pipe, need to establish a pressure difference across pipe.
 $\Delta P \Rightarrow$ drive flow of fluid.




If $P_2 > P_1$, fluid flow left-to-right
 { gate is pushed open.

If $P_1 > P_2$, fluid tries to flow right to left, but
 gets block by gate
 \Rightarrow one way valve.

If $P_2 > P_1$, but by just a tiny amount, then
 we don't apply sufficient torque to open gate
 { fluid current will be zero.

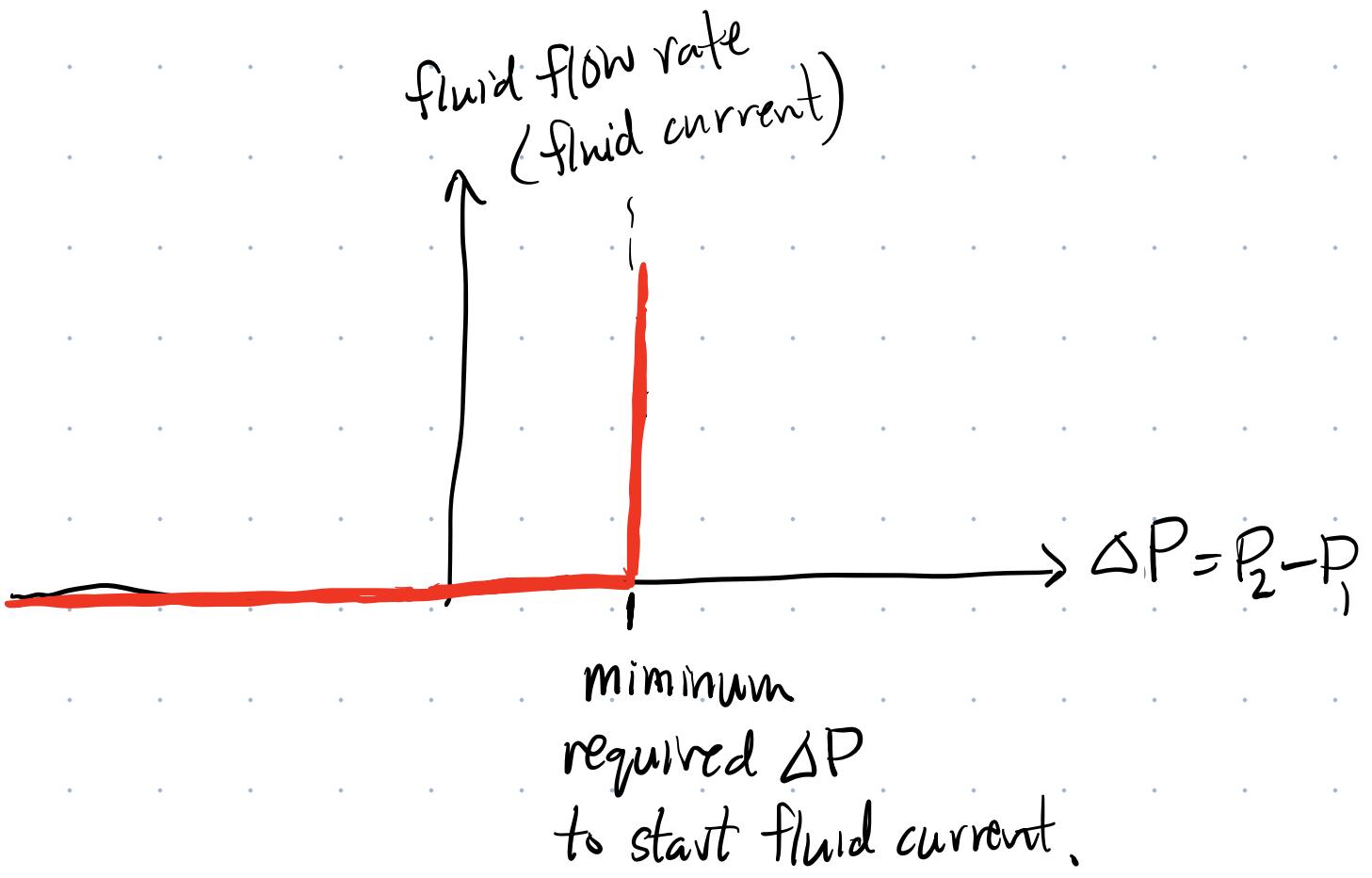Have to overcome a energy barrier to open gate
 { initiate the flow of fluid.



In electronics diodes act as a oneway valve of electric current.




circuit symbol of diode

If $V_a > V_b$, then $I = 0$


If $V_b - V_a > V_{\text{thresh}}$, then $I \neq 0$

Require voltage of p-side to be greater than voltage on n-side by at least $V_{\text{thresh}} \approx 0.7V$ for non-zero current.


Plot I-V characteristic

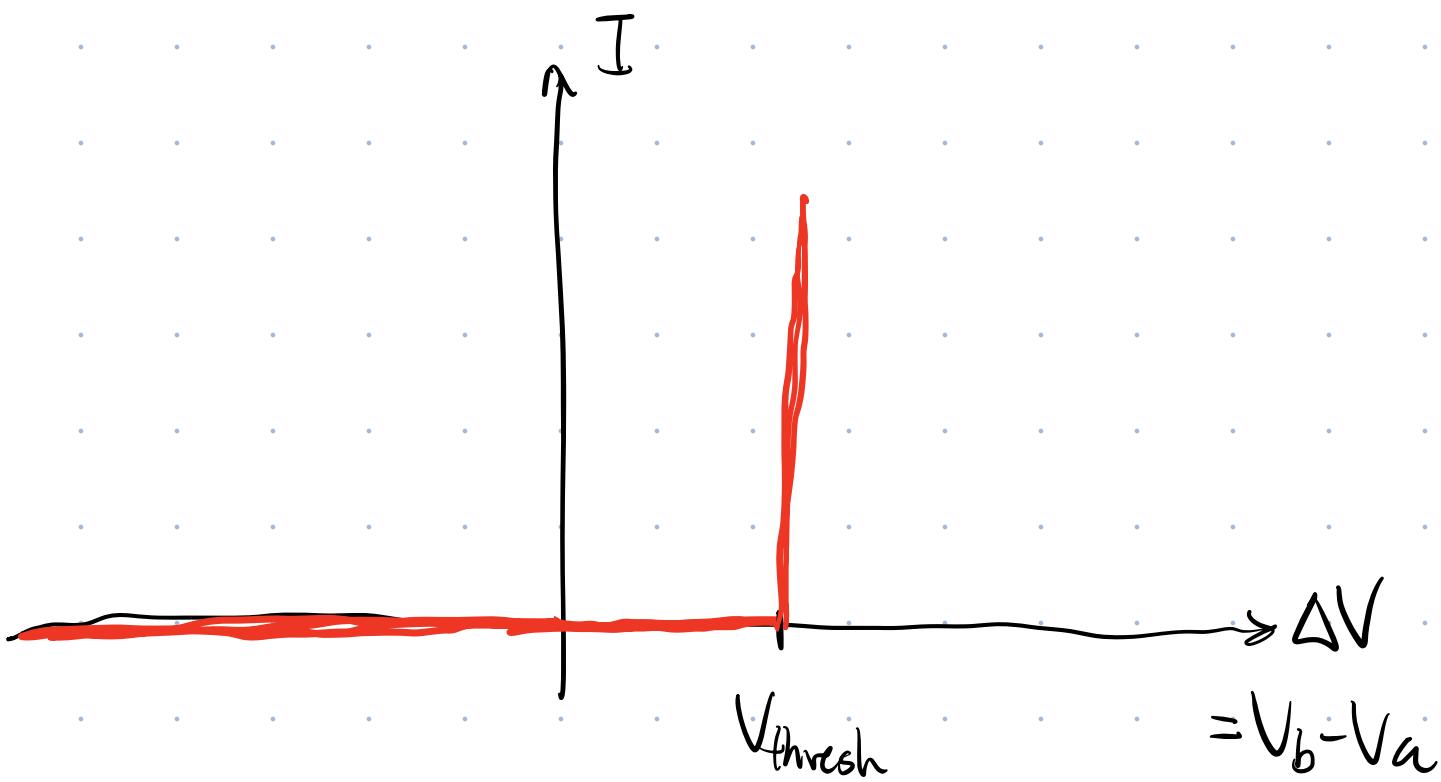

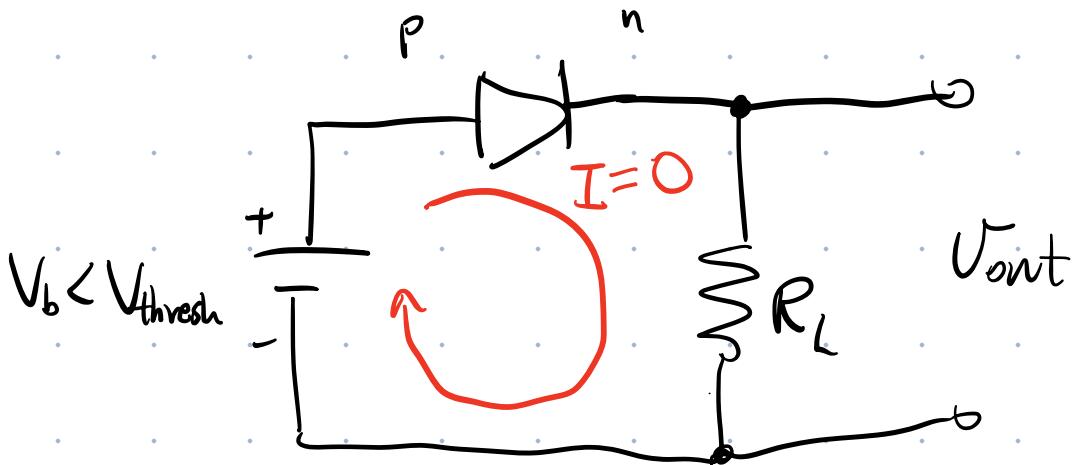Reverse-biased diode $V_b - V_a < V_{\text{thresh.}}$
 (no current)




↓ equiv. circuit

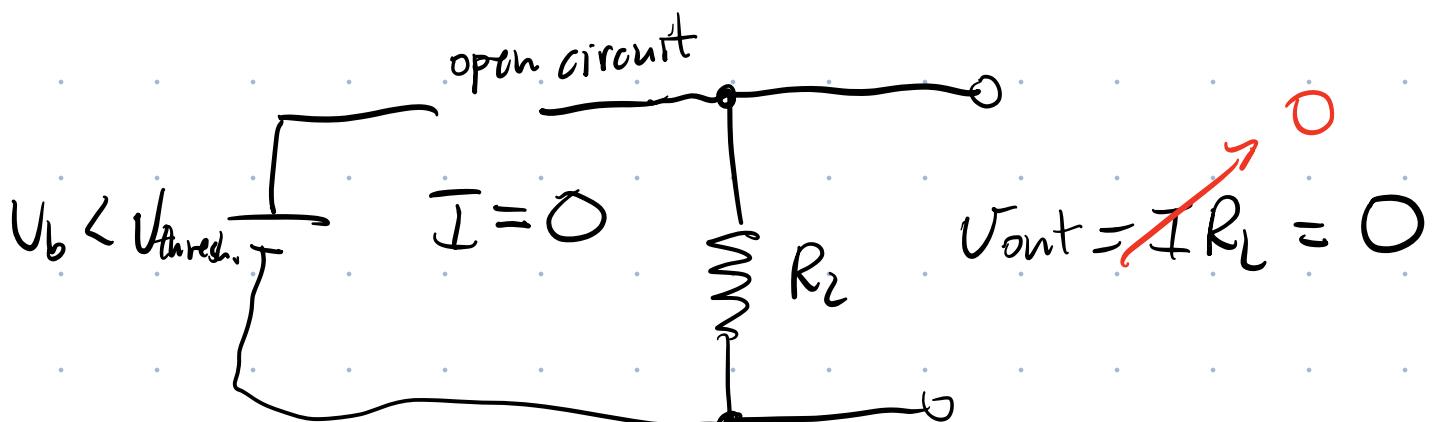


A reverse-biased diode is equiv. to an open circuit.

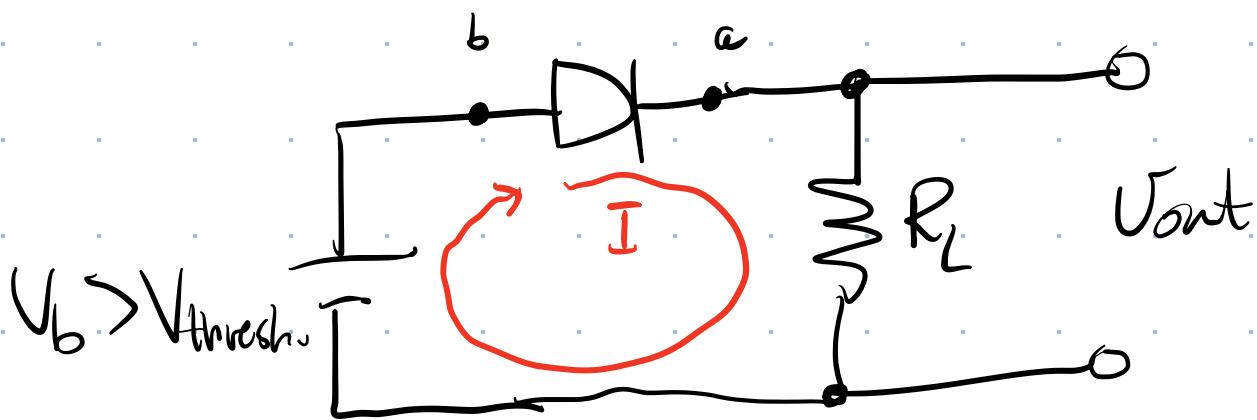Forward Biased diode (diode is "on", $I \neq 0$)



Know that a forward biased diode requires
 $V_b - V_a \approx V_{\text{thresh.}}$

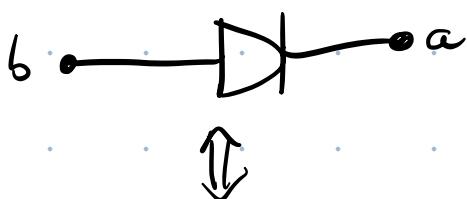In this case, the forward-biased diode acts like
a small battery



Equiv. circuit becomes:




Loop analysis $V_b - V_{\text{thresh.}} - IR_L = 0$

$$\therefore I = \frac{V_b - V_{\text{thresh.}}}{R_L}$$

$$V_{\text{out}} = IR_L = V_b - V_{\text{thresh.}}$$


Rectifier Circuit (AC-to-DC converter)

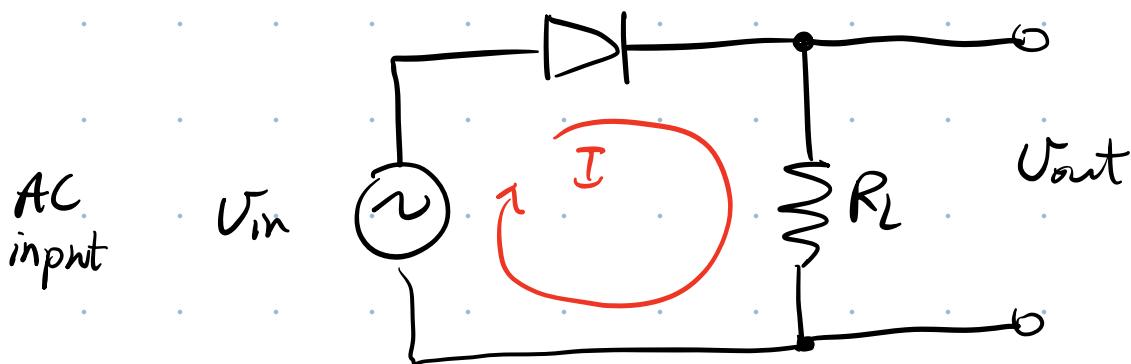

If $V_{\text{in}} < V_{\text{thresh.}}$, $I = 0$, $V_{\text{out}} = 0$ reverse biased


If $V_{\text{in}} > V_{\text{thresh.}}$, $I \neq 0$, $V_{\text{out}} \neq 0$ forward biased.
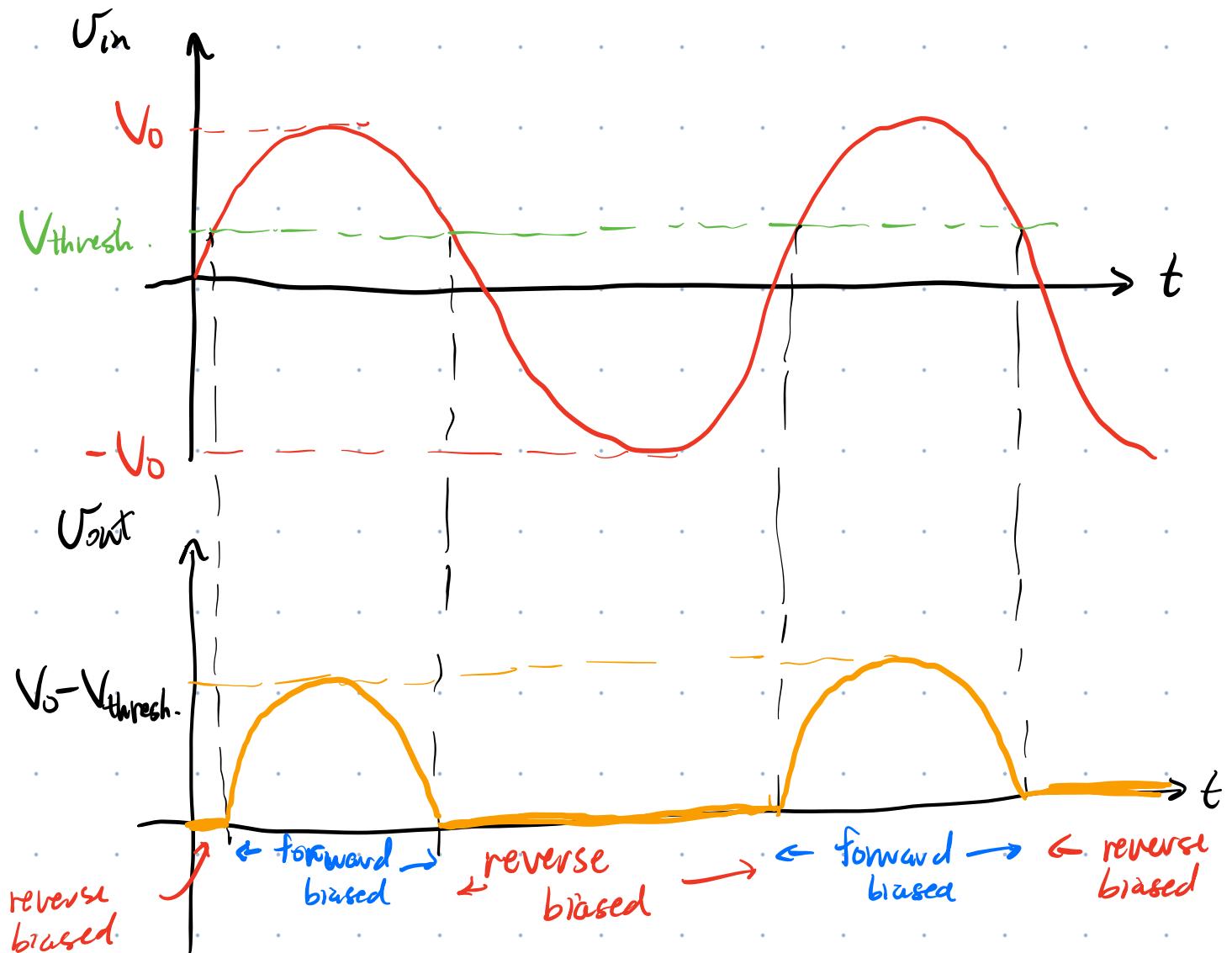
$$V_{\text{out}} = V_{\text{in}} - V_{\text{thresh.}}$$




We've made some progress b/c while $\bar{V}_{in} = 0$,
 $\bar{V}_{out} \neq 0$ (some positive value)

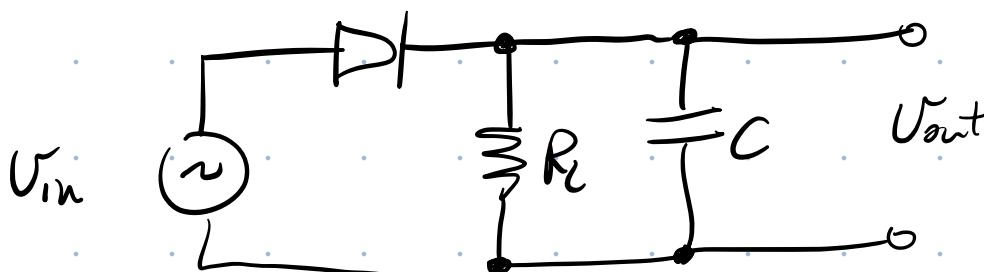To improve our AC-to-DC converter, put a cap. in parallel w/ R_L .




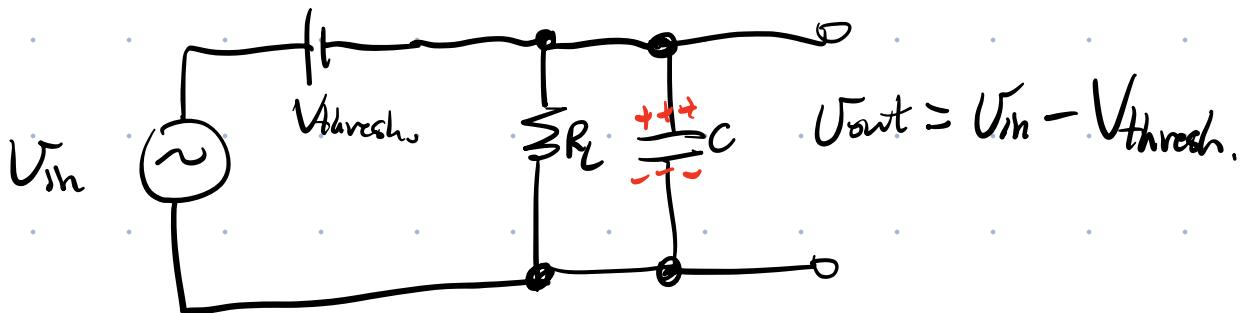The forward biased case doesn't change,
still find $V_{out} = V_{in} - V_{thresh}$.




Cap. C charges to V_{out} while diode is forward biased ($I \neq 0$).

Reverse biased case

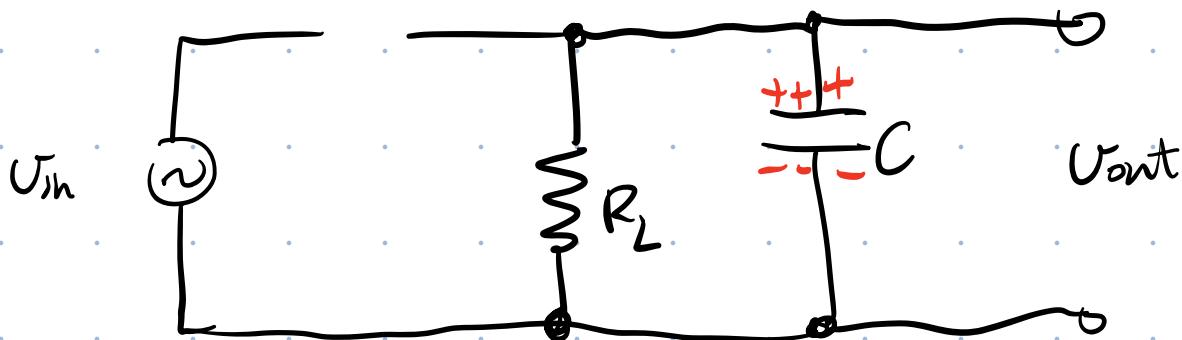

Now, the cap. C discharges through R_L with a time constant $\tau = R_L C$

Choose to make $\tau \gg T$ of V_{in} .

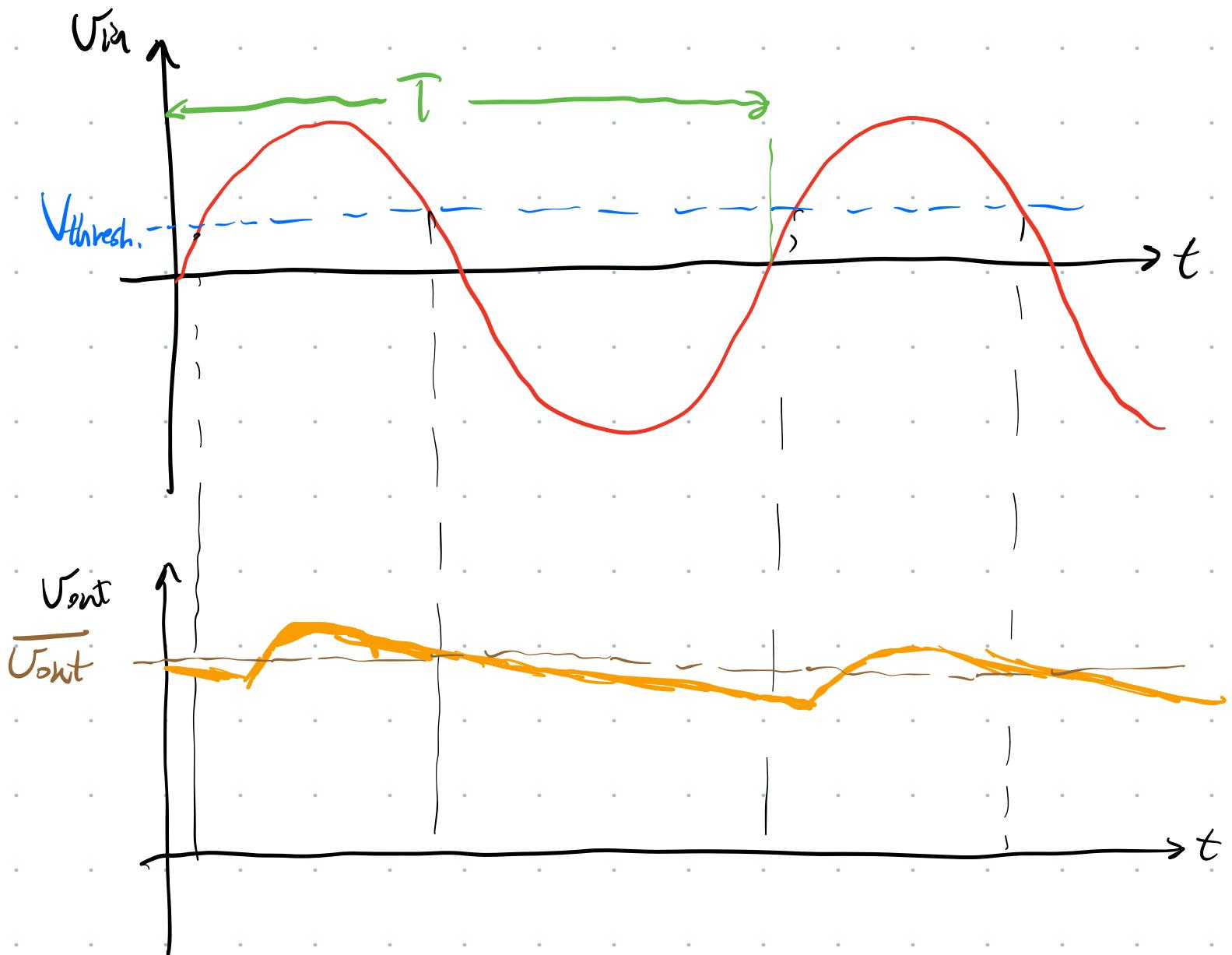

With the cap. in place, $\overline{V_{out}}$ increases & looks more like a constant DC voltage.