

Digital Electronics

In digital electronics, we will work w/ voltages that are in only one of two possible states

$$\begin{aligned} LO &\rightarrow 0 \\ HI &\rightarrow 1 \end{aligned}$$

Typically 0V will correspond to (LO, 0)  
5V " " " (HI, 1)

Digital signals are processed using logic gates.

Types of logic gates:

1. NOT (inverter)



(A logic gate, not an op amp).


## Inverter Truth Table

A	out = $\bar{A}$
0	1
1	0

possible inputs

All possible inputs are listed on left, & corresponding outputs are listed right on

## 2. AND

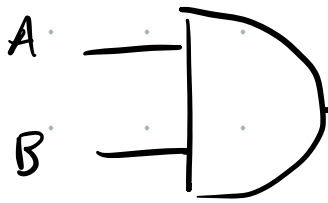

$$\text{out} = A \cdot B$$

read as "A AND B"


logic operation "AND", not multiplication

truth table

A	B	out = A · B
0	0	0
0	1	0
1	0	0
1	1	1

output is 1 unless both A AND B are 1.

## 3. OR gate

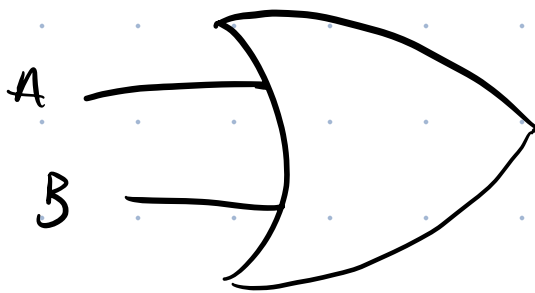

$$\text{out} = A + B$$



logical OR operation, not addition.

read as "A OR B"

Truth table

A	B	out = A+B
0	0	0
0	1	1
1	0	1
1	1	1

#### 4. NAND (NOT AND)

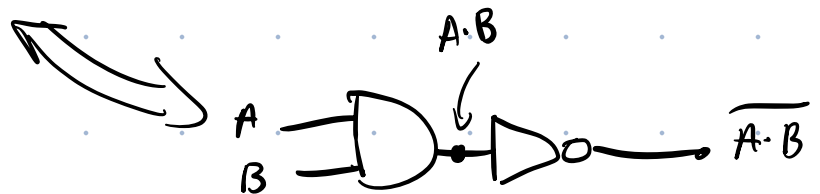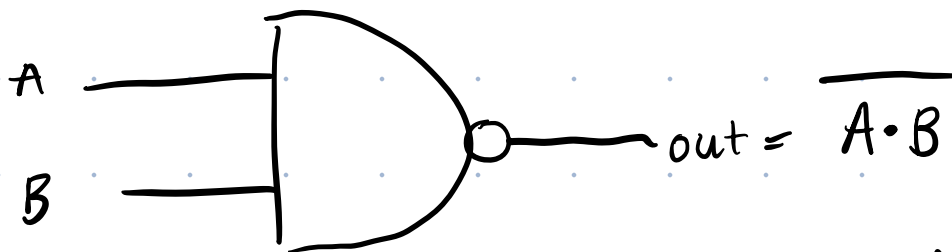


Truth table

A	B	$A \cdot B$	out = $\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Note: All of the other logic gates can be constructed using only NAND gates.  $\therefore$  NAND has become the industry standard.

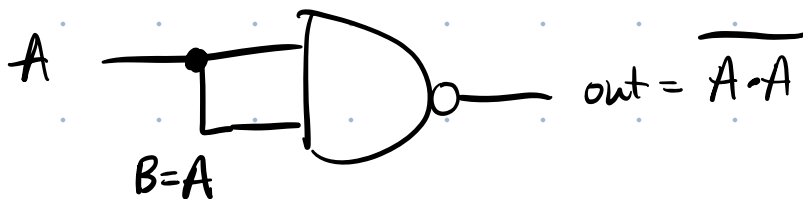Eg. Try connecting A & B inputs of a NAND together.





$A \neq B$

A	B	out = $\overline{A \cdot B}$
0	0	1
<del>0</del>	<del>1</del>	<del>1</del>
<del>1</del>	<del>0</del>	<del>1</del>
1	1	0

$\Rightarrow$

A	out = $\overline{A \cdot A}$
0	1
1	0

truth table of a NOT gate

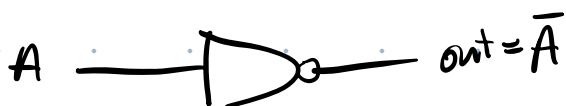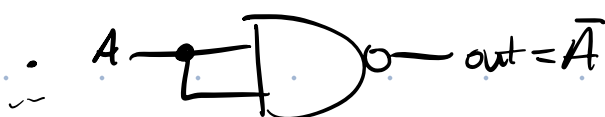

Exercise for the student: Design an OR gate using only NANDs


→ need 3 NANDs to make an OR

→ make use of NOT gate (above)

Exp. #7 on Thursday

Other Logic gates


NOR (NOT OR)

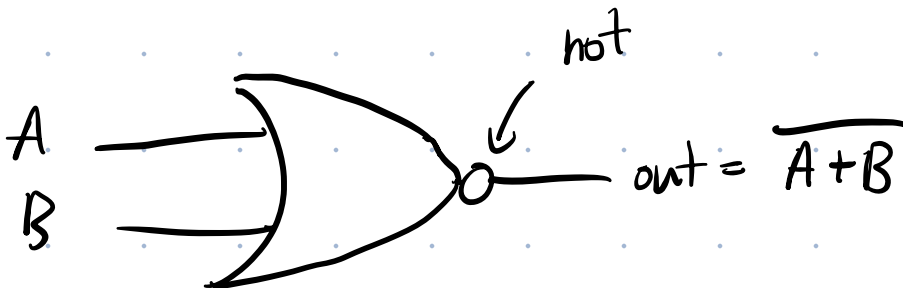

A	B	A+B	out = $\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

# XOR (Exclusive OR)


"exclusive OR" operation.

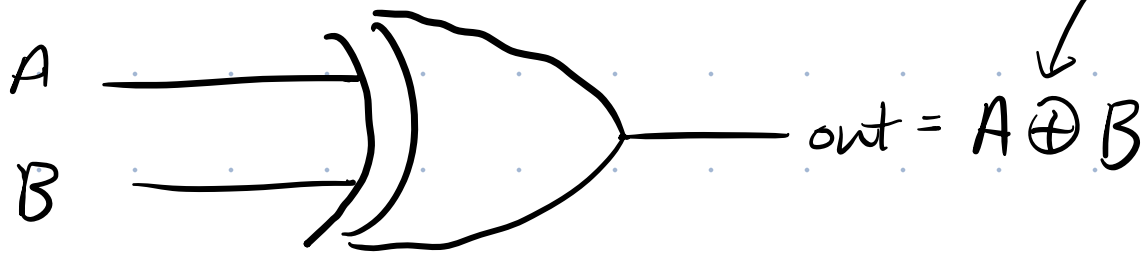

A	B	out = A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

like the OR gate output except the last line is "excluded" from being #1.

# XNOR (NOT Exclusive OR)

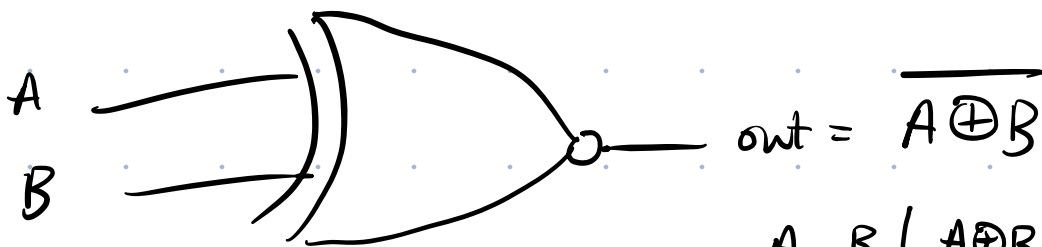


A	B	A ⊕ B	out = $\overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

# Experiment #7 Thursday (Digital Basics).

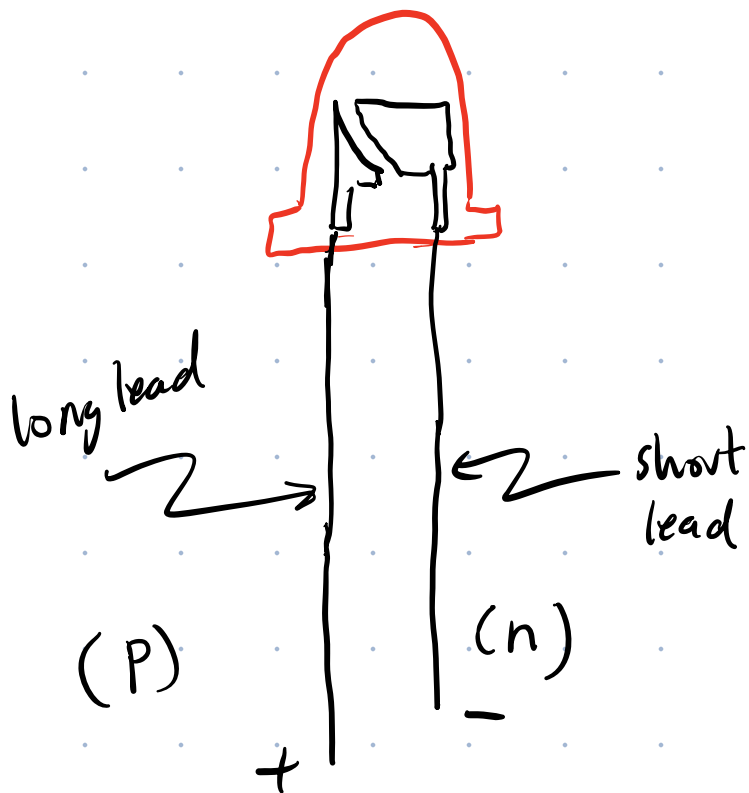Part 1: Test one of the available logic gates.  
(NOT, NAND).


Logic gates require +5V & gnd to operate.  
Check data sheets to identify where +5 & gnd go.

Use light-emitting diode (LED) to monitor  
the output of a logic gate.



when pos. terminal of an LED is higher in volt.  
than the neg. terminal by an amount  $V_{\text{thresh}}$ ,  
LED lights up. ( $\Delta V \sim 2V$ )

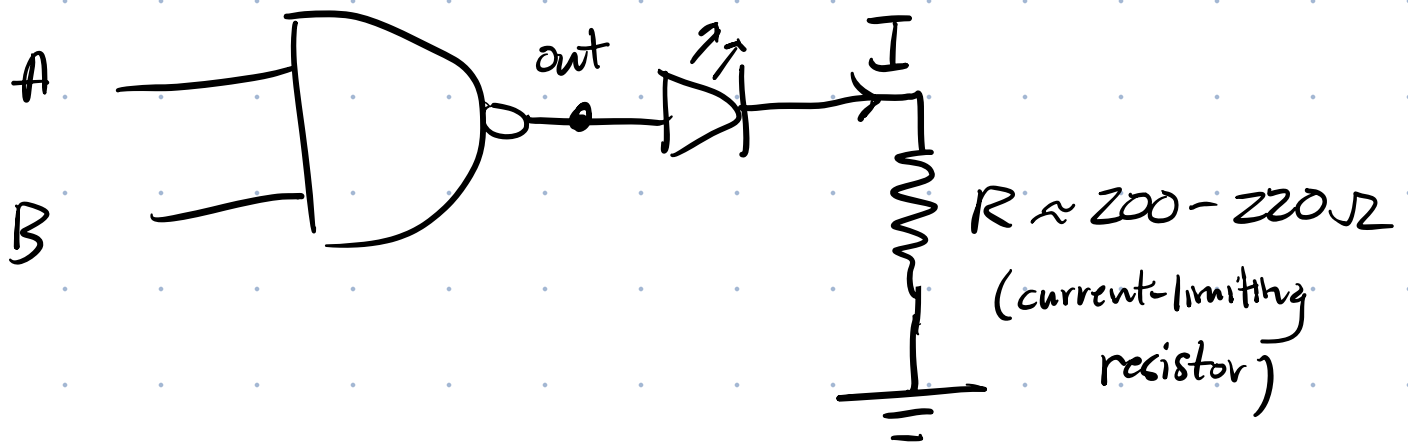To test a logic gate: (NAND, for example)



If  $\text{out} = 5V$ ,

$$\text{then } \therefore 5V - V_{\text{thresh}} - IR = 0$$

$$\therefore I = \frac{5V - V_{\text{thresh}}}{R}$$