 


Last Time:

Logic Gates & Truth tables.

Eg NAND gate



A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


Today: Flip-Flop & Binary Nos.

So far, all logic gate outputs depend on instantaneous states of inputs. Want to design a device that has some memory capability.

R-S Flip Flop
 ↑ ↑
 reset set.

The R-S Flip-Flop is a two-input device (R & S) with two outputs. State of outputs (Q, \bar{Q}) tells the user which of R or S was the last to be LO. That is, the flip flop "remembers" which of the two inputs was last to be LO.

R-S Flip Flop.

 

NAND truth table

What are the possible outputs (Q, \bar{Q})?

$$(Q, \bar{Q}) = (\cancel{0}, \cancel{0}), (0, 1), (1, 0), (\cancel{1}, \cancel{1})$$

0	0	1
0	1	1
1	0	1
1	1	0

Take $(S, R) = (1, 1)$ (i.e. both inputs H) as the default state for inputs.

Cannot have $(Q, \bar{Q}) = (0, 0)$ when $(S, R) = (1, 1)$
 " " " = $(1, 1)$ " " " " "

When $(S, R) = (1, 1)$, output of flip flop has two possible stable states. \Rightarrow output is bistable.

What happens if one of S or R momentarily drops to 0 ?

Case 1: Initial $S=1$ $R=1$ $Q=0$ $\bar{Q}=1$
↓ ↓ ↓ ↓
 0 1 1 0
↓ ↓ ↓ ↓
 1 1 1 0


When S is last to be 0 , $(Q, \bar{Q}) = (1, 0)$.

Case 2: Initial $S=1$ $R=1$ $Q=1$ $\bar{Q}=0$
↓ ↓ ↓ ↓
 0 1 1 0
↓ ↓ ↓ ↓
 1 1 1 0

It is still the case that, when S is last to be 0 , $(Q, \bar{Q}) = (1, 0)$.

Exercise for the student: Show that, regardless of the initial state of (Q, \bar{Q}) , allowing R to go LO temporarily "resets" the output to $(Q, \bar{Q}) = (0, 1)$.

Circuit you will build in Lab # 7 is

 

With the inverters in place, the default state of the input is $(S, R) = (0, 0)$.


Output is determined by which of S or R was last HI.

If S last HI, $(Q, \bar{Q}) = (1, 0)$

If R last HI, $(Q, \bar{Q}) = (0, 1)$

Digital Electronics

Consider the following noisy signal

 

Voltage signal w/ large fluctuations.

- In digital electronics, define a HI (1) as anything greater than threshold 1.
 - Define LO (0) as anything below threshold 2.
 - Signals between thresholds 1 & 2 are undefined.
- ⇒ we get some noise immunity by defining our thresholds for LO & HI signals.
- ⇒ stable digital signals even w/ large volt. fluct.

Binary Nos.

Only 2 digits: 0, 1 (base 2)

Decimal system (base 10) \rightarrow 10 digits (0, 1, 2, ..., 9)

Can represent any base 10 no. in the following way:

$$153_{10} = 1 \cdot 10^2 + 5 \cdot 10^1 + 3 \cdot 10^0$$

base 10

In the same way, we can express binary nos as.

$$\begin{aligned} 10110 &= 1 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0 \\ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 &= 16 + 0 + 4 + 2 + 0 \\ &= 22 \end{aligned}$$

$$10110_2 = 22_{10}$$

Note that $153_{10} = 10011001_2$

8-bit binary no.

0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9

First 10 binary nos.