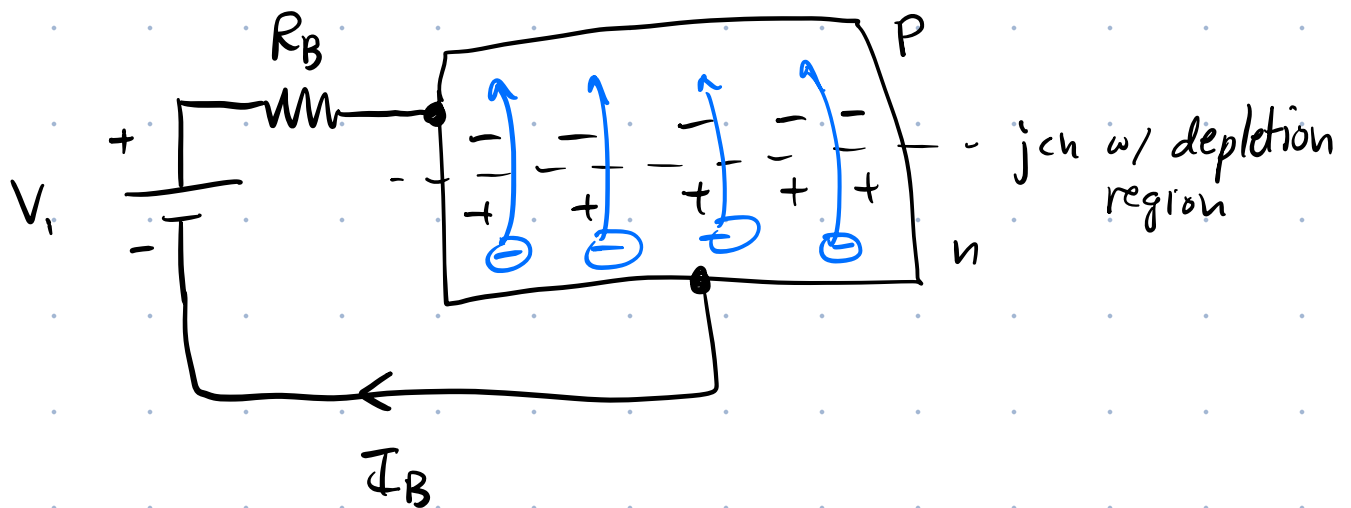


Bipolar Junction Transistor (BJT)


Start w/ a forward biased diode.



IF $V_i \geq V_D \approx 0.7\text{ V}$, get large conduction across jcn.


When making a transistor, n-region is much more heavily doped than p-region \rightarrow most of current is due to flow of e^- .

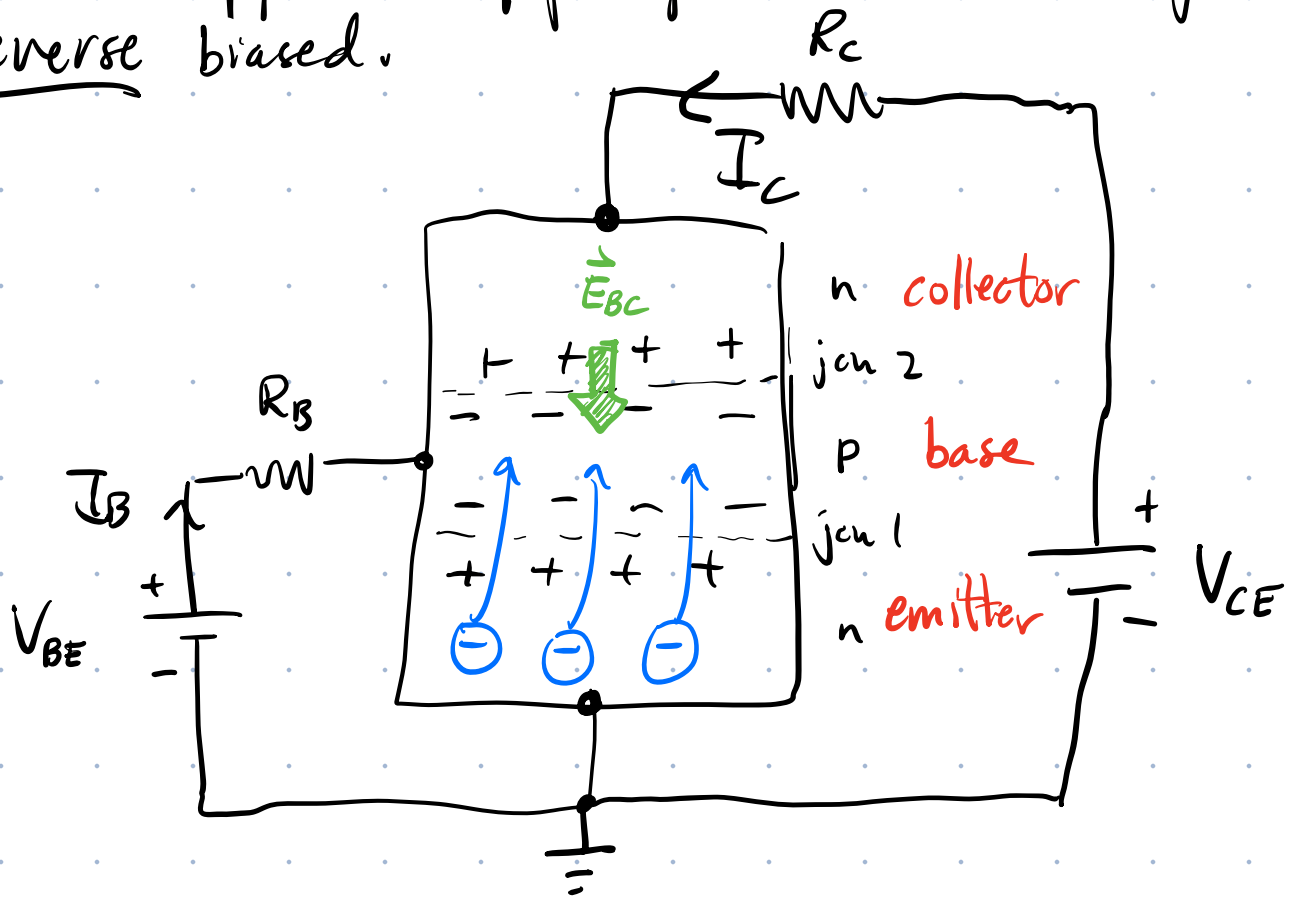To complete the BJT, a second p-n junction is created on opp. side of p-region. This second junction is reverse biased.



Electrons from emitter injected into the base. Those that reach the depletion region of the base-collector are swept across the junction by \vec{E}_{BC} . The base of the transistor is made thin to increase the prob. that e^- reach the base-collector junction.

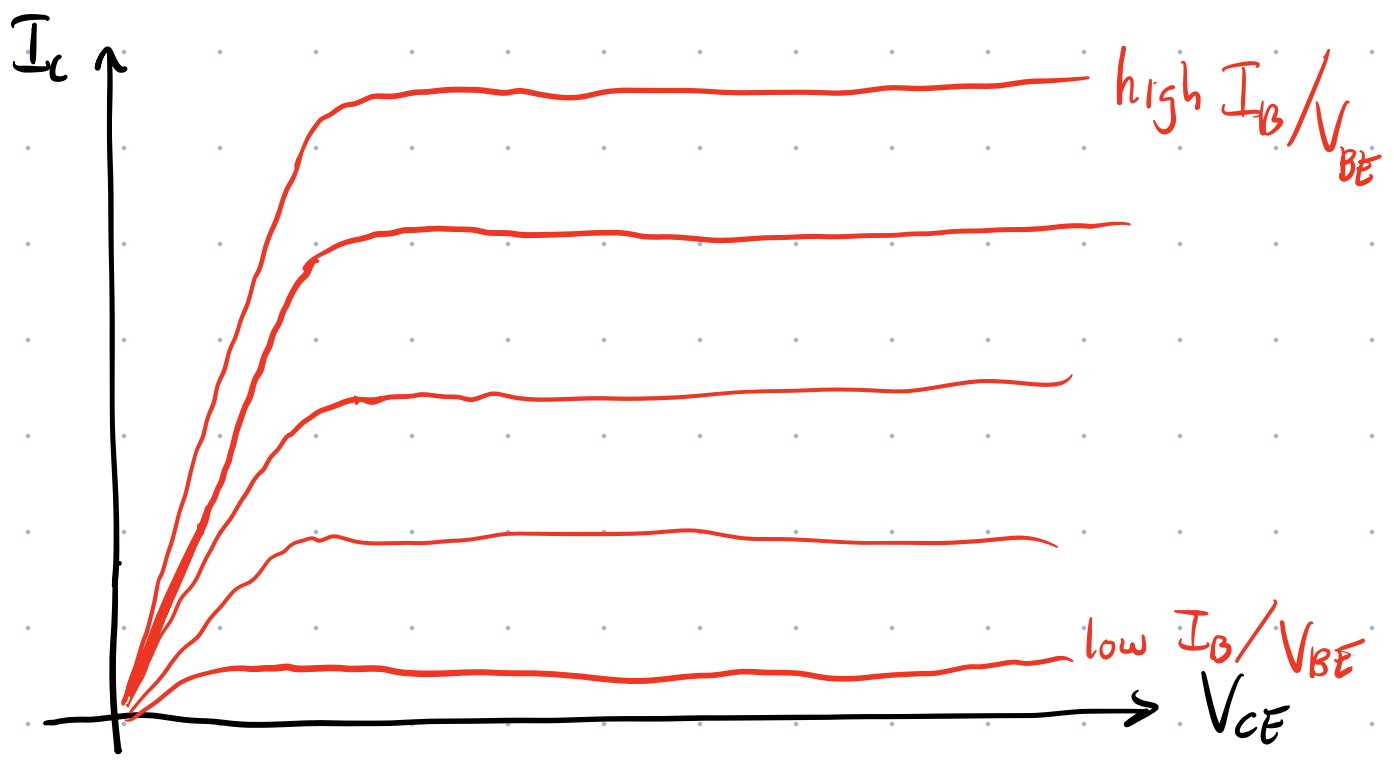Increasing V_{CE} extends the depletion region at base-collector junction which allows more e^- to be swept into the collector which increase I_C .





At some pt., essentially all e^- reach the collector & increasing V_{CE} no longer changes I_C .

Increasing $I_B = \frac{dq}{dt}$ (by increasing V_{BE})

increases the rate that e^- are injected into the emitter &, therefore, increases I_C for all values of V_{CE} .

Transistor circuit symbol (BJT, npn)

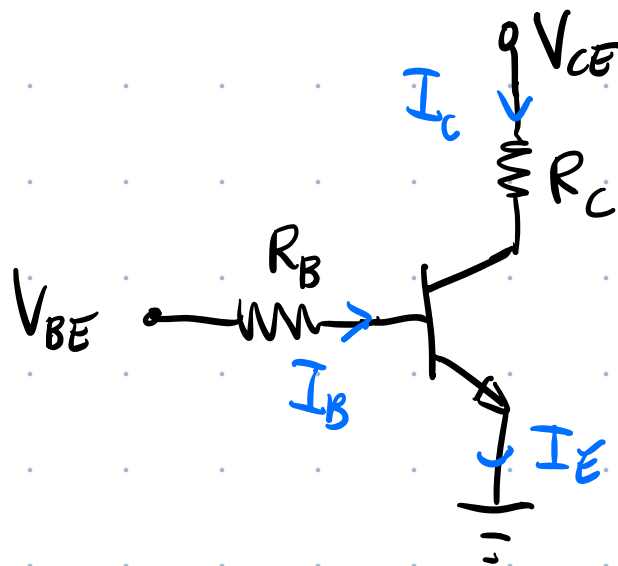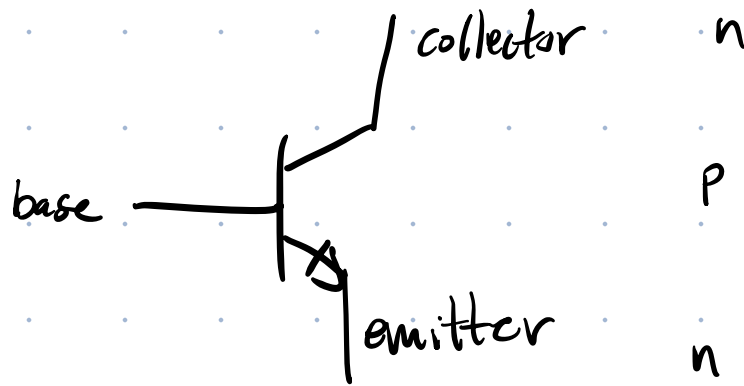

The circuit we've been analyzing above.

Because the base is thin, most e^- from emitter cross into the collector. $\therefore I_B$ is always small.

By jcn rule: $I_B + I_C = I_E$

But since I_B is small, $I_C \approx I_E$ or $I_C = \alpha I_E$
where $\alpha \approx 0.99$ typically.


$$\therefore I_B = I_E - I_C = I_E(1 - \alpha)$$

$$\therefore \frac{I_C}{I_B} = \frac{\alpha \cancel{I_E}}{(1 - \alpha) \cancel{I_E}} = \frac{\alpha}{1 - \alpha} \equiv \beta = 99$$

↑
beta

Get a large current gain ($I_C = \beta I_B$)
In this way transistor can be used as
a current amplifier.

Transistor as a Switch.

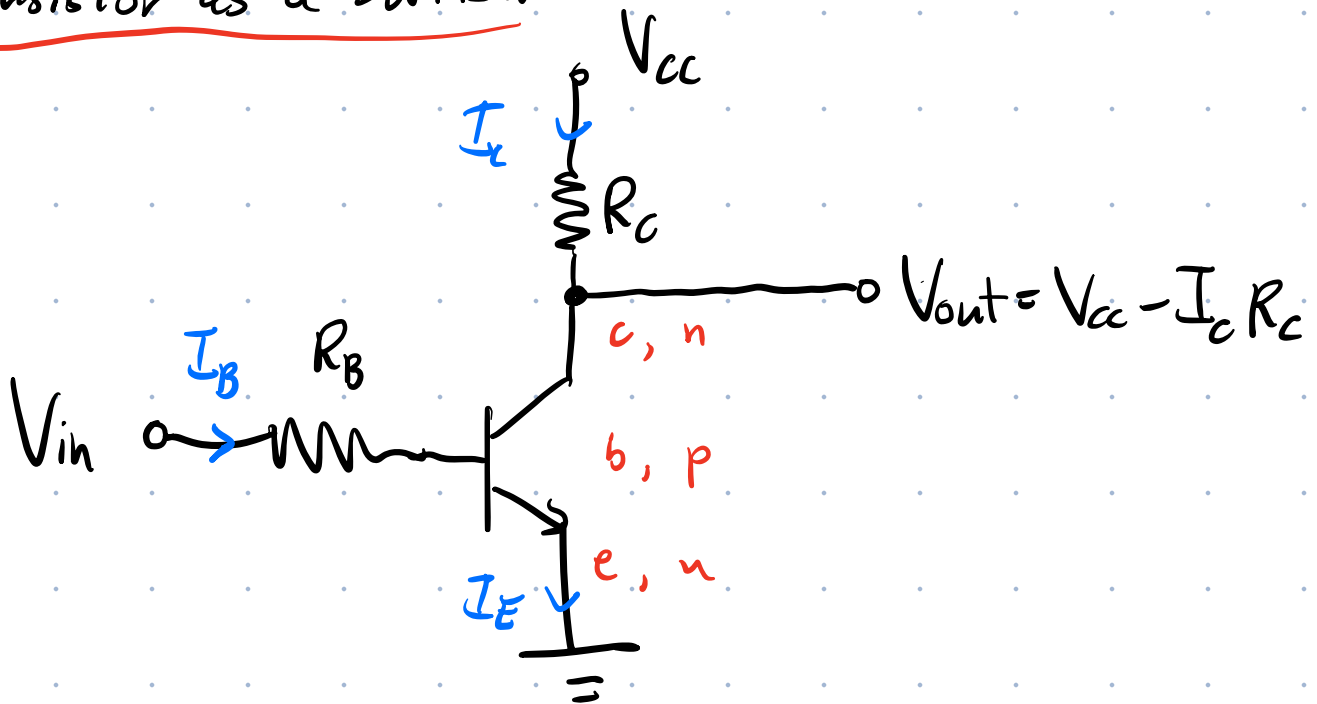

Case ① : $V_{in} < 0.7V$

\therefore B-E jcn is reverse biased

$$\Rightarrow I_c = 0.$$

$$\therefore V_{out} = V_{cc}$$

Case ② $V_{in} \gg 0.7V$ $\therefore I_B$ large
 $\rightarrow I_c$ large.

\therefore B-E jcn is forward biased.

$$\Rightarrow I_c \neq 0.$$

$\therefore V_{out} = V_{cc} - I_c R_c$ is small

Eventually, for sufficient I_c , both the B-E & B-C jcn become forward biased.

$$\Rightarrow V_{out} \approx 0.$$

Truth Table

$V_{in} = V_B$	I_c	V_{out}
0 (LO)	0	V_{cc} (HI)
V_{cc} (HI)	$\neq 0$	0 (LO)




turn current through transistor off and on using $V_{in} \rightarrow$ switch

$V_{in} = V_B$	V_{out}
0	1
1	0




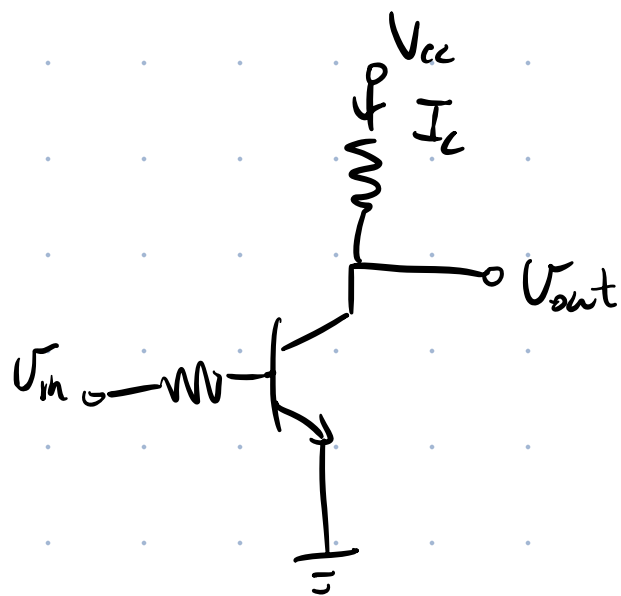truth table is that of an inverter (NOT gate).



What about other logic gates?

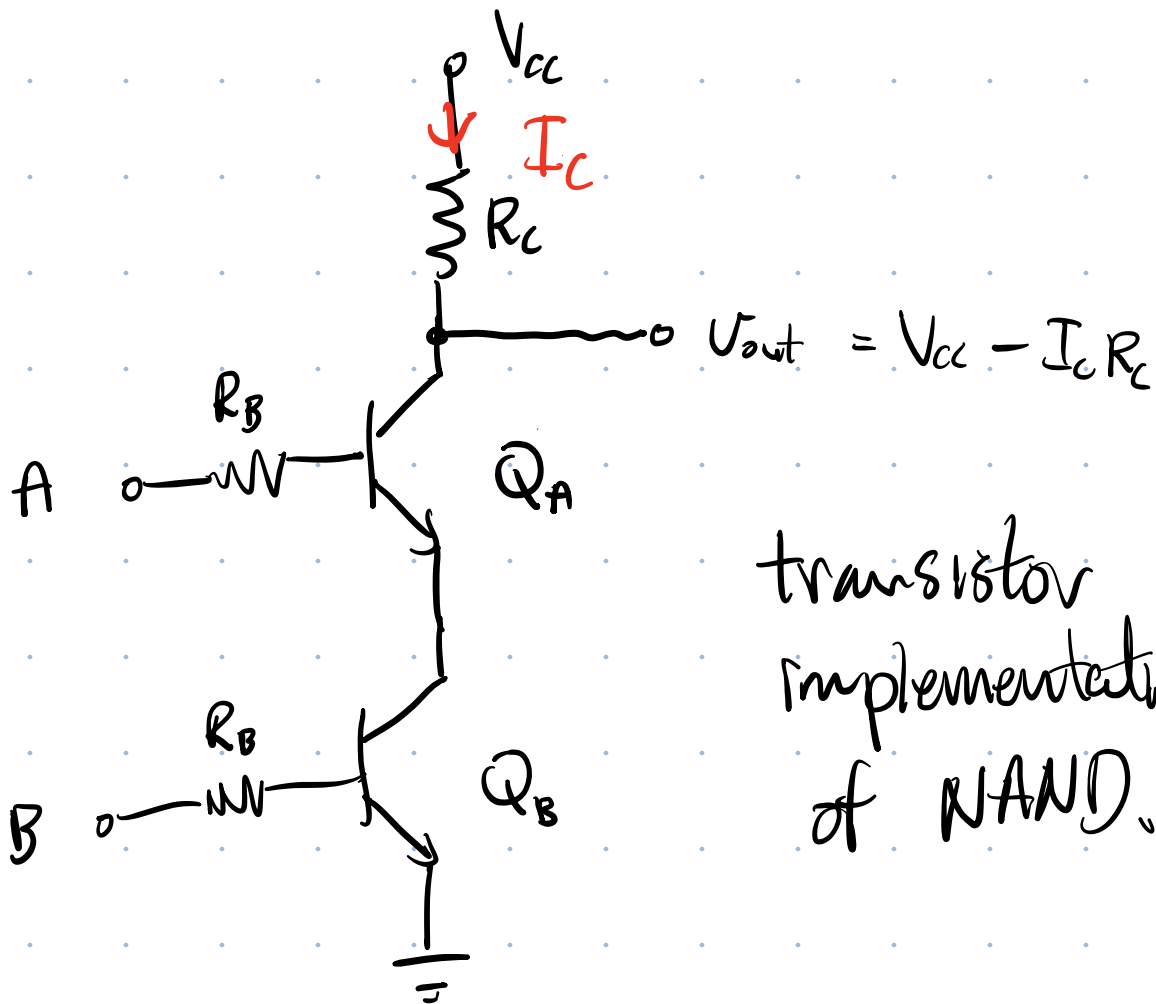Consider a series combination of two transistors.



transistor
implementation
of NAND.

A	B	Q_A	Q_B	I_C	V_{out}
0	0	OFF	OFF	0	1
0	1	OFF	ON	0	1
1	0	ON	OFF	0	1
1	1	ON	ON	$\neq 0$	0

A	B	Uont
0	0	1
0	1	1
1	0	1
1	1	0

NAND.