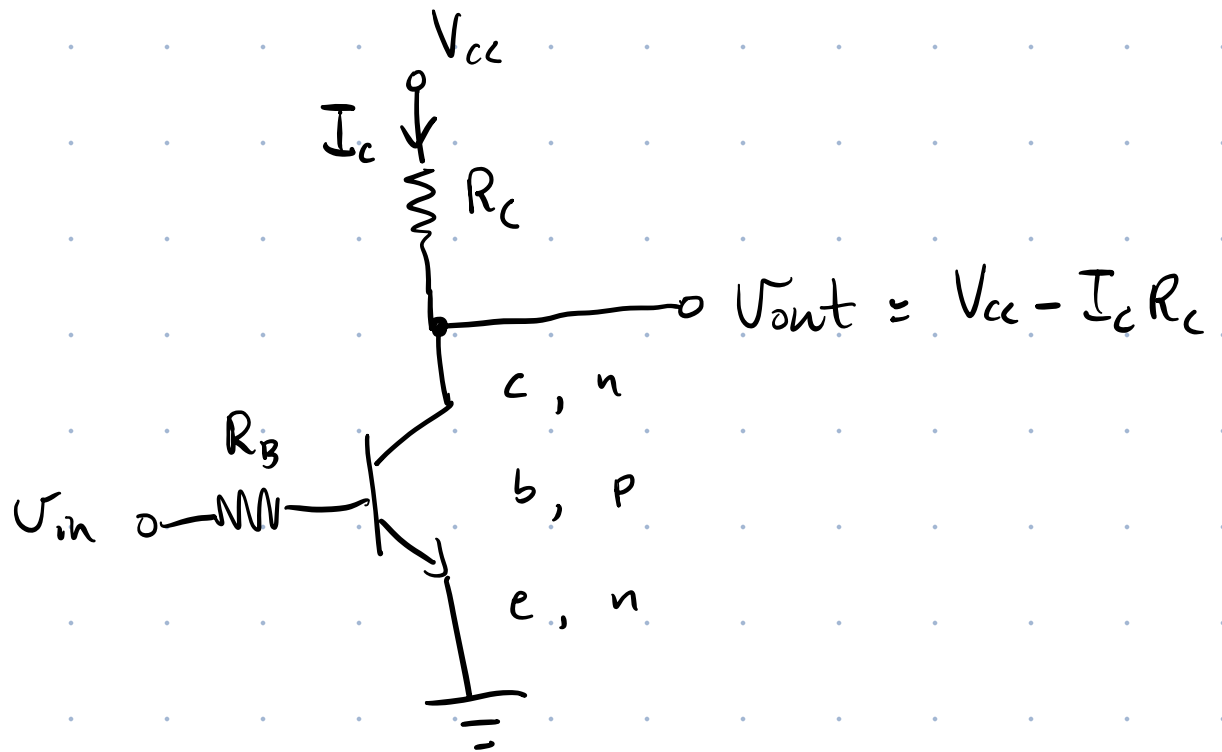


Last Time:


### Transistor Switch



If  $V_{in}$  is LO,  $I_c = 0$


If  $V_{in}$  is HI,  $I_c \neq 0$

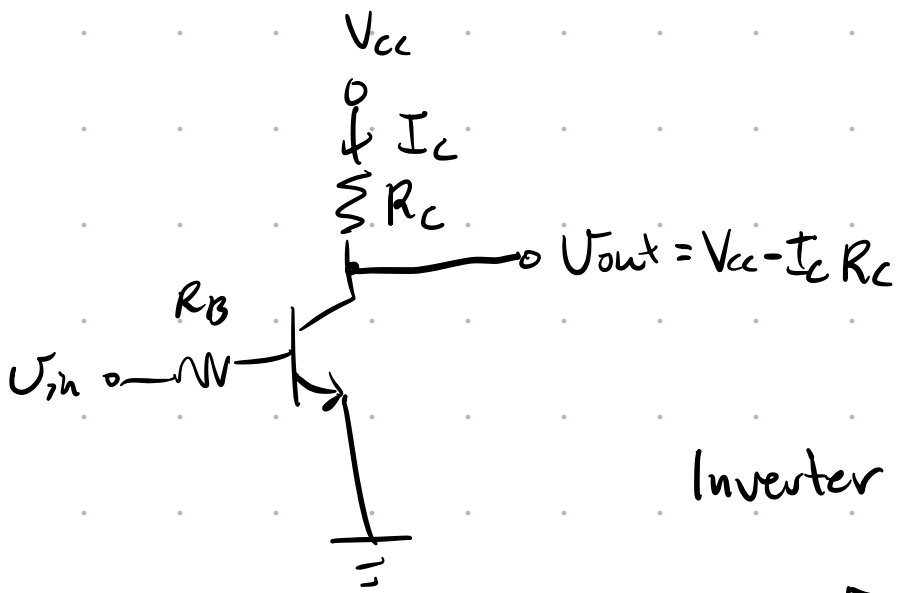} transistor acts as an electronic switch. The voltage at the base controls the current through the transistor




$U_{in}$	$U_{out}$
0	1
1	0

Inverter (NOT gate)

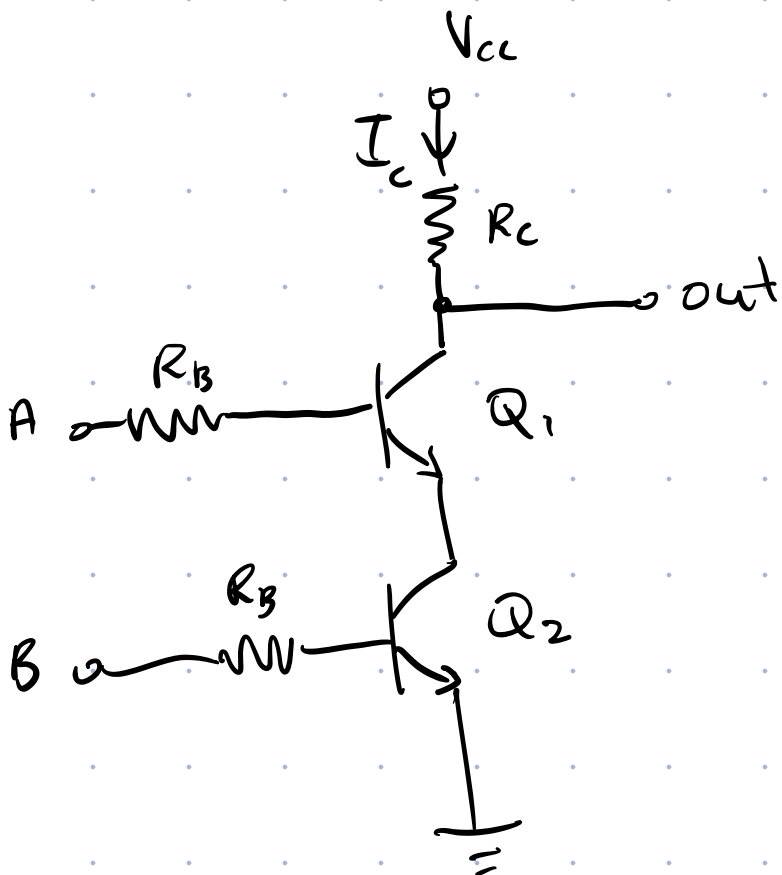


A	B	$Q_1$	$Q_2$	$I_C$	out
0	0	OFF	OFF	0	1
0	1	OFF	ON	0	1
1	0	ON	OFF	0	1
1	1	ON	ON	$\neq 0$	0

NAND gate

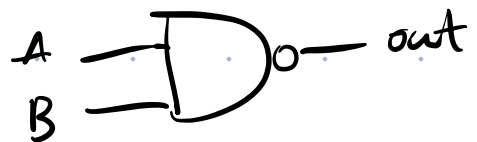


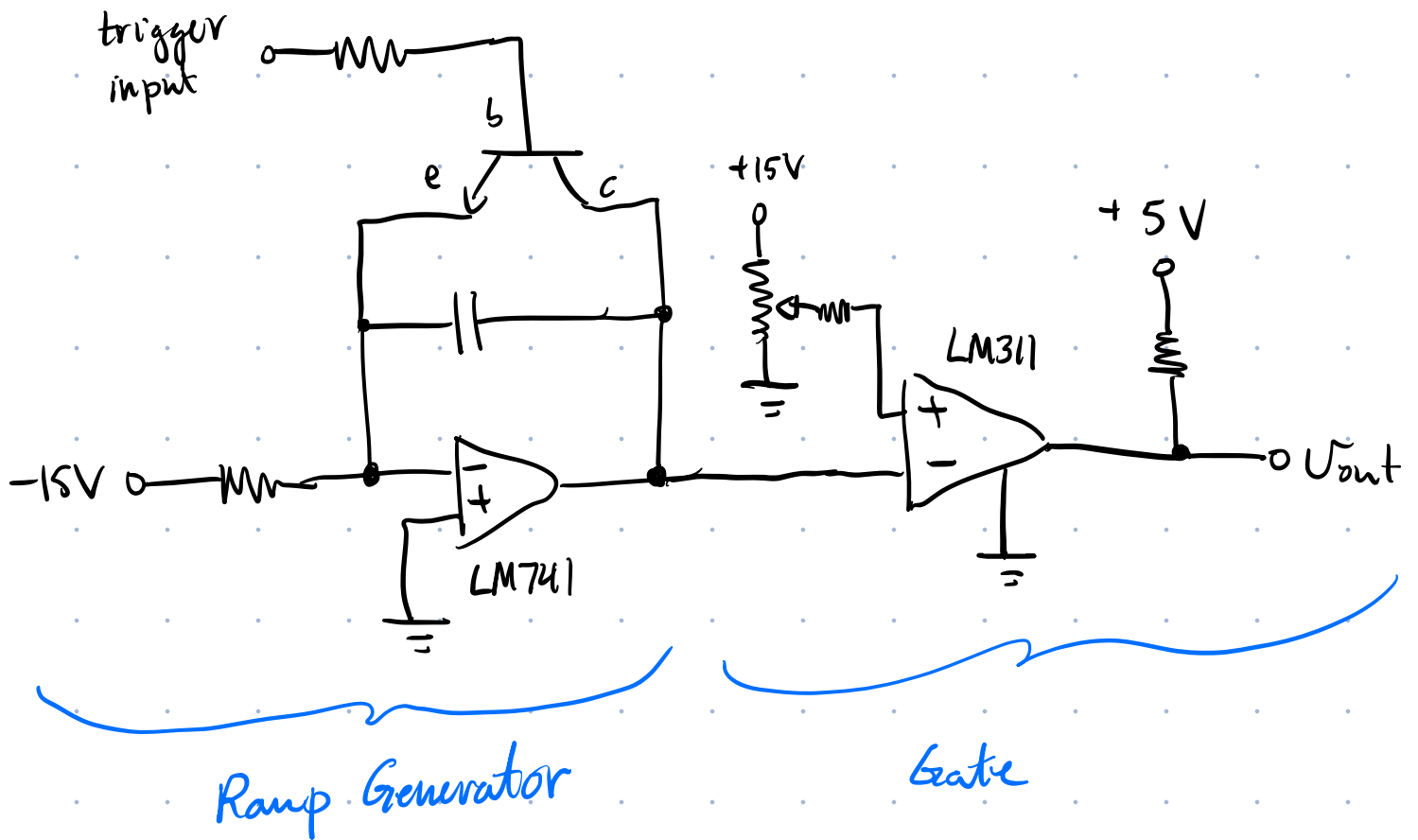Today: Prepare for Day 2 of ADC project in which you will build & test the following circuit:



# Ramp Generator:



Recall the integrator

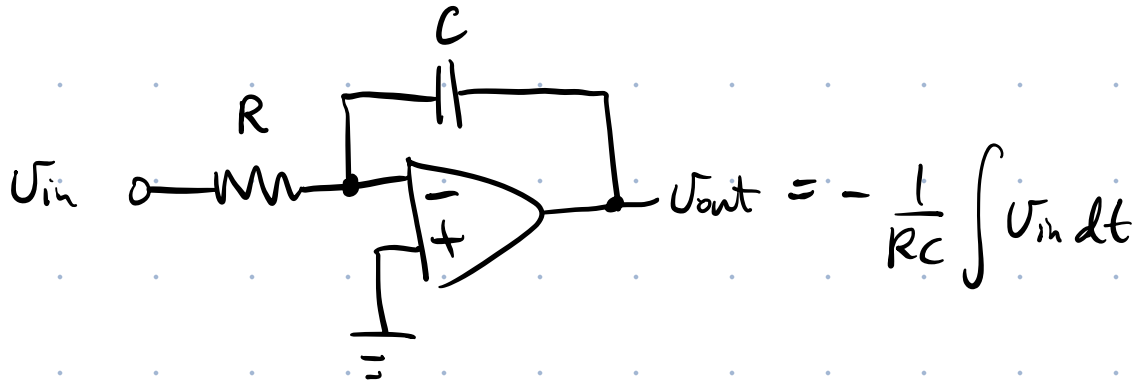


If we set  $V_{in} = -V_{cc}$  ( $-15V$ ), then

$$V_{out} = -\frac{1}{RC} \int \underbrace{(-V_{cc})}_{\text{const.}} dt = \frac{V_{cc}}{RC} \int dt$$

$$= \frac{V_{cc}}{RC} t$$

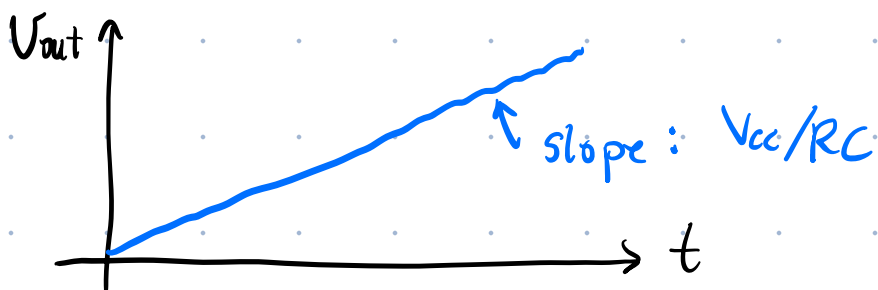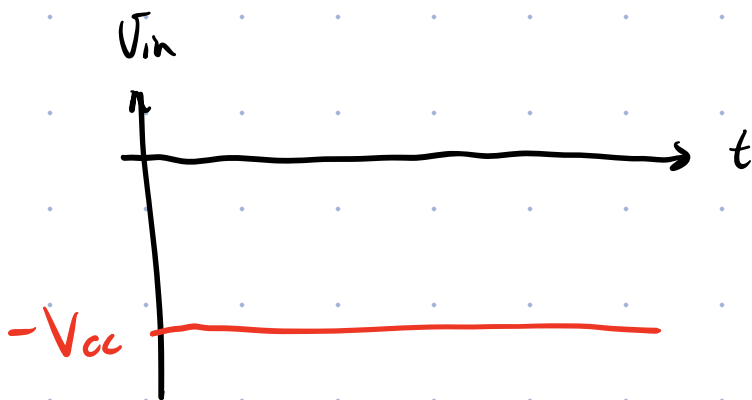

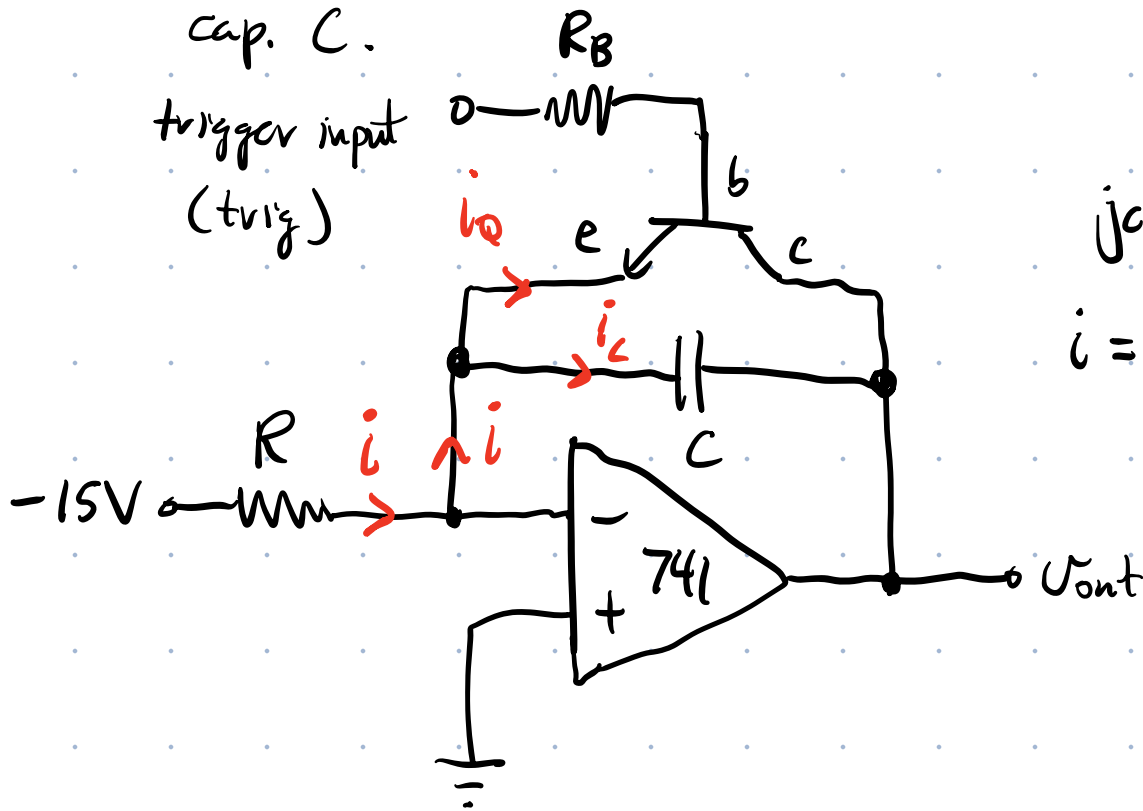Add a transistor switch in parallel w/ feedback cap. C.




junction rule:  
 $i = i_c + i_Q$

Case ①: Trig is LO.

In this case, no current passes through trans. since B-E is not forward biased.

$\Rightarrow i_Q = 0$  (all current goes through cap.)

Equiv. circuit is:


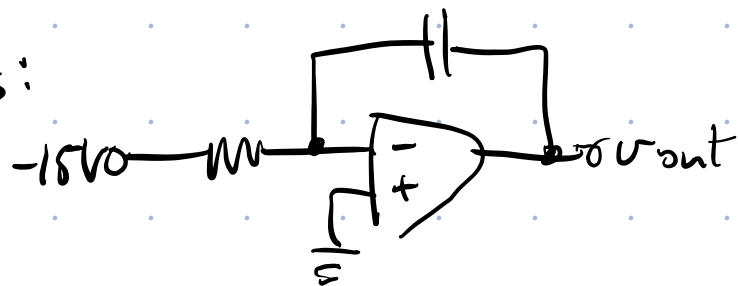


We are integrating.  $V_{out}$  is a ramp.


Case ②: Trig is H1.

∴ transistor Q is conducting.

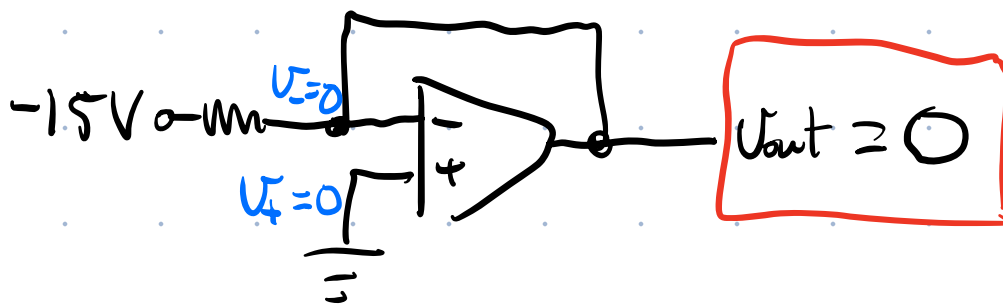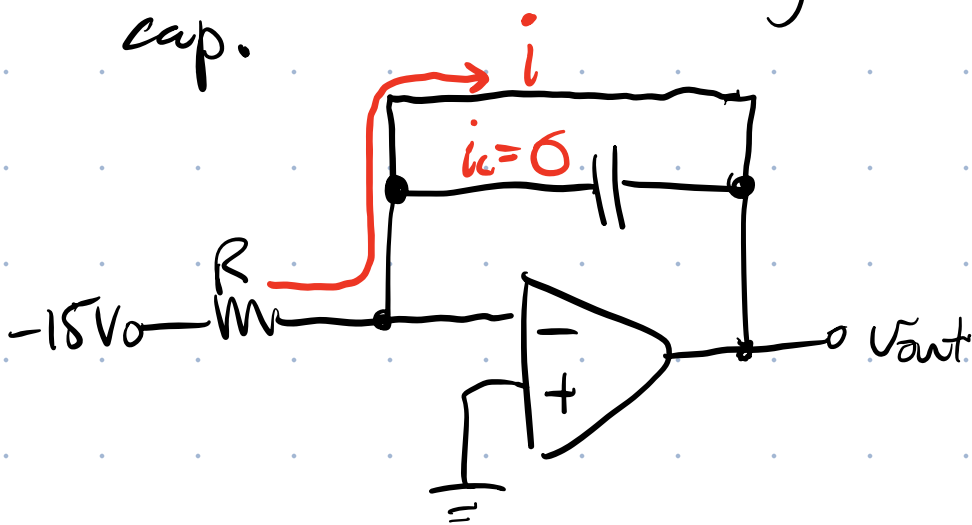
Transistor presents a very low impedance path for current. Effectively short circuit the cap.




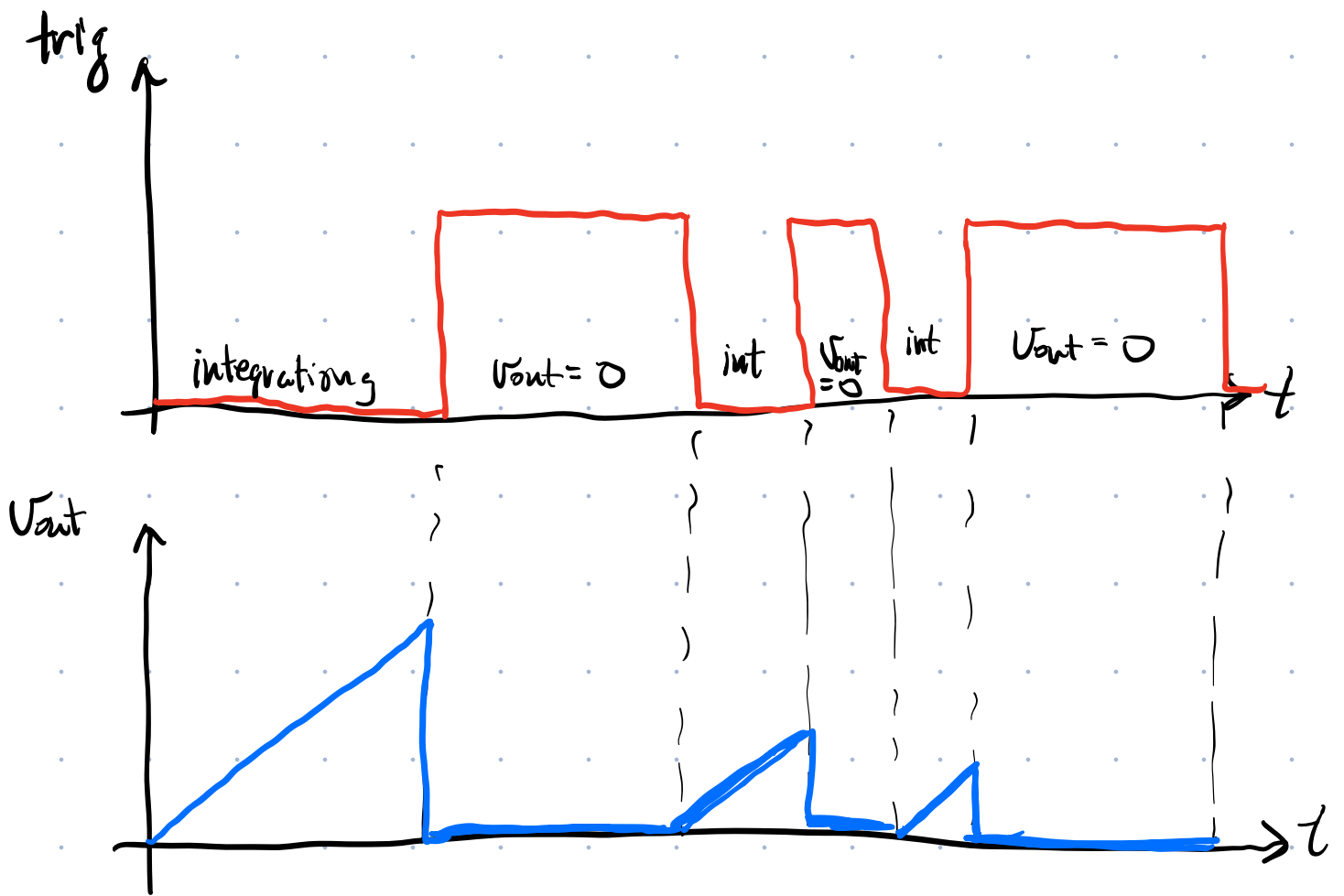To test the circuit in the lab, we can provide the trig. input a square from TTL output of fun gen.



Consider the following op amp circuit:

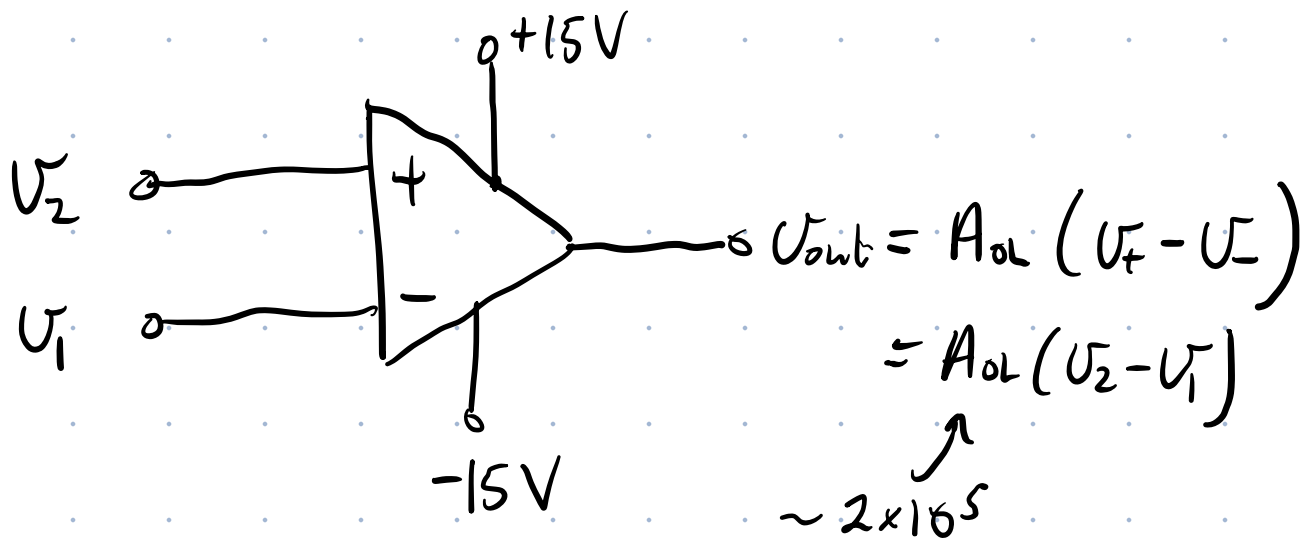

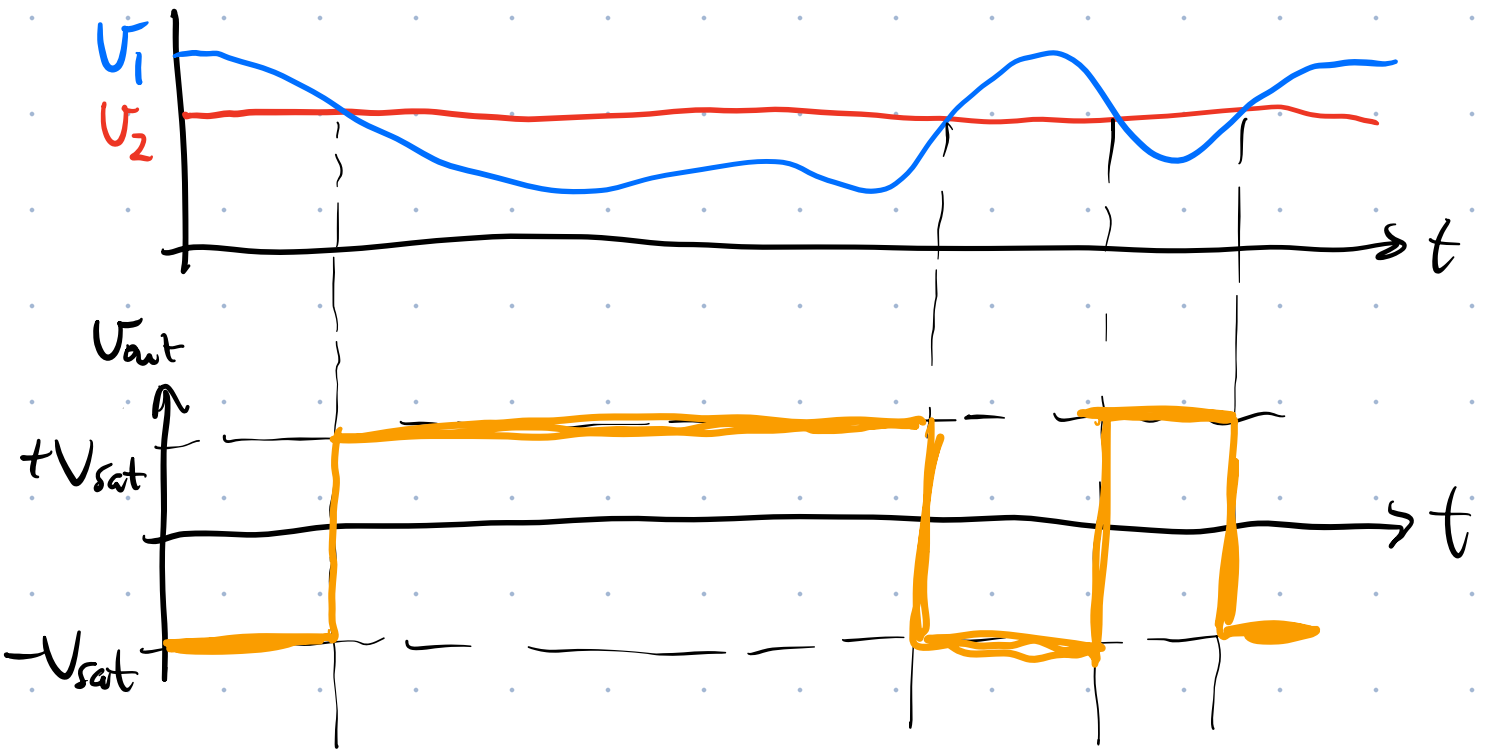


This is a type of comparator circuit.


$$\text{If } U_2 > U_1, \quad V_{out} = +V_{sat}$$

$$\text{if } U_2 < U_1, \quad V_{out} = -V_{sat}.$$

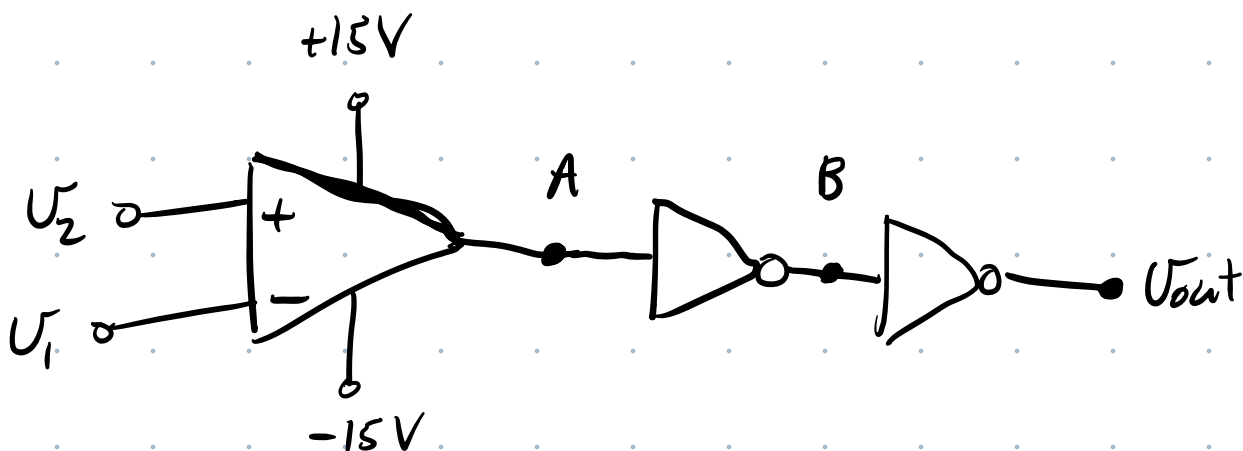We would like the output to be LO (0V) or HI (5V) so that it is compatible w/ digital circuits.





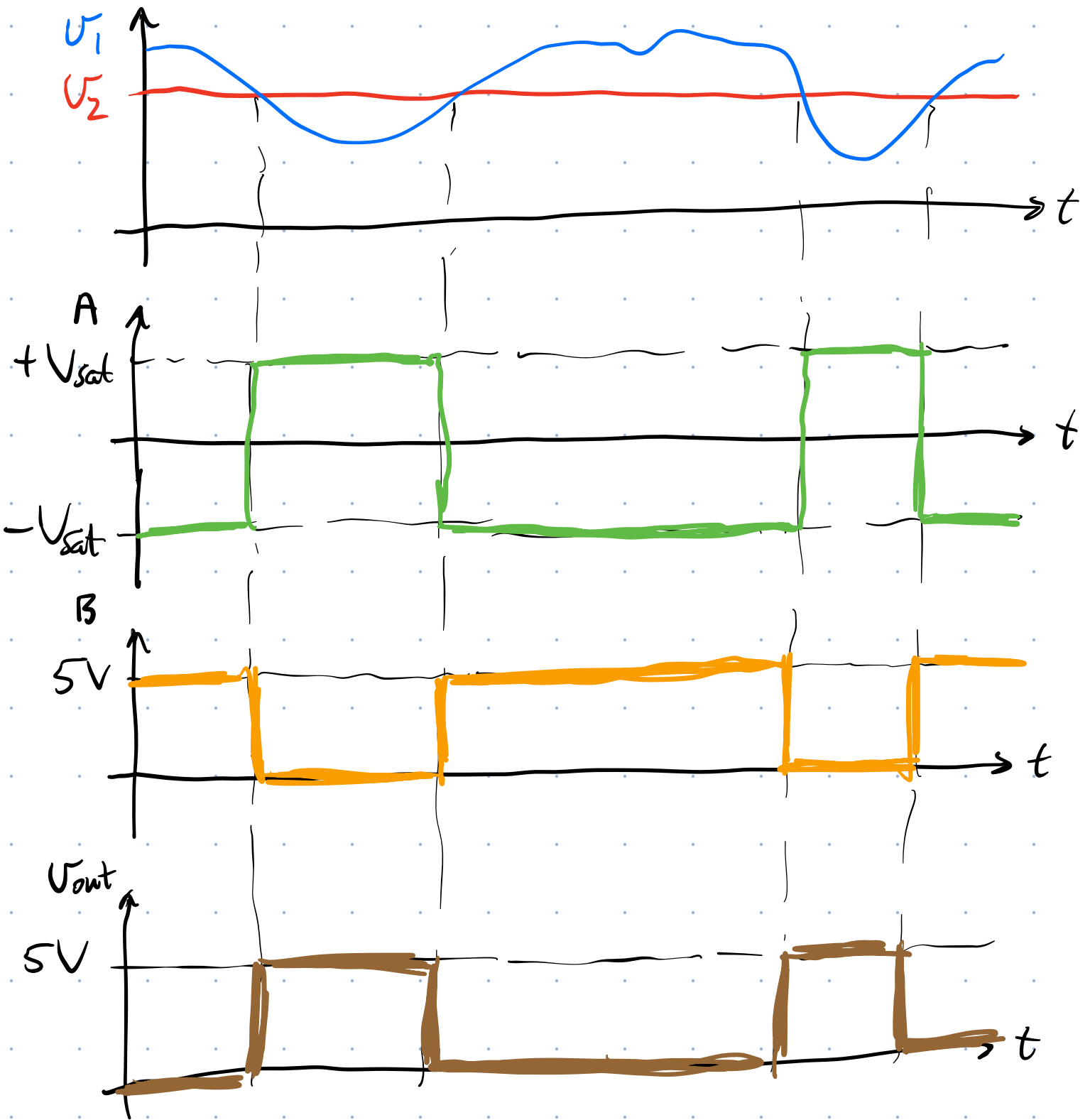

Now, if  $V_2 > V_1 \rightarrow V_{out}$  is H/L ✓  
 if  $V_2 < V_1 \rightarrow V_{out}$  is L/O

The LM311 comparator is essentially an opamp w/ two inverters (transistors) & comes as a chip.

## Ramp Generator + Comparator

