

PHYS 231


Assignment #2 on
Course website

Sept. 26, 2025

No lab next week

Lab #3 notebook due
Thurs. Oct. 9 @ start of lab 4a

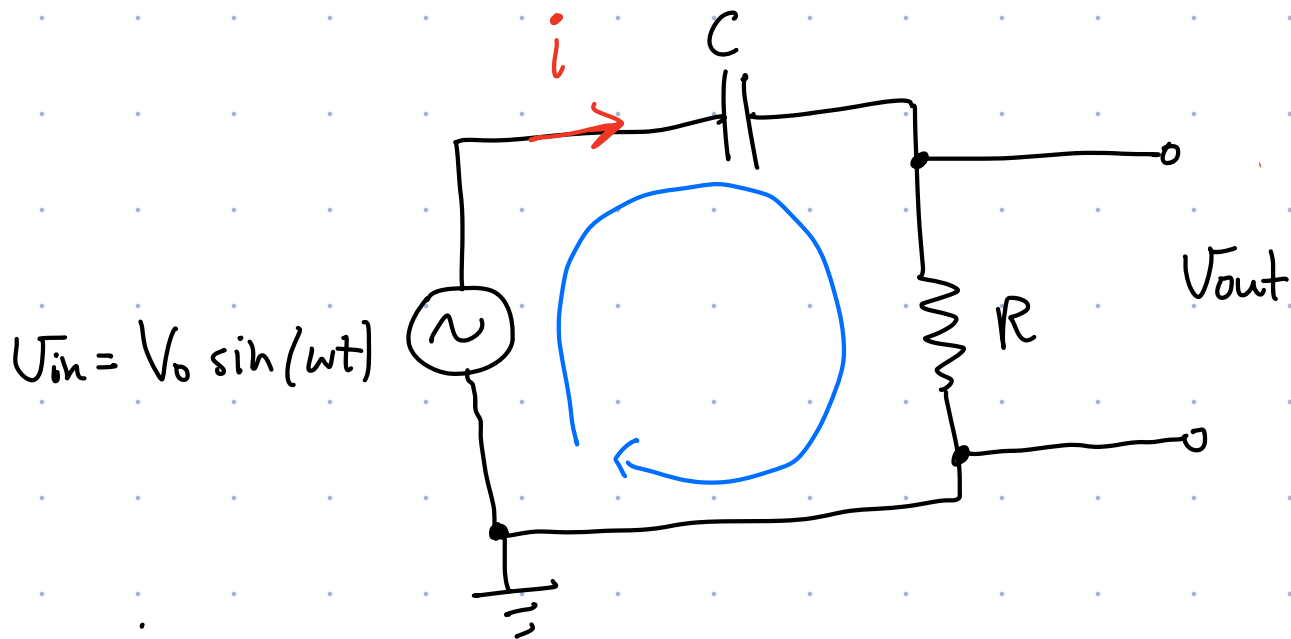Last Time: Frequency Response of an RC circuit



Found that:

$$i = I_0(\omega) \sin[\omega t - \phi(\omega)]$$

where

$$I_0(\omega) = \frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}$$

$$\tan \phi(\omega) = -\frac{1}{\omega RC}$$

Practical of this RC circuit w/ $V_{out} = iR$

$$\therefore V_{out} = \underbrace{I_0 R}_{\text{amplitude of output}} \sin[\omega t - \phi]$$

$$I_0 R = \frac{\omega V_0 R C}{\sqrt{1 + (\omega R C)^2}}$$

The ratio of input amplitude (V_0) to output amplitude ($I_0 R$)

$$\frac{I_0 R}{V_0} = \frac{\omega R C}{\sqrt{1 + (\omega R C)^2}}$$

Transfer fn
of RC circuit.

consider 3 case:

- (i) $\omega R C \ll 1$ (low freq)
- (ii) $\omega R C \gg 1$ (high freq)
- (iii) $\omega R C = 1$

(i) low freq. $\sqrt{1 + (\omega RC)^2} \approx 1$

$$\frac{I_0 R}{V_0} = \omega RC \sim \omega$$

(ii) high freq. $\omega RC \gg 1$

$$\sqrt{1 + (\omega RC)^2} \approx \omega RC$$


$$\therefore \frac{I_0 R}{V_0} \approx \frac{\omega RC}{\omega RC} = 1 \text{ (const)}$$

(iii) $\omega RC = 1$ (intermediate freq)

denom: $\sqrt{1 + (\omega RC)^2} = \sqrt{2}$

numer: $\omega RC = 1$
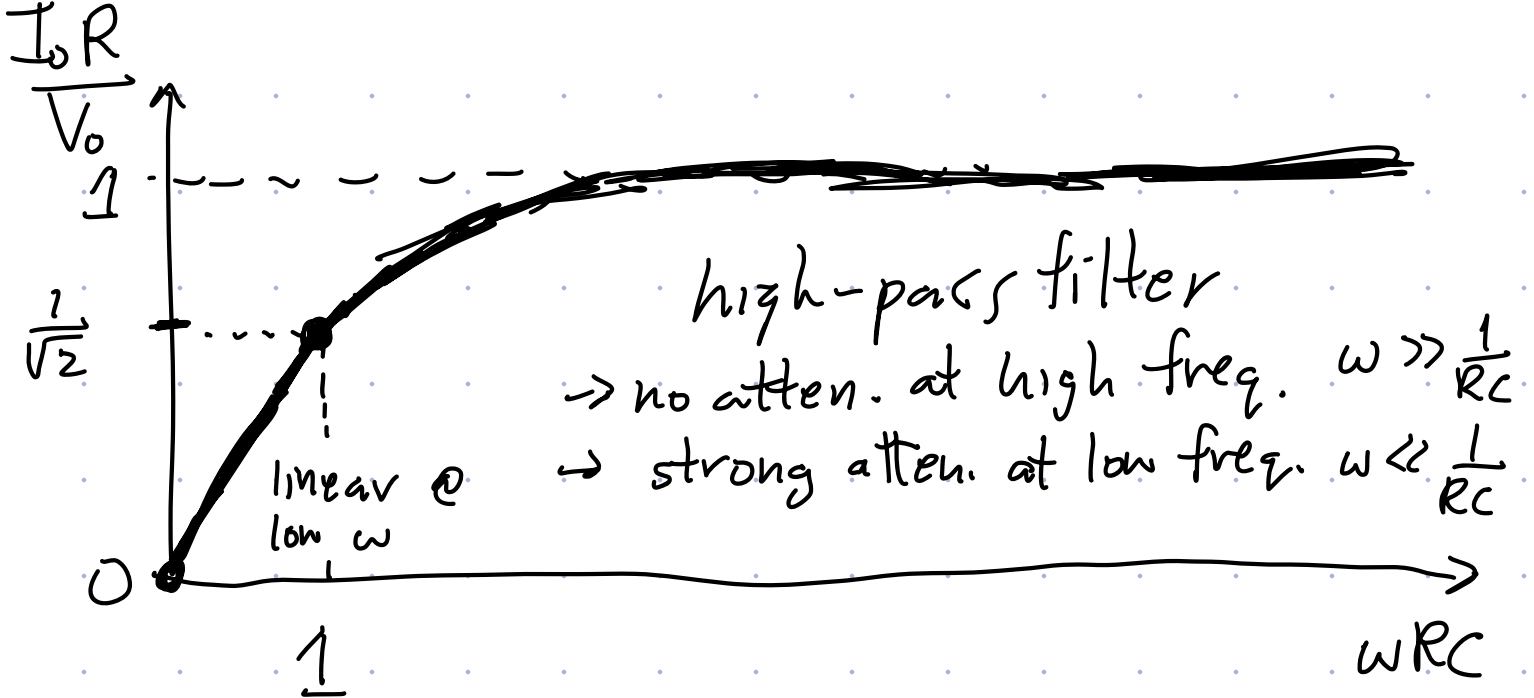
$$\frac{I_0 R}{V_0} = \frac{1}{\sqrt{2}} = 0.707$$



$$\left(\omega = \frac{1}{RC}, f = \frac{1}{2\pi RC} \right)$$

Solving the RC circuit driven by a sine wave wasn't too difficult, but involve lots of algebra and trig fns...

We need new mathematical tools so that we can solve these problems more efficiently.

Develop the idea of complex nos.

Definition: $\sqrt{-1} = \pm j$

This definition is useful because it allows to solve some problem that previously had no obvious sol'n.

Eg. Consider $x^2 - 2x + 4 = 0$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\begin{aligned} a &= 1 \\ b &= -2 \\ c &= 4 \end{aligned}$$

$$= \frac{2 \pm \sqrt{(-2)^2 - 4(1)(4)}}{2}$$

$$= 1 \pm \frac{\sqrt{-12}}{2}$$

$$= 1 \pm \frac{\sqrt{-1} \sqrt{4} \sqrt{3}}{\cancel{2}}$$

$$x = \begin{cases} 1 + j\sqrt{3} \\ 1 - j\sqrt{3} \end{cases}$$

In general, a complex no. z has a "real" part and an "imaginary".

$$z = x + jy$$

Real part
of complex
no z

$$\text{Re}[z] = x$$

anything in z
that doesn't involve
 j


Imaginary part
of z

$$\text{Im}[z] = y$$

anything that
multiplies j , but
not including j

both x & y are real numbers b/c they
don't involve j directly.


Draw the number line

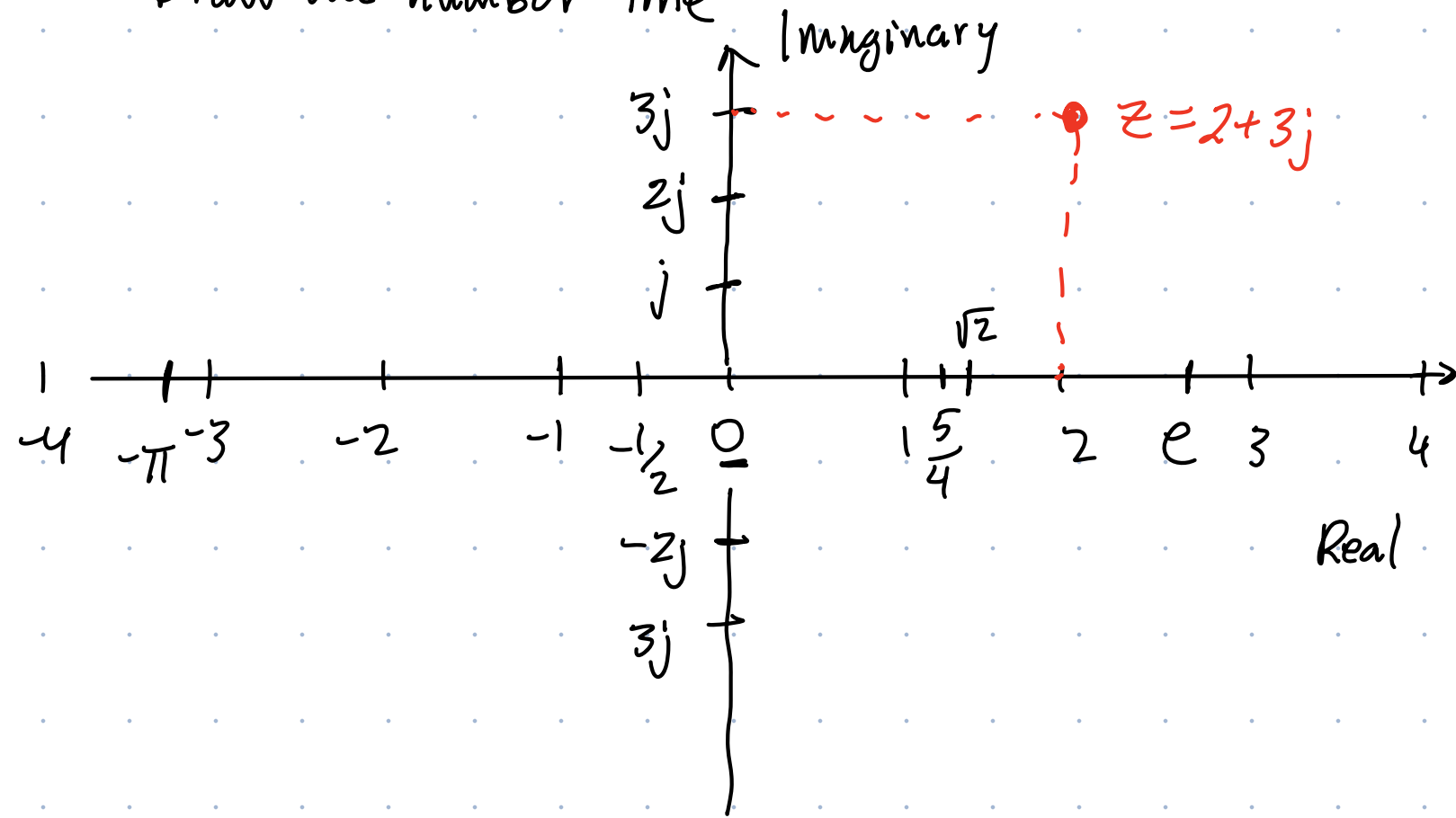

To extend the number line to include complex nos, we add a $\perp$ axis for the imaginary part of z .

Place $z = 2 + 3j$ on our coord. system.

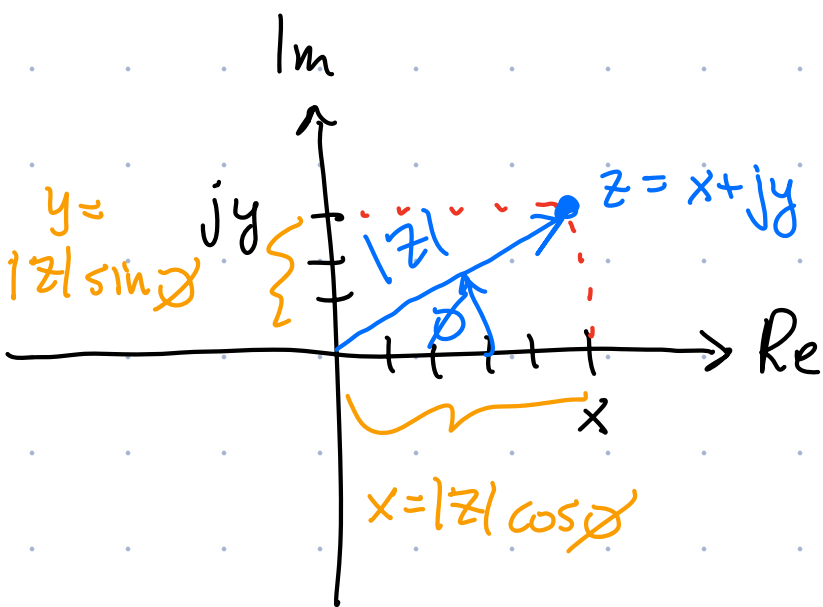Notice that, in many ways, $z = x + jy$ is similar to a 2-D vector $\vec{v} = x\hat{i} + y\hat{j}$.



complex plane


$$z = x + jy$$

Likewise, we can specify z as a dist. from origin to the point $z \Rightarrow |z|$
 magnitude or length of z

and an angle ϕ meas. from real axis.

$$\text{Re}[z] = x = |z| \cos \phi \quad (1)$$

$$\text{Im}[z] = y = |z| \sin \phi \quad (2)$$

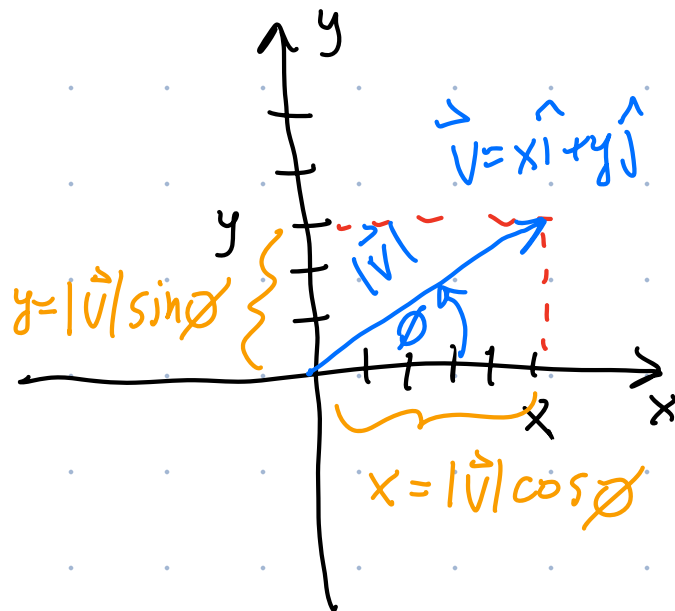

$$\vec{V} = x \hat{i} + y \hat{j}$$

$\vec{V} \Rightarrow |\vec{V}|$ and dir'n ϕ
 ↑ length of vector

$$x = |\vec{V}| \cos \phi$$

$$y = |\vec{V}| \sin \phi$$

$$|\vec{V}| = \sqrt{x^2 + y^2}$$

$$\tan \phi = \frac{y}{x}$$

$$|z| = \sqrt{x^2 + y^2}$$

$$\tan \theta = \frac{y}{x}$$

$$\text{If } z = x + jy$$

$$= |z| \cos \theta + j |z| \sin \theta$$

$$= |z| (\cos \theta + j \sin \theta)$$

Can represent any complex number in two ways:

"component form"

$$z = x + jy$$

"magnitude & phase"

$$z = |z| (\cos \theta + j \sin \theta)$$