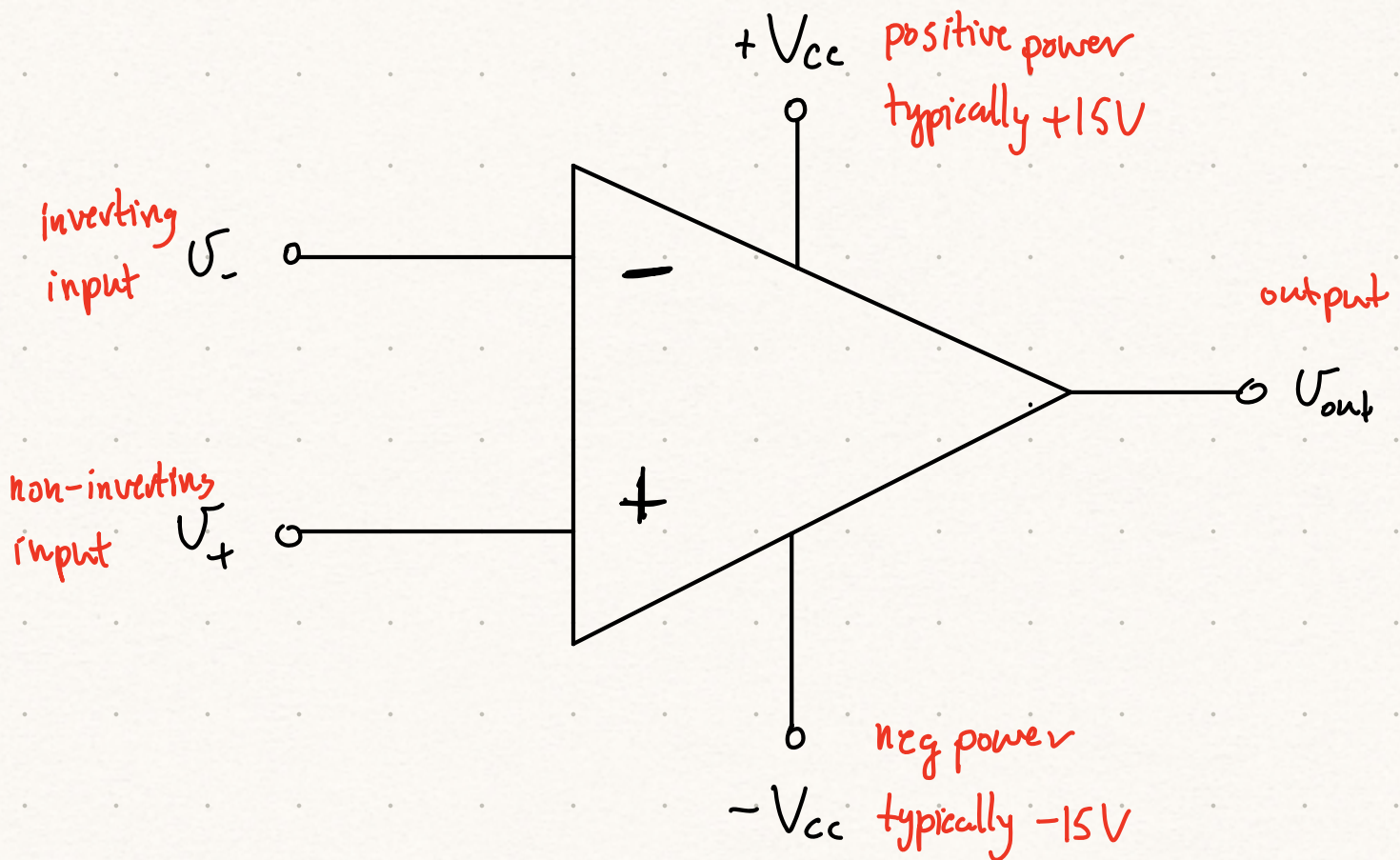


Today Operational Amplifiers (Op Amps)

An op amp is a device w/ :

- two inputs (V_- , V_+)
- one output (V_{out})
- two power terminals ($+V_{cc}$, $-V_{cc}$)



$+V_{cc}$ must be a positive constant (DC)
voltage (+15V)

$-V_{cc}$ must be a negative constant (DC)
voltage (-15V)

V_- , V_+ : the inverting & non-inverting inputs
can be positive or negative fns of time.

Treat the op amp as a black-box device that
performs the following operation:

$$V_{out} = A_{ol}(V_+ - V_-)$$


↑ "open loop" gain.


no feedback from output
to inputs.

In the lab we will use LM741 op amp & it is
designed to have an open loop gain of about:

$$A_{ol} \approx 2 \times 10^5 = 200,000 \text{ (large).}$$

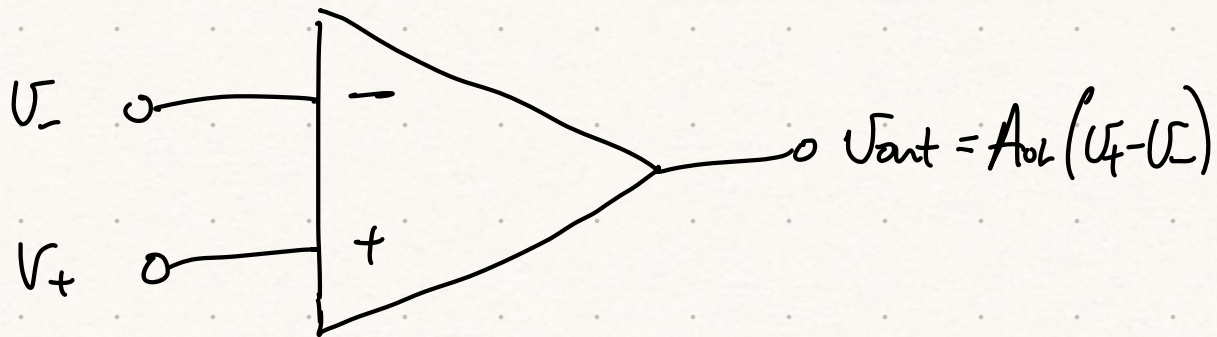In circuit diagrams, the power terminals $\pm V_{cc}$ are often omitted for clarity. However, the opamp always needs to be powered to fun properly.




Op amp limitation:

① $|V_{out}| \leq V_{sat} \approx V_{cc} - 1$

saturation (max/min) voltage

If $V_{cc} = 15V$, then $V_{sat} \approx 14V$.

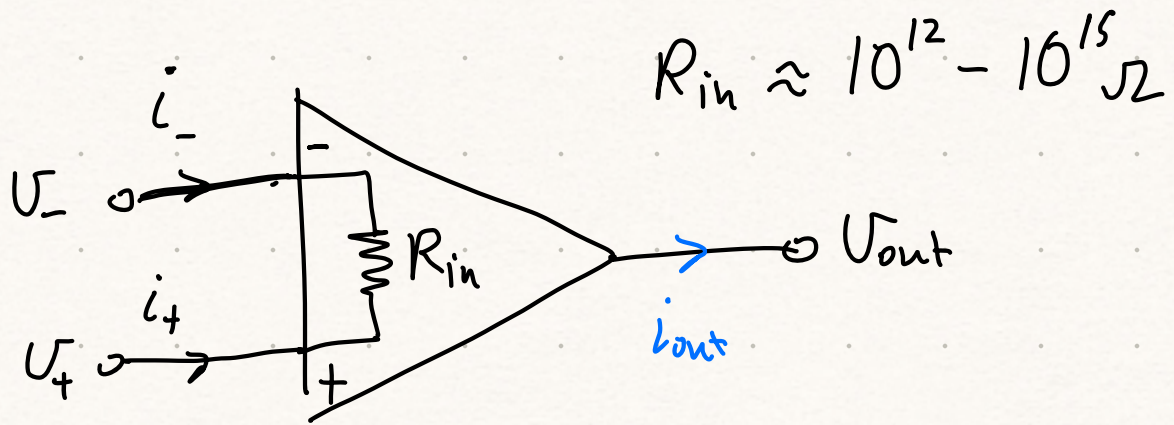Another characteristic of the op amp is that it has very large input resistance.



The large input resistance limits the current i_- & i_+ into op amp inputs. Usually ignore i_- & i_+ s.t. $i_- \approx i_+ \approx 0$.

If we assume $R_{in} \rightarrow \infty$, then $i_- \approx i_+ \approx 0$
 $\Rightarrow$ no current into or out of the op amp inputs.

Note that the current at the output i_{out} does not have to zero.


Op Amp Golden Rules

1. Op Amp input resistance $\rightarrow \infty$

$$i_- = i_+ = 0$$

no current into or
out of op amp inputs

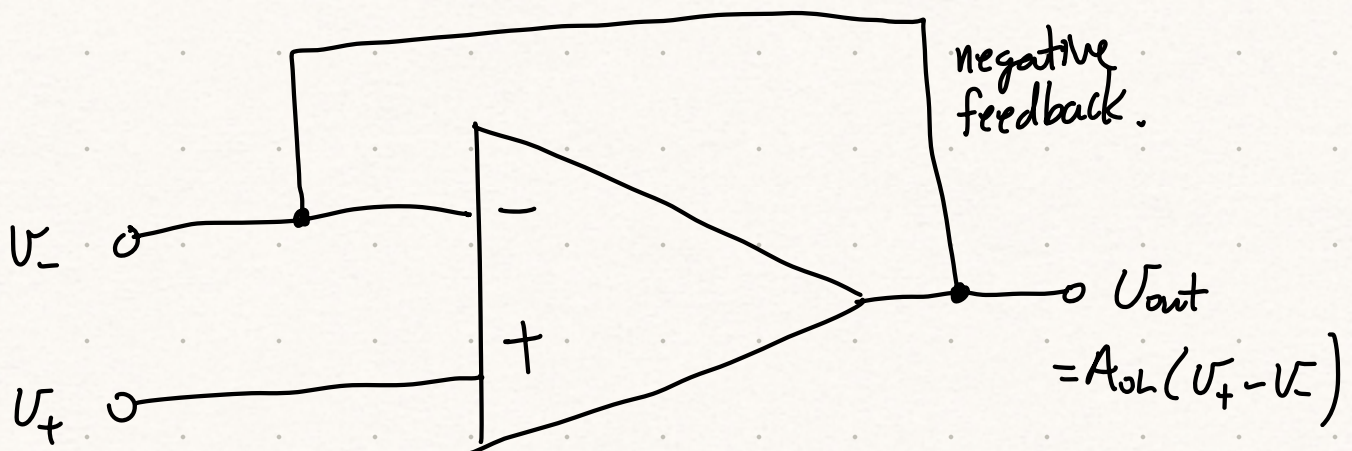2. The second golden rule applies to op amps
using negative feedback.



Know $V_{out} = A_{OL}(V_+ - V_-)$.

With our negative feedback, we require:

$$V_{out} = \underline{V_-}$$

$$\therefore V_- = A_{OL}(V_+ - V_-) \quad \text{solve for } V_-.$$

$$V_- + A_{OL} V_- = A_{OL} V_+$$

$$\therefore V_- (A_{OL} + 1) = A_{OL} V_+$$

$$\therefore V_- = \left(\frac{A_{OL}}{A_{OL} + 1} \right) V_+$$

If $A_{OL} \gg 1$ (as it always is),

then $\frac{A_{OL}}{A_{OL} + 1} \approx 1$ s.t.

$$V_- = V_+$$


2nd Golden Rule:

When using negative feedback.

$$V_+ = V_-$$

First op amp application (Lab #5)

Inverting amplifier

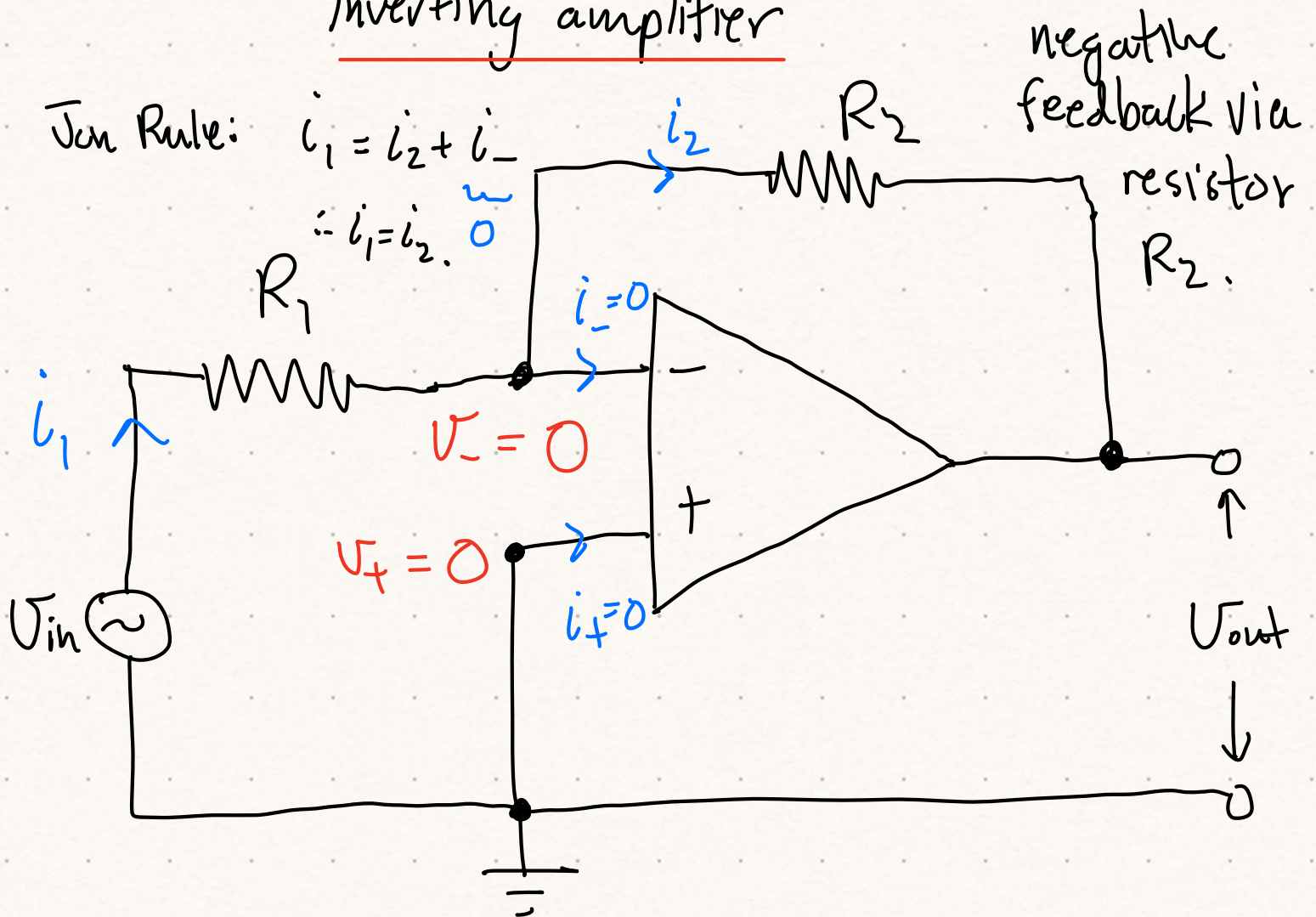


- non-inverting input is connected directly to gnd. $\therefore V_+ = 0$.
- if using negative feedback ✓, then by Golden Rule #2, $V_+ = V_- = 0$.

Golden Rule # 1. $i_- = i_+ = 0$

Results in $i_1 = i_2 \equiv i$

Golden Rule # 2 $V_- = V_+$

Since $V_+ = 0$, we have $V_- = V_+ = 0$

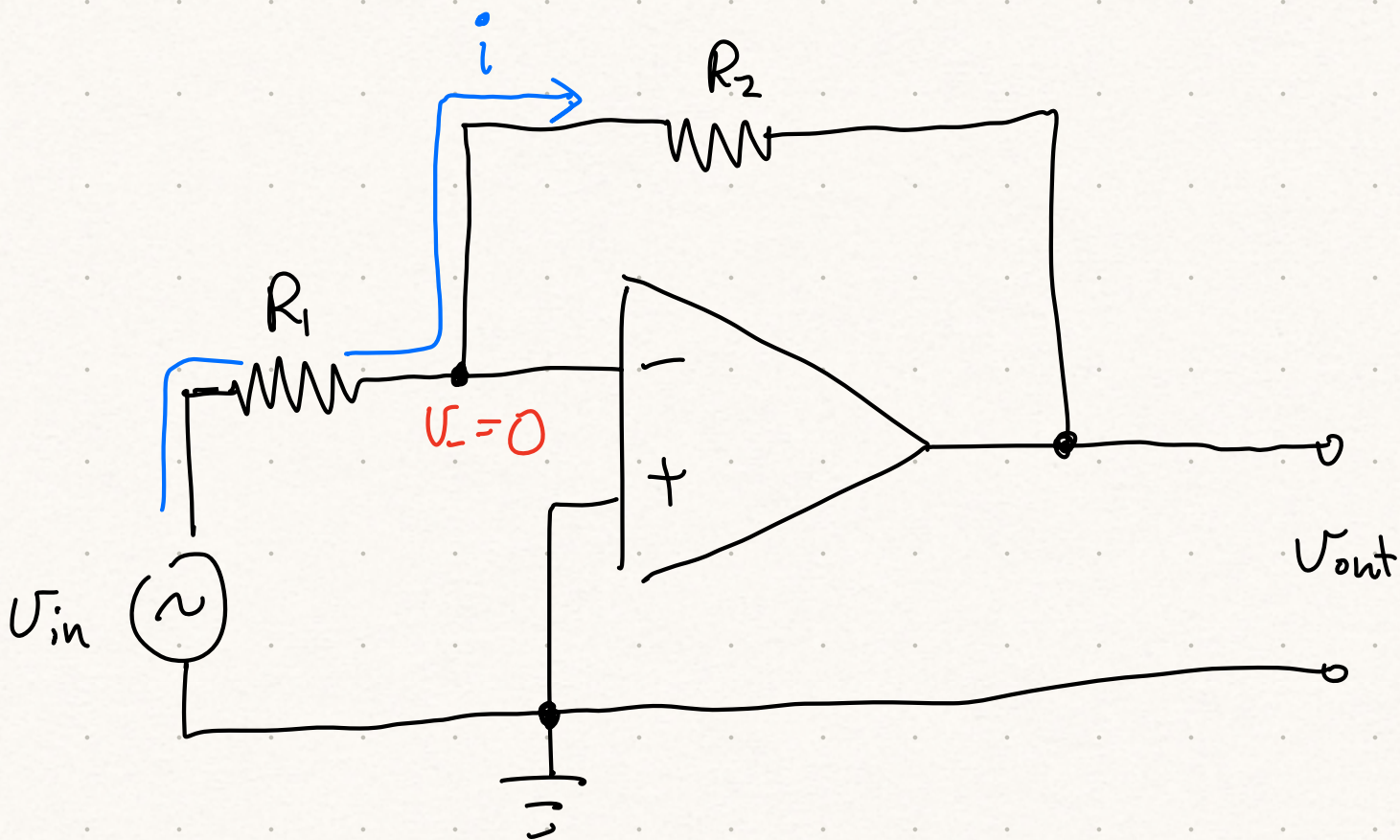

① Track changes in volt. from gnd to V_-

$$0 + V_{in} - iR_1 = \underbrace{V_-}_0 \Rightarrow i = \frac{V_{in}}{R_1}$$

② Track changes in volt. from V_- to V_{out}

$$\underbrace{V_-}_{0} - i R_2 = V_{out}$$

$$\therefore V_{out} = -i R_2 = -\left(\frac{V_{in}}{R_1}\right) R_2$$

$$\therefore V_{out} = - \frac{R_2}{R_1} V_{in}$$

inverting.

Gain of amplifier is set by the resistor ratio.