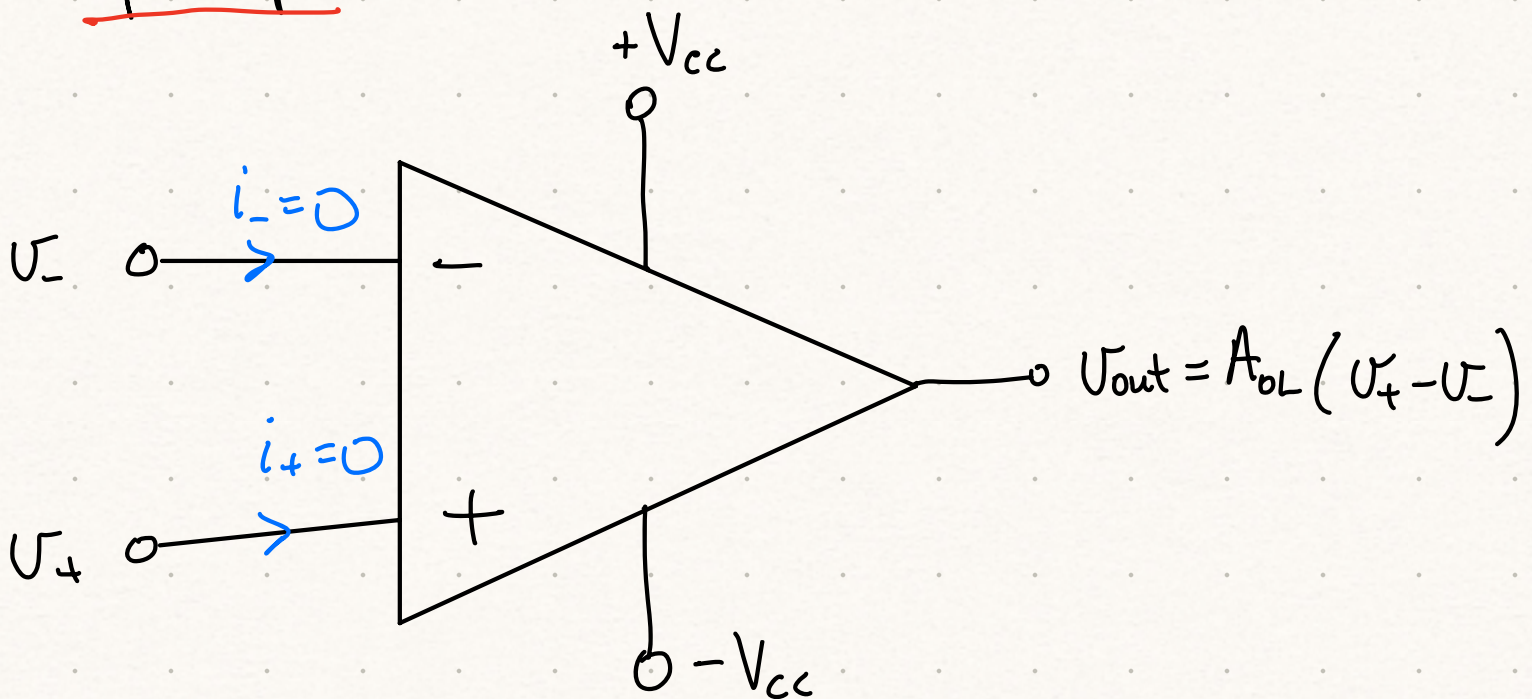


The PHYS 231 class on Friday, Oct. 24 is cancelled. In its place, I will record a 50-minute lecture and post it to the course website.

Last Time:


Op Amps



Golden Rules:

- ① No current into or out of op amp inputs $\Rightarrow i_+ = i_- = 0$
- ② When using negative feedback, the voltage difference across op amp inputs is zero.
 $\Rightarrow V_+ = V_-$

Inverting Amplifier

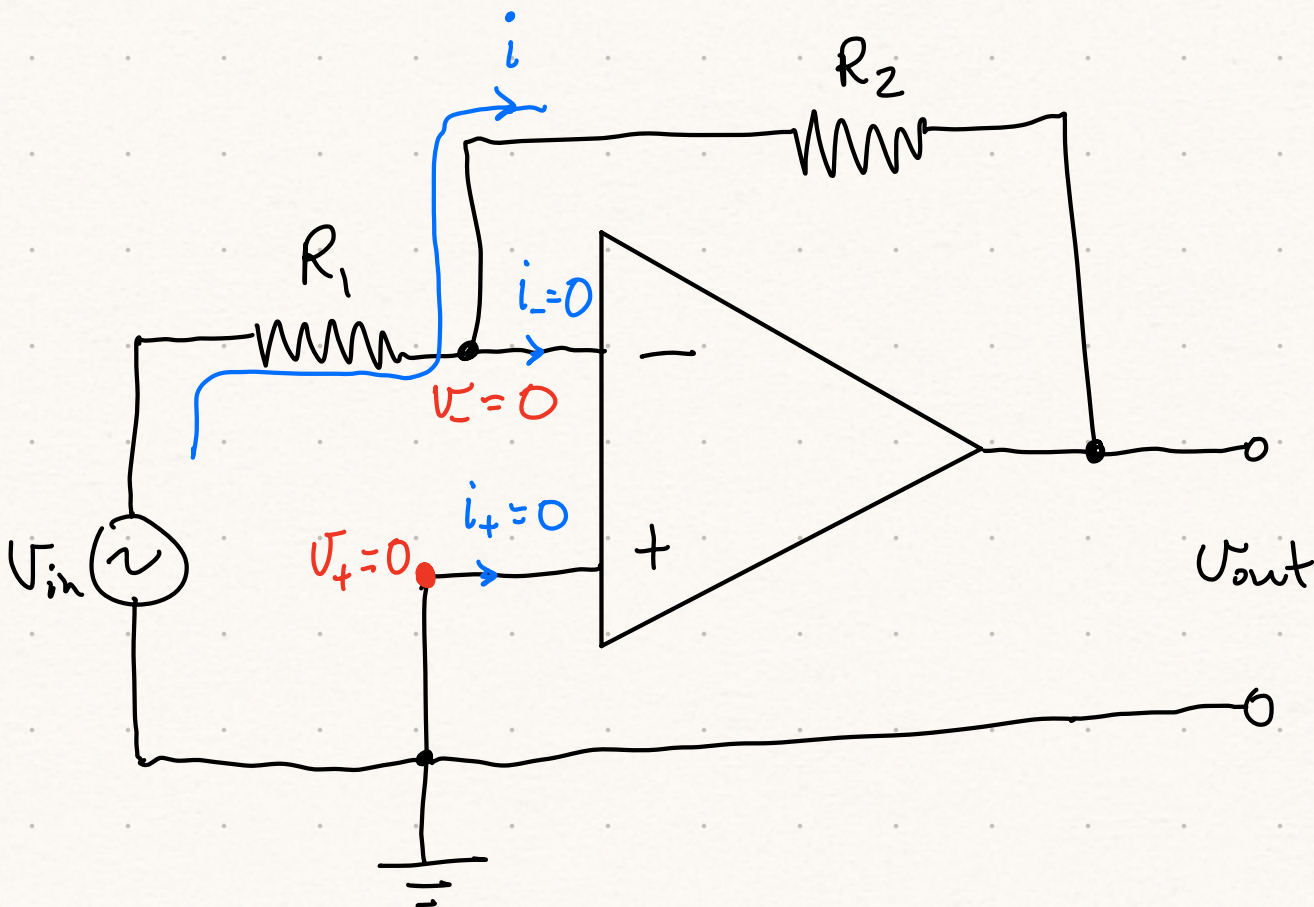

$$1. \quad V_{in} - iR_1 = V_- = 0 \Rightarrow i = \frac{V_{in}}{R_1}$$

$$2. \quad \cancel{V_-} - iR_2 = V_{out}$$

$$\therefore V_{out} = -\left(\frac{R_2}{R_1}\right) V_{in}$$

In Lab #5, you will use $R_2 = 100k\Omega$
 $R_1 = 1k\Omega$


$$\Rightarrow G = -100 \quad \text{amp. w/ a gain of } -100.$$

↑ inverting.

Recall that the op amp can output a maximum of $\pm V_{sat} \approx V_{cc} - 1V = 14V$ for $V_{cc} = 15V$.


$$\therefore V_{out, max} = \pm V_{sat}.$$

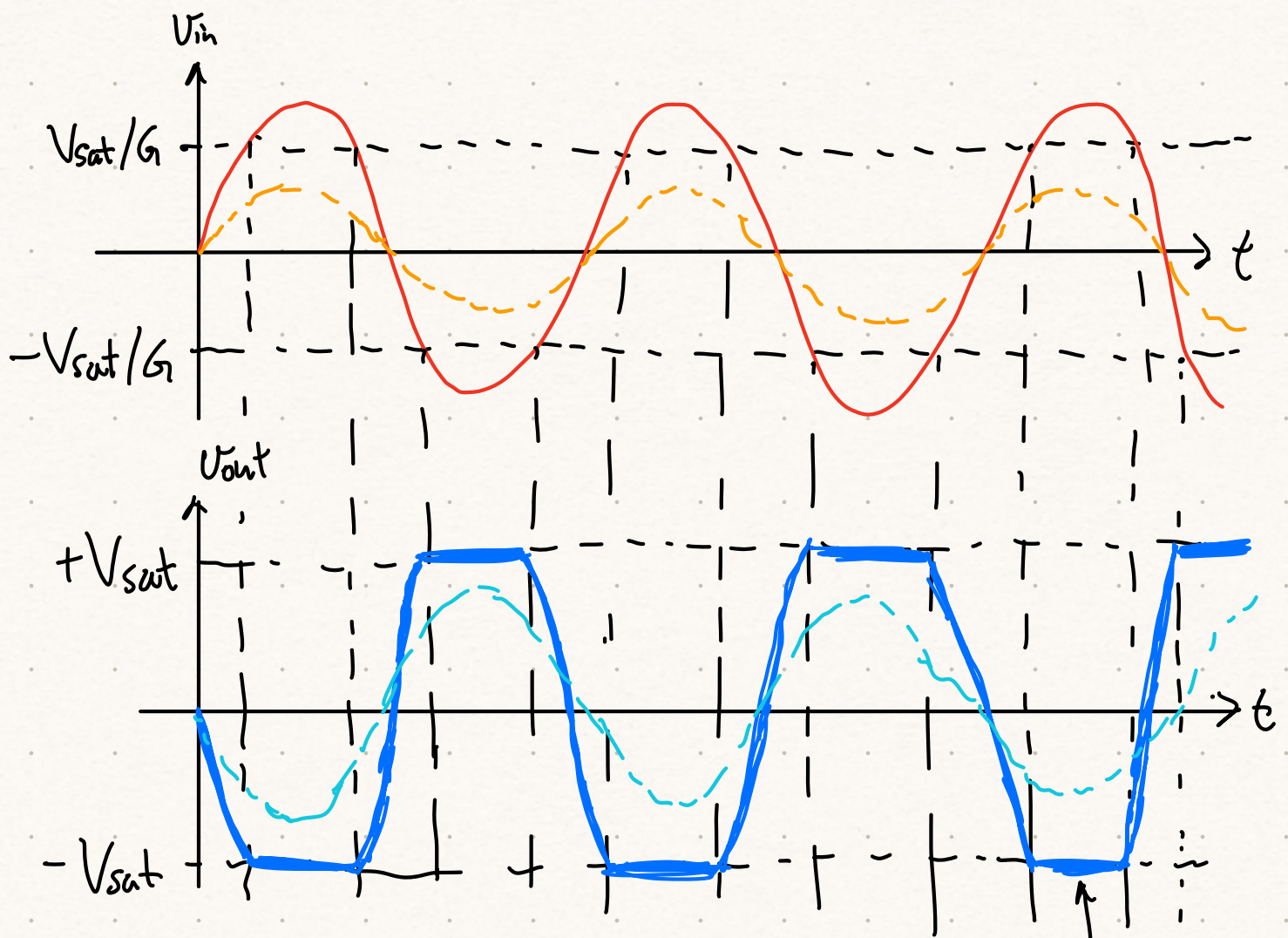To avoid saturating the output, we need to keep $V_{in} \leq \frac{V_{sat}}{G} \approx 140mV$.




Saturated or clipped op amp output.

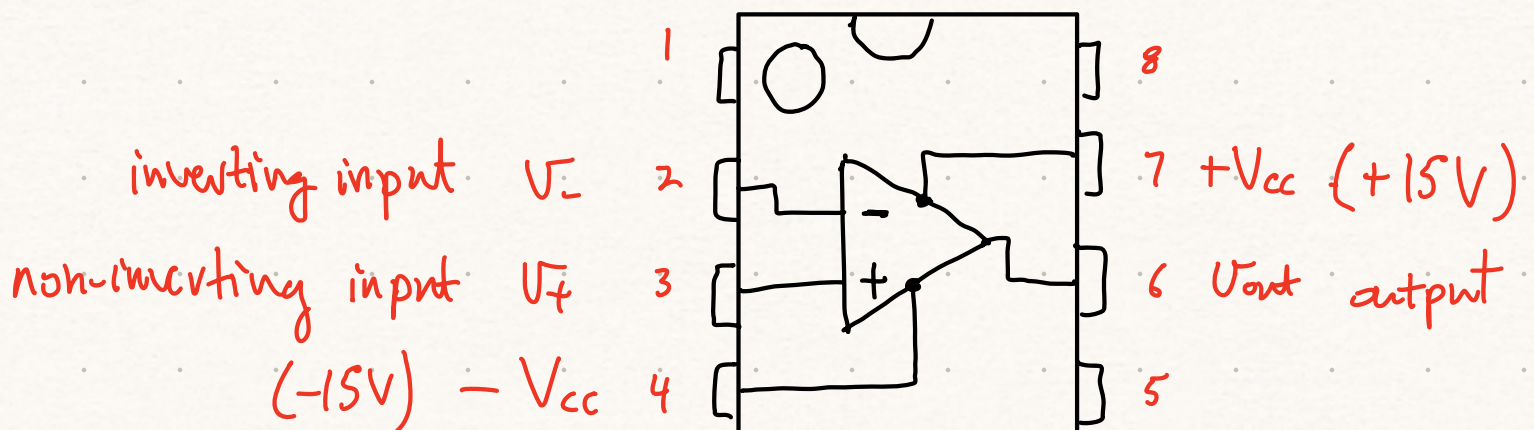Op amps come packaged as "integrated circuits" (ICs) or a "chip".




We will not use pins 1, 5, 8.

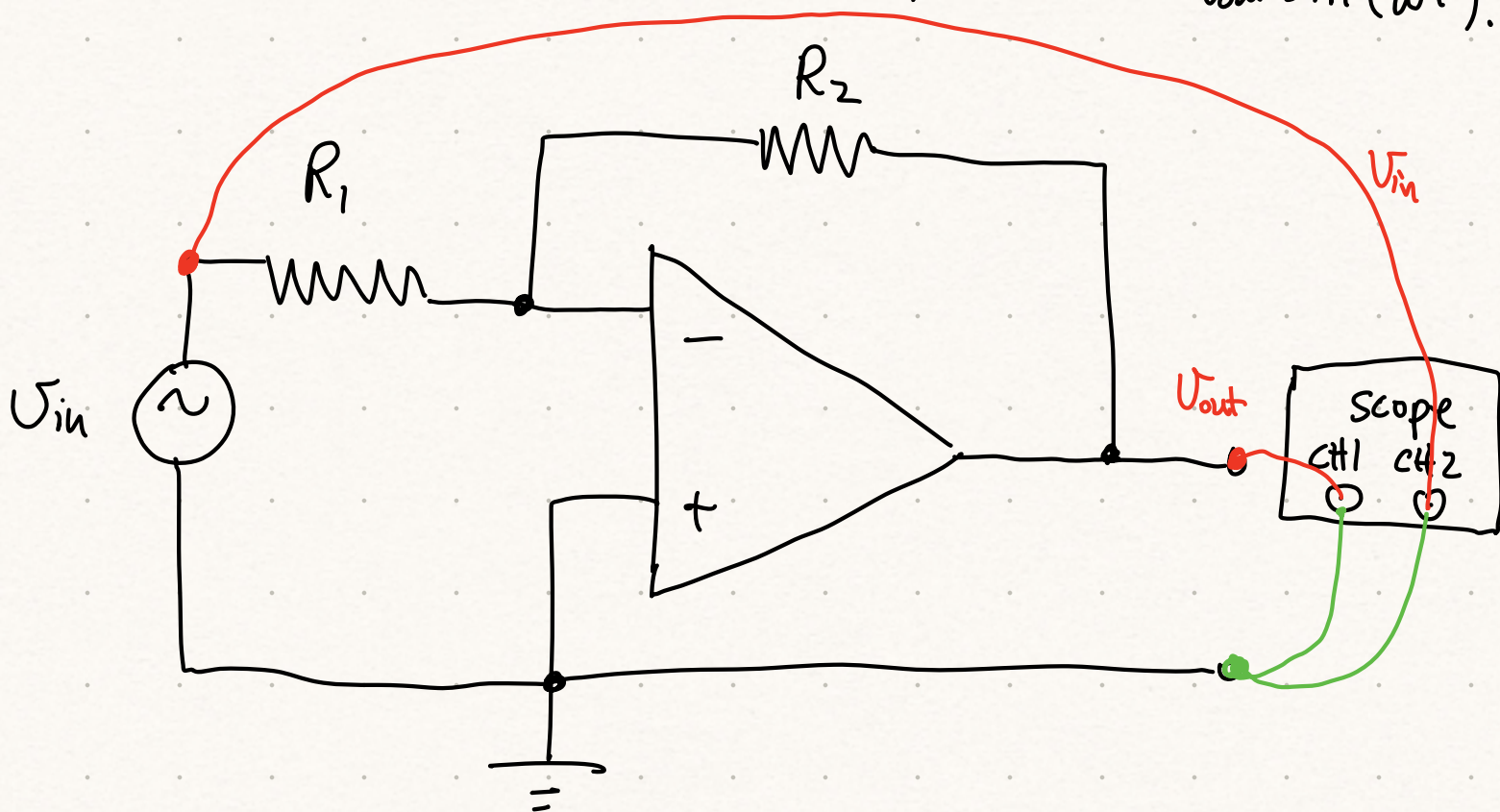In Lab #5, we will use a fcn generator to provide $V_{in} = V_0 \sin(\omega t)$. Meas. V_{in} & $V_{out} = -V_{out} \sin(\omega t)$.



Meas. amplitude of V_{in} (V_0) and amp. of V_{out} (V_{out}) as a fcn of freq. f .

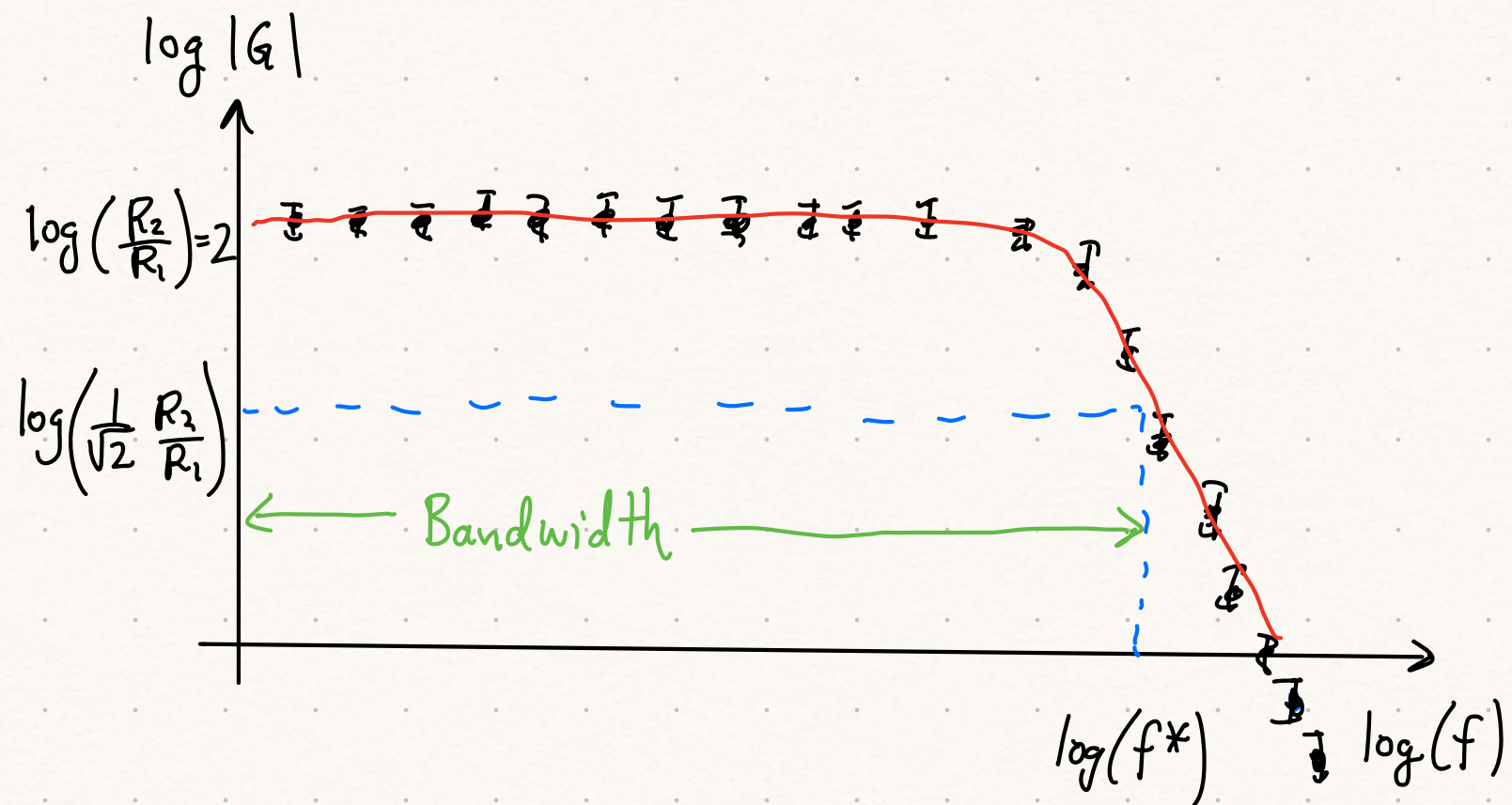Take the ratio $\frac{V_{out}}{V_0} = G$ to determine the circuit's gain vs freq.




At low enough freq., the $|G| = \frac{V_{out}}{V_o}$ is const,
or indep. of freq.

However, as freq is increased, eventually reach a point at which the gain decreases.

We define the "bandwidth" of the amplifier as the freq. f^* at which the gain falls to $\frac{1}{\sqrt{2}}$ of the low-freq. gain $G = \frac{R_2}{R_1}$.

The bandwidth (BW) $0 < BW < f^*$ defines the useful freq. range over which the amplifier works well.

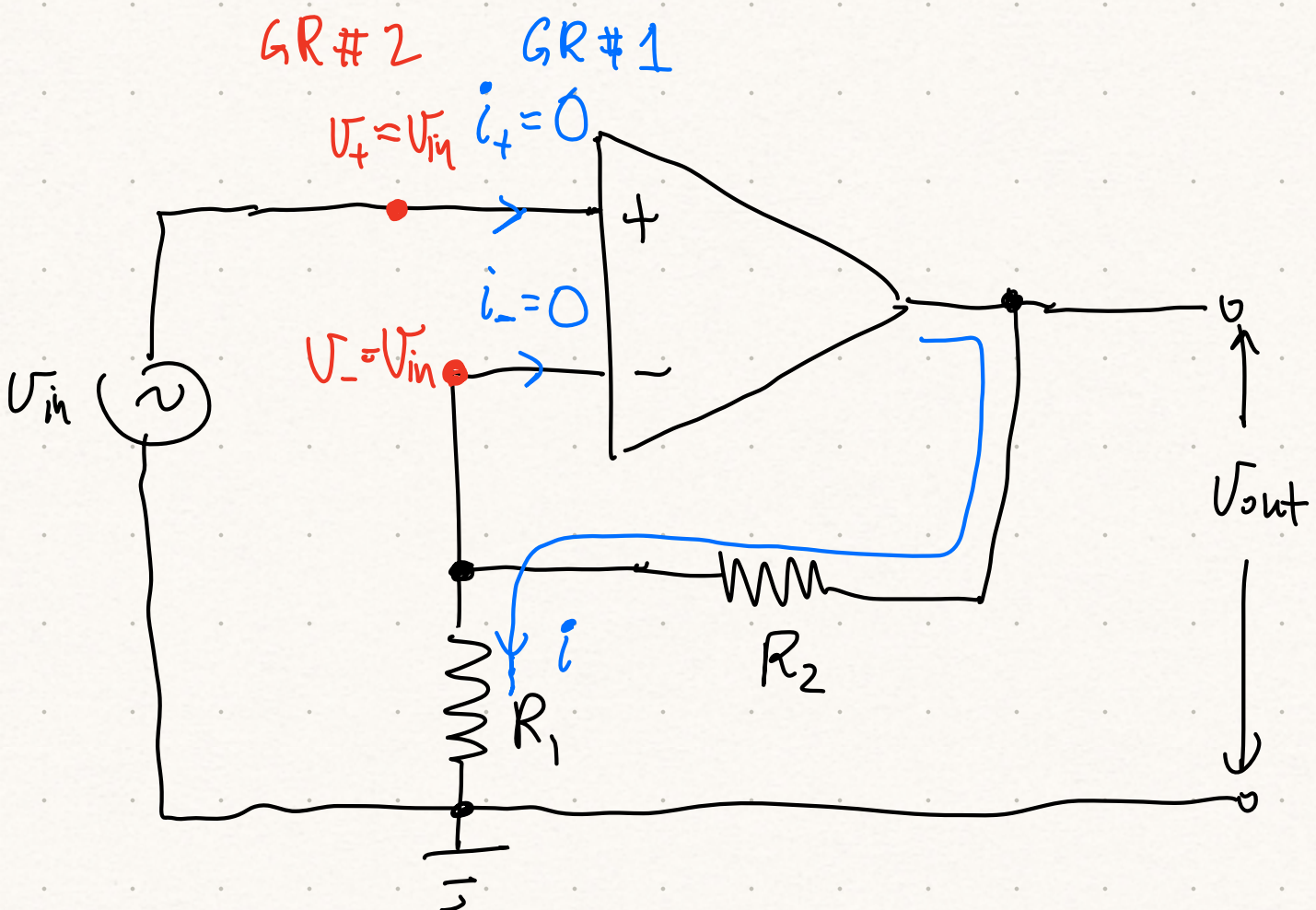Another op amp amplifier. $\rightarrow$ Non-inverting amp.



$\therefore$ Track volt. changes from V_- to gnd.

$$V_- - iR_1 = 0$$

$$\therefore V_{in} - iR_1 = 0 \Rightarrow$$

$$i = V_{in} / R_1$$

Track changes in volt. from V_{out} to gnd.

$$V_{out} - i(R_1 + R_2) = 0$$

$$\therefore V_{out} = i(R_1 + R_2)$$

$$\therefore V_{out} = \frac{V_{in}}{R_1} (R_1 + R_2) = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$\therefore \frac{V_{out}}{V_{in}} = G = \left(1 + \frac{R_2}{R_1}\right)$$

No negative sign.
 $\therefore$ non-inverting.

Here, the minimum possible gain is 1.
We cannot use the non-inverting amp to decrease the amp. of V_{in} @ V_{out} .