

Today: Digital Electronics & Logic Gates

In digital electronics, we work w/ voltages that are in only one of two possible states


$$L0 \rightarrow 0 \rightarrow 0V$$

$$H1 \rightarrow 1 \rightarrow 5V$$

Digital signals are processed using logic gates.

Types of logic gates:

1. NOT (inverter)

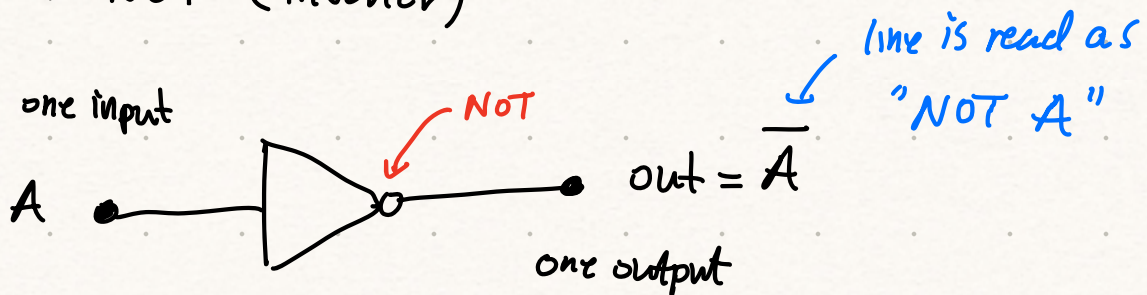


Inverter truth table

A	out = $\bar{A}$
0	1
1	0

In a truth table, list all possible inputs on left & corresponding outputs on right.

All other logic gates have two (or more) inputs.

2. AND

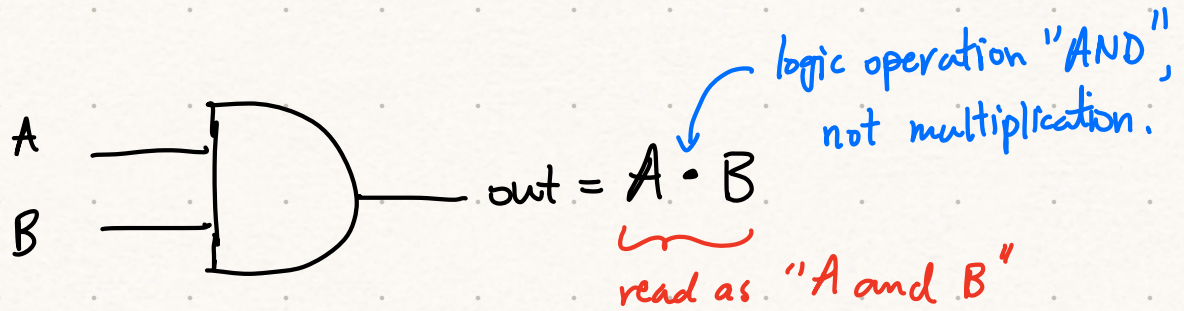


Truth table

A	B	out = A · B
0	0	0
0	1	0
1	0	0
1	1	1

outputs are like
the product of
the input states.

3. OR gate

read as "A OR B"


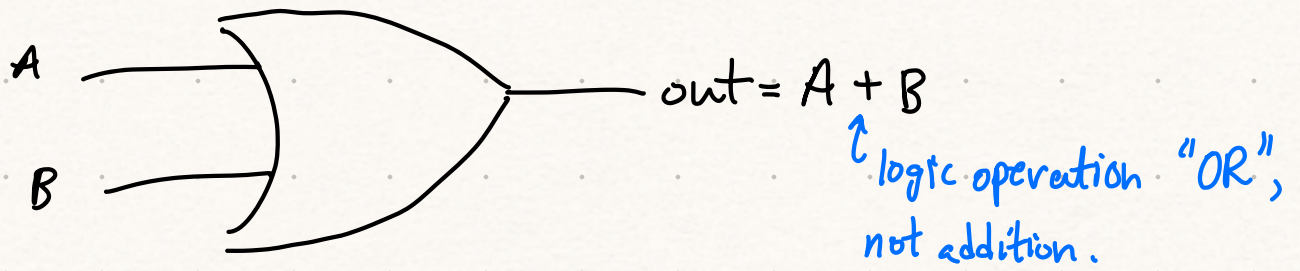


Truth table

A	B	out = $A + B$
0	0	0
0	1	1
1	0	1
1	1	1

4. NAND (NOT AND)

read as "A NAND B"
or "NOT A AND B".

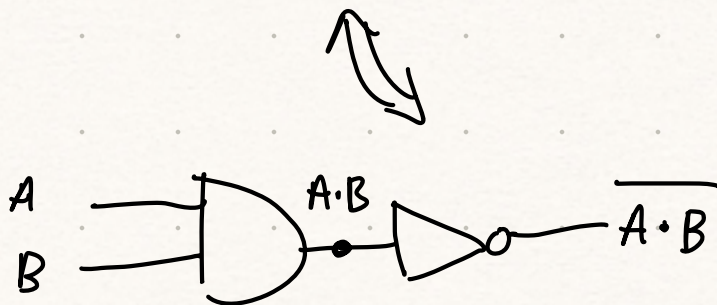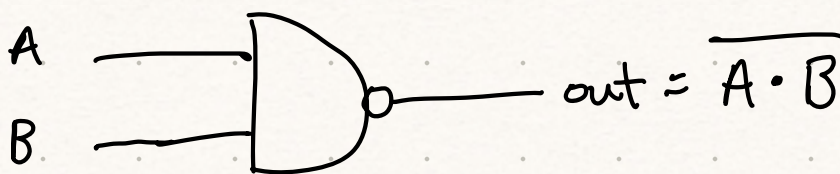


Truth Table

A	B	$A \cdot B$	out = $\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Note: All of the other logic gates can be constructed using only NAND gates. $\rightarrow$ NAND is industry standard.

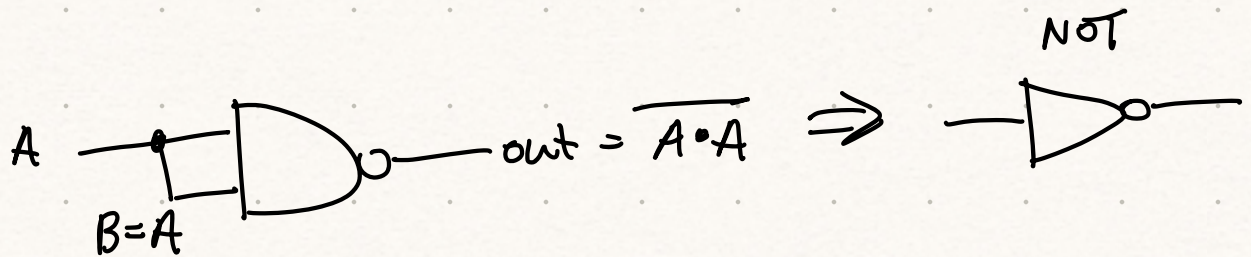Eg. Try connecting the inputs A and B of a NAND gate together



$A \neq B$

A	B	out = $\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0



A	out = $\overline{A}$
0	1
1	0


Exercise for the student: Design an OR gate using only NANDs

$\rightarrow$ need 3 NANDs to make an OR
 $\rightarrow$ make use of NOT gate above



Need for Lab #7 next week.


5. NOR (NOT OR)

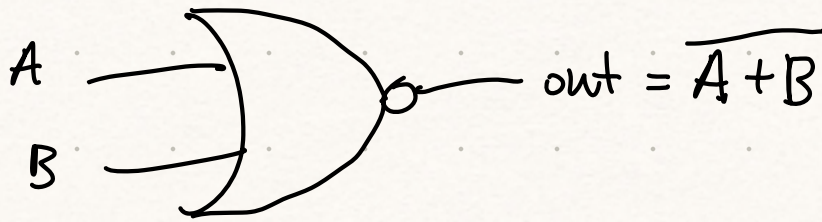

Truth table

A	B	$A+B$	$out = \overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

6. XOR (Exclusive OR)

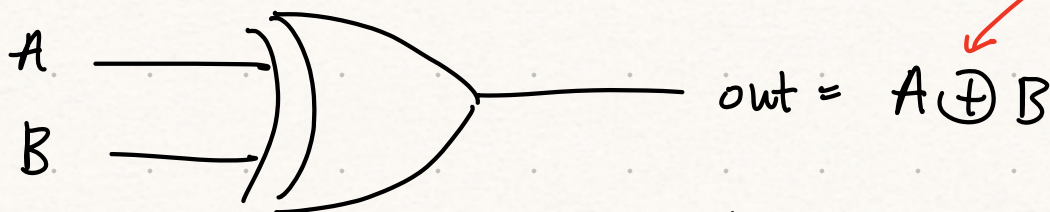


"exclusive OR" operation.

Truth Table

A	B	$out = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

like the OR gate truth table expect input $(A, B) = (1, 1)$ is excluded from producing $out = 1$.

2. XNOR (NOT exclusive OR)

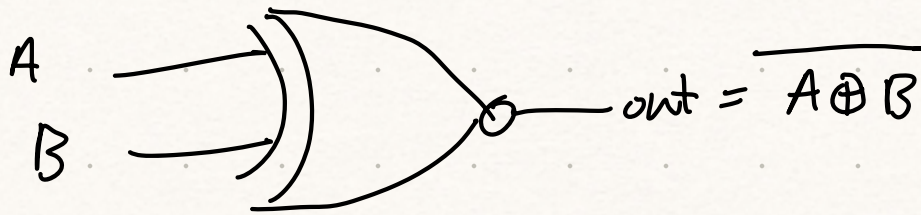

Truth Table

A	B	$A \oplus B$	$\text{out} = \overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1


Experiment #7 (Next week) Digital Basics

Part: Test one of the available logic gates.
(NOT, NAND)

Logic gates require +5V & gnd to operate.


Check data sheets to identify where +5V & gnd go.

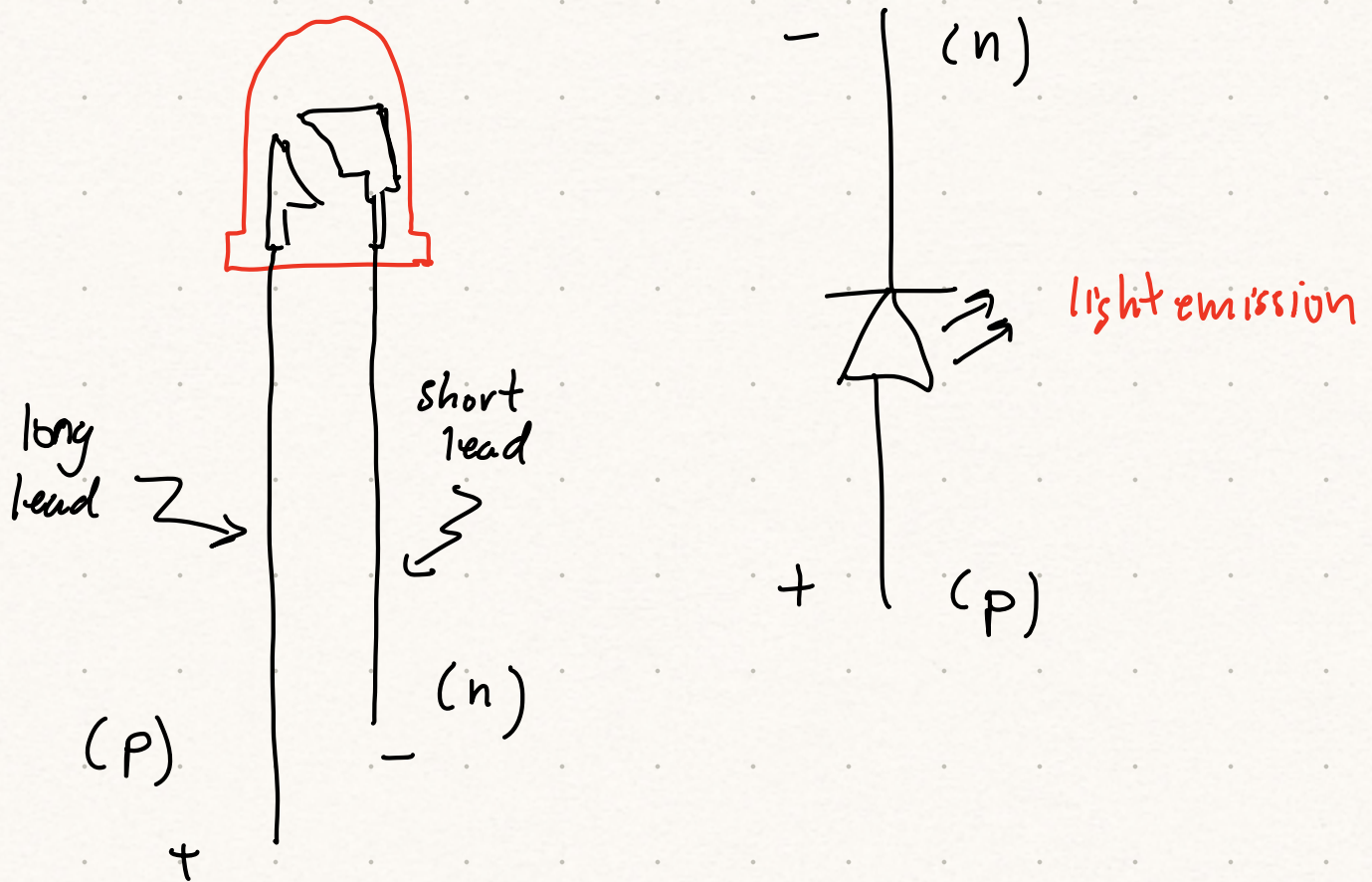Use light-emitting diodes (LEDs) to monitor the output of a logic gate.



When pos. terminal of an LED is higher in volt. than the neg. terminal by an amount V_{thresh} , LED lights up ($V_{\text{thresh}} \sim 2V$)

To test a logic gate (NAND)

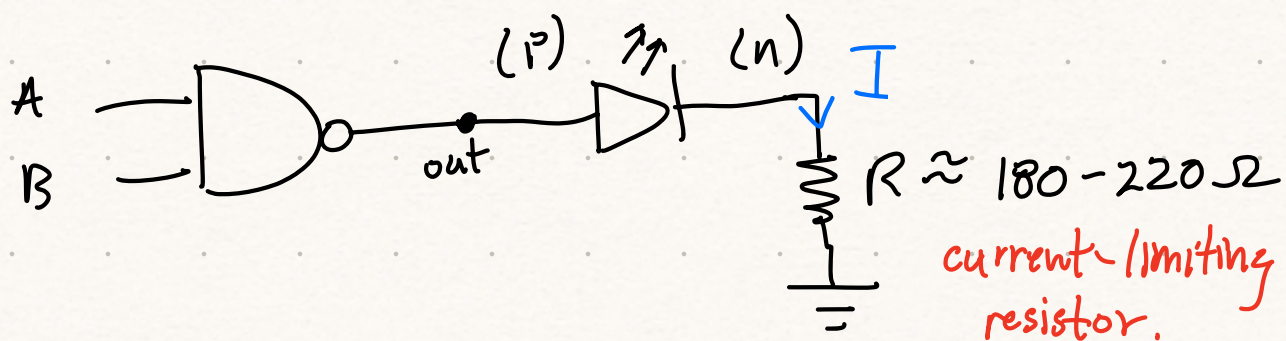

If $out = 5V$ (HI), then LED is conducting.

$$5V - V_{\text{thresh}} - IR = 0 \Rightarrow I = \frac{5V - V_{\text{thresh}}}{R}$$

$\uparrow$
potential barrier that
we need to overcome to
make the diode conduct current.