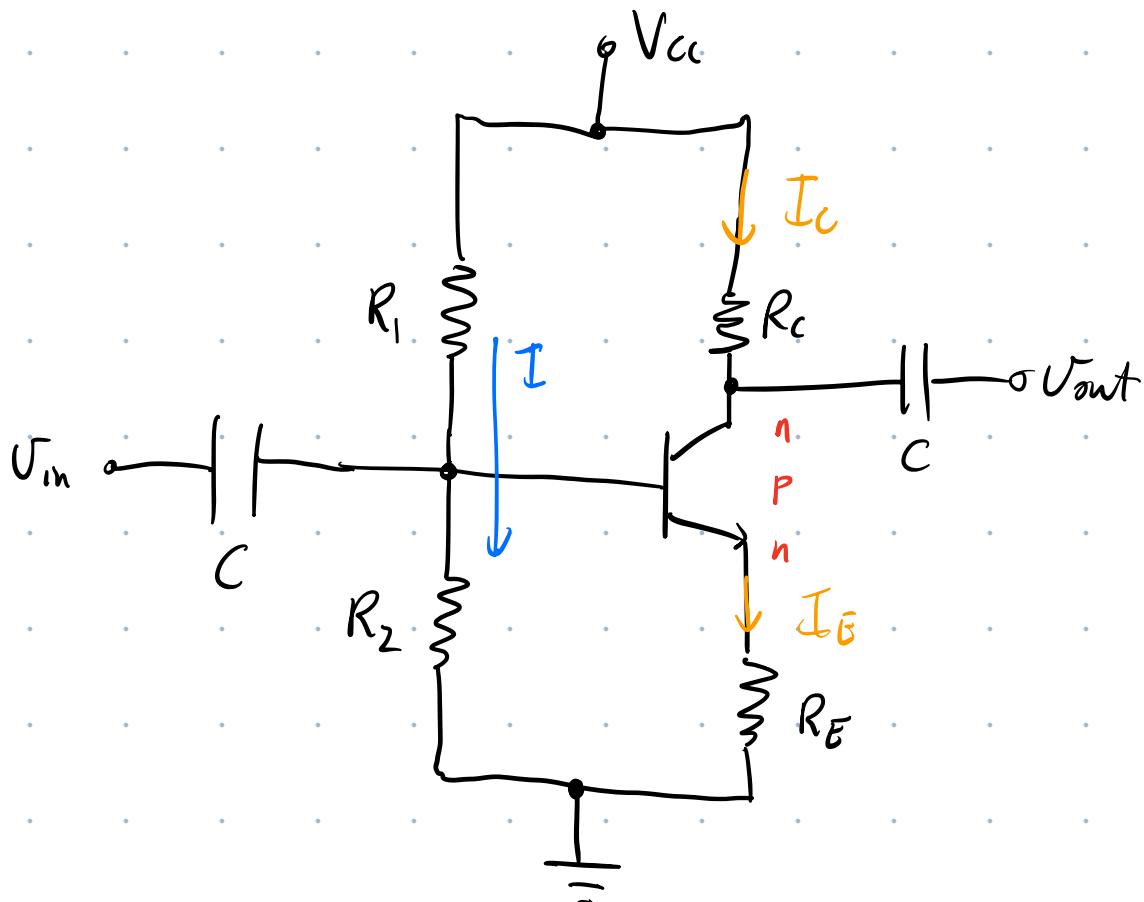


## Bipolar Junction Transistor (n-p-n configuration)


### Voltage Amplifier

Consider the following transistor circuit known as the "common emitter amplifier".



$V_{cc}$ ,  $R_1$ , &  $R_2$  are chosen to bias the transistor  
s.t. the B-E junction is forward biased & the  
B-C junction is reverse biased.

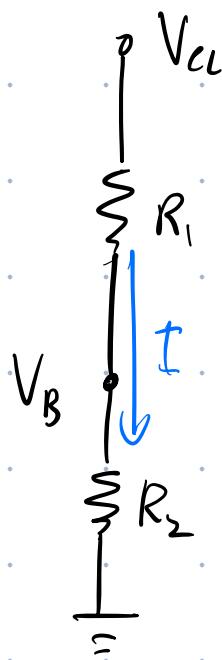Because  $I_B$  is small, we have (approximately):



$$V_{cc} - I(R_1 + R_2) = 0$$

$$\therefore I = \frac{V_{cc}}{R_1 + R_2}$$

$$\therefore V_B = IR_2 = V_{cc} \frac{R_2}{R_1 + R_2}$$


$$\text{require } V_B = V_{cc} \frac{R_2}{R_1 + R_2} \gtrsim 0.7 \text{ V}$$

To forward bias the B-E junction,

$$\text{On the other hand, } V_C = V_{cc} - I_C R_C$$

Require  $V_C > V_B$  to keep B-C jcn reverse biased.

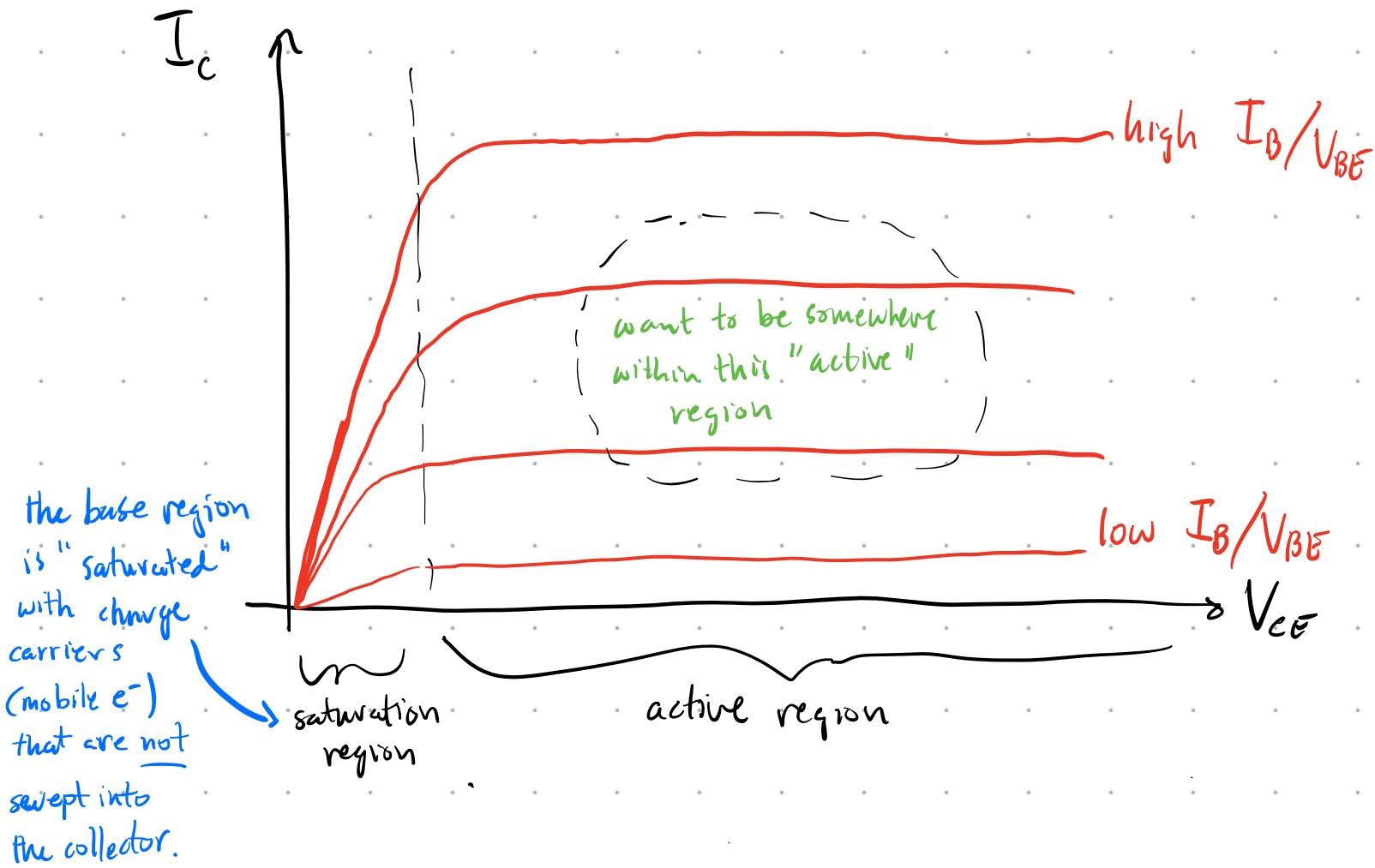Once proper biasing has been achieved, we are in the so-called "active" region of the I-V characteristic.




The purpose of the capacitors is to "decouple" the transistor from DC voltages at the input & output of the amplifier.

Recall that the impedance of a capacitor is  $Z_C = \frac{1}{j\omega C}$

$\therefore$  If  $\omega \rightarrow 0$  (DC), then  $Z_C \rightarrow \infty$ .  $\therefore$  The capacitors pass AC signals, but block DC.

Suppose  $V_{in} = V_0 \sin \omega t$ , where  $V_0$  is assumed to be much smaller than  $V_{cc}$ .

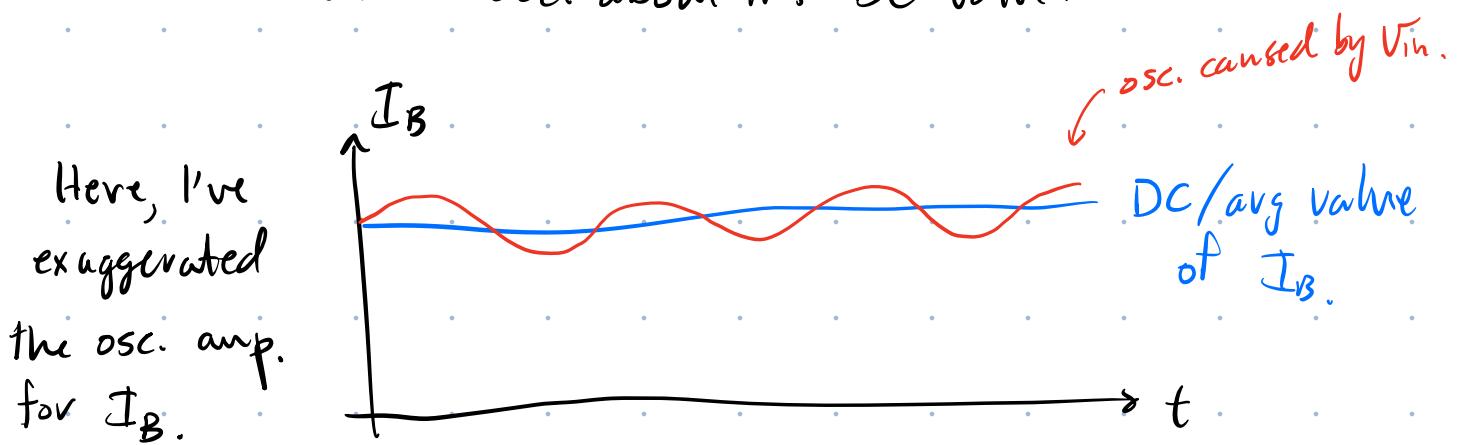In this case,  $V_{in}$  causes the base voltage and, therefore, current to osc. about its DC value.



Recall that small changes in  $I_B$  result in large changes to  $I_c$  (current amplifier)

Aside:

Some people like to think of the transistor as effectively a variable resistor. The "knob" that we use to tune the resistance is  $I_B$ . As  $I_B \uparrow$ , the resistance of the transistor decreases.

Because the B-E jcn is forward biased, the AC components of the voltages at the base & emitter are equal.

$$\therefore V_{in} = V_B = V_E \quad \left( \begin{array}{l} \text{Im using lower case } V/i \\ \text{for AC voltages/currents} \end{array} \right)$$

$$\therefore V_E = i_E R_E \Rightarrow i_E = \frac{V_E}{R_E} = \frac{V_B}{R_E}$$

If we assume  $\alpha \approx 1$  (recall  $I_C = \alpha I_E$  &  $\alpha \approx 0.99$ ), then we can write:

$$i_C \approx \frac{V_B}{R_E} = \frac{V_{in}}{R_E} \quad \otimes$$

We also know that the voltage at the collector is given by  $V_C = V_{cc} - I_C R_C$

But  $I_c$  has an AC component s.t. :

$$V_{out} = V_c = -i_c R_c$$

we get a neg. sign b/c  
as  $I_c \uparrow$ ,  $V_c = V_{cc} - I_c R_c \downarrow$

sub in  $\textcircled{1}$  for  $i_c$  to find

$$V_{out} = -\frac{R_c}{R_E} V_{in}$$

$\therefore$  the common-emitter  
amplifier is an inverting  
amplifier w/ gain

$$G_I = \frac{V_{out}}{V_{in}} = -\frac{R_c}{R_E}$$