

General Sol'n to transients in an LRC series circuit

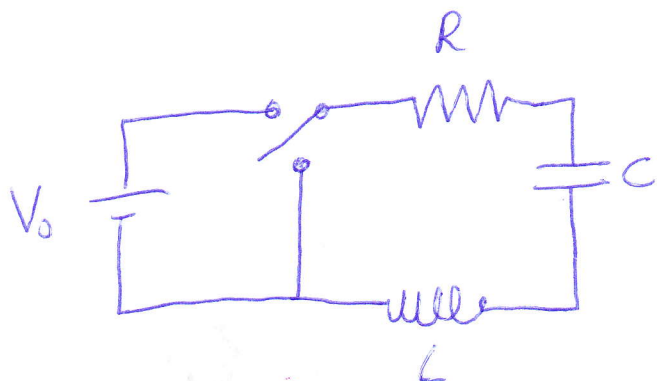


Fig. 1

K.V.R.

$$V_0 - IR - \frac{q}{C} - L \frac{dI}{dt} = 0$$

$$\therefore V_0 = L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q$$

① First, assume a sol'n of the form

⊕ $q(t) = q_h(t) + q_p$ where q_p is indep. of time.

then

$$V_0 = L \frac{d^2 q_h(t)}{dt^2} + R \frac{dq_h(t)}{dt} + \frac{1}{C} q_h(t) + \frac{1}{C} q_p$$

Time indep. parts must be equal:

$$\therefore \boxed{q_p = CV_0}$$

② Remaining time-dependent part is:

$$0 = L \frac{d^2 q_h(t)}{dt^2} + R \frac{dq_h(t)}{dt} + \frac{1}{C} q_h(t) \quad \text{homogeneous diff. eq'n.}$$

$$= \frac{d^2 q_h(t)}{dt^2} + \frac{R}{L} \frac{dq_h(t)}{dt} + \frac{1}{LC} q_h(t)$$

define $\gamma = \frac{R}{L}$ $\omega_0^2 = \frac{1}{LC}$

$$0 = \frac{d^2 q_h(t)}{dt^2} + \gamma \frac{dq_h(t)}{dt} + \omega_0^2 q_h(t)$$

① $\therefore \left(\frac{d^2}{dt^2} + \gamma \frac{d}{dt} + \omega_0^2 \right) q_h(t) = 0$
 like quadratic formula.

Aside. if $ax^2 + bx + c = 0$ then $x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

can be rewritten as:

$$= \frac{-b}{2a} \pm \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}}$$

$$\left(x + \frac{b}{2a} - \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} \right) \left(x + \frac{b}{2a} + \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} \right) = 0$$

check

$$x^2 + \frac{b}{a}x + \left(\frac{b}{2a}\right)^2 - \left[\left(\frac{b}{2a}\right)^2 - \frac{c}{a}\right] = 0$$

$$\therefore ax^2 + bx + c = 0 \quad \checkmark$$

Apply same factoring technique to the operator $\left(\frac{d^2}{dt^2} + \gamma \frac{d}{dt} + \omega_0^2\right)$

$$\begin{aligned} a &\rightarrow 1 & x &\rightarrow \frac{d}{dt} \\ b &\rightarrow \gamma \\ c &\rightarrow \omega_0^2 \end{aligned}$$

(i) becomes

$$(ii) \quad \left(\frac{d}{dt} + \frac{\gamma}{2} - \underbrace{\sqrt{\left(\frac{\gamma}{2}\right)^2 - \omega_0^2}}_{\equiv \beta}\right) \left(\frac{d}{dt} + \frac{\gamma}{2} + \underbrace{\sqrt{\left(\frac{\gamma}{2}\right)^2 - \omega_0^2}}_{\equiv \beta}\right) q_h(t) = 0$$

(3) Now assume that can find $q_1(t)$ & $q_2(t)$ such that:

$$(iii) \quad \left(\frac{d}{dt} + \frac{\gamma}{2} - \beta\right) q_1(t) = 0$$

$$(iv) \quad \left(\frac{d}{dt} + \frac{\gamma}{2} + \beta\right) q_2(t) = 0$$

Let's try $q_h(t) = q_1(t) + q_2(t)$ in Eq'n (ii)

$$\begin{aligned} &\left(\frac{d}{dt} + \frac{\gamma}{2} - \beta\right) \left(\frac{d}{dt} + \frac{\gamma}{2} + \beta\right) (q_1(t) + q_2(t)) \\ &= \underbrace{\left(\frac{d}{dt} + \frac{\gamma}{2} + \beta\right) \left(\frac{d}{dt} + \frac{\gamma}{2} - \beta\right) q_1(t)}_{=0 \text{ by (iii)}} + \underbrace{\left(\frac{d}{dt} + \frac{\gamma}{2} - \beta\right) \left(\frac{d}{dt} + \frac{\gamma}{2} + \beta\right) q_2(t)}_{=0 \text{ by (iv)}} = 0 \end{aligned}$$

∴ If (iii) & (iv) can be solved, then know that $q_n(t) = q_1(t) + q_2(t)$ is a sol'n to (i)

(4) Start w/ (iii) $\left(\frac{d}{dt} + \frac{\gamma}{2} - \beta\right) q_1(t) = 0$

∴ $\frac{dq_1(t)}{dt} = -\left(\frac{\gamma}{2} - \beta\right) q_1(t)$

∴ $\frac{dq_1(t)}{q_1(t)} = -\left(\frac{\gamma}{2} - \beta\right) dt$

Integrate

$\ln q_1(t) = -\left(\frac{\gamma}{2} - \beta\right)t + B$

∴ $q_1(t) = \underbrace{e^B}_{\equiv A_1} e^{-\left(\frac{\gamma}{2} - \beta\right)t}$

↙ integration const.

(v) $q_1(t) = A_1 e^{-\left(\frac{\gamma}{2} - \beta\right)t}$

Exact same procedure applied to (iv) gives:

(vi) $q_2(t) = A_2 e^{-\left(\frac{\gamma}{2} + \beta\right)t}$

$$\begin{aligned} \textcircled{5} \quad \therefore \text{ We get } q_h(t) &= q_1(t) + q_2(t) \\ &= (A_1 e^{\beta t} + A_2 e^{-\beta t}) e^{-\frac{\delta}{2} t} \end{aligned}$$

We need to use initial conditions to find A_1 & A_2 .

For this example, we'll assume that $\beta^2 = \left(\frac{\delta}{2}\right)^2 - \omega_0^2 < 0$

$$\text{Recall } \delta = \frac{R}{L} \quad \omega_0^2 = \frac{1}{LC}$$

\therefore assuming that $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} < 0 \Rightarrow R$ relatively small.

$\beta^2 < 0$ case referred to as the underdamped case

$$\begin{aligned} \text{Now } \beta &= \sqrt{\left(\frac{\delta}{2}\right)^2 - \omega_0^2} = \underbrace{\sqrt{-1}}_j \underbrace{\sqrt{\omega_0^2 - \left(\frac{\delta}{2}\right)^2}}_{\equiv \omega_1 \text{ (positive)}} = j\omega_1 \end{aligned}$$

$$\therefore q_h(t) = (A_1 e^{j\omega_1 t} + A_2 e^{-j\omega_1 t}) e^{-\frac{\delta}{2} t}$$

Recall Euler eq'n $e^{\pm j\phi} = \cos\phi \pm j\sin\phi$

$$\therefore q_h(t) = \left[A_1 (\cos\omega_1 t + j\sin\omega_1 t) + A_2 (\cos\omega_1 t - j\sin\omega_1 t) \right] e^{-\frac{\gamma}{2} t}$$

$$= \left[(A_1 + A_2) \cos\omega_1 t + j(A_1 - A_2) \sin\omega_1 t \right] e^{-\frac{\gamma}{2} t}$$

Clearly $q_h(t)$ is a real quantity. \therefore must have

$$A_1 - A_2 = 0 \quad \text{or} \quad A_1 = A_2 \equiv A$$

$$\therefore q_h(t) = 2A e^{-\frac{\gamma}{2} t} \cos\omega_1 t$$

still need to determine A!

(6) Returning to Fig. 1, let's assume that initially switch was in down position for a long time so that initially capacitor is uncharged.

Then at $t=0$ flip switch to up position.

$$\text{@ } t=0 \quad V_c = \frac{q}{C} = 0 \quad \text{i.e. @ } t=0 \quad q=0$$

Remember that the full sol'n for q is given by (A)

$$q(t) = q_h(t) + q_p$$


$$= 2Ae^{-\frac{\gamma}{2}t} \cos \omega_1 t + CV_0$$

\therefore @ $t=0$ must have

$$2A + CV_0 = 0 \quad \therefore A = -\frac{CV_0}{2}$$

So that finally

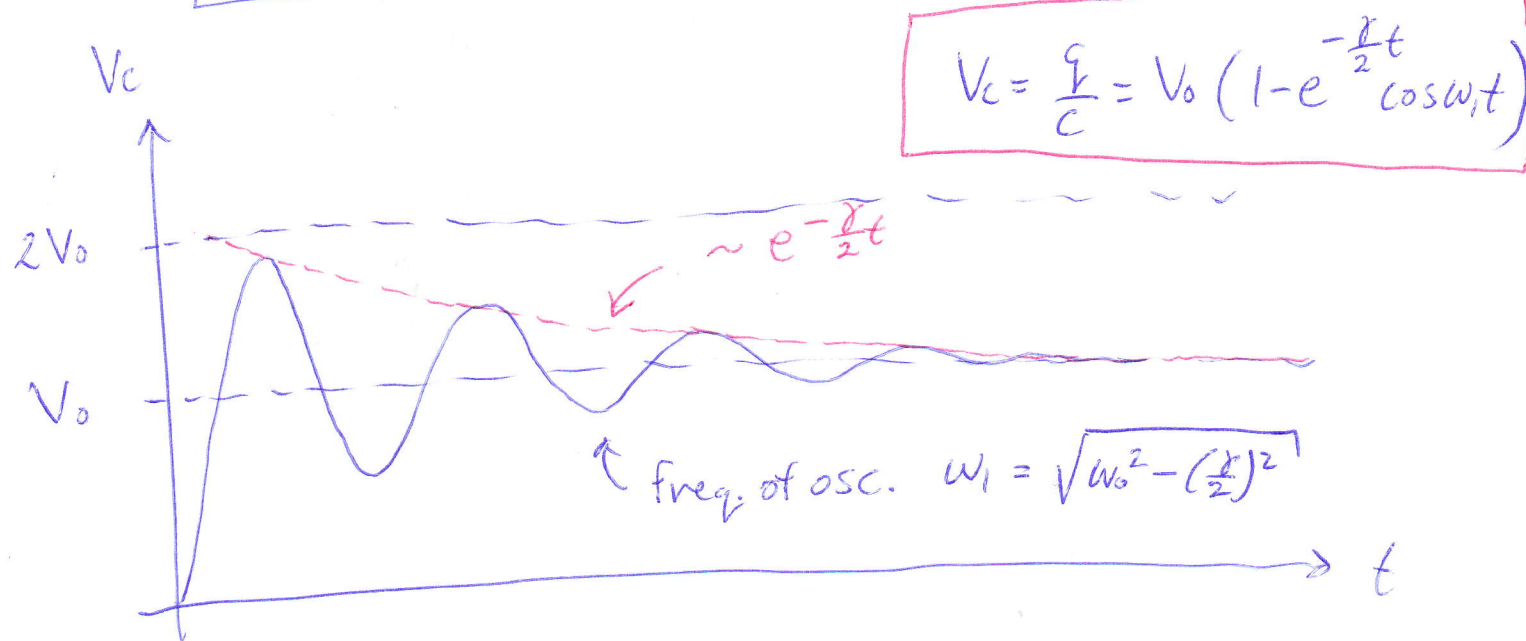(vii) $q(t) = CV_0 \left(1 - e^{-\frac{\gamma}{2}t} \cos \omega_1 t \right)$



Note that voltage across capacitor, at some instances in time, exceeds the voltage of the battery!

Let's try to understand this by considering the voltage across the inductor.

$$V_L = L \frac{dI}{dt} = L \frac{d^2q}{dt^2}$$

from (vii) $I = \frac{dq}{dt} = CV_0 \frac{\gamma}{2} e^{-\frac{\gamma}{2}t} \cos \omega_1 t + CV_0 e^{-\frac{\gamma}{2}t} \omega_1 \sin \omega_1 t$

$$\begin{aligned} \frac{d^2q}{dt^2} &= -CV_0 \left(\frac{\gamma}{2}\right)^2 e^{-\frac{\gamma}{2}t} \cos \omega_1 t - CV_0 \frac{\gamma}{2} e^{-\frac{\gamma}{2}t} \omega_1 \sin \omega_1 t \\ &\quad - CV_0 \frac{\gamma}{2} e^{-\frac{\gamma}{2}t} \omega_1 \sin \omega_1 t + CV_0 e^{-\frac{\gamma}{2}t} \omega_1^2 \cos \omega_1 t \end{aligned}$$

$$= -CV_0 \gamma \omega_1 e^{-\frac{\gamma}{2}t} \sin \omega_1 t$$

$$+ CV_0 e^{-\frac{\gamma}{2}t} \cos \omega_1 t \left[\omega_1^2 - \left(\frac{\gamma}{2}\right)^2 \right]$$

$$\therefore V_L = L \frac{d^2q}{dt^2} = \frac{-V_0 \gamma \omega_1}{\omega_0^2} e^{-\frac{\gamma}{2}t} \sin \omega_1 t + V_0 \frac{\left[\omega_1^2 - \left(\frac{\gamma}{2}\right)^2 \right]}{\omega_0^2} e^{-\frac{\gamma}{2}t} \cos \omega_1 t$$

$$V_R = IR$$

* Complicated! *

For example,
 plot V_C , V_L ,
 & V_R as
 a fun of time
 using values
 from Lab 4.

$V_0 = 5V$
 $R = 1000\Omega$
 $L = 20mH$
 $C = 1nF$


$\gamma = \frac{R}{L} = 5 \times 10^4 s^{-1}$

$\omega_0^2 = \frac{1}{LC} = 5 \times 10^{10} s^{-2} \Rightarrow \omega_0 = 2.24 \times 10^5 s^{-1}$

$\therefore \omega_i = \sqrt{\omega_0^2 - (\frac{\gamma}{2})^2} = 2.22 \times 10^5 s^{-1}$
 $\approx \omega_0$

See plots on the next page.

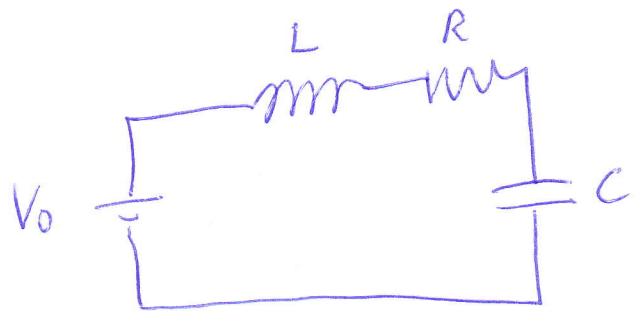
When switch is closed, have following circuit




From the plots can clearly see that

$V_0 = V_R + V_L + V_C$ s.t. Kirchhoff loop rule
 satisfied at all times.

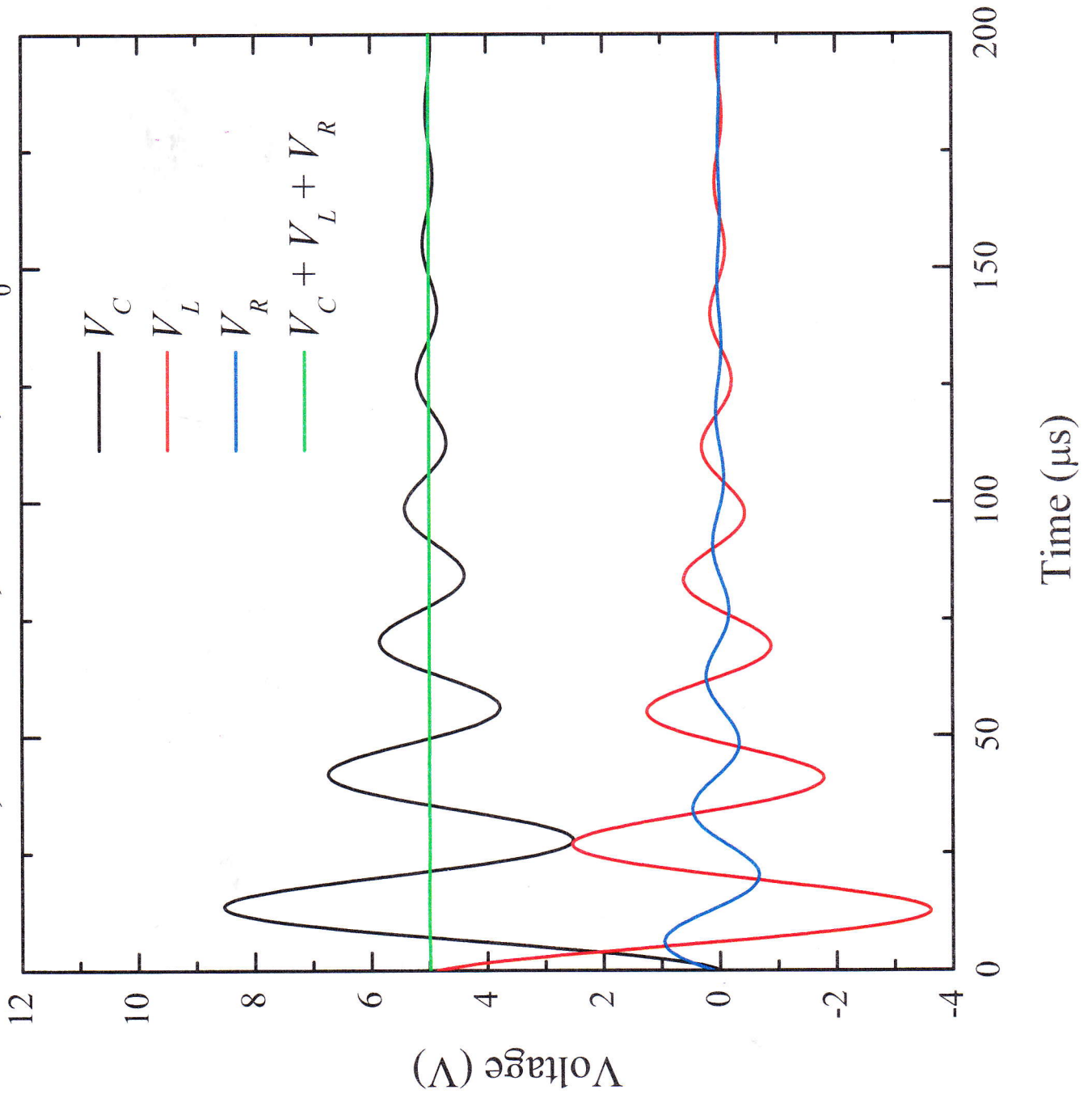Series LRC -circuit for an initially uncharged capacitor with:
 $R = 1 \text{ k}\Omega$, $L = 20 \text{ mH}$, $C = 1 \text{ nF}$, and $V_0 = 5 \text{ V}$



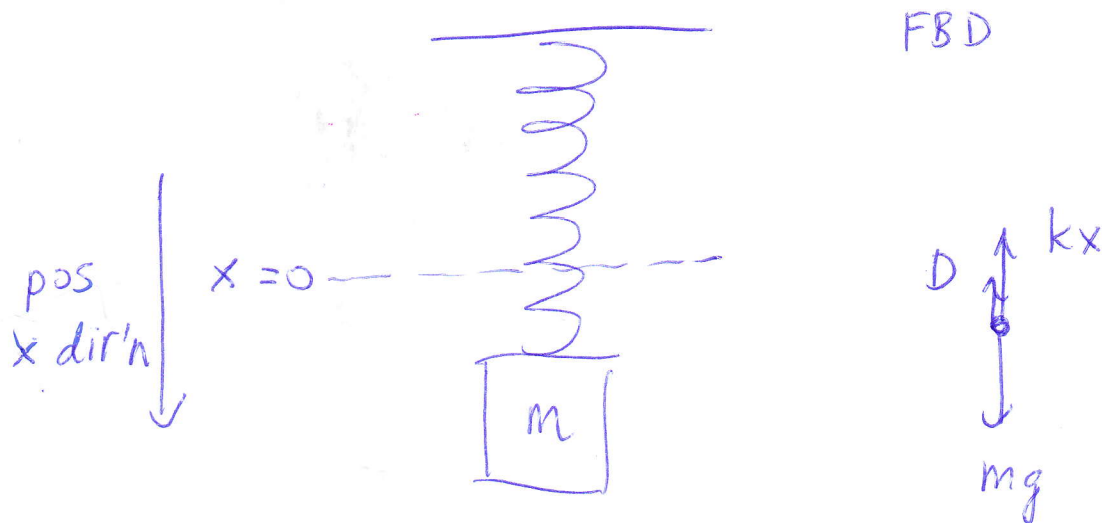Consider the mechanical analogy of mass on a spring experiencing viscous drag



assume
 $D = bV$
 (prop. to V)

$$ma = -kx - bV + mg$$

$$\therefore m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = mg$$

$$\text{or } \frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m} x = g$$

similar to our original diff. eq'n for LRC series circuit

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V_0$$

$$\text{or } \frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = \frac{V_0}{L}$$

If you had a mass suspended from a spring & you could suddenly change the value of the gravitational acceleration g ,

then mass would start oscillating about a new equilibrium position $(x_{eq} = \frac{mg}{k})$.

Of course, the instantaneous position could be greater than or less than x_{eq} .

For the LRC circuit, the equilibrium charge on the capacitor is $q_{eq} = CV_0$ ($= q_P$ on page 1)

If we suddenly make a change to the value of V_0 , charge will oscillate, but around a new equilibrium position.

- Let's push the analogy a little further...

For the mass on a spring, if spring is stretched beyond x_{eq} in pos. dir'n then acceleration $\frac{d^2x}{dt^2}$ is in neg. dir'n.

(and vice-versa).

Likewise, for the LRC circuit, if capacitor charge is greater than q_{eq} , then $\frac{d^2q}{dt^2} \propto V_L$ is negative.

Take a look at the plots on page 10.

- Also, for mass on a spring, $v = \frac{dx}{dt}$ is max as mass passes through x_{eq} & $\frac{dx}{dt} = 0$ when mass is a turning point

Likewise, for LRC circuit, if capacitor charge is passing through q_{eq} , then $\frac{dq}{dt} \propto V_R$ is a maximum,

$\frac{dq}{dt} \propto V_R$ is zero when q is a max or min.

Look at the plots on page 10.

Note $q \propto V_C$

As a last point, consider the energy.

Energy stored in capacitor is

$$U_C = \frac{1}{2C} q^2$$

Energy stored in inductor is

$$U_L = \frac{L}{2} I^2$$

Know $q(t) = CV_0(1 - e^{-\frac{\gamma}{2}t} \cos \omega_1 t)$

$$I(t) = CV_0 e^{-\frac{\gamma}{2}t} \left[\frac{\gamma}{2} \cos \omega_1 t + \omega_1 \sin \omega_1 t \right]$$

Using the same component values on page (9),

can plot U_C & U_L as a fun of time.

The power (energy per unit time) dissipated by the resistor is $I^2 R$

$$U_R = \int_0^t I^2 R dt$$

The sum of the energy stored in C , L , and energy consumed by R , should total the energy provided by the battery (voltage source).

Power provided by battery (source) is

$$P_{\text{source}} = I \cdot V$$


$$\therefore U_{\text{source}} = \int_0^t I V dt$$

The plot on page (16) shows U_R, U_L, U_C

& verifies that $U_R + U_L + U_C = U_{\text{source}}$

(energy is conserved at all times)

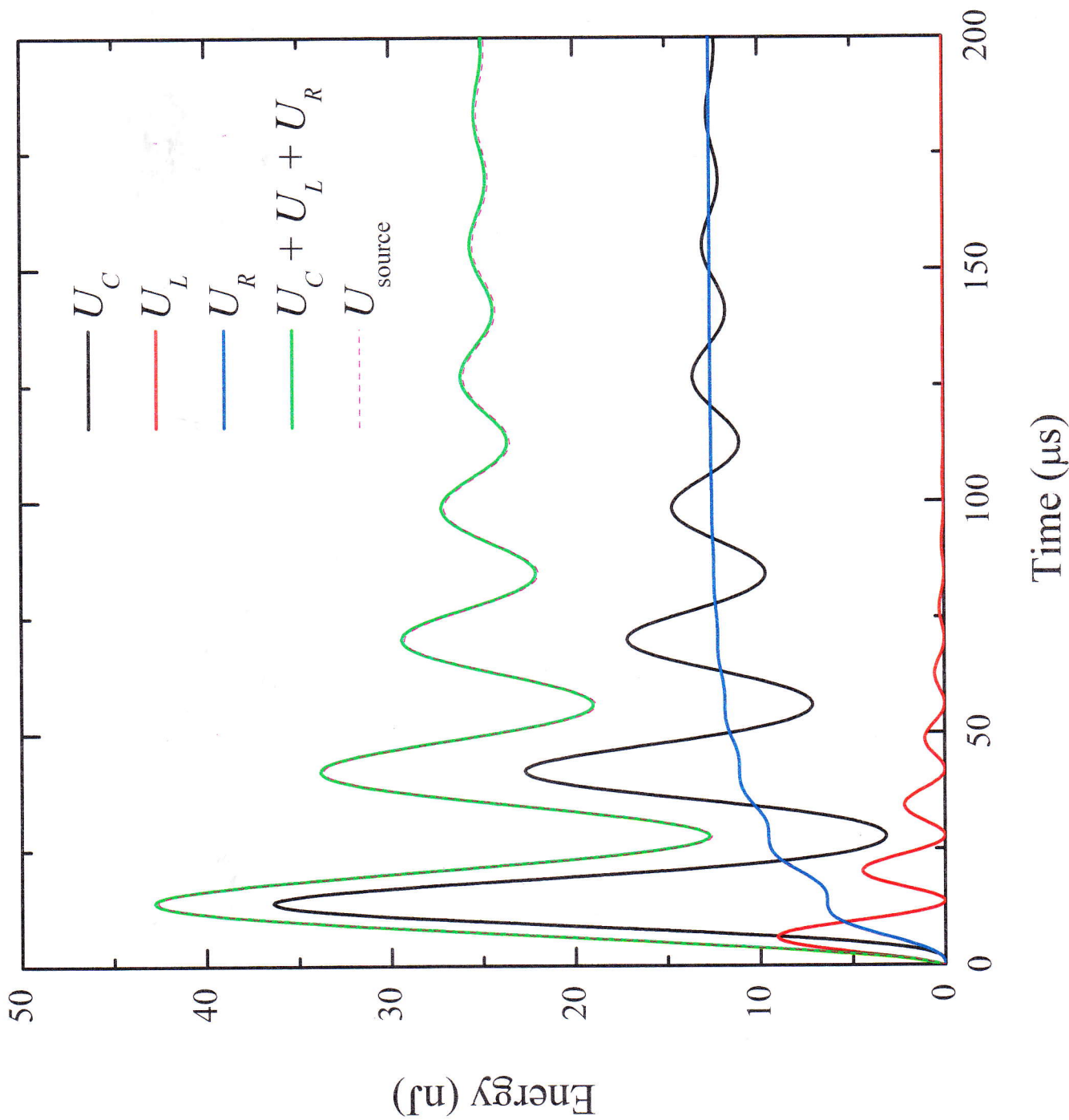Series LRC -circuit for an initially uncharged capacitor with:
 $R = 1 \text{ k}\Omega$, $L = 20 \text{ mH}$, $C = 1 \text{ nF}$, and $V_0 = 5 \text{ V}$ (energy analysis)



Return to (viii) & (ix)

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = \underbrace{mg}_{F_G}$$

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V_0$$

For mechanical system kinetic energy is $\frac{1}{2} m v^2 = \frac{1}{2} m \left(\frac{dx}{dt} \right)^2$

Analogous quantities in LRC circuit are

$$\left. \begin{array}{l} m \rightarrow L \\ v = \frac{dx}{dt} \rightarrow I = \frac{dq}{dt} \end{array} \right\} \therefore \text{K.E.} = \frac{1}{2} m v^2$$

$$\boxed{\frac{1}{2} L I^2 = U_L}$$

Magnetic energy stored by inductor corresponds to K.E. of mass.


When mass moves through equil. position, v is a max & K.E. peaks.

When charge on cap. goes through equil. charge, I is a max & U_L peaks.

(pos. or neg)


See plots of $V_R \propto I$ & U_L on page (18).

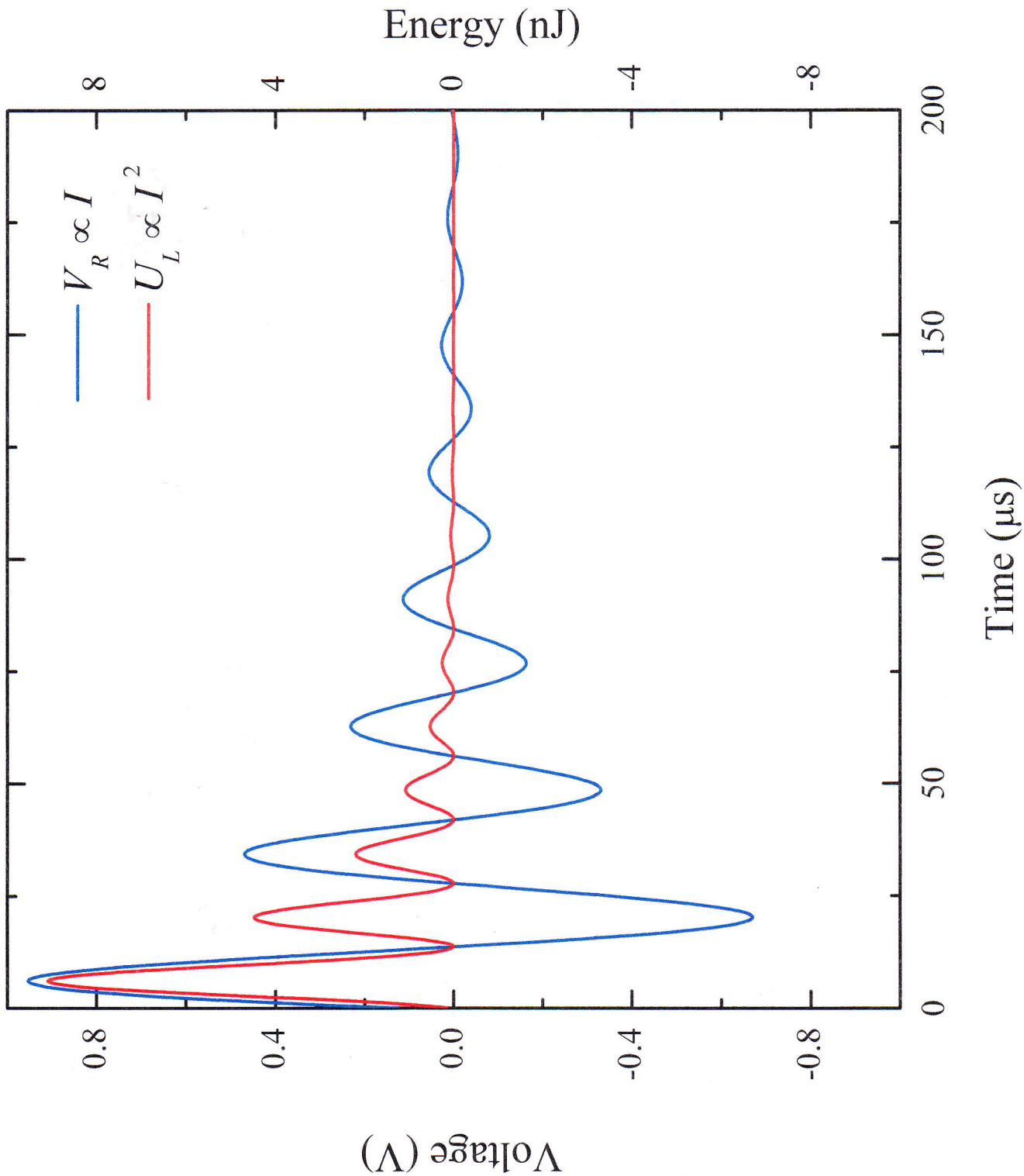Series LRC-circuit for an initially uncharged capacitor with:
 $R = 1 \text{ k}\Omega$, $L = 20 \text{ mH}$, $C = 1 \text{ nF}$, and $V_0 = 5 \text{ V}$



Consider P.E. of mech. system. Measure P.E. wr.t $x=0$.

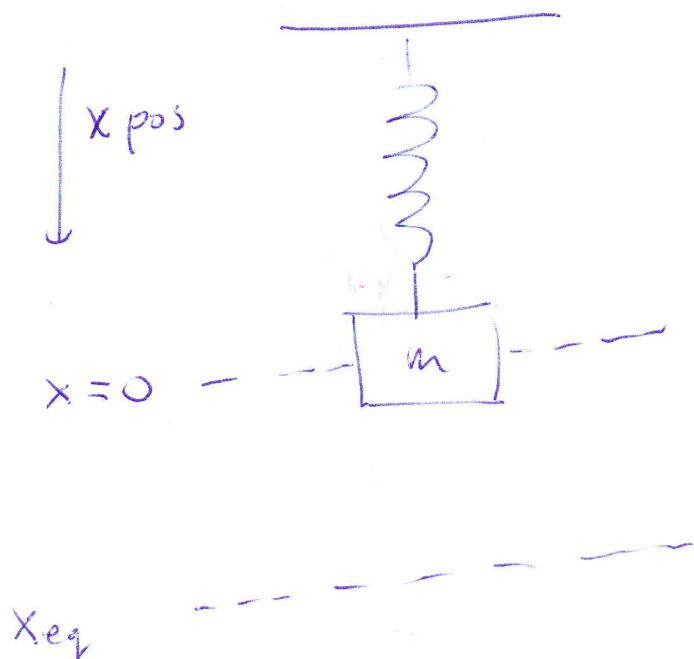If could suddenly increase g , would establish new equil. pos. x_{eq} .



$$P.E. = \frac{1}{2} k x^2$$

$$\text{Equil. P.E. is } \frac{1}{2} k x_{eq}^2$$

$$= \frac{1}{2} k \left(\frac{mg}{k} \right)^2$$

$$= \frac{1}{2} \frac{F_g^2}{k}$$

Mechanical P.E. w/ oscillate about the value $\frac{F_g^2}{2k}$


Peaks & dips of P.E. correspond to where v is instantaneously zero (turning points).

In LRC circuit, $P.E. = \frac{1}{2} k x^2 \Rightarrow \frac{q^2}{2C} = U_C.$

When current is instantaneously zero ($V_R \propto I$), get peaks & dips in U_C .

See plots of $V_R \propto I$ & U_C on page (20).

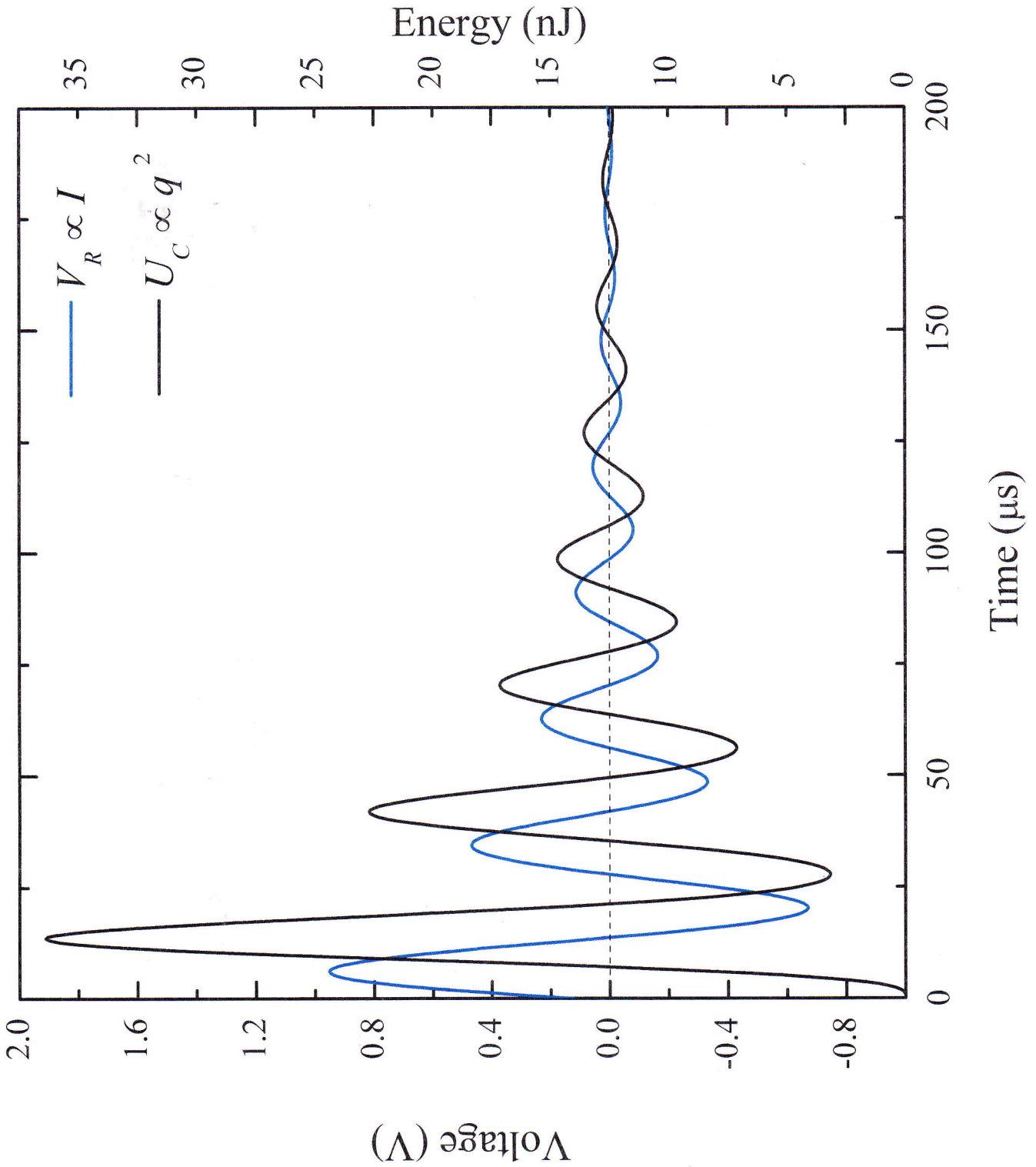Series LRC -circuit for an initially uncharged capacitor with:
 $R = 1 \text{ k}\Omega$, $L = 20 \text{ mH}$, $C = 1 \text{ nF}$, and $V_0 = 5 \text{ V}$




Finally power dissipated by resistor is $P_R = I^2 R$

$$\begin{aligned} \therefore U_R &= \int I^2 R = R \int I^2 dt \Rightarrow b \int v^2 dt = \int (bv) v dt \\ &= \int (bv) \left(\frac{dx}{dt} dt \right) \\ &= \int D dx = \text{work by drag force.} \end{aligned}$$

Power supplied by battery is $P_{\text{source}} = I \cdot V_0$

$$\begin{aligned} \therefore U_{\text{source}} &= \int V_0 I dt = V_0 \int I dt \Rightarrow F_G \int v dt = F_G \Delta x \\ &\quad \underbrace{\hspace{10em}} \\ &\quad \text{work by force of gravity.} \end{aligned}$$

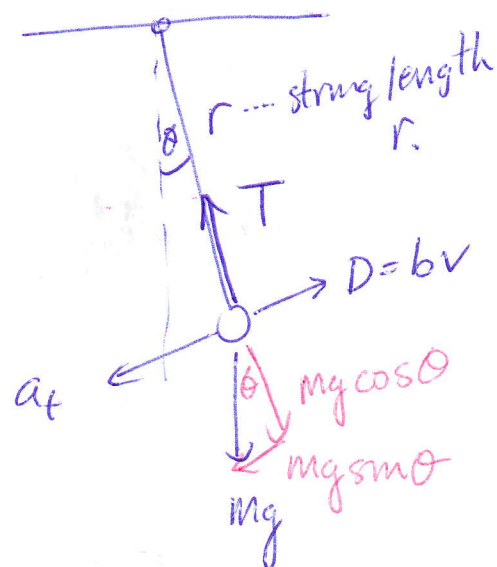Now, just for fun, let's see if we can think of another mechanical analogy \Rightarrow pendulum.



$$m a_t = m g \sin \theta - b v$$

$$a_t = r \alpha = r \ddot{\theta} = r \frac{d^2 \theta}{dt^2}$$

$$v = r \omega = r \dot{\theta} = r \frac{d\theta}{dt}$$

$$\therefore m r \frac{d^2 \theta}{dt^2} + b r \frac{d\theta}{dt} - m g \sin \theta = 0$$


small angle approx $\sin \theta \approx \theta$

$$m \frac{d^2 \theta}{dt^2} + b \frac{d\theta}{dt} - \frac{m g}{r} \theta = 0$$

} like eq'ns (viii) & (ix) on page (11), but there is no constant (V_0 or F_G) on r.h.s.

Need a mechanism to shift equilibrium position.

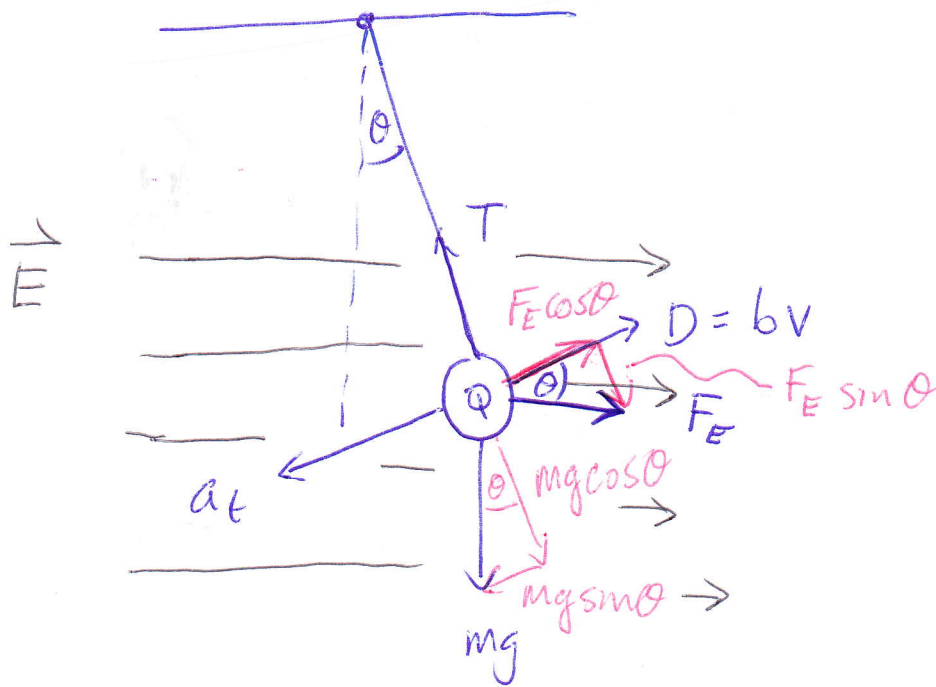Consider the following modification, place charge Q on bob of the pendulum & apply a horizontal electric field.



Now

$$ma_t = mg \sin \theta - bv - F_E \cos \theta$$

$$mr\alpha = mg \sin \theta - br\omega - F_E \cos \theta$$

$$mr \frac{d^2\theta}{dt^2} = mg \sin \theta - br \frac{d\theta}{dt} - F_E \cos \theta$$

small angle approx

$$\sin \theta \approx \theta$$

$$\cos \theta \approx 1$$

$$\therefore mr \frac{d^2\theta}{dt^2} = mg\theta - br \frac{d\theta}{dt} - F_E$$

Finally,

$$F_E = -mr \frac{d^2\theta}{dt^2} - br \frac{d\theta}{dt} + mg\theta$$

Like (viii) & (ix)

Can shift equil. position of pendulum by tuning either the charge Q or the electric field \vec{E}

$$(\vec{F}_E = Q\vec{E})$$