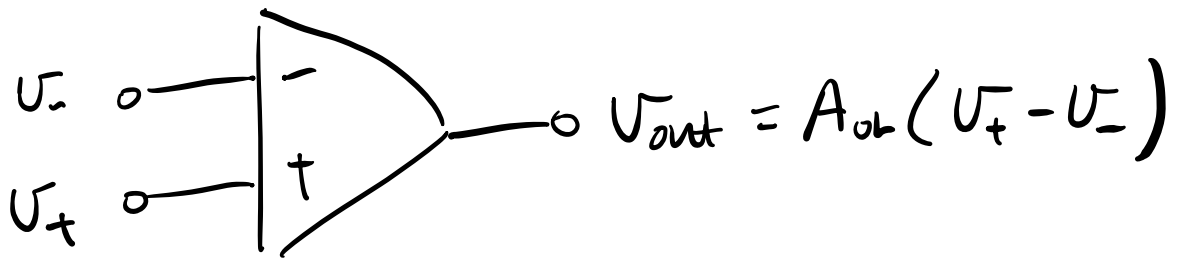


PHYS 231 - Nov. 1, 2023

Last Time: Op Amps




Golden Rules:

1. Current into/out of op amp inputs is zero. $\Rightarrow i_+ = i_- = 0$

2. When using negative feedback,

$$V_+ = V_-.$$

Inverting Amplifier (Lab #5).

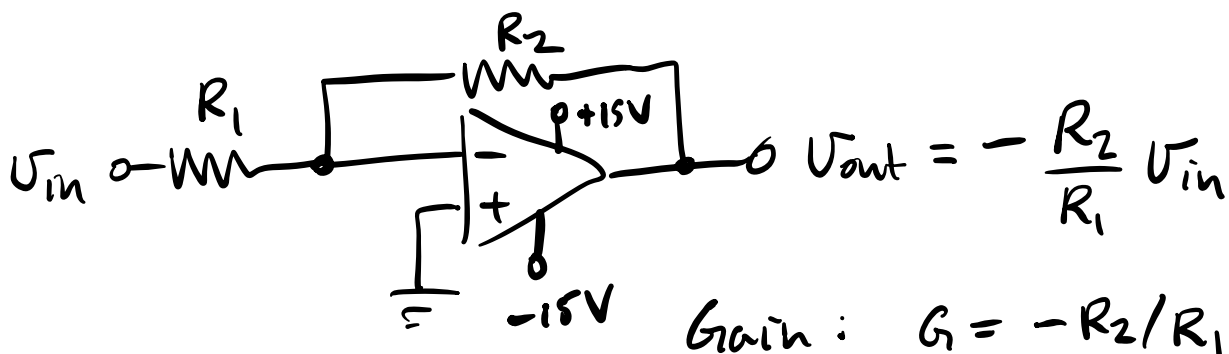

Tomorrow's Lab:

Build inverting amplifier using


$$R_1 = 1k\Omega$$

$$R_2 = 100k\Omega.$$


$$V_{in} = V_0 \sin(\omega t)$$

V_{out} is meas. w/ osc.

Limitations:

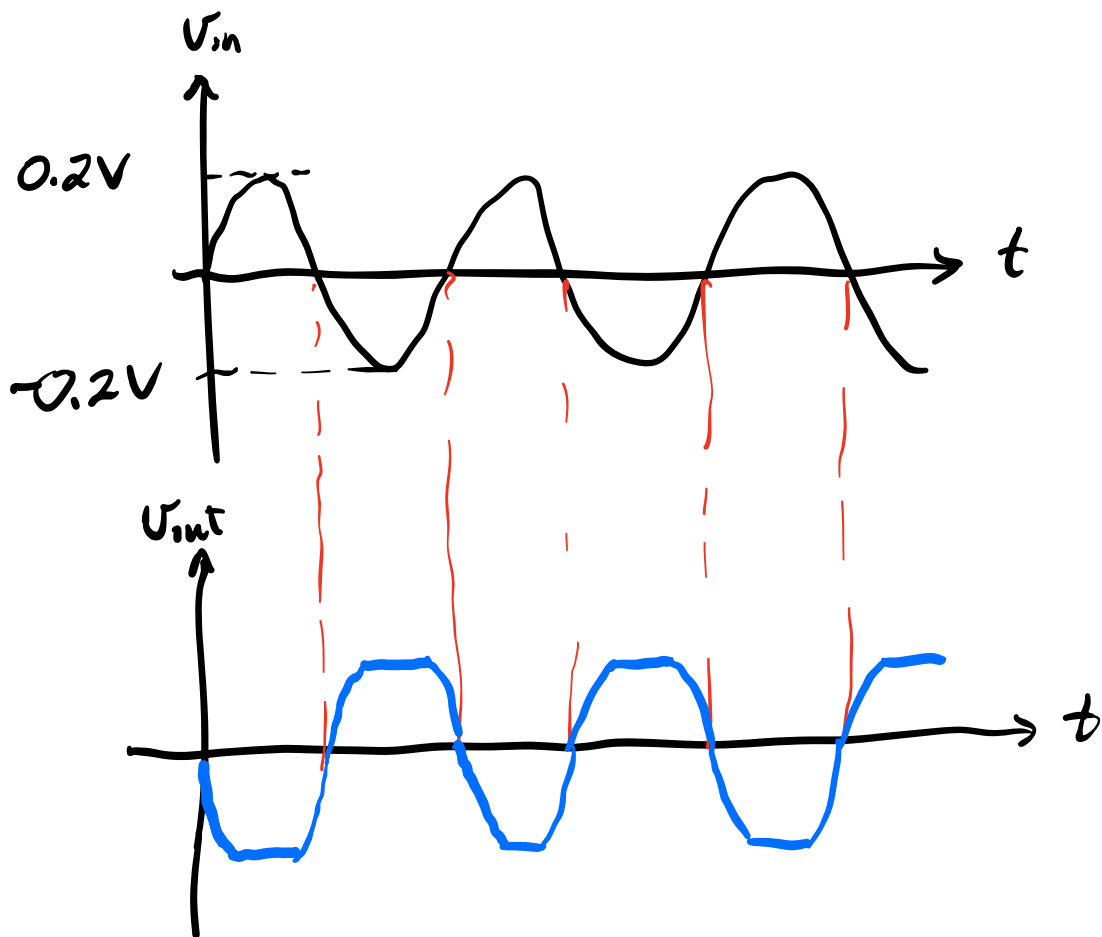


- Meas. $|G|$ vs f .
- Plot $\log |G|$ vs $\log f$.

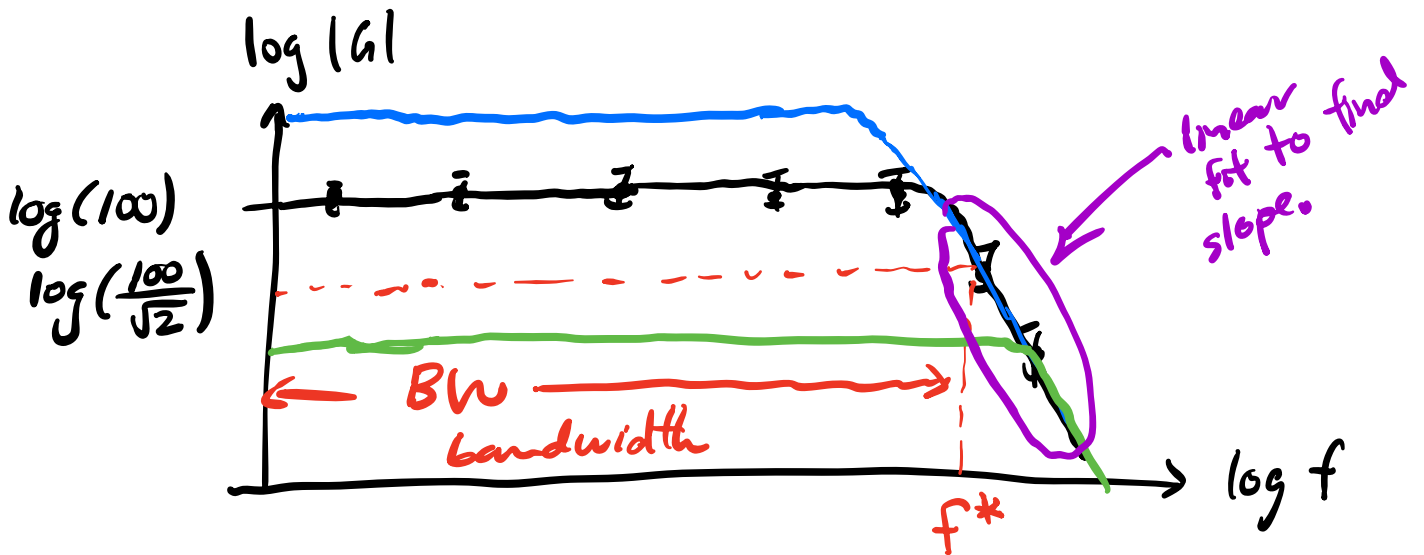


Inverting amplifier has a gain-bandwidth product that is const.

$$|G| \cdot BW = C \quad (\text{const})$$

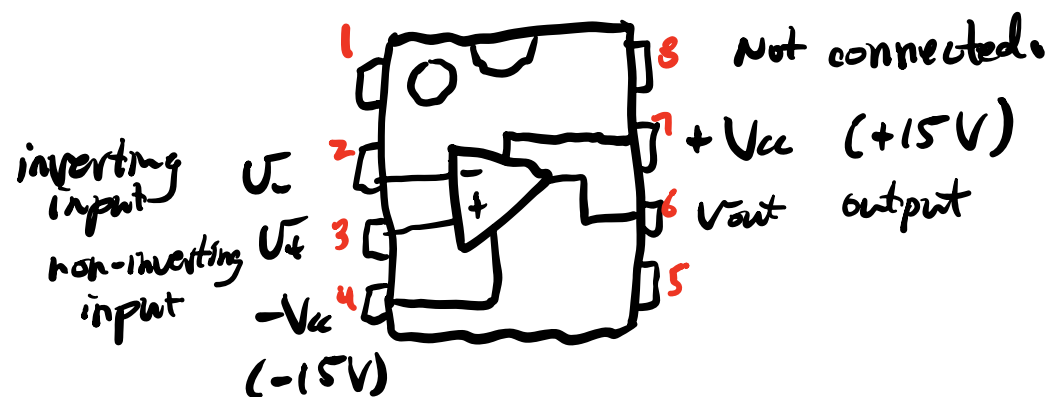
LM741 op amp that you'll use comes on a chip (IC's) integrated circuits.



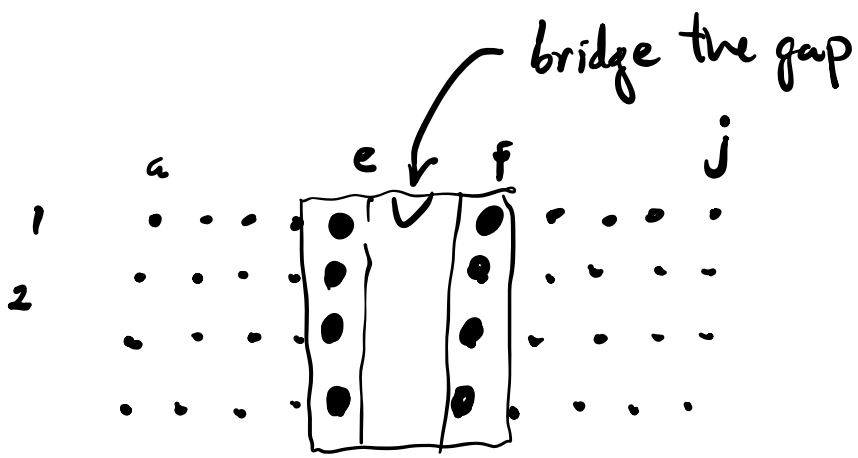

More Op amp applications:

1. Non-inverting amplifier

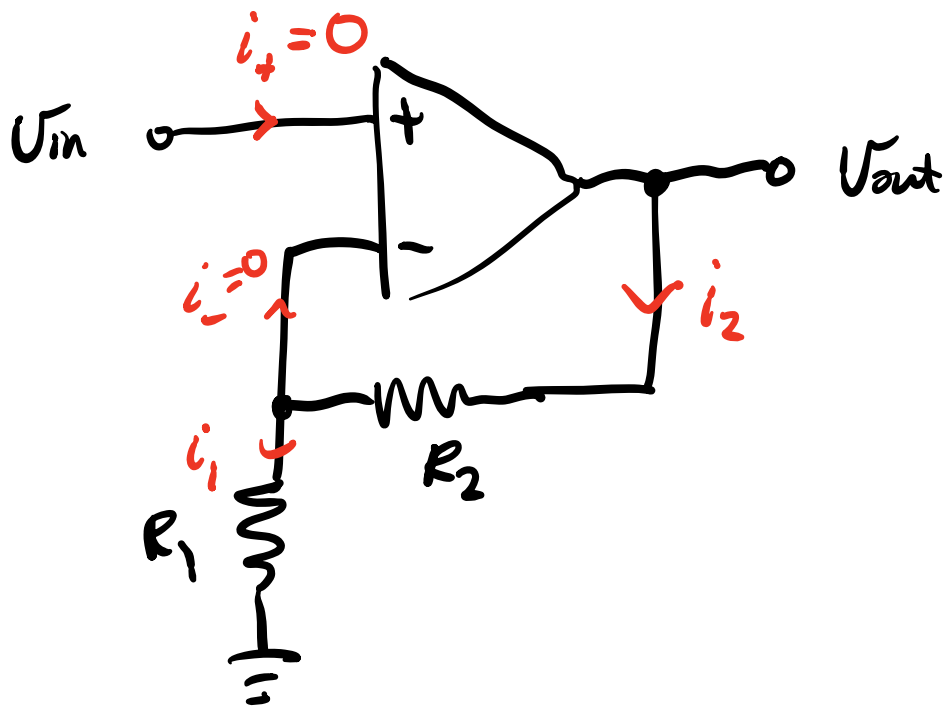


Apply op amp Golden rules.

Sum rule $i_2 = i_1 + i_-$

First Golden rule: $i_- = 0$

$i_+ = 0$

$i_2 = i_1 \equiv i$

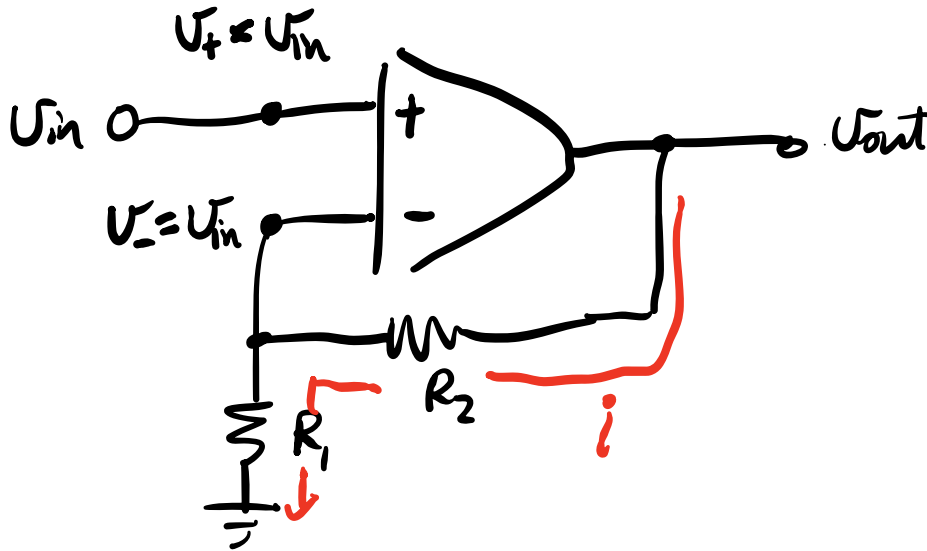

2nd Golden Rule: $U_+ = U_-$

Since $U_+ = U_{in}$

require $U_- = U_{in}$

Start from U_- † work towards gnd.

$U_- - iR_1 = 0$
 $\underbrace{U_-}_{U_{in}}$

\Rightarrow

$i = \frac{U_{in}}{R_1}$

$$V_{out} - i(R_1 + R_2) = 0$$

$$\therefore V_{out} = i(R_1 + R_2)$$


$$\therefore V_{out} = \frac{V_{in}}{R_1} (R_1 + R_2)$$

$$\frac{V_{out}}{V_{in}} = G = \left(1 + \frac{R_2}{R_1} \right)$$


non-inverting
amplifier gain.

Minimum possible gain of 1
(take $R_2 = 0$, $R_1 \rightarrow \infty$).

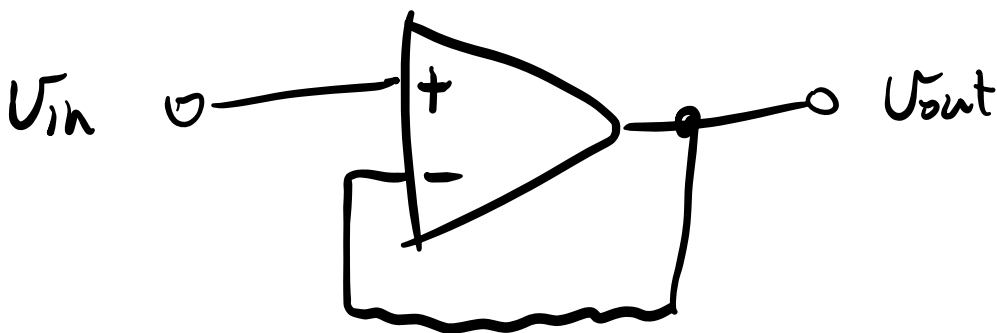Buffer circuit ($R_2 \rightarrow 0$, $R_1 \rightarrow \infty$)



Another Example:

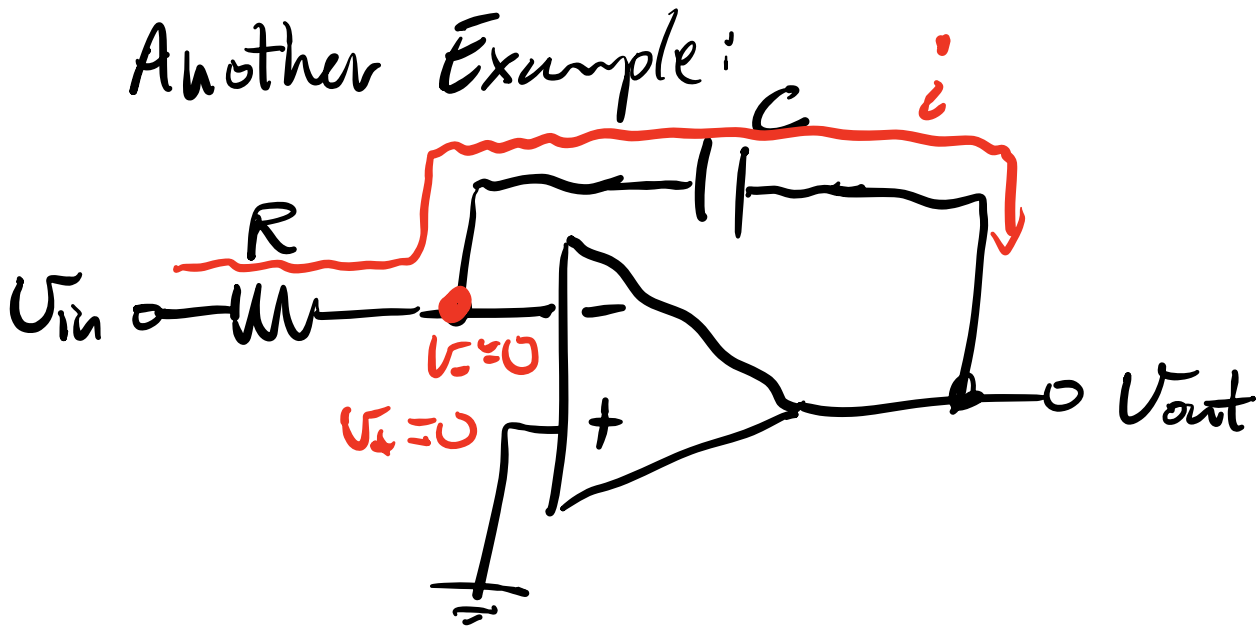

From U_{in} to U_-

$$U_{in} - iR = U_- = 0$$

$$i = \frac{U_{in}}{R}$$

From U_- to U_{out}

$$U_- - U_C = U_{out}$$

$$U_{out} = -\frac{q}{C}$$

$$C = \frac{q}{U_C}$$

$$\therefore U_C = \frac{q}{C}$$

know $i = \frac{dq}{dt}$

$$q = \int i dt$$

$$V_{out} = -\frac{1}{C} \int i dt$$

$$V_{out} = -\frac{1}{C} \int \frac{V_{in}}{R} dt$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

If Put in $V_{in} = \text{const}$

$$V_{out} = -\frac{1}{RC} V_{in} t$$

