

PHYS 231 - Nov. 22, 2023

- Today:
1. Preview Day 1 of Analog-to-Digital Converter (ADC) final Project.
 2. Binary Numbers.



Day 1 of ADC:

- build and test:

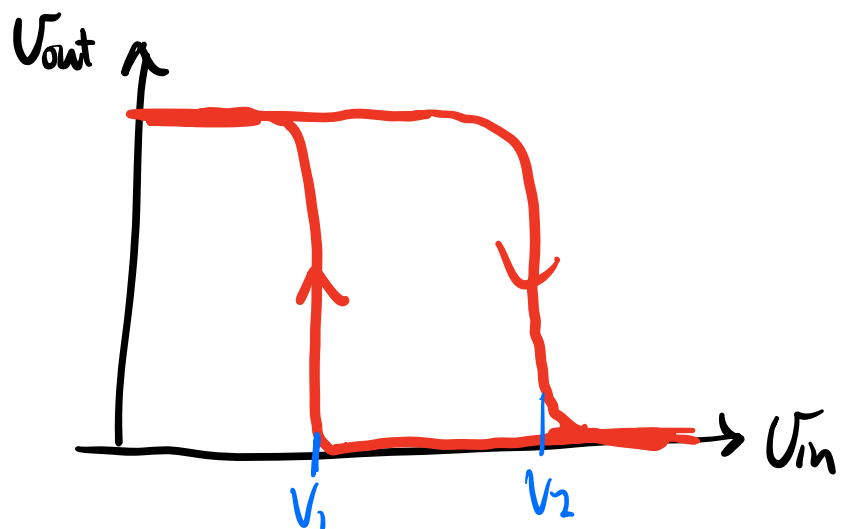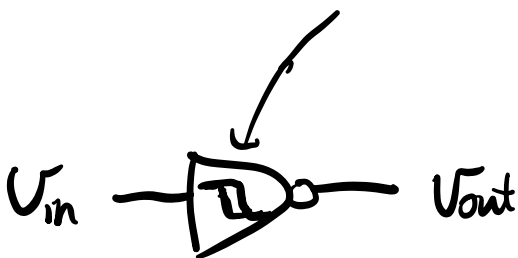1. Clock generator
2. Reset Pulse generator
3. Flip-Flop.
4. Counter (pair of $\div 10$)

Analysis of circuits ① & ②.


Inverters that we use in the lab have hysteresis.



Hysteresis implies that the $H \rightarrow L$ & $L \rightarrow H$ transitions occur at different values of V_{in} . This property is important for circuits ① & ②.


Square-Wave Generator.

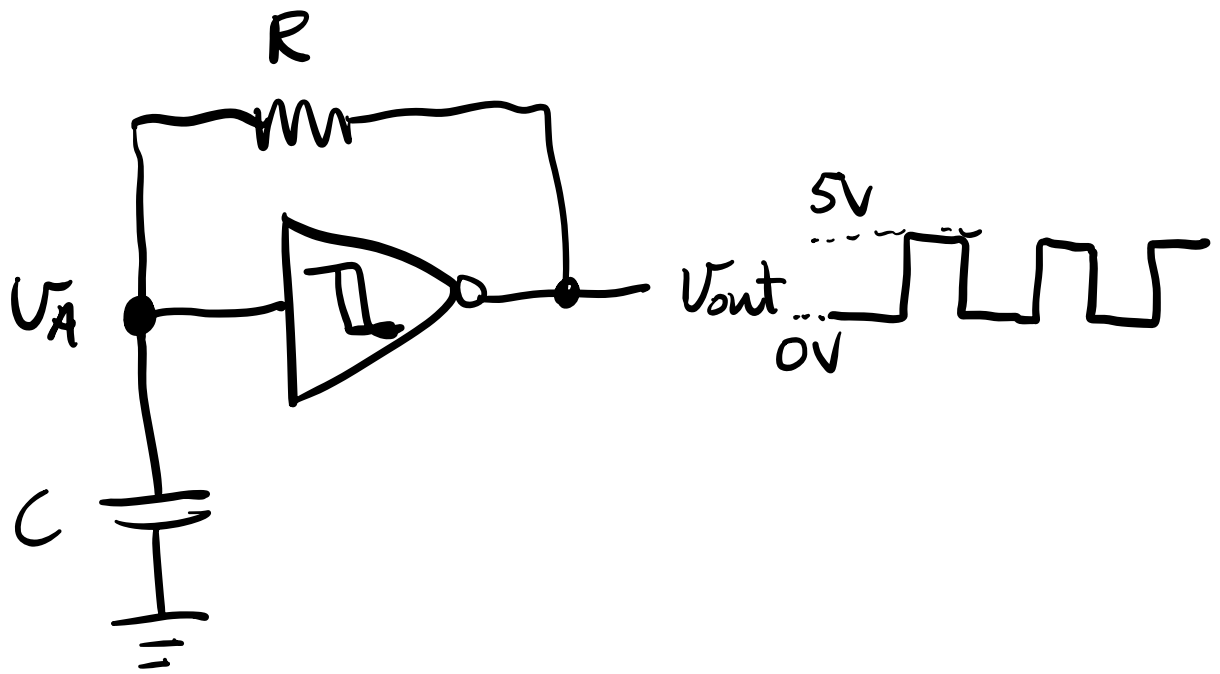No input volt. supplied to this circuit. We can meas. volt. V_A at input of inverter using an osc.




Assume that initially V_A is LO & V_{out} is HI.

Equivalent circuit, in this case is:

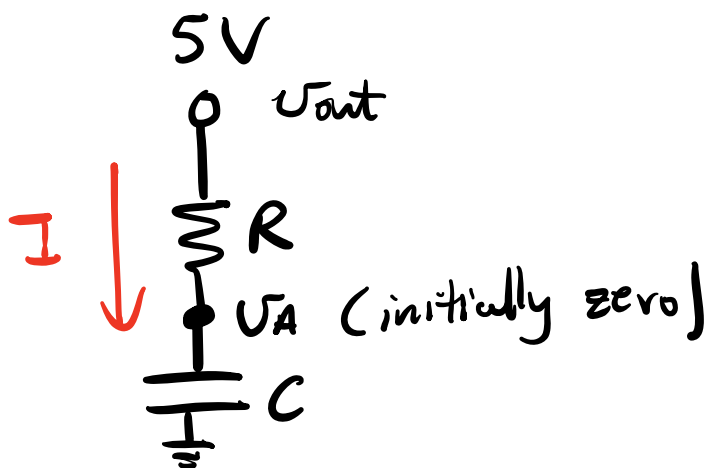


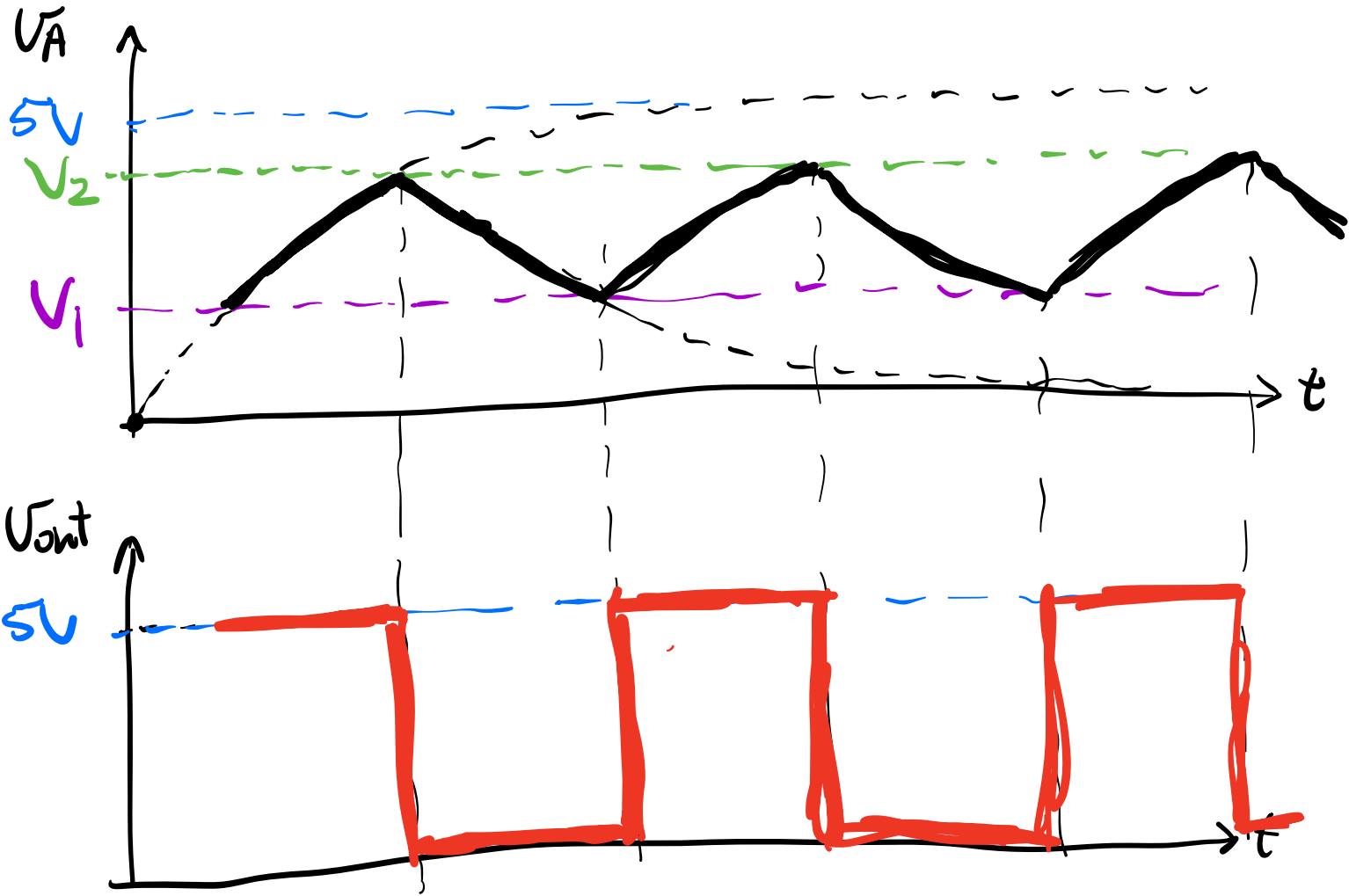Initially, capacitor is uncharged. However, as time evolves, the cap. will charge b/c of current through R.



Assume now that U_A is HI & U_{ont} is LO.

Equivalent circuit for this case is:

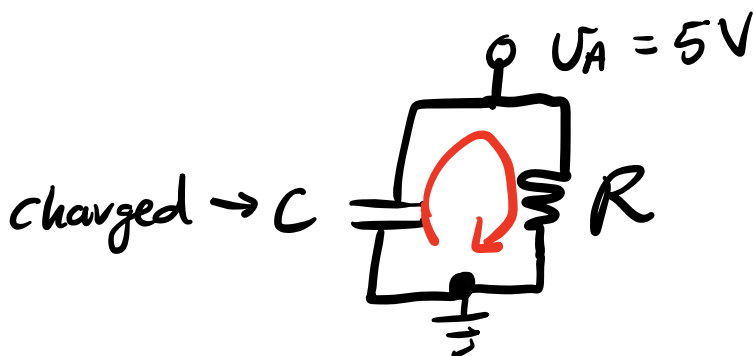

Cap. starts to discharge through resistor R.

Capacitor discharges until V_A reaches V_1 at which pt., the out transitions from LO \rightarrow HI.

Repeated charging & discharging of the capacitor causes the output of the inverter to osc. between HI & LO states \rightarrow sq. wave osc.


The period of the osc. is determined by the RC charging/discharging time constant.

Circuit ① includes a variable resistor which allows us to tune the period of our sq. wave output.

- Resistance across outer two leads is const. $R = 10\text{ k}\Omega$

- Resistance between left & centre leads is x , where


$$0 < x < 10\text{ k}\Omega.$$

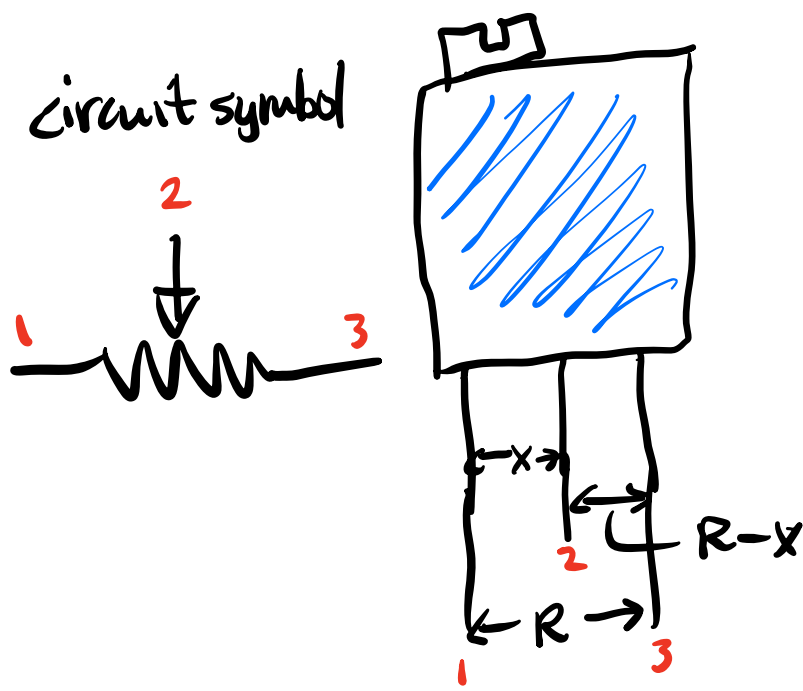

Change the value of x using screw at top.


Between the right & centre leads, the resistance is $R-x$ ($0 < R-x < 10k\Omega$)

Circuit ①


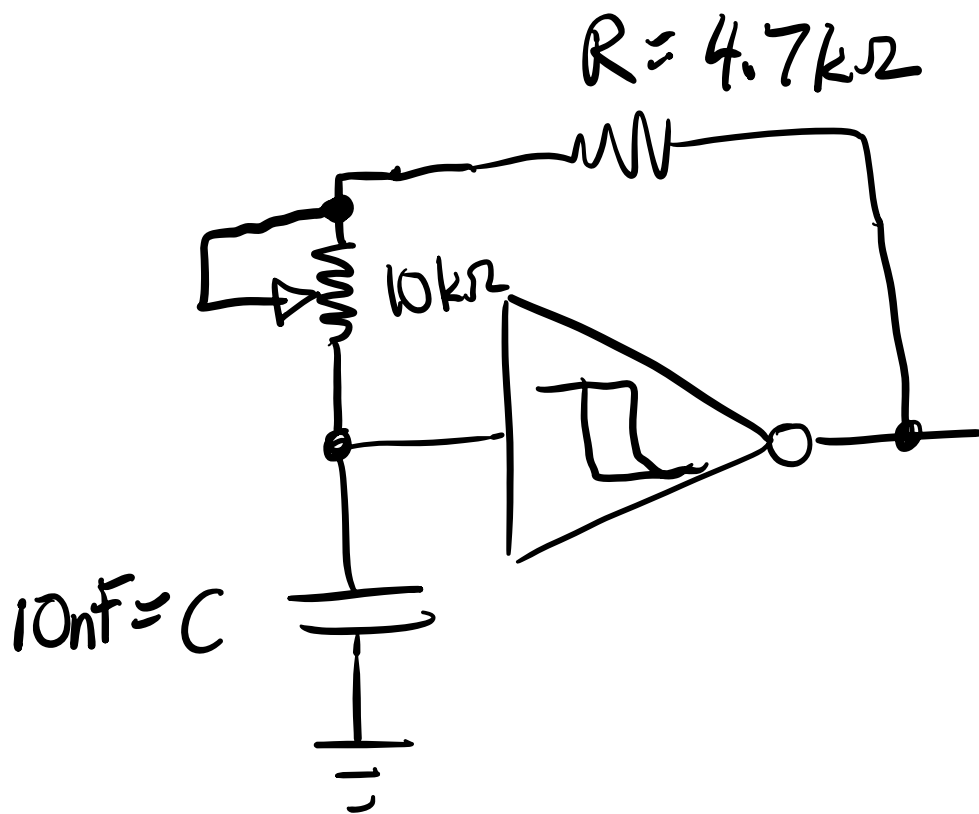



Now total resistance in feedback loop is $R+x$ (assuming we've short circuited the $R-x$ resistance).

Circuit ②

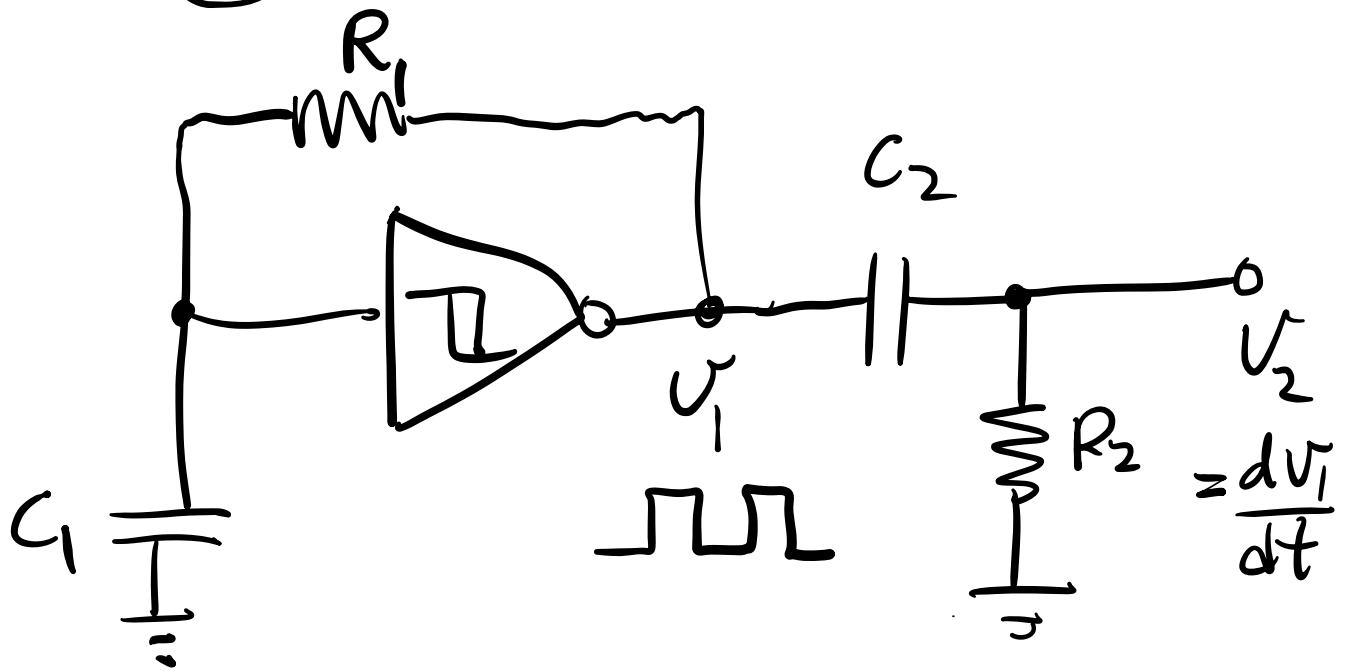

If $U_2 = \frac{dU_1}{dt}$, then:

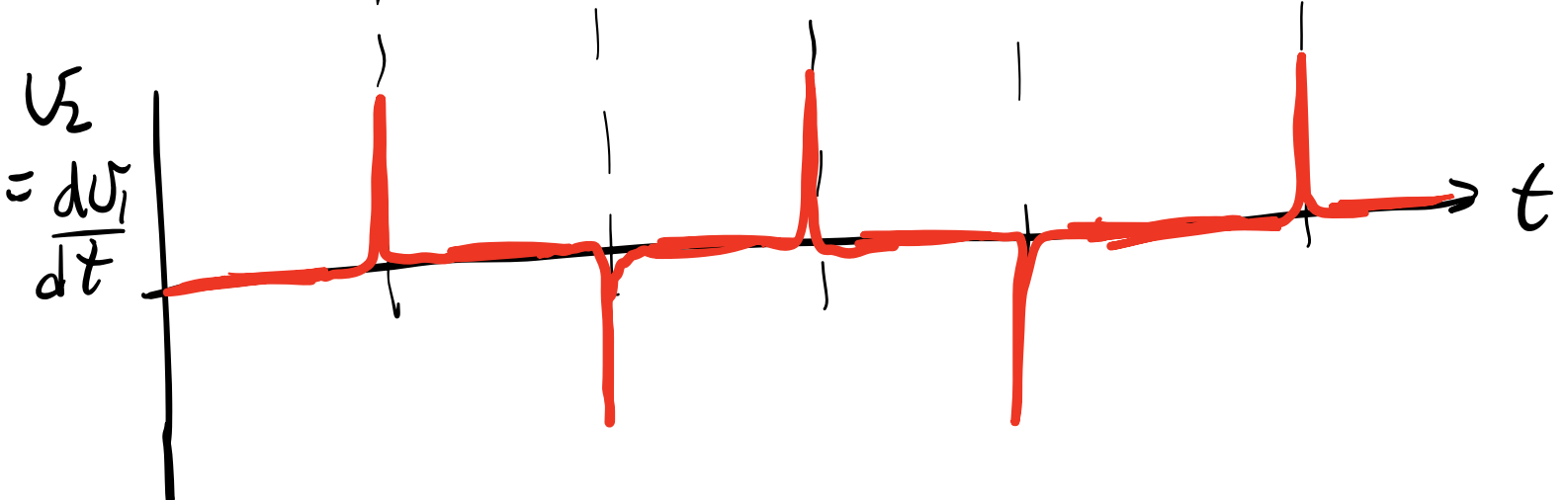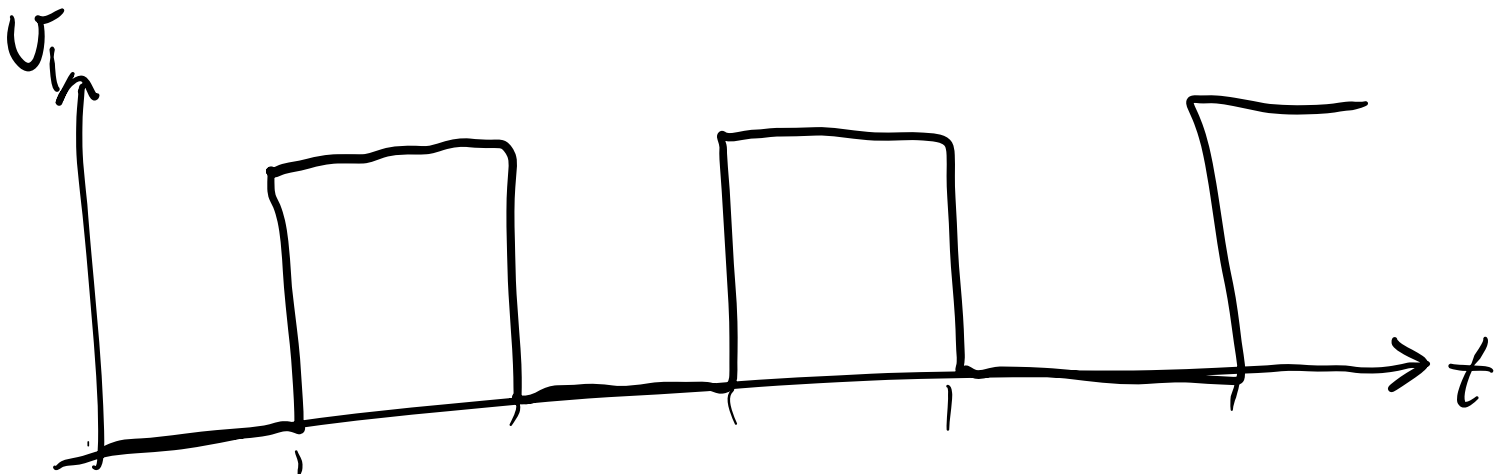

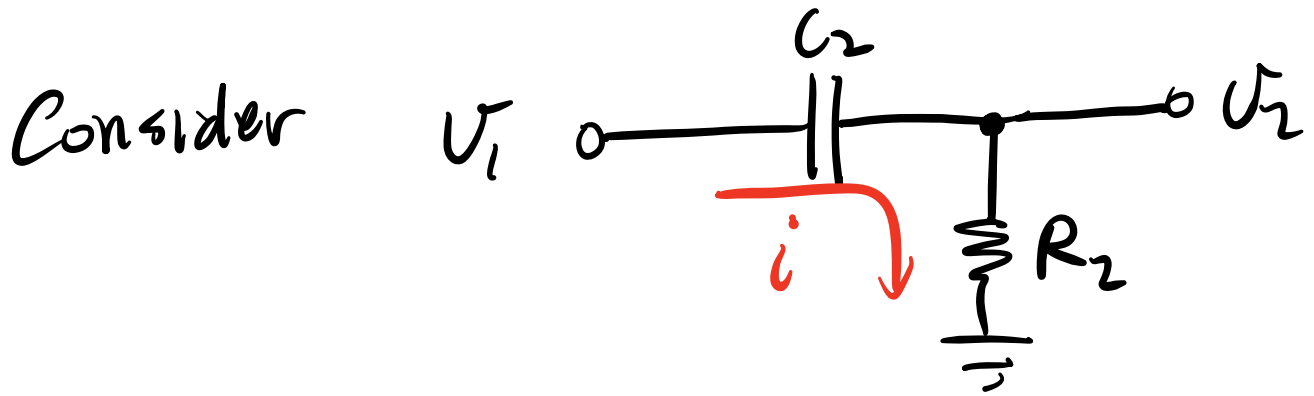

$$V_1 - V_{C_2} = V_2$$

know $C_2 = \frac{q}{V_{C_2}}$

$$\therefore V_{C_2} = V_1 - V_2$$

$$\therefore V_{C_2} = \frac{q}{C_2}$$

$$\therefore q = C_2 (V_1 - V_2)$$

approximation: assume $V_1 \gg V_2$

If this assumption is valid, then

$$q \approx C_2 V_1$$

$$\therefore i = \frac{dq}{dt} \approx C_2 \frac{dV_1}{dt}$$

since $V_2 = i R_2$,

$$V_2 = R_2 C_2 \frac{dV_1}{dt}$$

Complete circuit ②.

