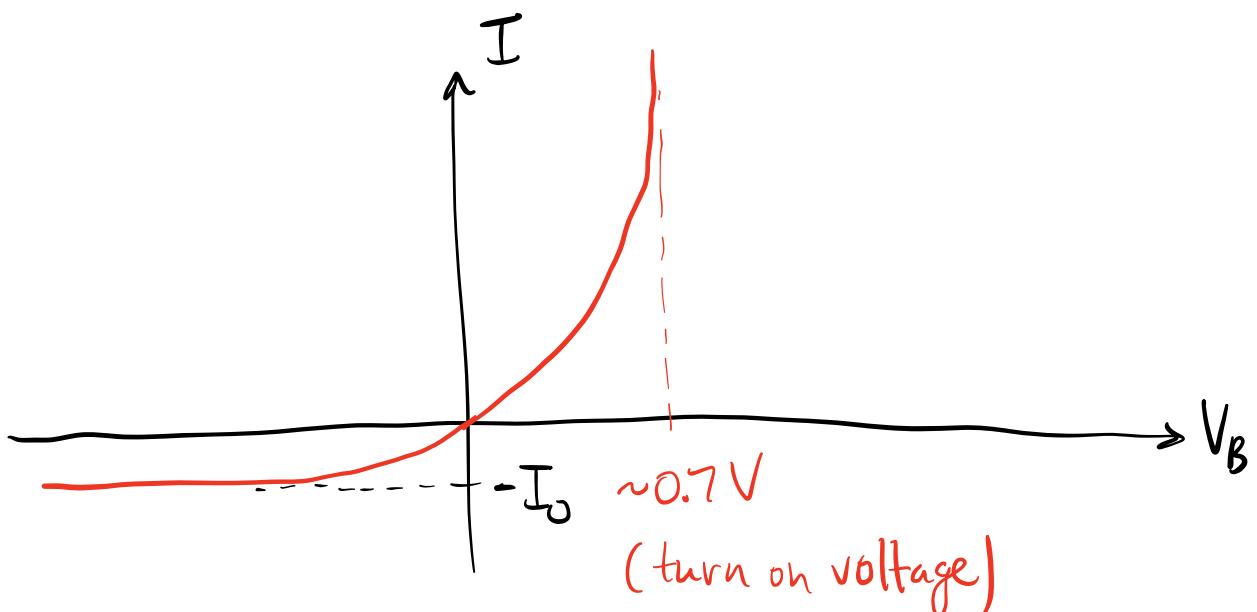



PHYS 231 - Nov. 29, 2023

Last Time: Diode current.


$$I = I_0 \left(e^{eV_B/k_B T} - 1 \right)$$



Approximate I-V characteristic as:

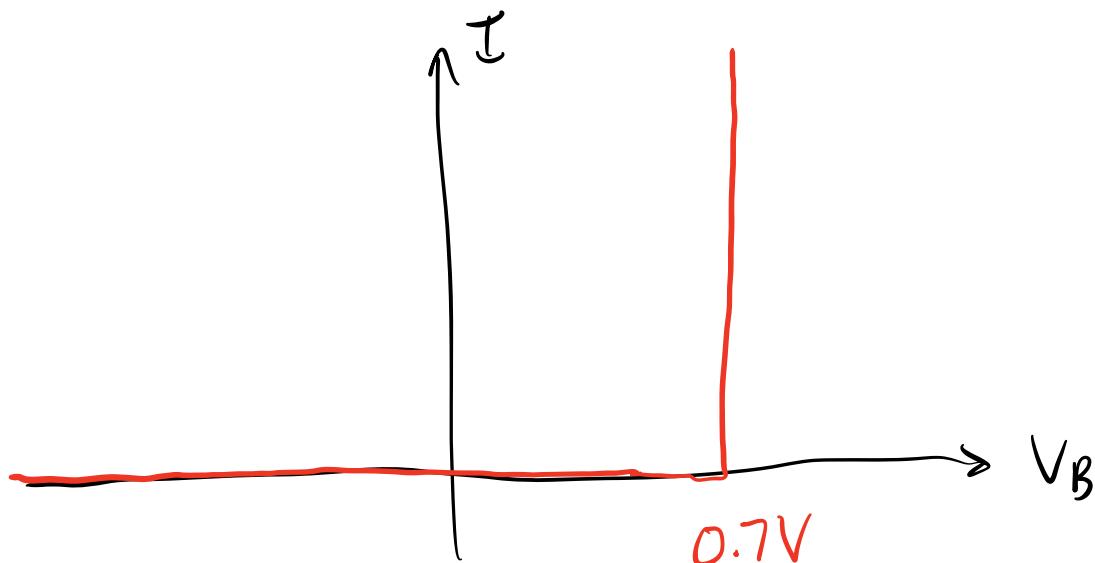


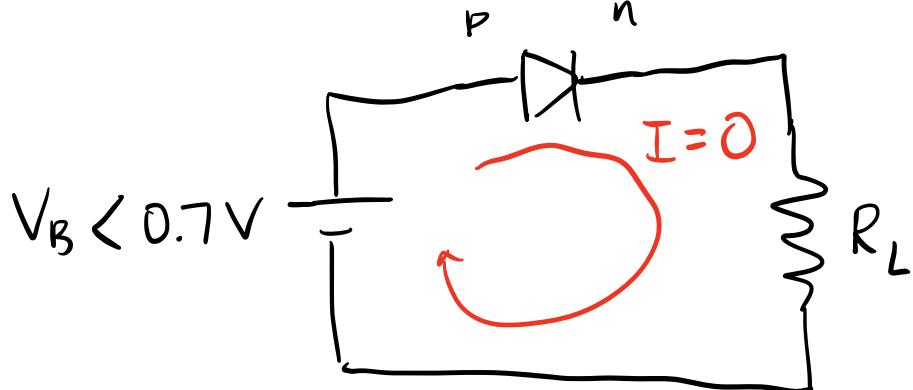Reverse biased diode: diode "off", no current




Equiv. Circuit :
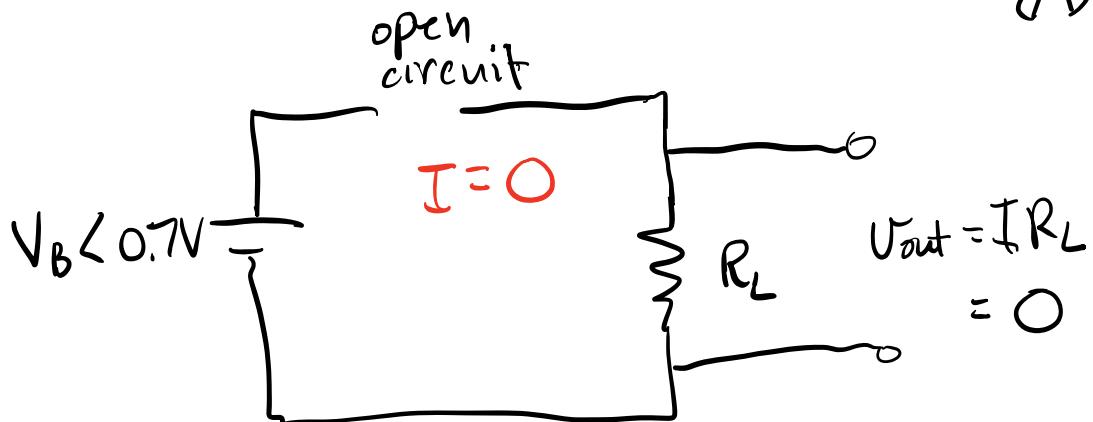
$$\rightarrow \text{diode} \Rightarrow -\cancel{\times}-$$





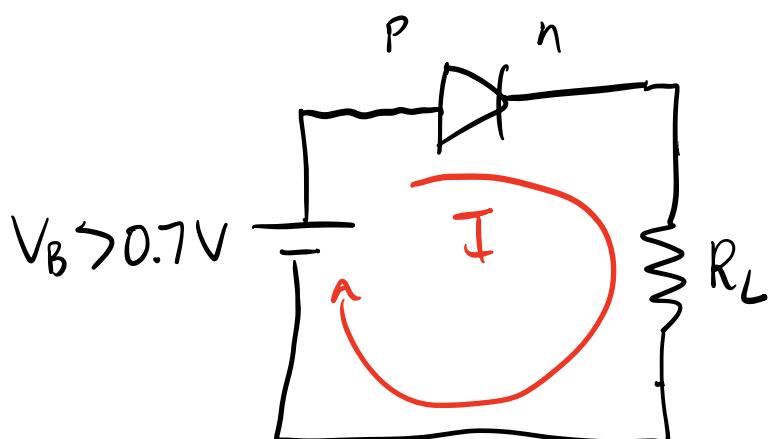Forward Biased Diode: diode "on", $I \neq 0$.




Must overcome the 0.7V turn on voltage before current flows.

Equivalent circuit

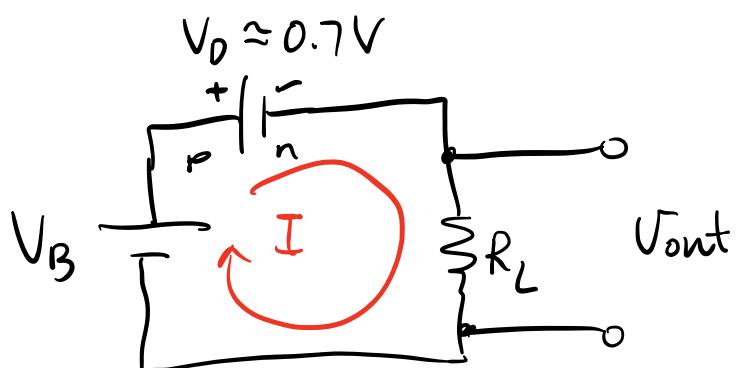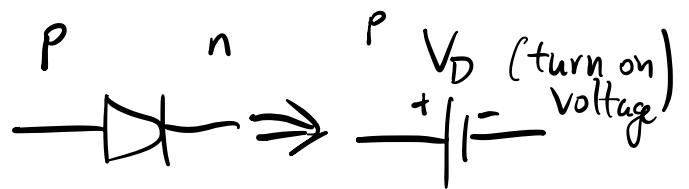


$$I = \frac{V_B - V_D}{R_L} \quad V_{out} = IR_L = V_B - V_D$$

Rectifier Circuit (AC-to-DC conversion)

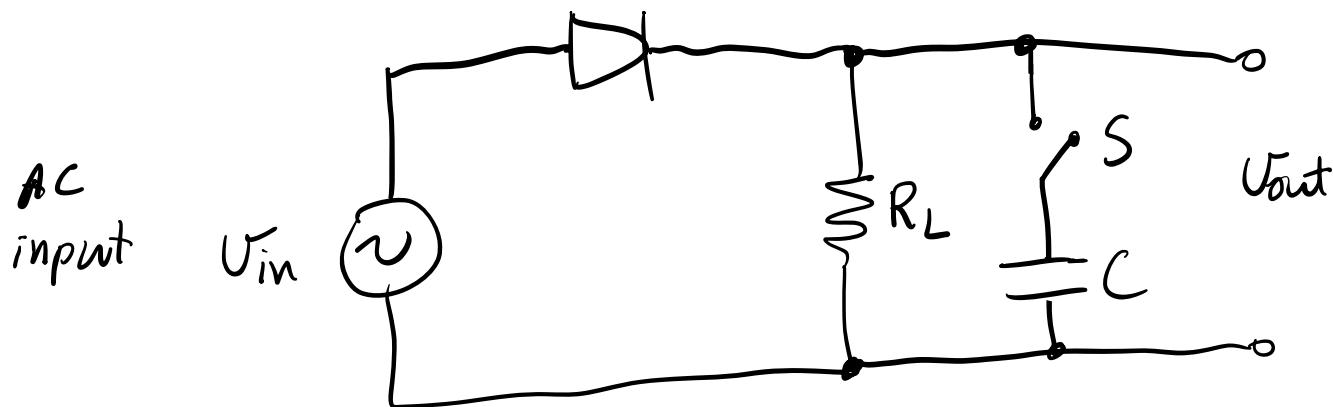

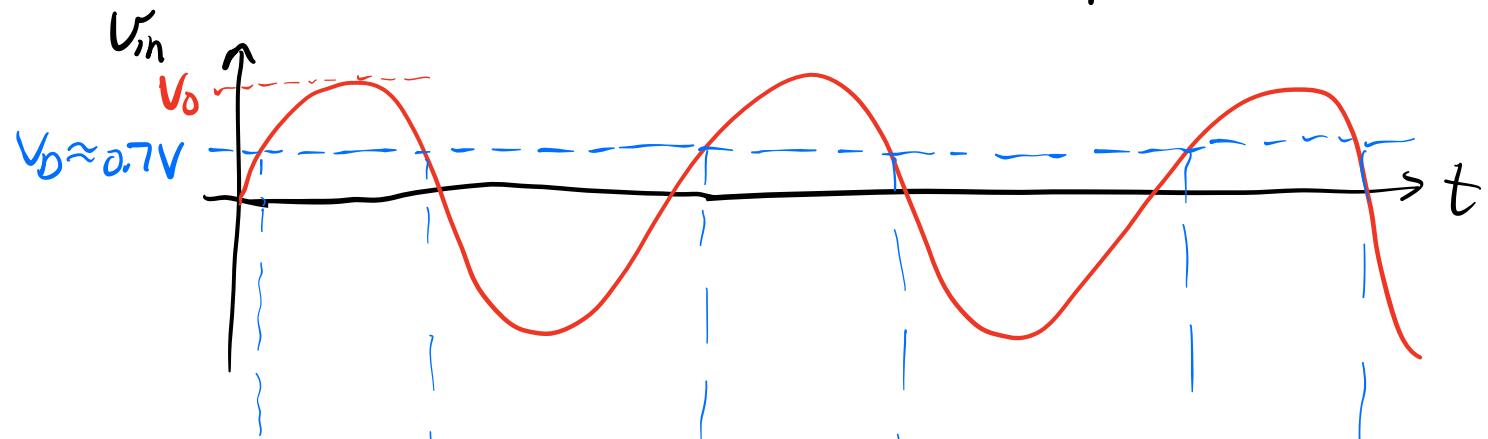Plot V_{in} & V_{out} w/ switch open & the closed.




V_{out} w/ S open. (no cap.)



When $V_{in} < V_D \approx 0.7V$, no current $\Rightarrow V_{out} = 0$.

When $V_{in} > V_D$, $V_{out} = V_{in} - V_D$


V_{out} w/ S closed ($C \parallel R_L$)

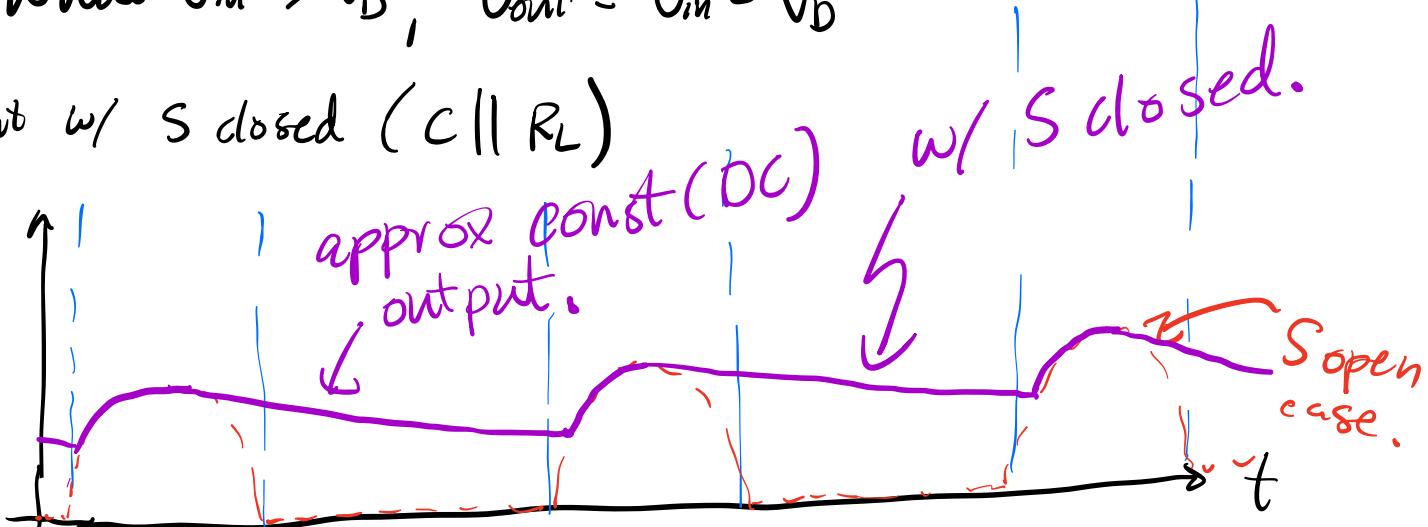

No change when diode is forward biased.

Still expect $V_{out} = V_{in} - V_D$ when cap is in place.

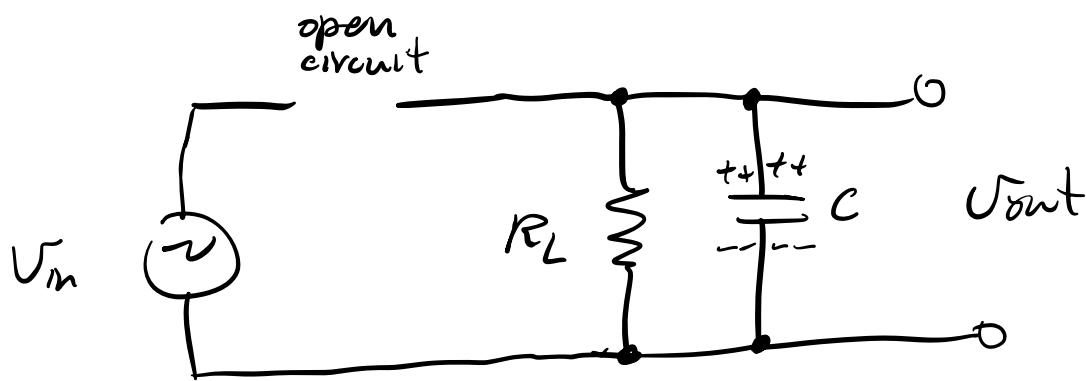When $V_{in} < V_D$ if diode is reverse biased,
equiv. circuit becomes:




Cap charges when diode is forward biased.

Cap discharges through R_L when diode is reverse biased. Make the time const.

$R_L C$ long so discharge is slow.

Bipolar Junction Transistor (BJT)

Start w/ a forward biased diode

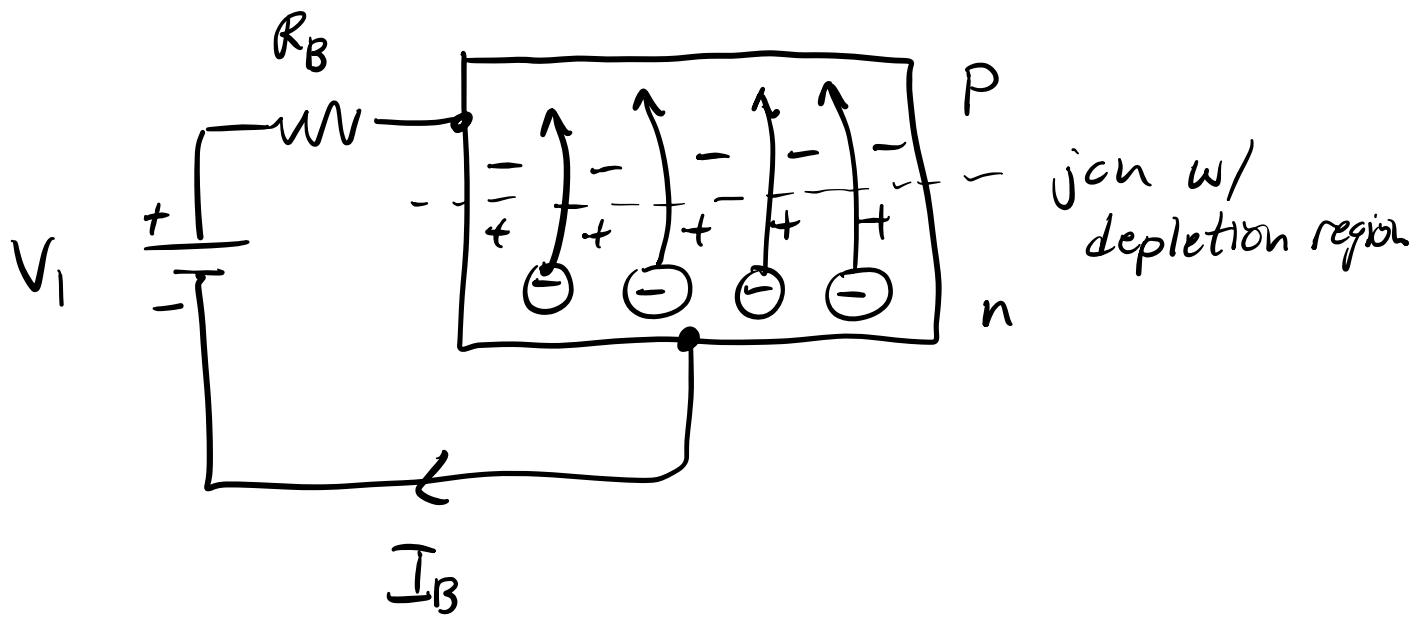


If $V_1 \geq V_D \approx 0.7V$, get large conduction across jch.


When making a transistor, n-region is much more heavily doped than p-region. \Rightarrow most of current is due to flow of e^- .

To complete the BJT, a second p-n junction is created on opp. side of p region.


n-p-n transistor.

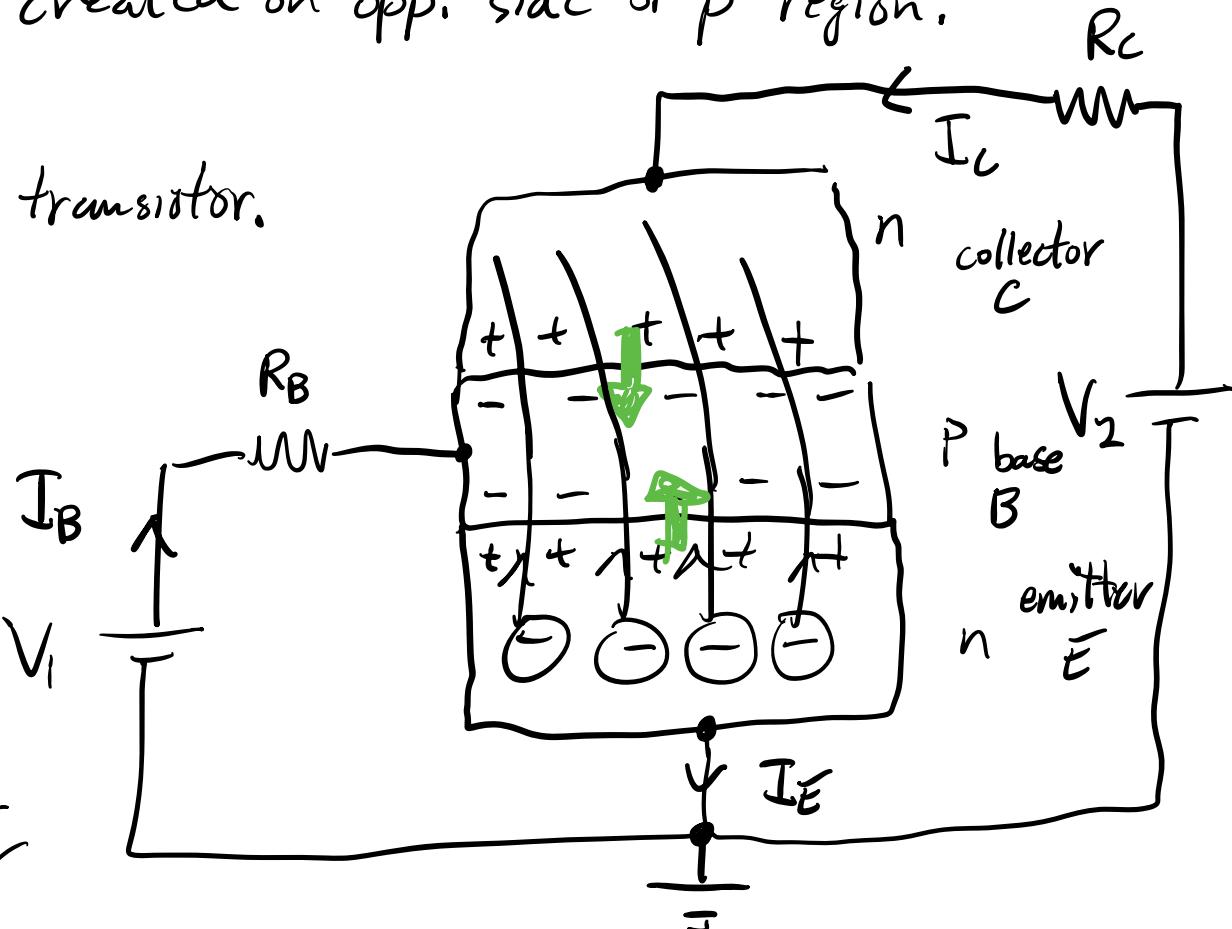

Circuit symbol for n-p-n transistor is

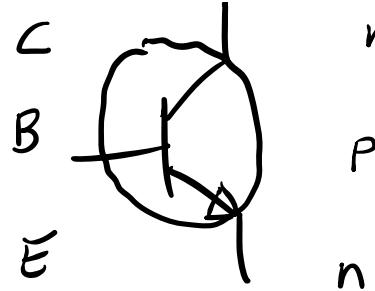

Schematic of circuit above.

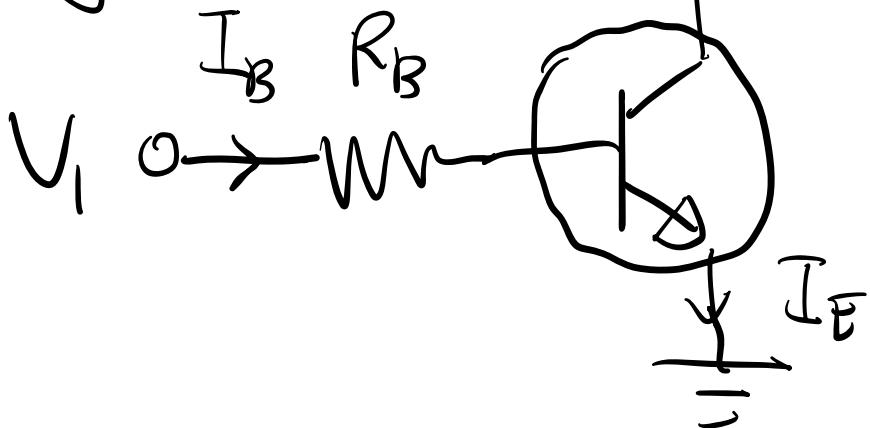

Base of a BJT is made very thin.

∴ most of e^- from emitter cross the base region & are swept into the collector
 $\Rightarrow I_B$ is, therefore, always very small.

By jcn rule : $I_B + I_C = \bar{I}_E$

Since I_B is small, $I_C \approx \bar{I}_E$

$$I_C = \alpha \bar{I}_E \quad \text{typically } \alpha \approx 0.99$$


$$\begin{aligned} I_B &= \bar{I}_E - I_C \\ &= \bar{I}_E (1-\alpha) \end{aligned}$$

$$\therefore \frac{I_C}{I_B} = \frac{\alpha \bar{I}_E}{(1-\alpha) \bar{I}_E} = \frac{\alpha}{1-\alpha} \approx 99$$

$$\therefore I_C \approx 99 I_B$$

large current gain.
→ current amplifier.

Transistor as a Switch.

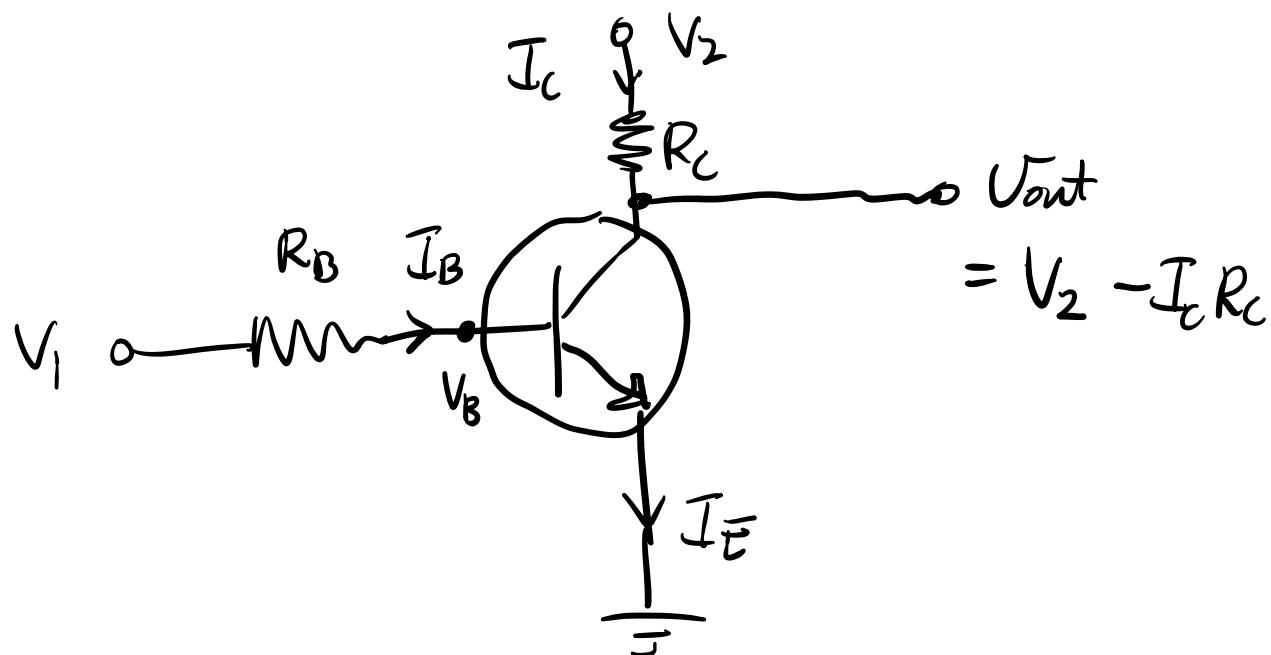

Since I_B is always small

$$V_1 - \cancel{I_B R_B}^0 = V_B \quad \therefore V_1 \approx V_B$$

- ① $V_1 < 0.7V$, $B-E$ jcn is reverse biased
 { $I_E = I_C = 0$.

$$V_{out} = V_2 - \cancel{I_C R_C}^0 \quad V_{out} = V_2.$$

For example, if $V_1 = 0$ & $V_2 = 5V$

$$\begin{array}{c|c} V_1 & V_{out} \\ \hline 0 & 5V \end{array} \Rightarrow \begin{array}{c|c} V_1 & V_{out} \\ \hline 0 & 1V \end{array}$$

② $V_1 > 0.7V$, B-E is forward biased
 $I_C \neq 0$.

$$V_{out} = V_2 - I_C R_C \approx 0$$

If $V_1 = 5V$ (HI), $V_{out} \approx 0V$ (LO)

Truth Table

V_1	V_{out}
LO	HI
HI	LO

Inverter.