

PHYS 231 - Oct. 18, 2023

Last Time:

Euler's Eq'n: $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

Complex nos. can be expressed as:

$$z = x + jy = |z| (\cos \theta + j \sin \theta) = |z| e^{j\theta}$$

$$|z| = \sqrt{x^2 + y^2}$$

$$x = |z| \cos \theta$$

$$\tan \theta = \frac{y}{x}$$

$$y = |z| \sin \theta$$

Complex Conjugate:

$$\begin{aligned} z^* &= x - jy = |z| (\cos \theta - j \sin \theta) \\ &= |z| e^{-j\theta} \end{aligned}$$

Why define the complex conjugate of z ?
→ It can be used to find the magnitude of z .

Consider $z = x + jy = |z| e^{j\theta}$

then $z^* = x - jy = |z| e^{-j\theta}$

$$\begin{aligned} \therefore z z^* &= (x + jy)(x - jy) \\ &= x^2 - \cancel{jxy} + \cancel{jxy} - \underbrace{j^2}_{+1} y^2 \end{aligned}$$

$$z z^* = x^2 + y^2 = |z|^2$$

$$\boxed{\therefore |z| = \sqrt{z z^*}}$$

z times its conjugate z^* must result in a purely real number → no j 's.

Try $z z^* = (|z| e^{j\theta}) (|z| e^{-j\theta})$
 $= |z|^2 \quad \checkmark$ same as above.

Example:

Suppose $z = \frac{1}{3+2j}$

Express z in the form:

(a) $z = x + jy \rightarrow$ find x & y

(b) $z = |z| e^{j\theta} \rightarrow$ find $|z|$ & θ

(a) Strategy to remove "j's" from btm is to mult. top & btm by complex conjugate (c.c.) of the btm.

$$z = \frac{1}{3+2j} \frac{(3-2j)}{(3-2j)} = \frac{3-2j}{3^2 + \cancel{6j} - \cancel{6j} - j^2 2^2} \quad \begin{matrix} 1 \\ \nearrow \end{matrix}$$

$$z = \frac{3 - 2j}{13} = \frac{3}{13} - \frac{2}{13}j$$

$$x = \frac{3}{13} \quad y = -\frac{2}{13}$$


$$(b) \quad |z|^2 = x^2 + y^2 = \frac{3^2}{13^2} + \frac{2^2}{13^2} \\ = \frac{\cancel{13}}{13^2} = \frac{1}{13}$$

$$\therefore |z| = \frac{1}{\sqrt{13}}$$

$$\tan \phi = \frac{y}{x} = \frac{-2/\cancel{13}}{3/\cancel{13}} \Rightarrow \tan \phi = -\frac{2}{3}$$

$$\phi = \tan^{-1}\left(-\frac{2}{3}\right) = -\tan^{-1}\left(\frac{2}{3}\right)$$

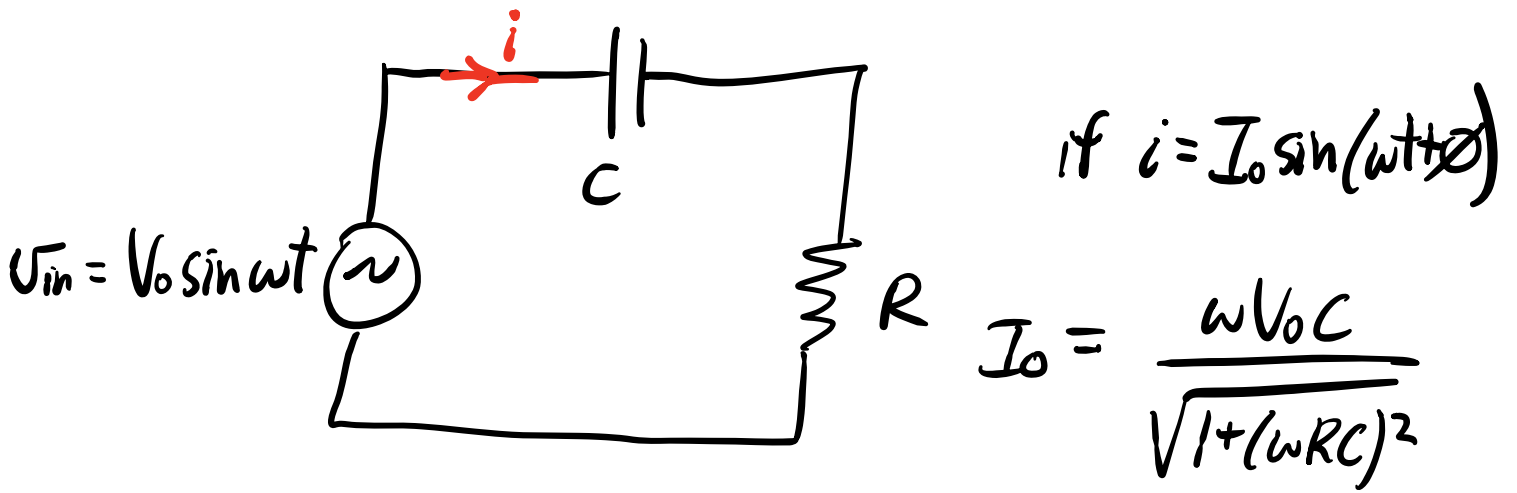Previously solve for the current in the following RC circuit:



Suppose, for convenience, we express


$$V_{in} \text{ as } V_{in} = V_0 e^{j\omega t}$$

$$\text{Then } V_{in} = V_0 e^{j\omega t} = V_0 (\cos \omega t + j \sin \omega t)$$

If we take the imaginary part, recover the original form of V_{in} .

$$\text{Im}[V_{in}] = V_0 \sin \omega t$$

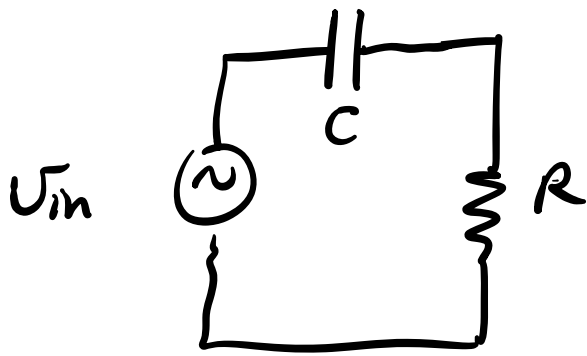→ do calc. using complex exponential,
 can recover correct forms for results if
 we take the Im component in the end.



Loop Rule:

$$V_{in} - V_C - V_R = 0$$

$$V_{in} = \frac{q}{C} + iR$$

Take time deriv. of this expression

$$\frac{dV_{in}}{dt} = \frac{1}{C} \underline{i} + R \underline{\frac{di}{dt}}$$

Know that $\frac{dV_{in}}{dt} = \frac{d}{dt} (V_0 e^{j\omega t})$
 $= \underline{j\omega V_0 e^{j\omega t}}$

Like we did for V_{in} , express i as complex exponential:

$$i = I_0 e^{j(\omega t + \phi)} = \underline{I_0 e^{j\omega t} e^{j\phi}}$$

Then $\frac{di}{dt} = \underline{j\omega I_0 e^{j\omega t} e^{j\phi}}$

subbing in the results, we have:

$$\textcircled{A} \quad j\omega V_0 e^{j\omega t} = \frac{I_0}{C} e^{j\omega t} e^{j\vartheta} + j\omega R I_0 e^{j\omega t} e^{j\vartheta}$$

$$j\omega V_0 = I_0 e^{j\vartheta} \left(\frac{1}{C} + j\omega R \right)$$

We're trying to find I_0 & ϑ , so solve for $I_0 e^{j\vartheta}$

$$I_0 e^{j\vartheta} = \frac{j\omega V_0}{\frac{1}{C} + j\omega R} = \frac{j\omega V_0 C}{\underbrace{1 + j\omega RC}_{\equiv Z}}$$

Remove j 's from demon. of Z .

$$I_0 e^{j\vartheta} = \frac{j\omega V_0 C}{1 + j\omega RC} \frac{(1 - j\omega RC)}{(1 - j\omega RC)}$$

$$I_0 e^{j\phi} = \frac{\omega V_0 C (j + \omega RC)}{1 + (\omega RC)^2} = x + jy$$

$$x = \frac{\omega V_0 C \omega RC}{1 + (\omega RC)^2} \quad y = \frac{\omega V_0 C}{1 + (\omega RC)^2}$$

$$|z| = \sqrt{x^2 + y^2} = \frac{\omega V_0 C}{1 + (\omega RC)^2} \sqrt{(\omega RC)^2 + 1}$$


$$\therefore |z| = \frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}$$

$$\tan \phi = \frac{y}{x} = \frac{1}{\omega RC}$$

$$\therefore I_0 e^{j\phi} = \underbrace{\frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}}_{I_0} e^{j\phi} \quad \uparrow \quad \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

Experiment #4 - Day

LRC circuit transients

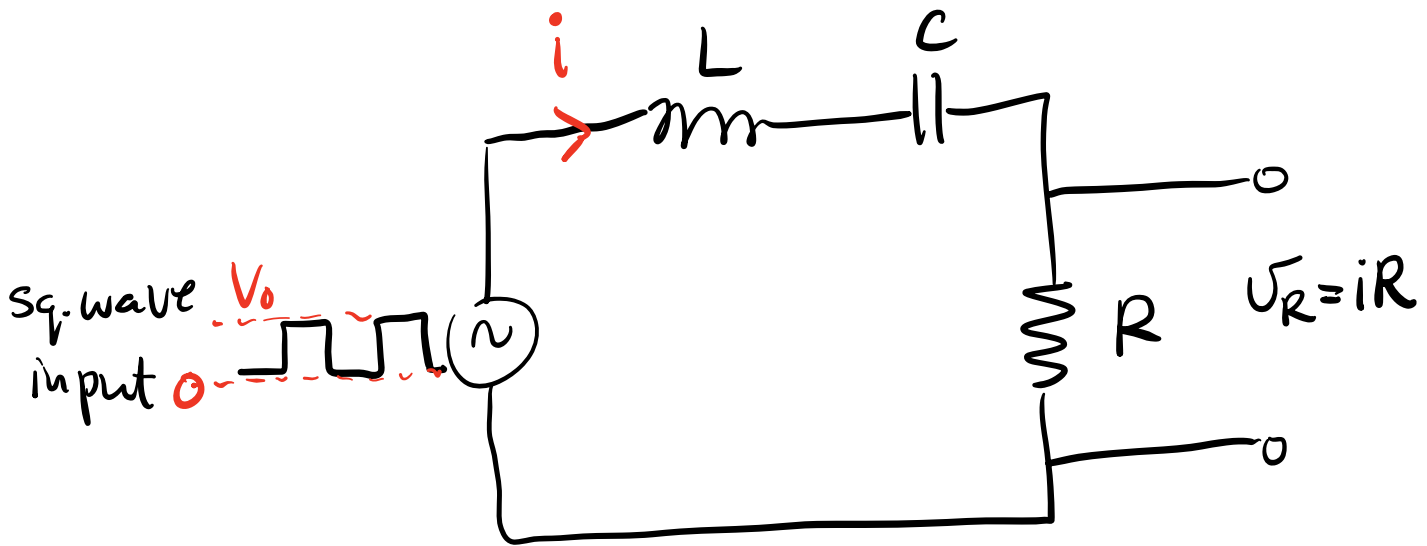

From Sept. 27, 2023 notes...


For an underdamped circuit in which

$$\omega_0 \gg \frac{\gamma}{2}$$

$$\text{where } \omega_0 = \frac{1}{\sqrt{LC}} \quad \{ \quad \gamma = \frac{R}{L}$$

$$i \approx \omega_0 C V_0 e^{-(\gamma/2)t} \sin(\omega_0 t)$$
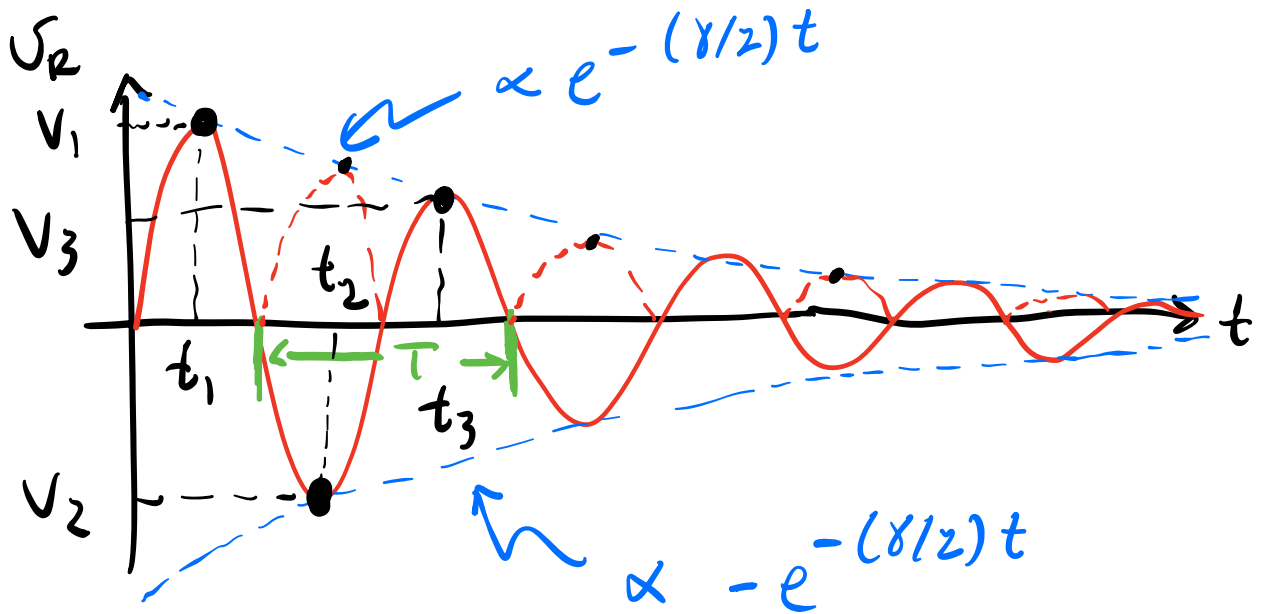
$$\therefore V_R = iR \approx \omega_0 RC V_0 e^{-(\gamma/2)t} \sin(\omega_0 t)$$



meas. $\omega_0 = \frac{2\pi}{T} \Rightarrow$ compare to expected value of $\omega_0 = \frac{1}{\sqrt{LC}}$

Finding γ .

time	$ V_R _{\text{min, max}}$
t_1	$V_1 \pm \Delta V_1$
t_2	$ V_2 \pm \Delta V_2$
t_3	$V_3 \pm \Delta V_3$
t_4	$ V_4 \pm \Delta V_4$
\vdots	\vdots
t_N	$ V_N \pm \Delta V_N$

$$V_{\text{meas}} = V_0 e^{-(\delta/2)t}$$

$$\underbrace{\ln V_{\text{meas}}}_y = \underbrace{\ln V_0}_b + \underbrace{\left(-\frac{\delta}{2}\right)}_m \underbrace{t}_x$$

Plot $\ln V_{\text{meas}}$ vs t

$$\text{slope } m = -\frac{\delta}{2}$$

$$\text{Find } \delta = -2m$$

use Δm to also find $\Delta \delta$

compare meas. δ to expected
value of $\frac{R}{L}$.