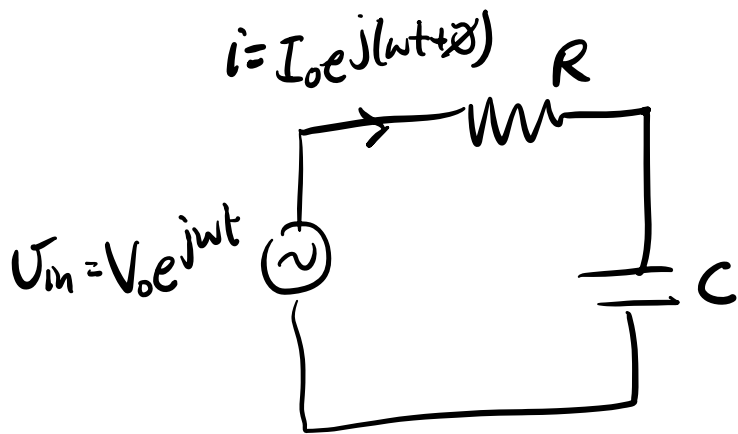


Last Time: RC circuit



Found:

$$I_0 = \frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

Useful result:

$$\textcircled{\#} \quad \underbrace{j\omega V_0 e^{j\omega t}}_{V_{in}} = \underbrace{\frac{I_0}{C} e^{j\omega t} e^{j\phi}}_i + j\omega R \underbrace{I_0 e^{j\omega t} e^{j\phi}}_i$$

$$j\omega V_{in} = \frac{i}{C} + j\omega R i$$

Divide by $j\omega$

$$V_{in} = \frac{i}{j\omega C} + iR$$

Fun gen.
voltage.

must be
voltage across
Capacitor

voltage across
 R

$$V_{in} = i \left(\frac{1}{j\omega C} + R \right)$$

Now have voltage across resistor is

usual $iR = V_R$


impedance of the
resistor is $Z_R = R$

& voltage across cap. is $iZ_C = V_C$

impedance of capacitor.

$$Z_C = \frac{1}{j\omega C}$$

For our RC circuit:

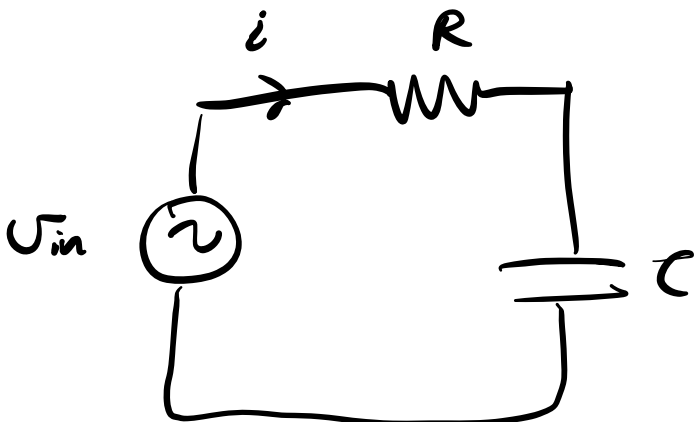

KVR:


$$V_{in} - V_R - V_C = 0$$

$$V_{in} - iR - iZ_C = 0$$


$$V_{in} = i(R + Z_C)$$

Can combine impedances in series & parallel in the same way we do for resistors.

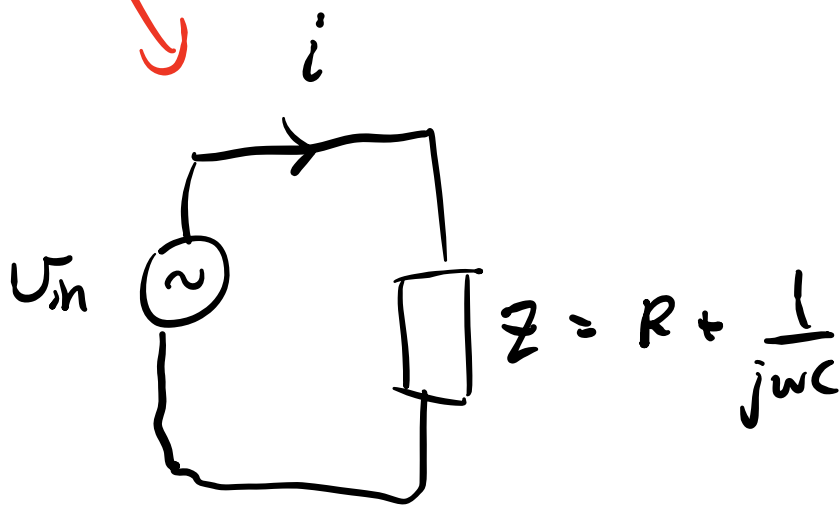Eg. series combo. of R & C gives an equiv. impedance of $Z = Z_R + Z_C$
 $= R + \frac{1}{j\omega C}$



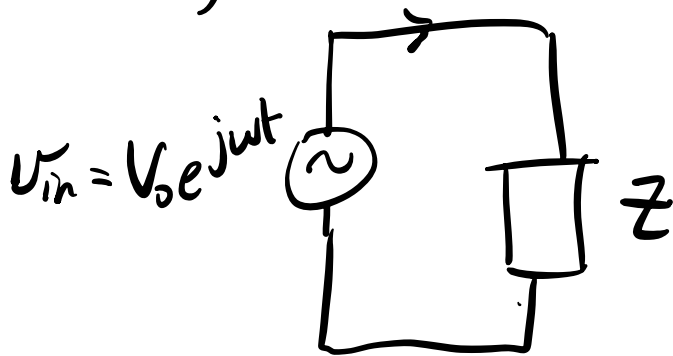Any circuit w/ a single volt. source V_{in} & any comb. of R, C, L can be represented by $i = I_0 e^{j(\omega t + \phi)}$



Goal: Analyze this general circuit s.t. we can determine I_0 & ϕ .

$$V_{in} = iZ$$

\therefore

$$i = \frac{V_{in}}{Z}$$

replace $V_{in} = V_0 e^{j\omega t}$
 $i = I_0 e^{j\omega t} e^{j\phi}$

Z is the net impedance of circuit.

Z is complex & any complex number can be written in the form $Z = |Z| e^{j\phi_z}$

ϕ : phase of current.

ϕ_z : phase of impedance Z . $\tan \phi_z = \frac{\text{Im}[Z]}{\text{Re}[Z]} = \frac{y}{x}$

$$I_0 e^{j\omega t} e^{j\phi} = \frac{V_0 e^{j\omega t}}{|Z| e^{j\phi_z}}$$

$$I_0 e^{j\phi} = \frac{V_0}{|Z|} e^{-j\phi_z}$$


must be equal.

$$\therefore I_0 = \frac{V_0}{|Z|}$$

$$\begin{aligned} \phi &= -\phi_z \\ &= -\tan^{-1}\left(\frac{\text{Im}[Z]}{\text{Re}[Z]}\right) \end{aligned}$$

Important Results
for finding current.

Example: RC circuit.

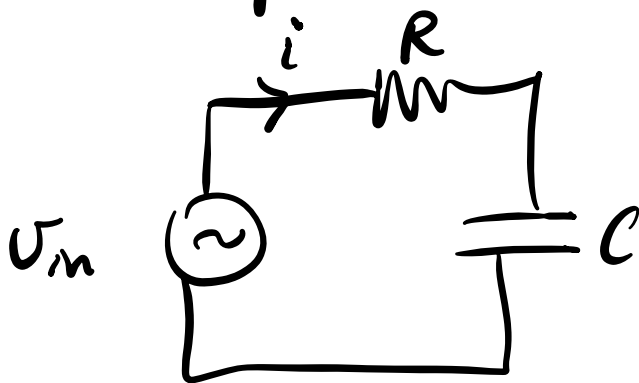

know $I_0 = \frac{V_0}{|Z|}$

$$\phi = -\tan^{-1}\left(\frac{\text{Im}[Z]}{\text{Re}[Z]}\right)$$

$$Z = R + \frac{1}{j\omega C} \cdot \frac{j}{j} = R - \frac{j}{\omega C}$$

$\underbrace{\hspace{10em}}_{Z_c}$

$$\begin{aligned} x &= R \\ y &= -\frac{1}{\omega C} \end{aligned}$$

$$|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{1}{\omega C} \sqrt{1 + (\omega RC)^2}$$

$$\therefore \bar{I}_0 = \frac{V_0}{|Z|} = \frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}$$

same
as before.

$$\tan \phi_z = \frac{y}{x} = \frac{-1/\omega C}{R} = -\frac{1}{\omega RC}$$

$$\therefore \phi_z = \tan^{-1}\left(-\frac{1}{\omega RC}\right) = -\tan^{-1}\left(\frac{1}{\omega RC}\right)$$

$$\therefore \phi = -\phi_z = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

same
as before.

Impedance of an Inductor

Recall volt. across an inductor is given by

$$V_L = L \frac{di}{dt}$$

Express $i = \bar{I}_0 e^{j(\omega t + \phi)}$

$$\therefore \frac{di}{dt} = j\omega \underbrace{I_0 e^{j(\omega t + \theta)}}_i = j\omega i$$

$$\therefore v_L = L(j\omega i) = i(j\omega L)$$

$$\therefore v_L = i Z_L$$

↑
 volt. across inductor

↑
 current in inductor

← inductor impedance
 $Z_L = j\omega L$

$$\text{Note } [Z_L] = [Z_C] = [Z_R] = \Omega$$

$$[\omega L] = \Omega$$

$$[L] = H = \frac{\Omega}{[\omega]} = \Omega s$$


$$\left[\frac{1}{\omega C}\right] = \Omega$$

$$[C] = F = \frac{1}{\Omega [\omega]} = \frac{s}{\Omega}$$

$$[LC] = \Omega s \frac{s}{\Omega} = s^2$$

Current in an LRC circuit.

$$i = I_0 e^{j(\omega t + \theta)}$$

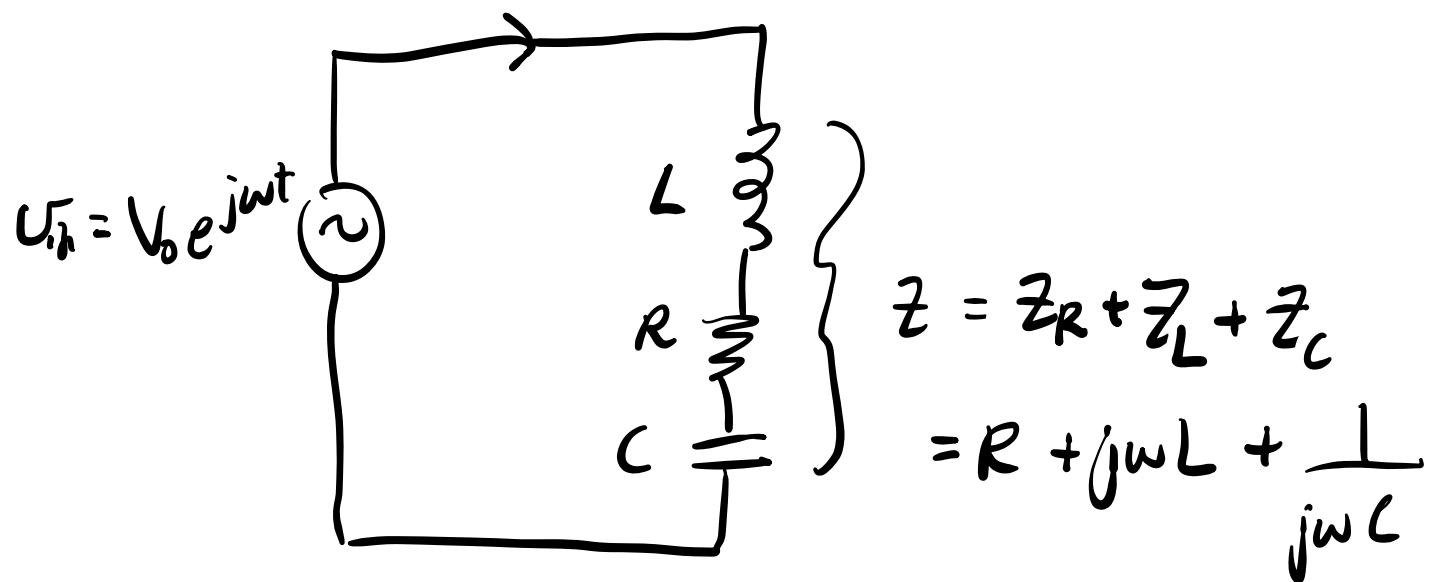

$$\therefore Z = \underbrace{R}_x + j \underbrace{\left(\omega L - \frac{1}{\omega C}\right)}_y$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = R \sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}$$

$$\tan \theta_z = \frac{y}{x} = \frac{\left(\omega L - \frac{1}{\omega C}\right)}{R} = \omega \frac{L}{R} - \frac{1}{\omega RC}$$

$$\therefore I_0 = \frac{V_0}{|Z|} = \frac{V_0/R}{\sqrt{1 + \left(\omega \frac{L}{R} - \frac{1}{\omega RC}\right)^2}}$$

$$\phi = -\phi_z = \tan^{-1} \left(\frac{1}{\omega RC} - \omega \frac{L}{R} \right)$$