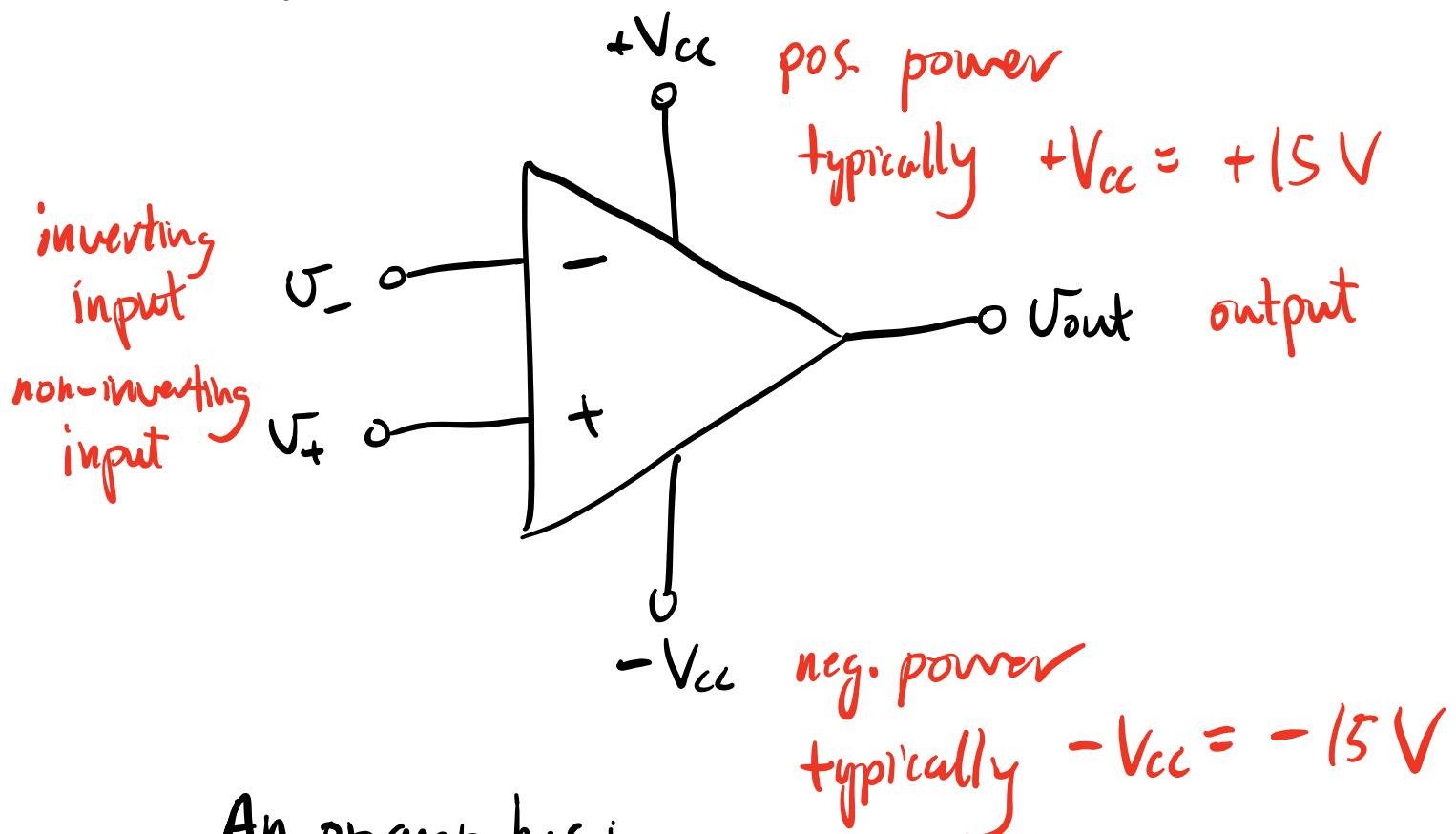


## Today: Operational Amplifiers (Op Amps)



An opamp has:

- two inputs
- one output
- two power terminals

The two inputs  $V_-$  &  $V_+$  can each be positive or negative voltages.

Treat the op amp as a black-box device  
(not concerned with internal structure).


Op Amp is designed s.t.

$$V_{\text{out}} = A_{\text{OL}} (V_+ - V_-)$$

$A_{\text{OL}}$  is called the "open loop" gain of the op amp. For the device that we'll use in PHYS 231 (LM 741)

$$A_{\text{OL}} \approx 2 \times 10^5$$

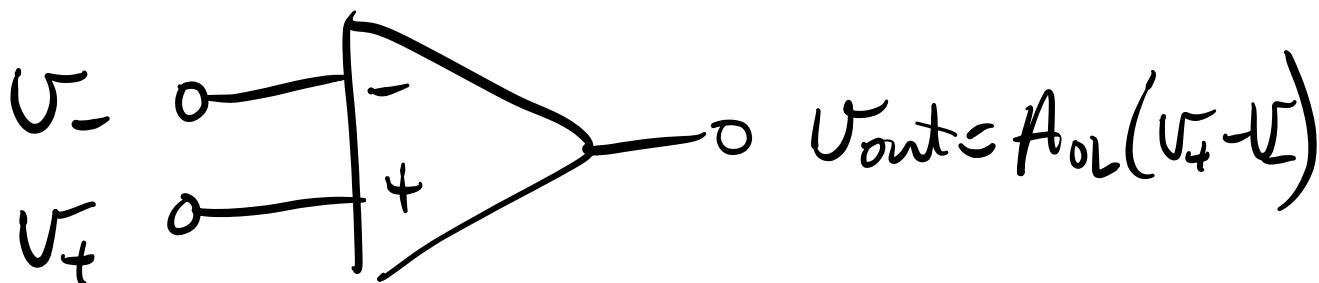In circuit diagrams, the power terminals are often omitted for clarity (to reduce clutter). However, the opamp always needs to be powered with  $\pm 15\text{V}$ .




## Limitations:

$$\textcircled{1} \quad |V_{\text{out}}| \leq V_{\text{sat}} \approx V_{\text{cc}} - 1 \text{ V}$$

Saturation volt.

if  $V_{\text{cc}} = 15 \text{ V}$ ,  $V_{\text{sat}} \approx 14 \text{ V}$

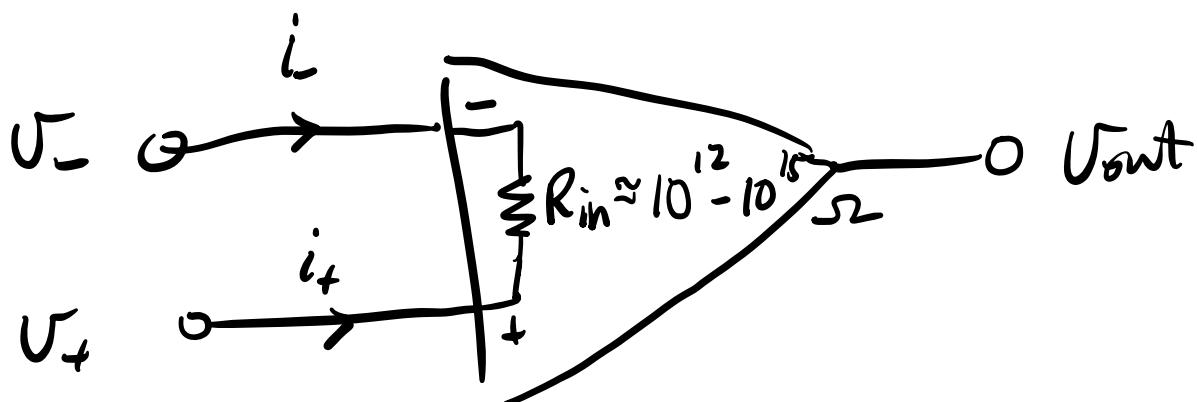\textcircled{2} The input impedance/resistance of the op amp is very high.



Assume  $R_{\text{in}} \rightarrow \infty$  s.t.  $i_- = i_+ = 0$

No current flows into or out of the op amp, inverting & non-inverting inputs.

Note: Output can have non-zero current.


Sec. 6.3 in Textbook.

## Op Amp Golden Rules.

1. Op Amp input impedance  $\rightarrow \infty$ .

$$i_- = i_+ = 0$$

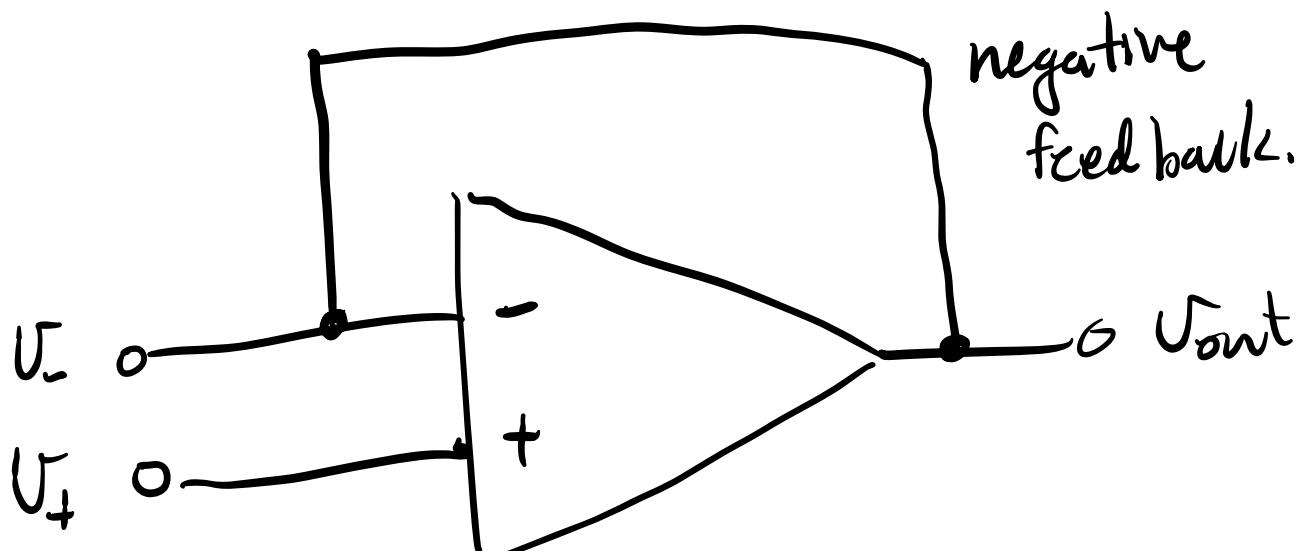2. The second opamp Golden Rule applies to opamp circuits using negative feedback.



If the feedback loop is broken, then we have the "open loop" case.

Know  $V_{out} = A_{OL}(V_+ - V_-)$

w/ negative feedback drawn above,  
we require  $\underline{V_{out}} = \underline{V_-}$

$$\begin{aligned}\therefore V_- &= A_{OL}(V_+ - V_-) \\ &= A_{OL} V_+ - A_{OL} V_-\end{aligned}$$

$$\therefore V_- (1 + A_{OL}) = A_{OL} V_+$$

$$\therefore V_- = \left( \frac{A_{OL}}{A_{OL} + 1} \right) V_+$$


If  $A_{OL} \gg 1$  (always the case)

$$V_- \approx V_+$$

2nd Golden Rule : When using negative feedback, volt. difference across op amp inputs is zero  $\Rightarrow V_- = V_+$

First Op Amp Application :

Inverting Amplifier.

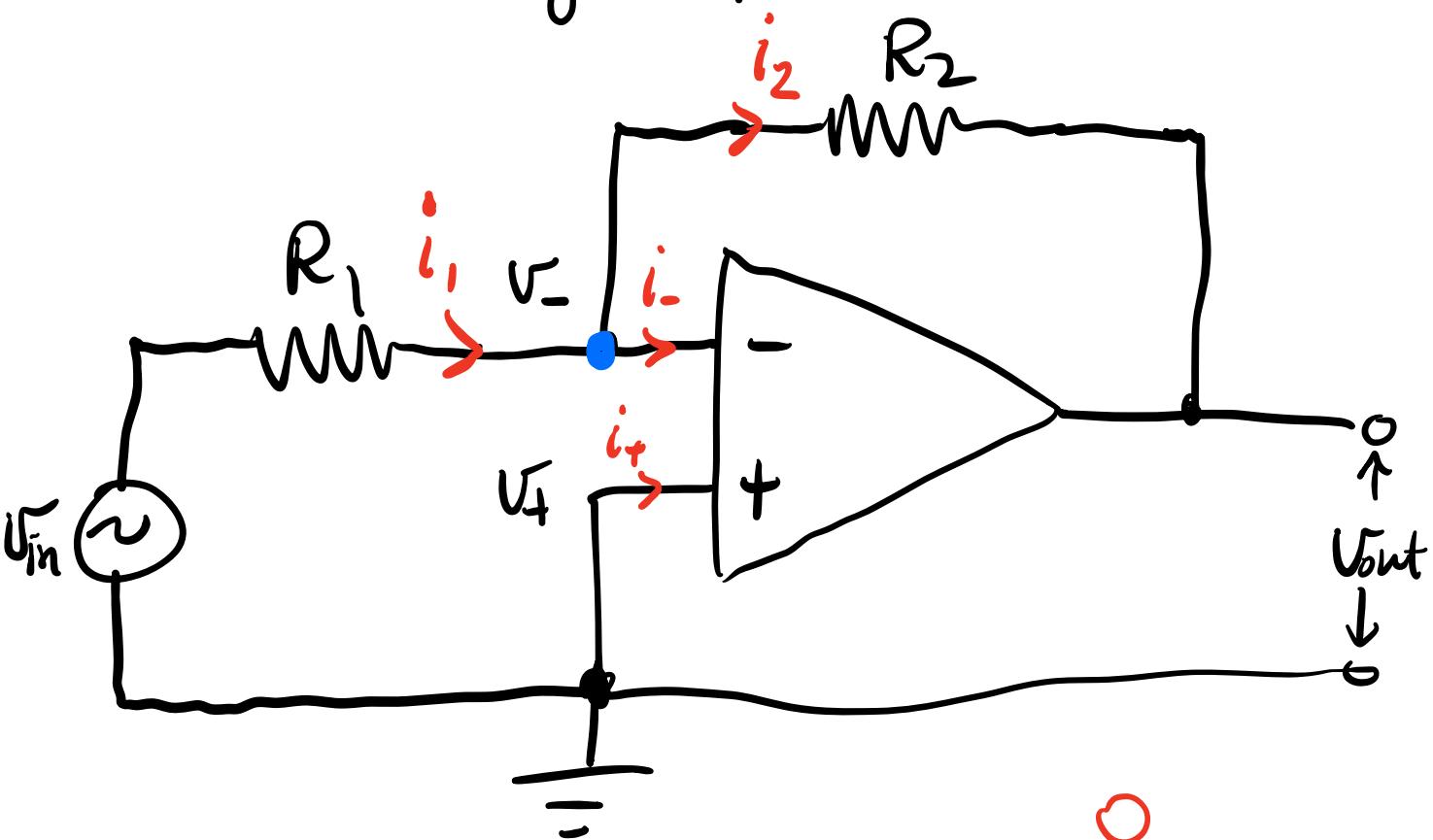


Jon Rule @ •

$$i_1 = i_- + i_2$$

$$\therefore i_1 = i_2 \equiv i$$

By GR #1  $i_- = i_+ = 0$

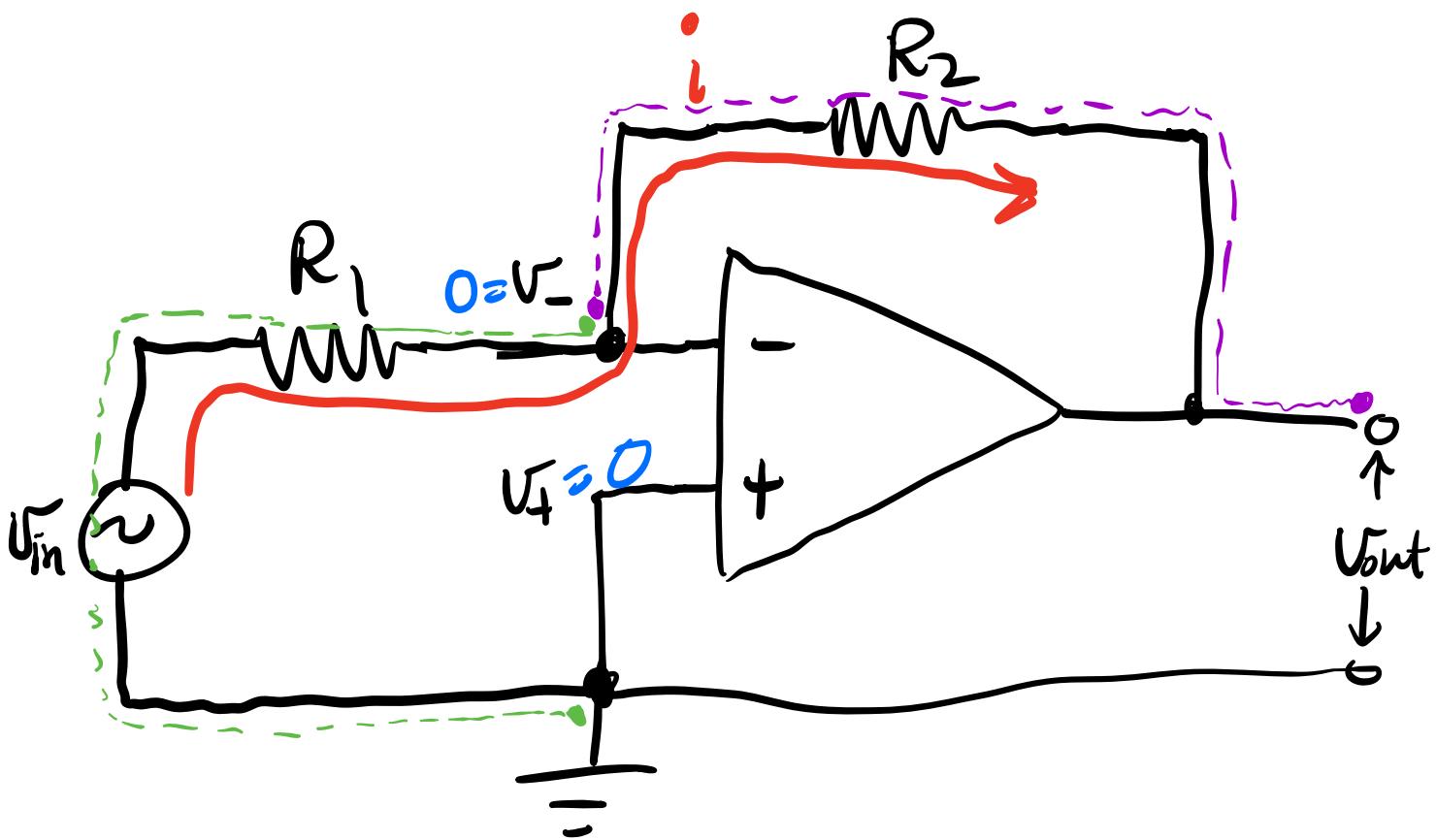

Effectively, the first GR makes this like a single-loop circuit (outer loop) that includes  $V_{in}$ ,  $R_1$ ,  $R_2$ ,  $V_{out}$ ,  $i$ .

By the second GR,  $V_- = V_+$ .

But...  $V_+ = 0$  b/c of direct connection to ground.  $\therefore V_+ = V_- = 0$ .

Consider Kirchhoff voltage loop analysis from ground to  $V_- = 0$ .

$$0 + V_{in} - iR_1 = V_- = 0$$

$$\Rightarrow \boxed{i = \frac{V_{in}}{R_1}}$$

We now know current.

Following the purple path, loop rule analysis requires:

$$V_- = 0 - iR_2 = V_{out}$$

$$\therefore V_{out} = -iR_2$$

$$\therefore V_{out} = -\left(\frac{V_{in}}{R_1}\right)R_2$$

$$\therefore V_{\text{out}} = - \underbrace{\frac{R_2}{R_1}}_{\text{Gain}} V_{\text{in}}$$

Gain of our amplifier.

Gain  $< 0$  is called an inverting amplifier.