



PHYS 231 - Oct. 3, 2023

- Pls. submit Assign. #1 on Thursday, Oct. 5, 2023 at the start of your lab.
- Assignment #2 will be posted on the course website this week.

Previously: Solved differential equations to find $i(t)$ in RC & LRC circuits
→ Transient response.

- You will analyze the transient response of an LR circuit in assignment #2.
- Today: Analyze the frequency response of an RC circuit. i.e. how does i vary with frequency (instead of time).

RC Circuit Freq. Response

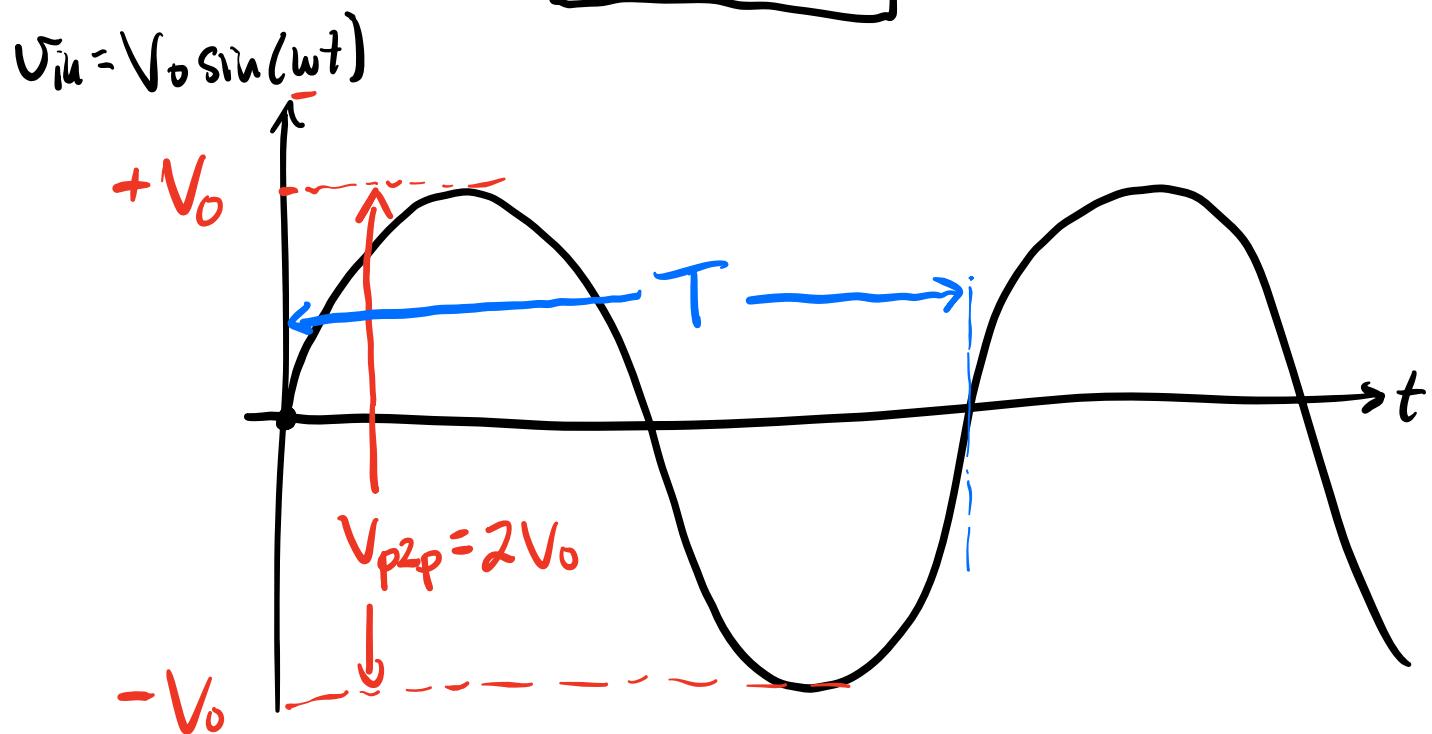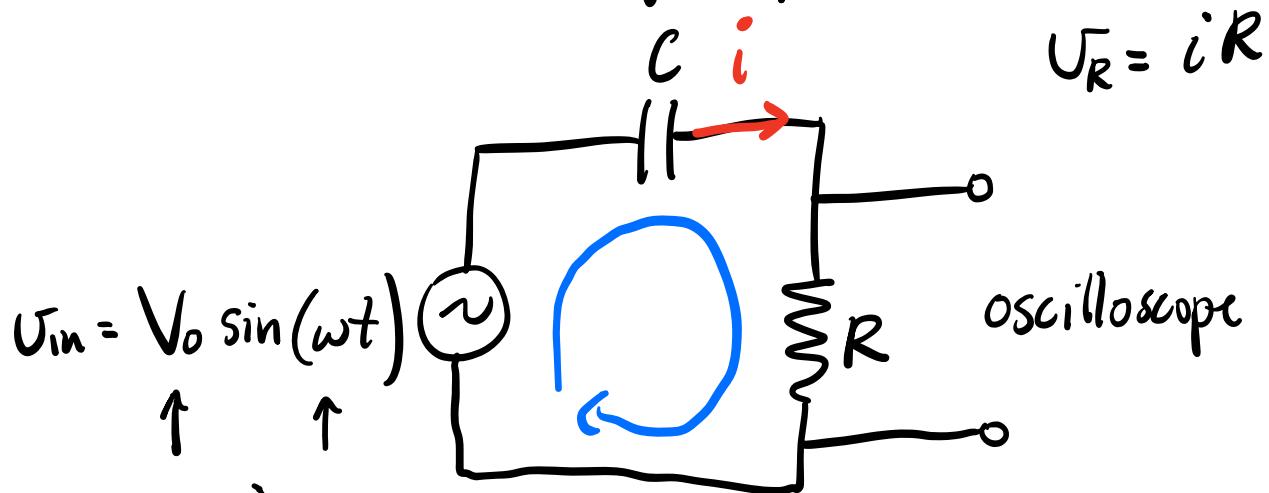

V_0 : amplitude

T : period (time to complete one full cycle).

$f = \frac{1}{T}$ is the frequency. $[f] = \text{Hz}$

$$\omega = 2\pi f = \frac{2\pi}{T} : \text{angular freq.}$$

$$[\omega] = \frac{\text{rad}}{\text{s}}$$

Observations from Part 4 of Lab #2:

- current also osc. sinusoidally
{} has the same freq. as V_{in} .
- current is out of phase w/ V_{in} .
The obs. phase depends on ω .
- The amplitude of the current
depends on ω .

Assume that the current in the RC circuit
is of the form:

$$i = I_0(\omega) \sin [\omega t + \phi(\omega)]$$

↓ ↑
 freq. depend. amplitude freq. depend. phase.

↙ ↑
 same freq. as V_{in}

Goal: Determine how $I_o(\omega)$ & $\mathcal{D}(\omega)$ depend on freq. & the circuit components.

KVL:

$$V_{in} - V_c - V_R = 0$$

$$V_{in} - \frac{q}{C} - i'R = 0$$

Take a time derivative of this expression

$\frac{dV_{in}}{dt} = \frac{1}{C}i + R \frac{di}{dt}$ differential eq'n in i .

Know $V_{in} = V_0 \sin \omega t$

$$\frac{dV_{in}}{dt} = \omega V_0 \cos \omega t$$

$$i = I_0 \sin(\omega t + \mathcal{D})$$

$$\frac{di}{dt} = \omega I_0 \cos(\omega t + \mathcal{D})$$

sub into

#

$$\omega V_0 \cos \omega t = \frac{I_0}{C} \sin(\omega t + \phi) + \omega I_0 R \cos(\omega t + \phi)$$

Use the following trig identities:

$$\sin(\omega t + \phi) = \sin \omega t \cos \phi + \cos \omega t \sin \phi$$

$$\cos(\omega t + \phi) = \cos \omega t \cos \phi - \sin \omega t \sin \phi$$

$$\omega V_0 \cos \omega t = \frac{I_0}{C} \left(\underline{\sin \omega t} \cos \phi + \underline{\cos \omega t} \sin \phi \right)$$

$$+ \omega I_0 R \left(\underline{\cos \omega t} \cos \phi - \underline{\sin \omega t} \sin \phi \right)$$

$$\left\{ \sin \omega t \left(\frac{I_0}{C} \cos \phi - \omega I_0 R \sin \phi \right) \right.$$

$$\left. + \cos \omega t \left(\frac{I_0}{C} \sin \phi + \omega I_0 R \cos \phi - \omega V_0 \right) \right) = 0$$

This expression must be valid at All times.

at some particular times will have

$$\sin \omega t = 0 \quad \left\{ \begin{array}{l} \cos \omega t \neq 0. \end{array} \right.$$

At these times, require

①

$$\frac{I_0}{C} \sin \theta + \omega I_0 R \cos \theta - \omega V_0 = 0$$

a b

At other times, $\cos \omega t = 0 \quad \left\{ \sin \omega t \neq 0 \right.$

∴ it must also be true that :

②

$$\frac{\overline{I}_0^1}{C} \cos \theta - \omega \overline{I}_0^1 R \sin \theta = 0$$

Now, we try to solve Eqs ① & ② for $\theta(\omega) \& I_0(\omega)$.

Start w/ Eq'n ②.

$$\frac{1}{C} \cos \phi = \omega R \sin \phi$$

↓ divide by $\omega R \cos \phi$


$$\frac{1}{\omega RC} = \tan \phi \Rightarrow \boxed{\phi(\omega) = \tan^{-1}\left(\frac{1}{\omega RC}\right)}$$

Freq. dependence of the phase of the current.

Return to

$$\tan \phi = \frac{\sin \phi}{\cos \phi} = \frac{\text{opp}}{\text{adj}} = \frac{1}{\omega RC}$$

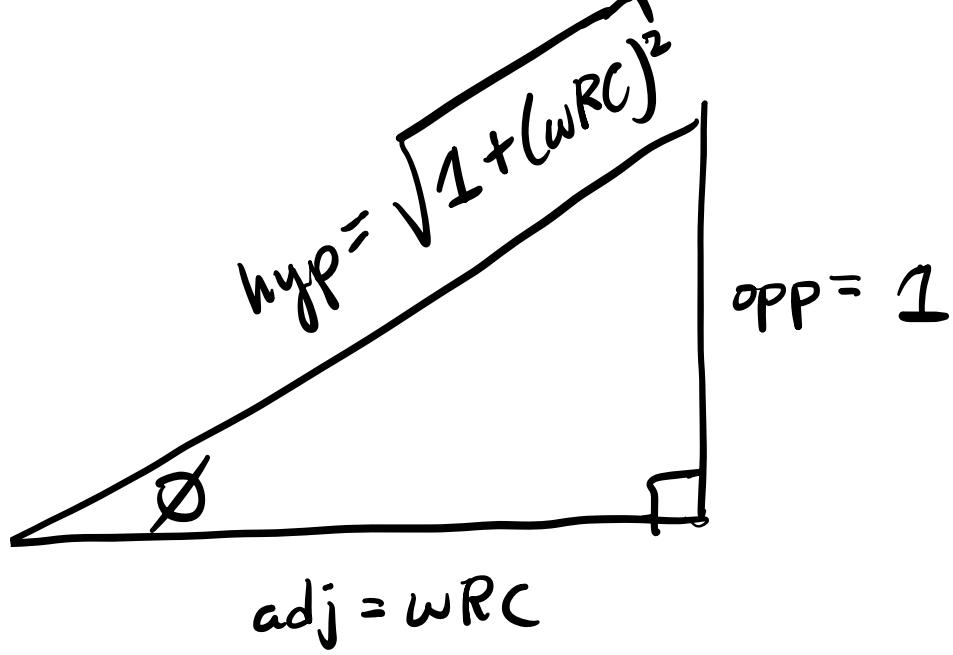Strategy: Construct a right-angle triangle
w/ opp = 1 adj = ωRC



$$\sin \phi = \frac{\text{opp}}{\text{hyp}} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad (a)$$

$$\cos \phi = \frac{\text{adj}}{\text{hyp}} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \quad (b)$$

Sub (a) & (b) into Eq'n ①.

$$\text{Eq'n ①: } \frac{I_o}{C} \sin \phi + \omega I_o R \cos \phi - \omega V_0 = 0$$

$$\rightarrow \frac{I_o}{C} \frac{1}{\sqrt{1 + (\omega RC)^2}} + \omega I_o R \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} - \omega V_0 = 0$$


solve for $I_0(\omega) \rightarrow$ Exercise for the student

$$I_0 = \frac{\omega V_0 C}{\sqrt{1 + (\omega RC)^2}}$$

Show the current amplitude I_0 varies w/ freq. ω .

Lab #3 Preview


Charging a capacitor through a resistor

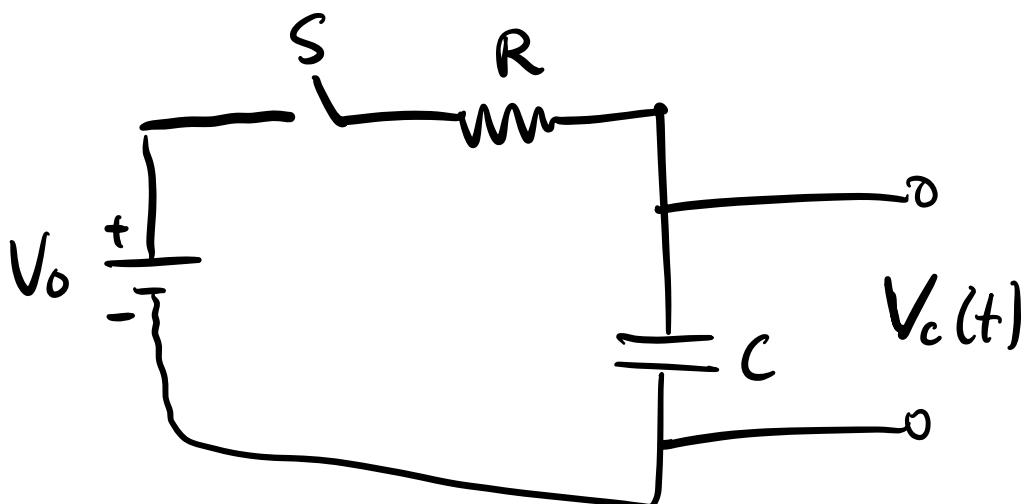

$$V_c(t) = V_0 \left(1 - e^{-t/\tau}\right) \text{ where } \tau = RC$$




Discharging Capacitor through resistor

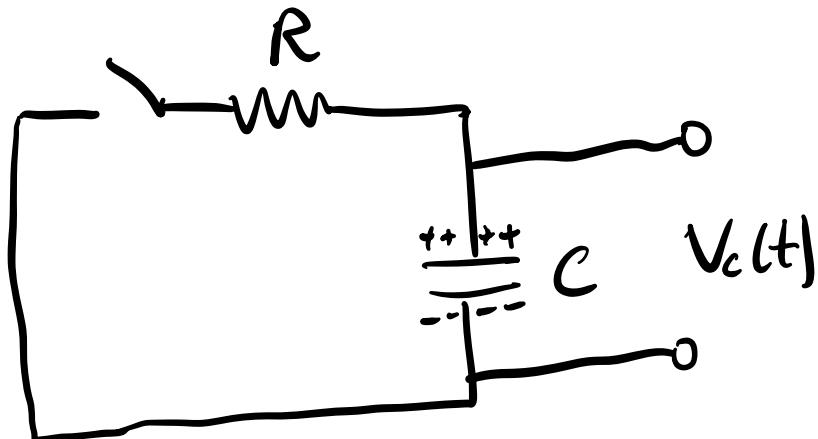


Capacitor initially charged to V_0 .
Close switch at time $t=0$.

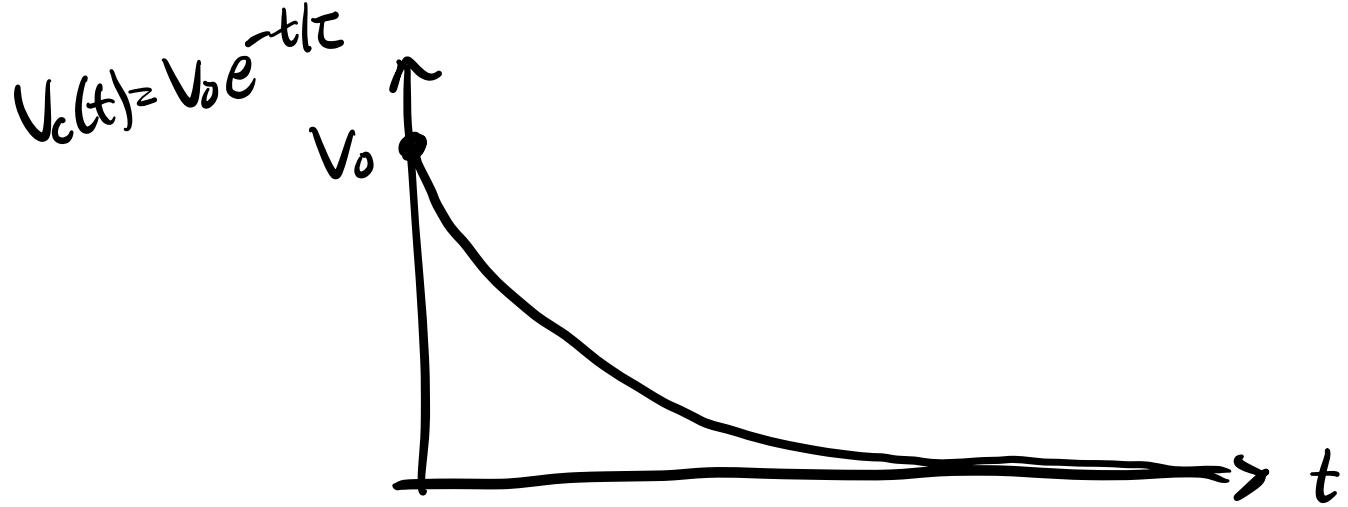
$$V_c(t) = V_0 e^{-t/\tau} \quad \tau = RC$$



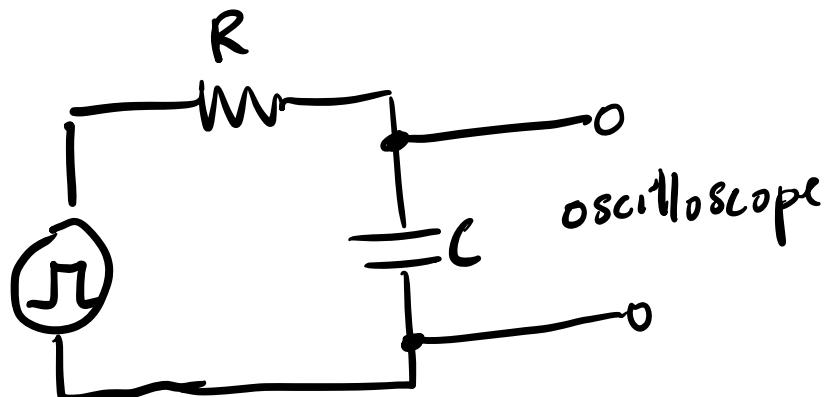In the Lab, you will construct
the following circuit:



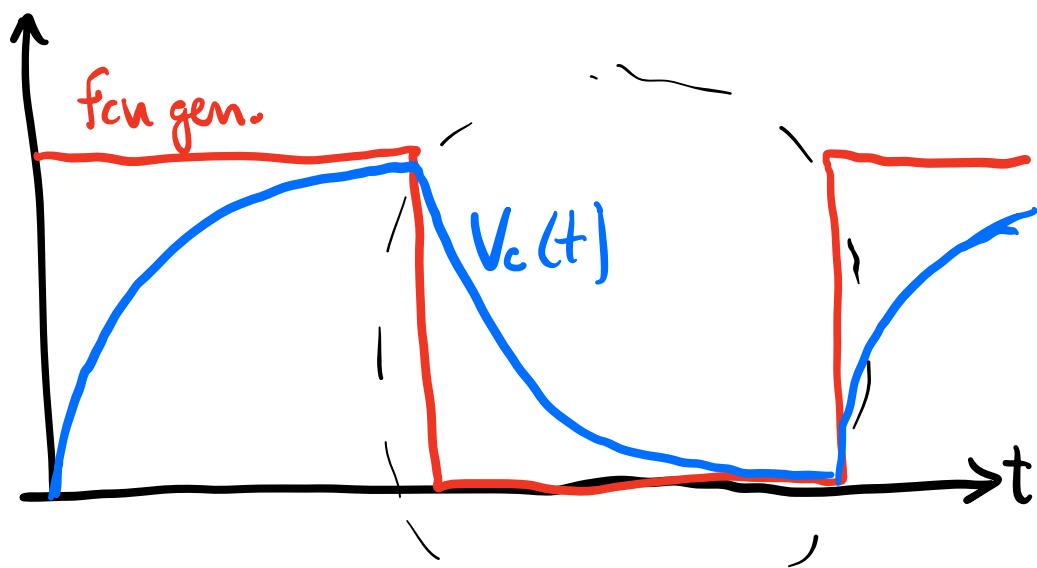fun gen. is
set to a low
freq - square wave.



Goal is to make a quick estimate of time const $\tau = RC$.

To estimate τ , find the value of $V_c(t=\tau)$.

$$V_c(t) = V_0 e^{-t/\tau} \text{ (discharging),}$$

\therefore when $t=\tau$

$$V_c(t=\tau) = V_0 e^{-\tau/\tau} = \frac{V_0}{e} = .368 V_0$$

