

PHYS 231 - Sept. 13, 2023


Last Time:

$$|\Delta V_c| = \frac{Q}{C}$$

$$|\Delta V_R| = IR = R \frac{dQ}{dt}$$

$$|\Delta V_L| = L \frac{dI}{dt} = L \frac{d^2Q}{dt^2}$$

LRC circuit

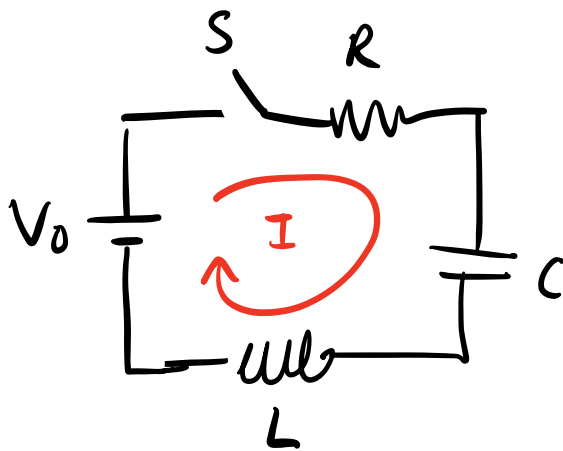


$$V_0 = \frac{1}{C}Q + R \frac{dQ}{dt} + L \frac{d^2Q}{dt^2}$$

2nd order differential eq.

Can solve for time dependence of Q .

Will look at this sol'n later in the course.

RC Circuit

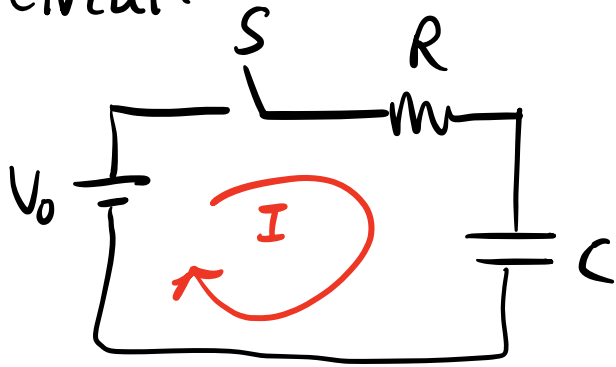

Assume capacitor uncharged at $t=0$ when switch is closed.

Initial Condition: $Q(t=0) = 0$.


$$V_0 = \frac{1}{C} Q + R \frac{dQ}{dt}$$

First order differential eq.

$$\Rightarrow CV_0 = Q + RC \frac{dQ}{dt}$$

A long time after switch is closed ($t \rightarrow \infty$) reach a new equilibrium ($\frac{dQ}{dt} = 0$)

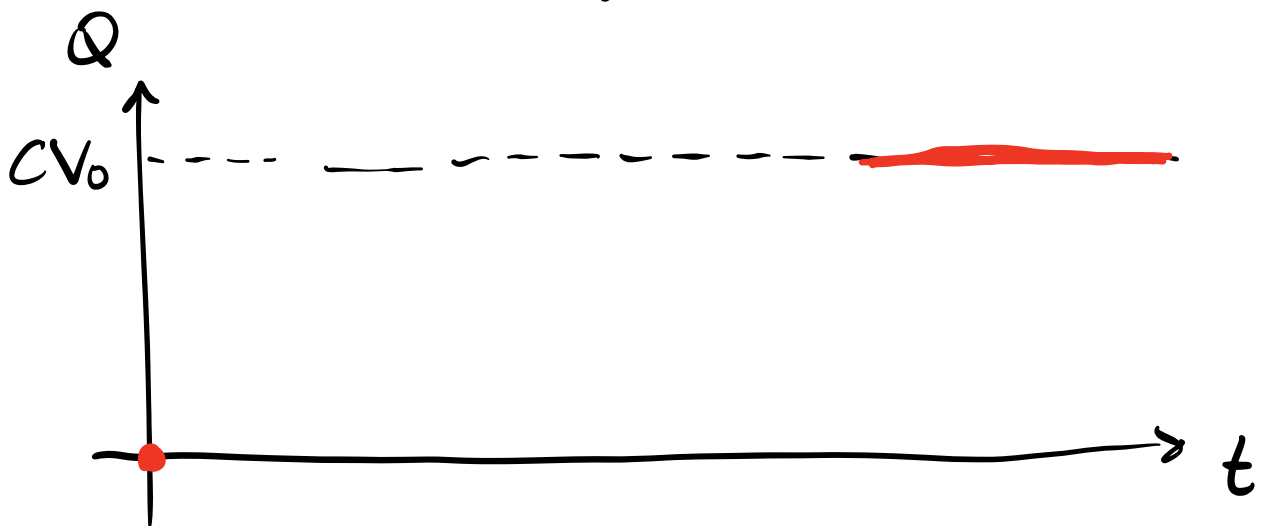When this happens, get $Q_0 = CV_0$ @ $t \rightarrow \infty$.



Express $Q(t)$ as sum of some time-dep. $Q_h(t)$ and a constant Q_0 ($t \rightarrow \infty$).

$$Q(t) = Q_h(t) + \underbrace{Q_0}_{CV_0} \quad \textcircled{1}$$

Sub $\textcircled{1}$ into our first-order diff. eq'n.

$$\cancel{CV_0} = \left(Q_h(t) + \cancel{CV_0} \right) + RC \frac{d}{dt} \left(Q_h(t) + CV_0 \right)$$

↑
called "homogeneous" sol'n.

$$\therefore 0 = Q_h(t) + RC \frac{dQ_h(t)}{dt}$$

$$Q_h(t) = -RC \frac{dQ_h(t)}{dt} \quad (\text{mult. by } dt)$$

$$Q_h(t) dt = -RC dQ_h(t) \quad (\text{divide by } -RC Q_h(t))$$

$$-\frac{1}{RC} dt = \frac{dQ_h(t)}{Q_h(t)} \quad (\text{integrate})$$

define $RC = \tau$ (time constant),

$$-\frac{1}{\tau} \int dt = \int \frac{dQ_h(t)}{Q_h(t)}$$

$$-\frac{1}{\tau} t + B = \ln Q_h(t)$$

↑
integration const.

$$\begin{aligned} \therefore Q_h(t) &= e^{(-t/\tau + B)} \\ &= e^{-t/\tau} \underbrace{e^B}_{\equiv B'} \end{aligned}$$

$$\therefore Q_h(t) = B' e^{-t/\tau}$$

Since $Q(t) = Q_h(t) + CV_0$

$$= B' e^{-t/\tau} + CV_0.$$

Still need to find B' .

Using initial condition $Q(t=0) = 0$ to find B' .

$$Q(t=0) = 0 = B' + CV_0$$


$$\therefore B' = -CV_0$$

Final sol'n for $Q(t)$ is:

$$Q(t) = -CV_0 e^{-t/\tau} + CV_0$$

$$Q(t) = CV_0 [1 - e^{-t/\tau}]$$

$$\tau \equiv RC$$

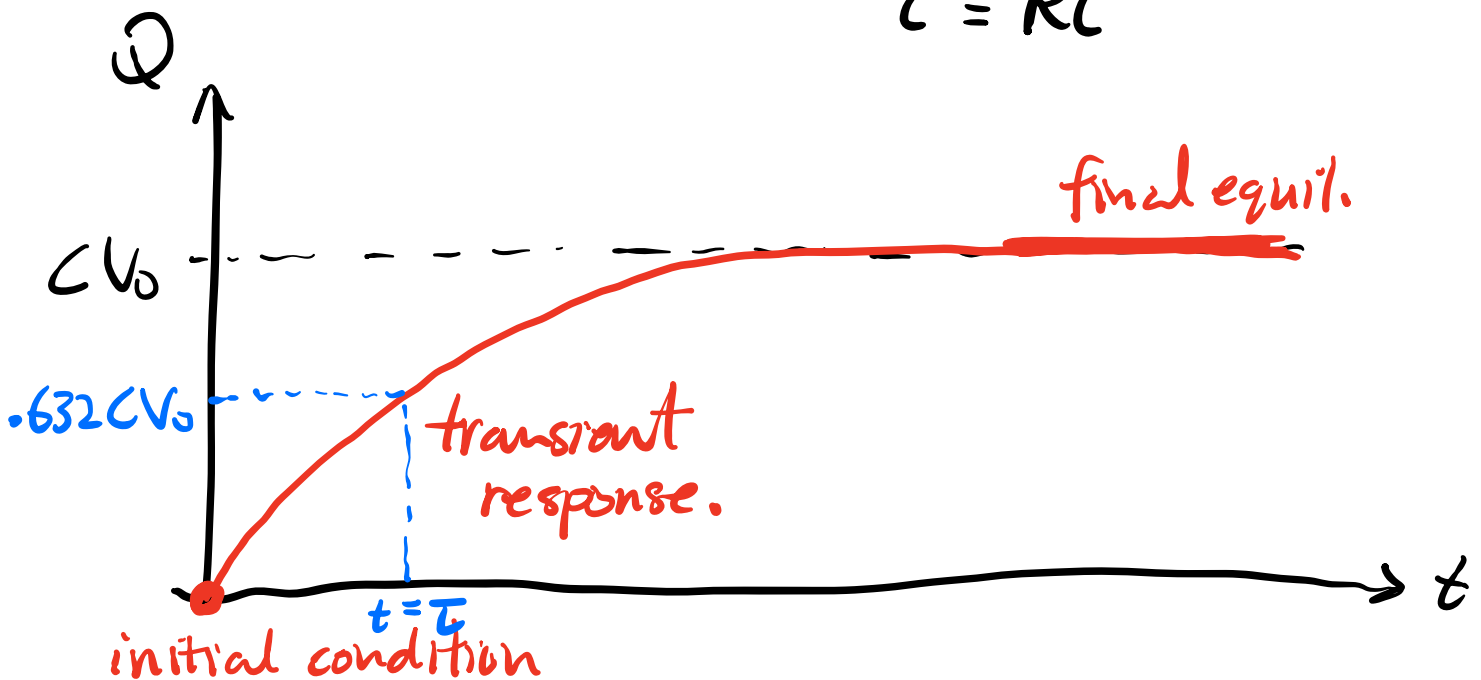


Find the charge on capacitor when
 $t = \tau$

$$Q(t=\tau) = CV_0 \underbrace{[1 - e^{-1}]}_{0.632}$$

To find the current, take time derivative of charge.

$$\begin{aligned} I &= \frac{dQ}{dt} = \frac{d}{dt} (CV_0 [1 - e^{-t/\tau}]) \\ &= -CV_0 \frac{d}{dt} e^{-t/\tau} \\ &= \frac{CV_0}{\tau} e^{-t/\tau} \end{aligned}$$

$$I = \frac{V_0}{R} e^{-t/\tau}$$

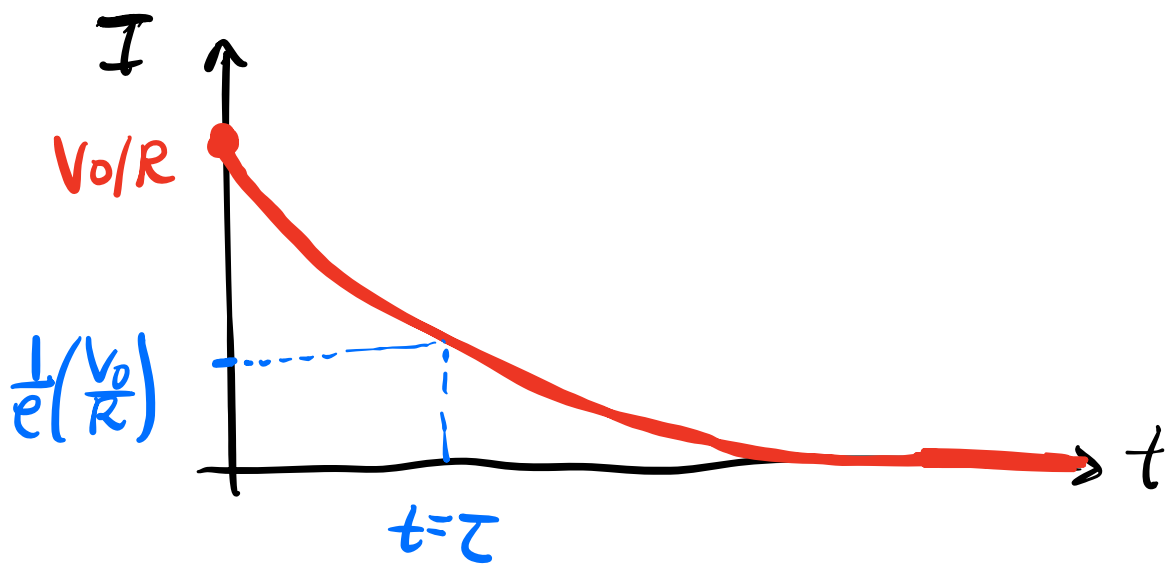


Uncertainties & Propagation of Errors.

Every quantity that is measured has an associated uncertainty.

Experiment: Drop a penny from a tall building & meas time for it to reach the grd. For each trial we will meas. a unique fall time.

trial #	time (s)
1	148.25
2	151.1
3	150.4
⋮	⋮
N	149.7

Plot the measured data as a histogram

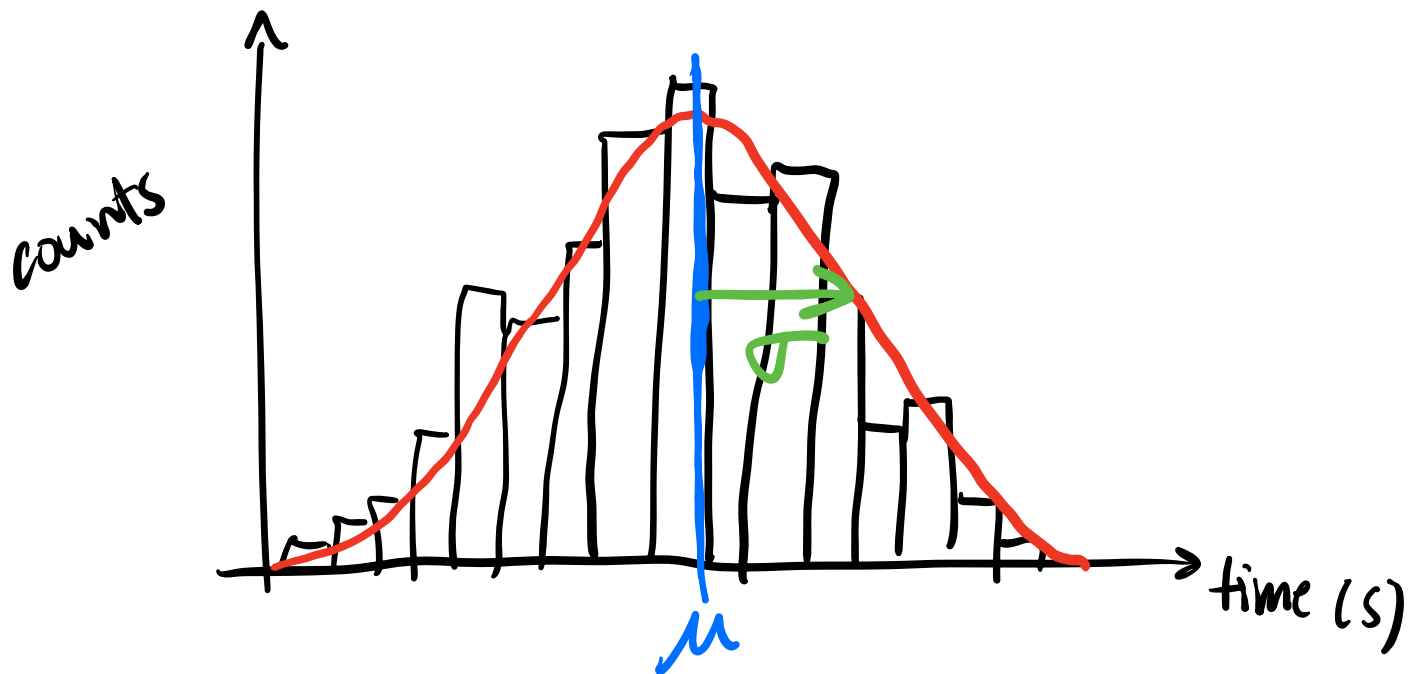

If the uncertainty in the meas. is random, then the data will follow a Gaussian or normal dist'n (Bell curve).

Can characterize the shape of the dist'n using the mean or average μ .

$$\mu = \frac{1}{N} \sum_{i=1}^N t_i$$

and the standard deviation, σ .

σ characterizes the width of the dist'n.

$$\sigma = \sqrt{\frac{1}{N-1} \sum_{i=1}^N (t_i - \mu)^2}$$