


PHYS 231 - Sept. 25, 2023

Assign #1 is online.

Due Wed. Oct. 4.

No classes Oct. 2 & Oct. 9
 $\underbrace{\text{Oct. 2}}_{\text{T\{R}}$ $\underbrace{\text{Oct. 9}}_{\text{Thanksgiving.}}$

Today: Series LRC circuit (Lab #4)

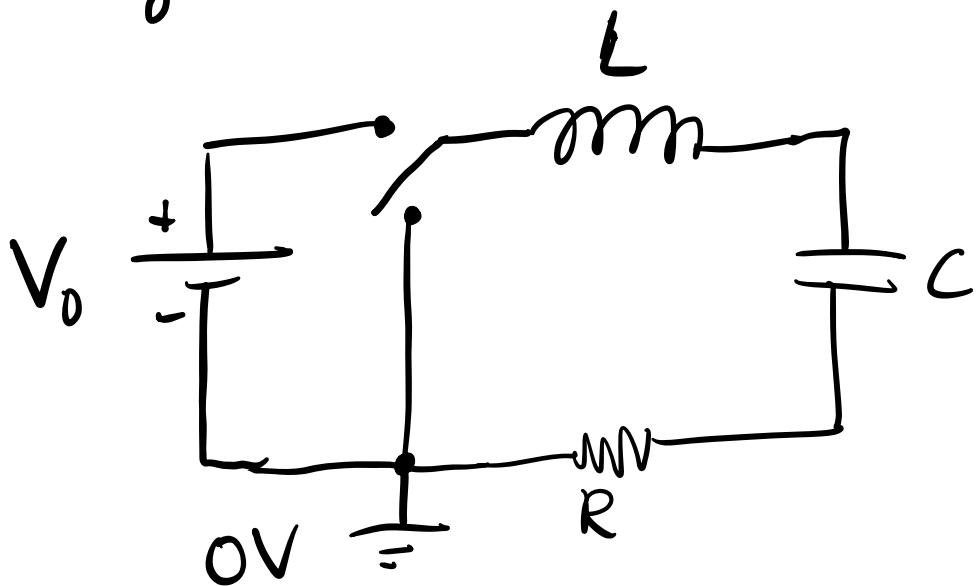

When the switch is in the "up" position,
K.V.R. requires:

$$V_0 - V_L - V_C - V_R = 0$$

$$V_0 - L \frac{d^2 q}{dt^2} - \frac{q}{C} - R \frac{dq}{dt} = 0$$

$$\therefore \frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = \frac{V_0}{L}$$

(a)

Second order diff. eq'n. \Rightarrow solve for $q(t)$.

You will encounter $\{\}$ solve this diff. eq'n
in MATH 225 & PHYS 216 next term.


If you like, see full sol'n on PHYS 231
website (optional reading, not required).

Start by assuming $q(t) = q_0 + q_n(t)$


...

Consider the mechanical analogy to the LRC circuit:

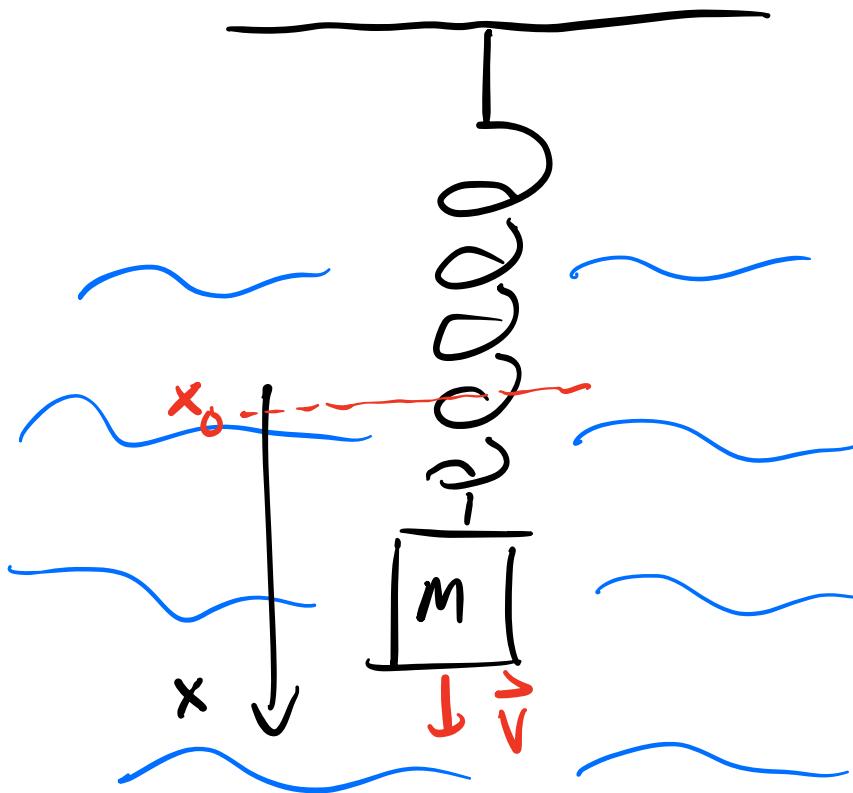
Mass hanging from a ceiling by a spring suspended in a viscous fluid.



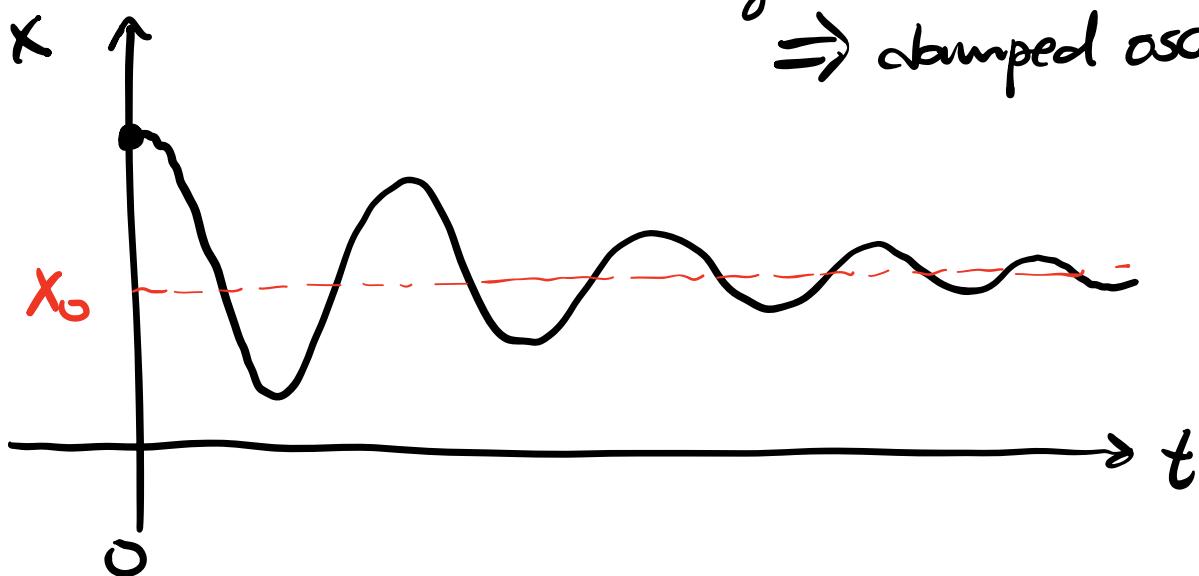If we stretch spring past its equil. s' then release the mass from rest, the mass will osc. & the amp. of osc. will decrease w/ time due to viscous drag.
⇒ damped osc.



FBD for mass on spring

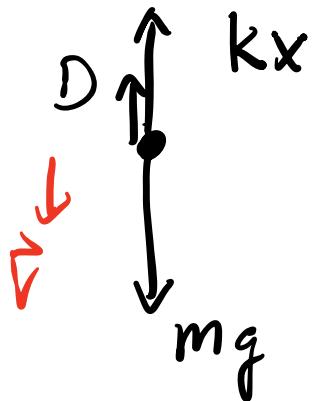

assume that
the drag force
is given by $D = bV$

drag coefficient

Newton's
Second Law

$$\underbrace{ma}_{\text{net force}} = mg - bv - kx$$

net force

$$v = \frac{dx}{dt} \quad a = \frac{d^2x}{dt^2}$$

$$\therefore mg = m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx$$

divide by m:

$$g = \frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m} x$$

(b)

Mathematically Eqs @ Ⓛ Ⓜ are identical. ∵ sol'n for $x(t)$ in Ⓜ gives us insight into the sol'n for $q(t)$ in Ⓛ.


For the mass on a spring, can find the equil. position that we reach when $t \rightarrow \infty$ by setting $\frac{dx}{dt} = \frac{d^2x}{dt^2} = 0$ in Ⓜ.

$$\text{Get } q = \frac{k}{m} x_0 \quad \xrightarrow{\text{equil. position}} \quad x_0 = \frac{mg}{k}$$


For the LRC circuit, can find equil. charge in the same way ($\frac{dq}{dt} = \frac{d^2q}{dt^2} = 0$ in Eqn Ⓛ).

$$\Rightarrow \frac{1}{LC} q_0 = \frac{V_0}{L} \quad \boxed{q_0 = CV_0}$$

Mass on a spring when oil

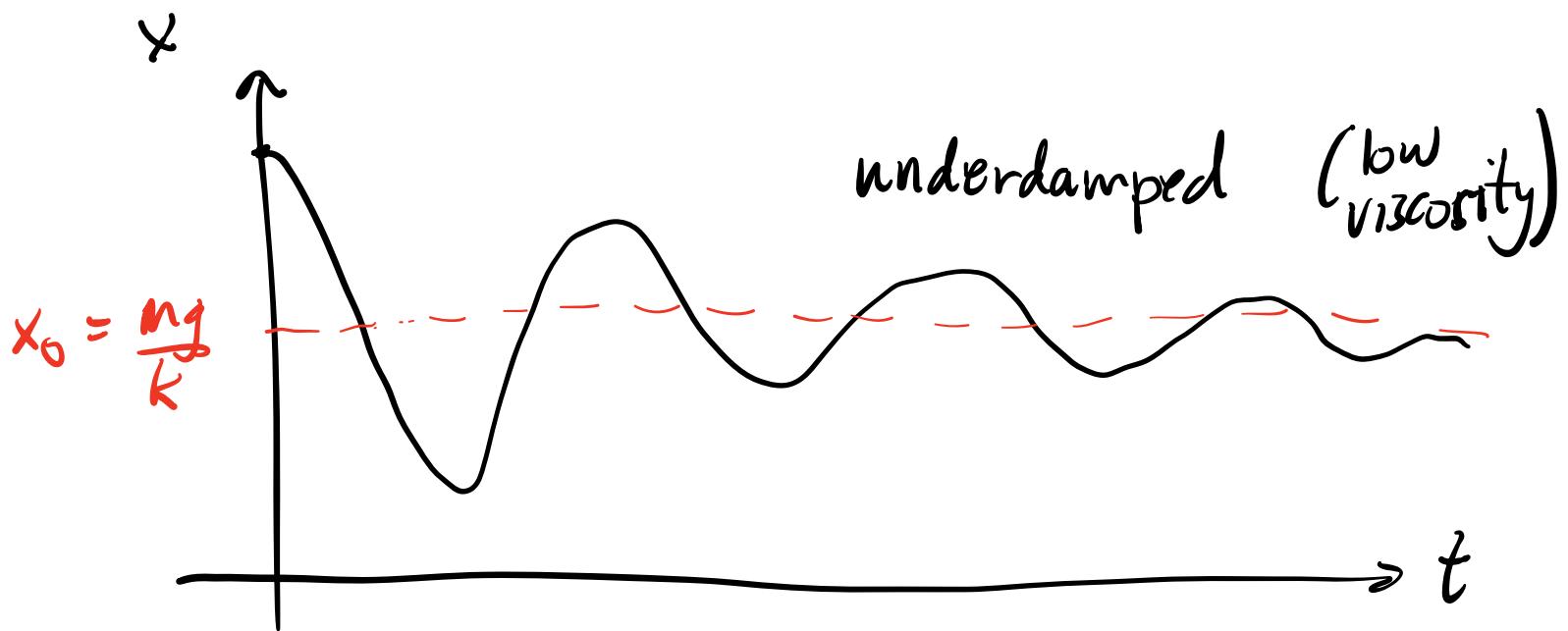

Mass on a spring in honey

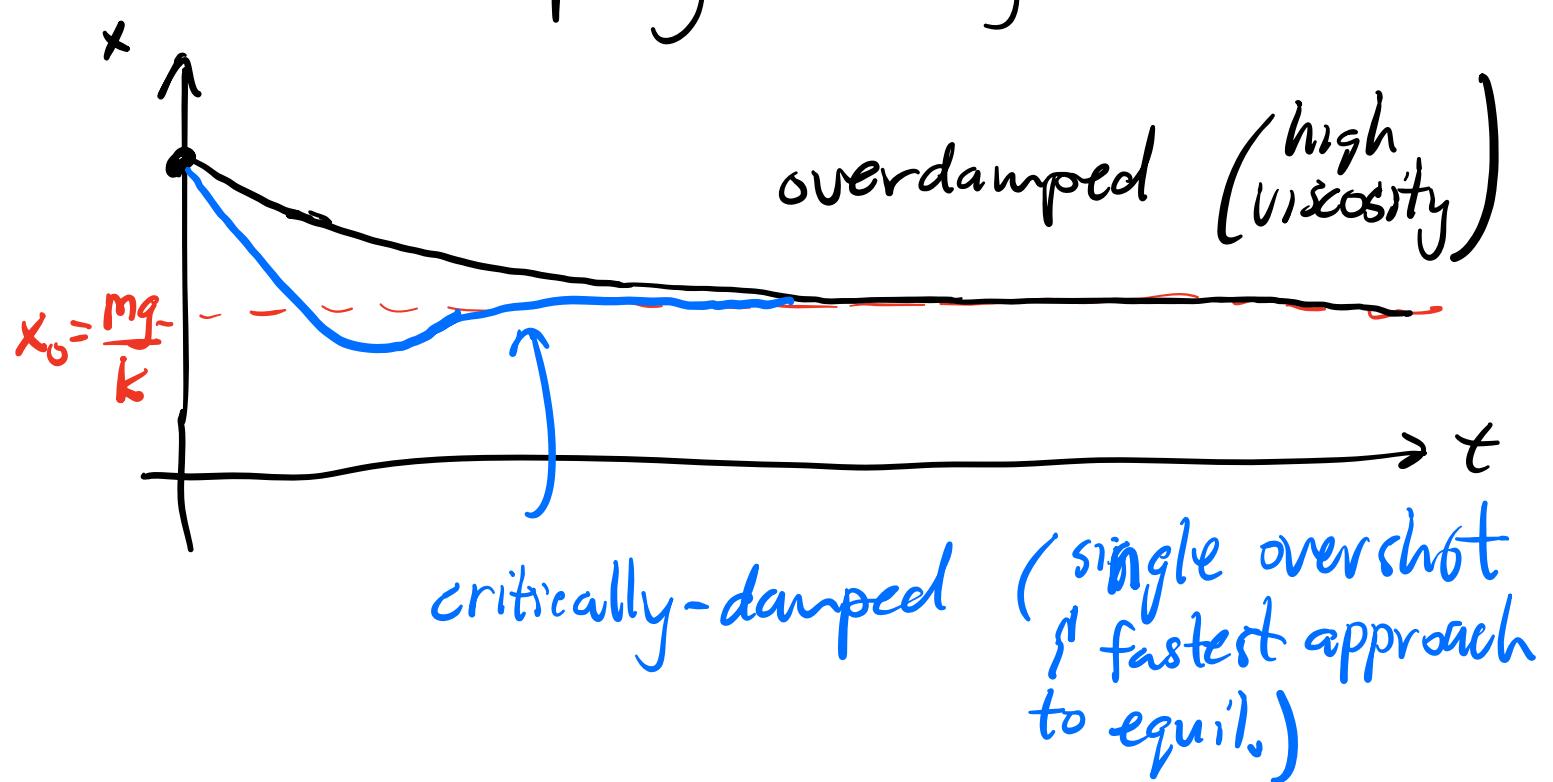

For the LRC circuit, we will focus on the underdamped case.

For underdamping, we require:

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}} \rightsquigarrow \text{i.e. } R \text{ small for under-damping.}$$

