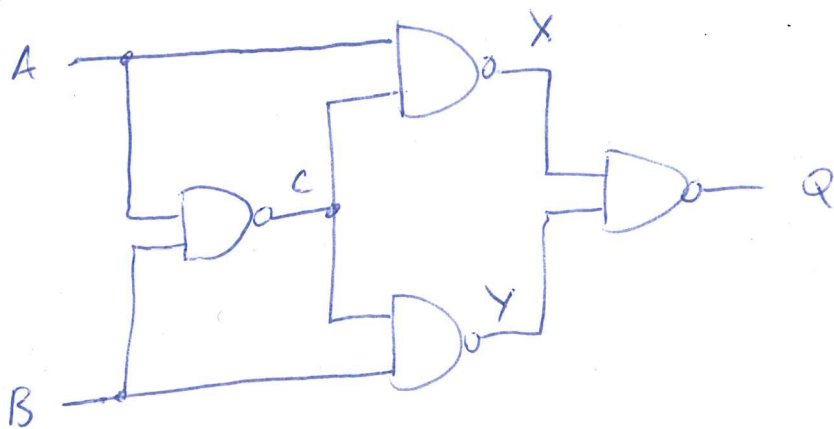


1. (a)



NAND

0	0	1
0	1	1
1	0	1
1	1	0

Truth table

A	B	c	X	Y	Q
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0


This is equivalent to the XOR truth table

$$Q = A \oplus B$$



2.5

1 (b)

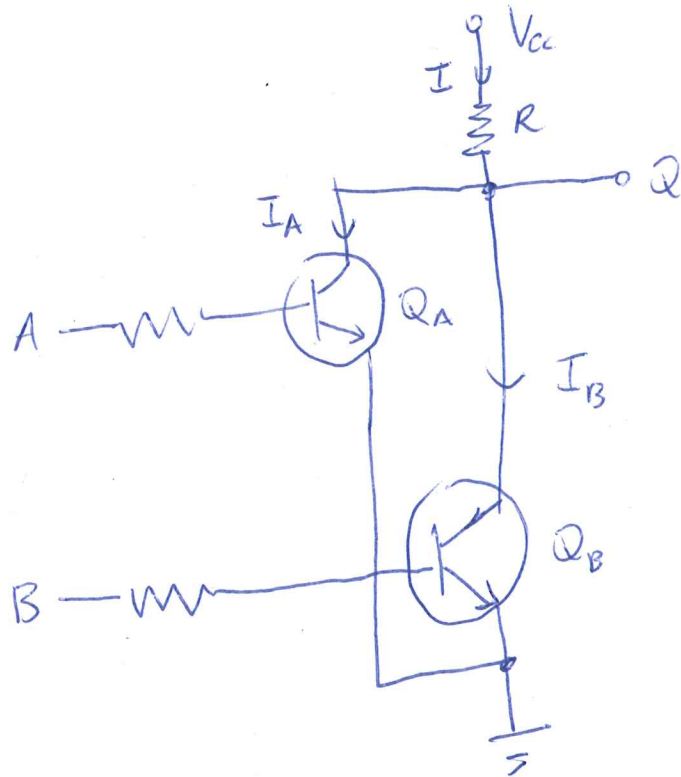

$$I = I_A + I_B$$

Truth table

A	B	QA	QB	IA	IB	Q = Vcc - IR
0	0	OFF OFF	OFF	0	0	1 (Vcc)
0	1	OFF	ON	0	≠ 0	0
1	0	ON	OFF	≠ 0	0	0
1	1	ON	ON	≠ 0	≠ 0	0

2.5

Equivalent to NOR truth table

$$Q = \overline{A + B}$$

2. (a)

A	B	$A \cdot B$	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A+B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

①

equivalent $\therefore \overline{A \cdot B} = \overline{A+B}$

A	B	$A+B$	$\overline{A+B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

①

equivalent $\therefore \overline{A+B} = \overline{A} \cdot \overline{B}$

(b)

A	B	C	$A+B$	$(A+B) \cdot C$	$A \cdot C$	$B \cdot C$	$A \cdot C + B \cdot C$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	0	1	1
1	0	0	1	0	0	0	0
1	0	1	1	1	1	0	1
1	1	0	1	0	0	0	0
1	1	1	1	1	1	1	1

①

equivalent $\therefore (A+B) \cdot C = A \cdot C + B \cdot C$

(c)

A	\bar{A}	$A \cdot \bar{A}$
0	1	0
1	0	0


$\therefore A \cdot \bar{A} = 0 \quad \forall A$
 (1)

(d)

A	A	$A \cdot A$
0	0	0
1	1	1

$\therefore A \cdot A = A \quad \forall A$
 (1)

3.

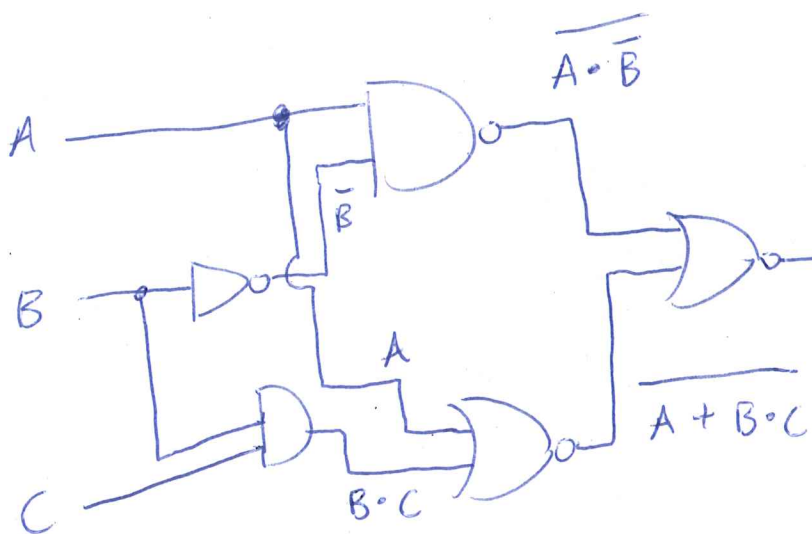

$Q = \overline{A \cdot \bar{B}} + \overline{A + B \cdot C}$
 (1)

$$Q = \overline{A \cdot \overline{B}} + \overline{A + B \cdot C}$$

①

use de Morgan's theorem

$$\overline{X + Y} = \overline{X} \cdot \overline{Y}$$

$$= \overline{\overline{A \cdot \overline{B}}} \cdot \overline{\overline{A + B \cdot C}}$$

①

use $\overline{\overline{X}} = X$

$$= (A \cdot \overline{B}) \cdot (A + B \cdot C)$$

use $(X + Y) \cdot Z = X \cdot Z + Y \cdot Z$

$$= A \cdot \overline{B} \cdot A + A \cdot \overline{B} \cdot B \cdot C$$

①

use $\overline{B} \cdot B = 0$
 $\{ \} \cdot X = 0 = 0$

$$\therefore Q = A \cdot \overline{B} \cdot A$$

use $X \cdot Y \cdot Z = X \cdot Z \cdot Y$

$$\therefore Q = A \cdot A \cdot \overline{B}$$

use $A \cdot A = A$ ①

$$\therefore Q = A \cdot \overline{B}$$


proof

X	Y	Z	X · Y	X · Y · Z	X · Z	X · Z · Y
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	1	0
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	1	1	1	1


↑
equivalent

$$\therefore X \cdot Y \cdot Z = X \cdot Z \cdot Y$$

∴ an equivalent circuit is

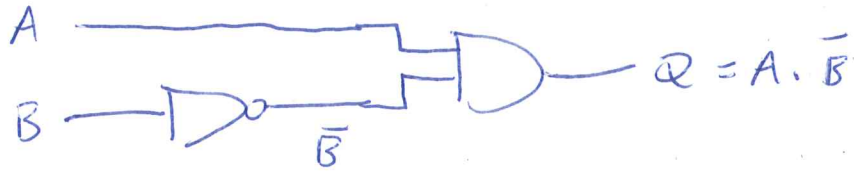

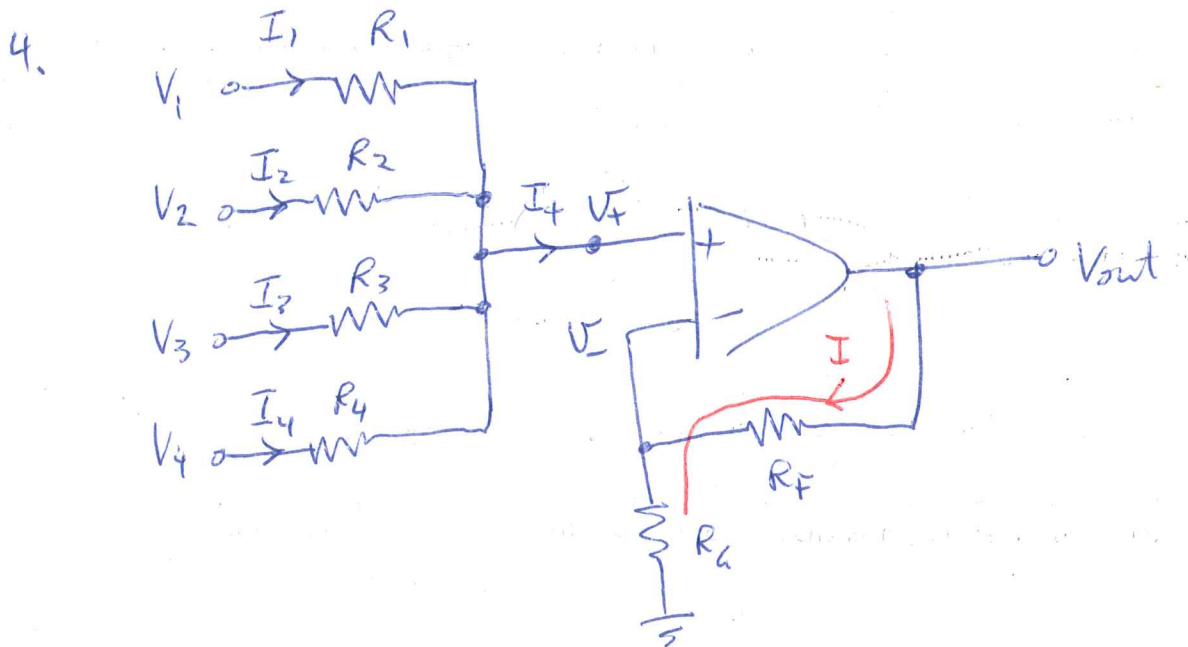Note that input C has no effect whatsoever on the output Q.



(a) start by finding V_-

$$V_{out} - I R_F - I R_G = 0$$

$$\therefore I = \frac{V_{out}}{R_F + R_G} \quad (1)$$

$$V_- = I R_G = V_{out} \frac{R_G}{R_F + R_G} \quad (2)$$

by Golden rule⁽²⁾, know

$$V_- = V_+ = V_{out} \frac{R_G}{R_F + R_G}$$

Find I_1 : $V_1 - I_1 R_1 = V_-$

$$\therefore I_1 = \frac{V_1 - V_-}{R_1} = \frac{1}{R_1} \left(V_1 - V_{out} \frac{R_G}{R_F + R_G} \right) \quad (1)$$

In the same way

$$I_j = \frac{1}{R_j} \left[V_j - V_{out} \frac{R_G}{R_F + R_G} \right]$$

where $j = 1, 2, 3, 4$.

By jcn rule $I_1 + I_2 + I_3 + I_4 = I_+$ (1)

but Golden Rule #1 says $I_+ = 0$.

$$\therefore \sum_j I_j = 0$$

$$\therefore \sum_j \frac{1}{R_j} \left[V_j - V_{out} \frac{R_G}{R_F + R_G} \right] = 0 \quad (1)$$

distribute the sum

$$\sum_j \frac{V_j}{R_j} - V_{out} \frac{R_G}{R_F + R_G} \sum_j \frac{1}{R_j} = 0$$

Solve for V_{out}

$$V_{out} = \frac{R_F + R_G}{R_G} \frac{\sum_j \frac{V_j}{R_j}}{\sum_j \frac{1}{R_j}}$$

so finally:

$$V_{out} = \left(1 + \frac{R_F}{R_G}\right) \left[\sum_{j=1}^4 \frac{1}{R_j}\right]^{-1} \sum_{j=1}^4 \frac{V_j}{R_j} \quad (1)$$

(b) Take $R_1 = 10 \text{ k}\Omega$
 $R_2 = 5 \text{ k}\Omega$
 $R_3 = 2.5 \text{ k}\Omega$
 $R_4 = 1.25 \text{ k}\Omega$ } $\left[\sum_j \frac{1}{R_j}\right]^{-1} = \frac{2}{3} \text{ k}\Omega$

$R_F = 20 \text{ k}\Omega$
 $R_G = 10 \text{ k}\Omega$ } $1 + \frac{R_F}{R_G} = 3$

$$\therefore V_{out} = (2 \text{ k}\Omega) \sum_{j=1}^4 \frac{V_j}{R_j}$$

V_4	V_3	V_{R2}	V_{R1}	$\sum \frac{V_j}{R_j}$	V_{out}
0	0	0	0	0	0
0	0	0	5	$0.5 \frac{V}{k\Omega}$	1 V
0	0	5	0	1	2
0	0	5	5	1.5	3
0	5	0	0	2	4
0	5	0	5	2.5	5
0	5	5	0	3	6
0	5	5	5	3.5	7
5	0	0	0	4	8
5	0	0	5	4.5	9
5	0	5	0	5	10
5	0	5	5	5.5	11
5	0	5	0	6	12
5	5	0	0	6.5	13
5	5	0	5	7	14
5	5	5	0	$7.5 \frac{V}{k\Omega}$	15 V
5	5	5	5		

2

out of 8