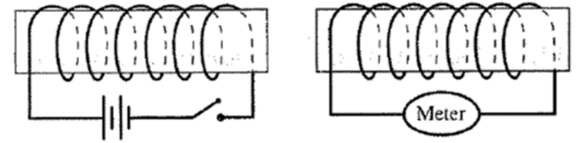


(2pts) 1.

- a. Just after the switch on the left coil is closed, does current flow right to left or left to right through the current meter of the right coil? Or is the current zero?



- b. Long after the switch on the left coil is closed, does current flow right to left or left to right through the current meter of the right coil? Or is the current zero?