
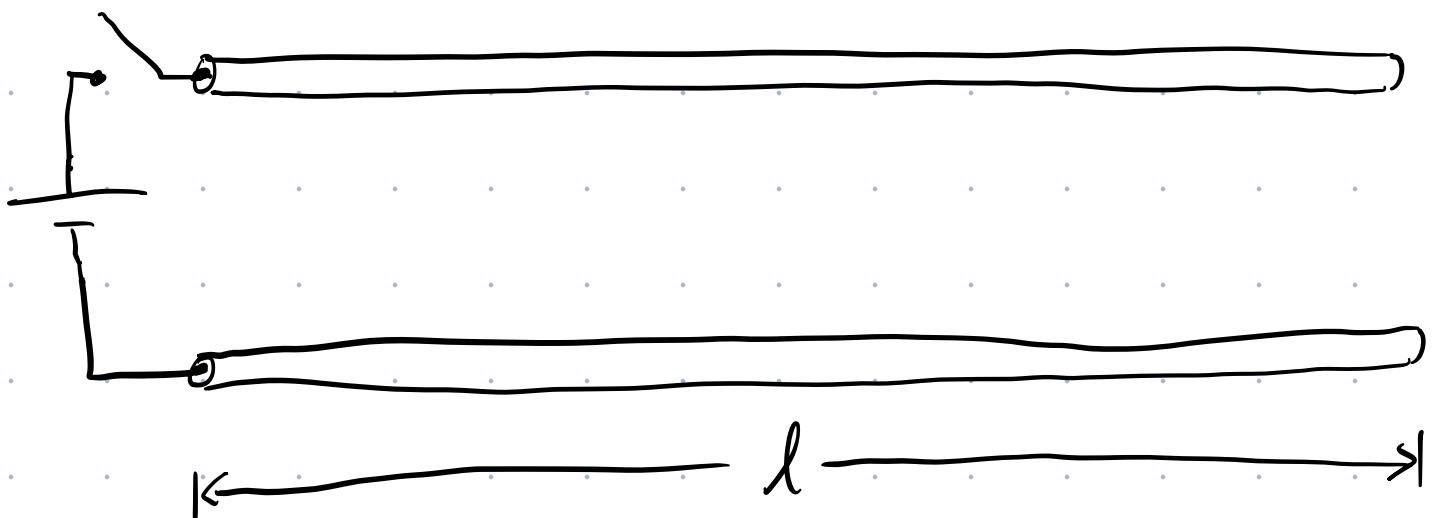



Last Time: Transmission lines.

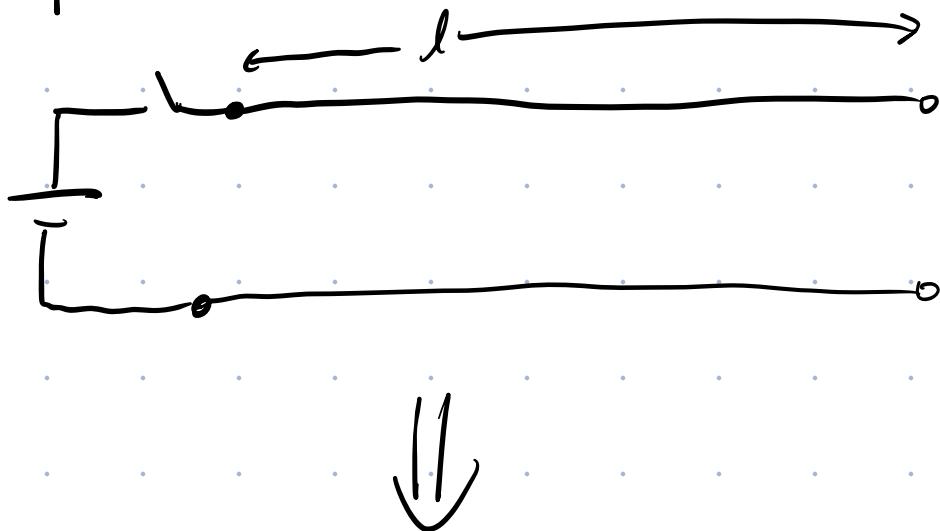Pair of parallel conductors. All transmission lines have a capacitance per unit length  $C_e$  ( $[C_e] = F/m$ )  
{ an inductance per unit length  $L_e$  ( $[L_e] = H/m$ )




Model parallel wires as LC circuit.



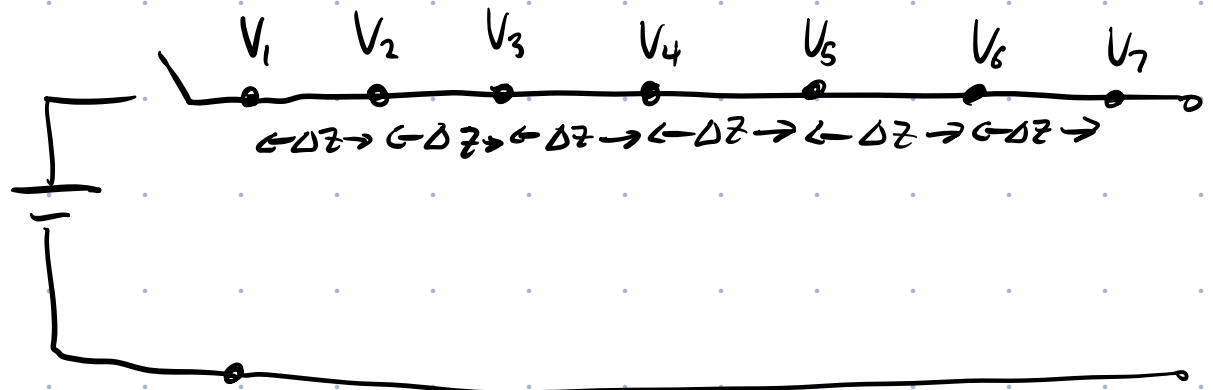


Expect  $V_1 > V_2 > V_3 \dots > V_7$  a short time after switch is closed. Simple LC circuit model fails for long trans. lines b/c can only have one volt. diff. across L.

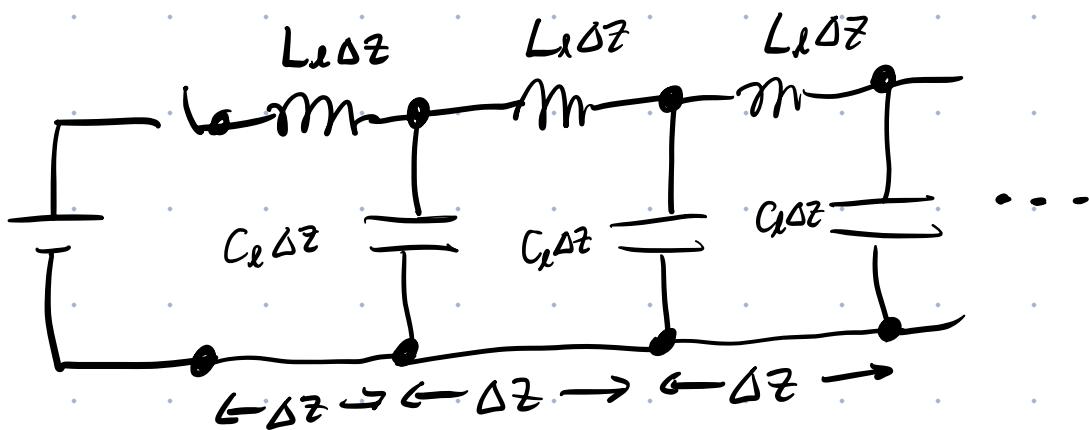Model long trans. line using a distributed LC network.



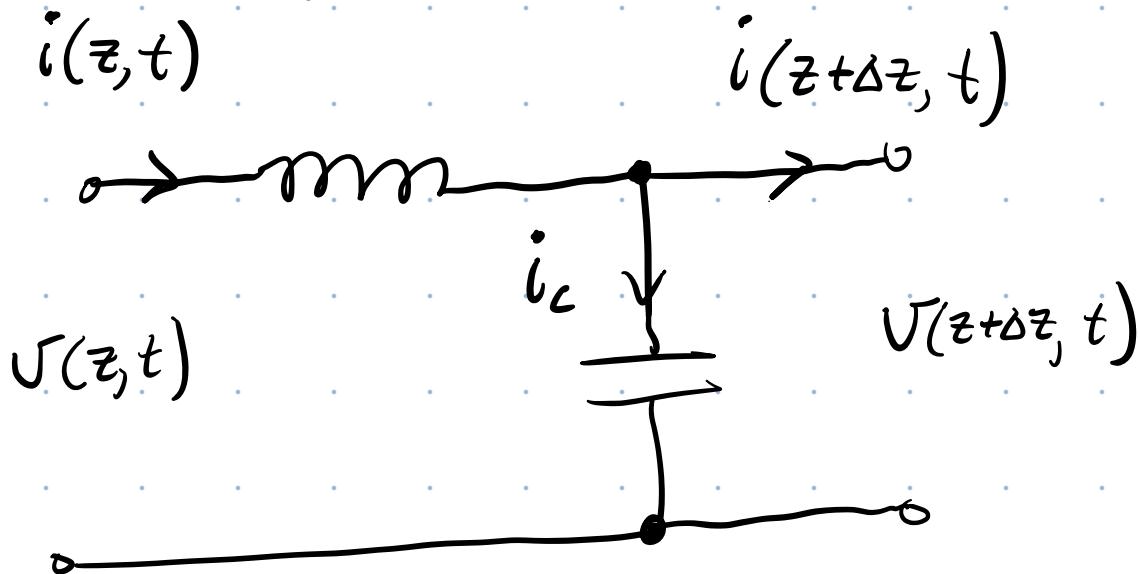Consider a single branch of this circuit:



Kirchhoff Loop Rule :

$$V(z, t) - L_L \Delta z \frac{\partial i(z, t)}{\partial t} = V(z + \Delta z, t)$$

$$\therefore \frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} = -L_L \frac{\partial i(z, t)}{\partial t}$$

In limit  $\Delta z \rightarrow 0$ , we have

$$\boxed{\frac{\partial V(z, t)}{\partial z} = -L_L \frac{\partial i(z, t)}{\partial t}} \quad \textcircled{1}$$

## Kirchhoff Jon Rule:

$$V(z+\Delta z, t)$$

$$\boxed{i(z, t) = i_c + i(z+\Delta z, t)}$$

$$C = \frac{q}{V_C} \Rightarrow q = CV_C \Rightarrow i_c = \frac{dq}{dt} = C \frac{dV_C}{dt}$$

$C_e \Delta z$

$$\rightarrow i(z, t) = C_e \Delta z \frac{\partial V(z+\Delta z, t)}{\partial t} + i(z+\Delta z, t)$$

$$\therefore \frac{i(z+\Delta z, t) - i(z, t)}{\Delta z} = -C_e \frac{\partial V(z+\Delta z, t)}{\partial t}$$

limit  $\Delta z \rightarrow 0$ :

$$\boxed{\frac{\partial i(z, t)}{\partial z} = -C_e \frac{\partial V(z, t)}{\partial t}}$$

(z)

To make further progress, we will assume that  $v$  &  $i$  are harmonic (sinusoidal) signals.

$$v(z, t) = V(z) e^{j\omega t}$$

$$i(z, t) = \bar{I}(z) e^{j\omega t}$$



position-dependent amplitudes.

From ①

$$\frac{\partial}{\partial z} \left[ V(z) e^{j\omega t} \right] = -L_L \frac{\partial}{\partial t} \left[ \bar{I}(z) e^{j\omega t} \right]$$

$$\cancel{\frac{\partial V(z)}{\partial z}} e^{j\omega t} = -j\omega L_L \bar{I}(z) e^{j\omega t}$$

#

$$\therefore \cancel{\frac{\partial V(z)}{\partial z}} = \boxed{-j\omega L_L \bar{I}(z)}$$

Let's take second derivative of  $V$  w.r.t.  $z$

$$\frac{d^2 V(z)}{dz^2} = -j\omega L_L \boxed{\frac{d \bar{I}(z)}{dz}}$$

From ②

$$\frac{\partial}{\partial z} \left[ I(z) e^{j\omega t} \right] = -C_L \frac{\partial}{\partial t} \left[ V(z) e^{j\omega t} \right]$$

$$\therefore \frac{d \bar{I}(z)}{dz} = -j\omega C_L V(z)$$

$$\therefore \frac{d^2 \bar{I}(z)}{dz^2} = -j\omega C_L \frac{d V(z)}{dz}$$

$$\therefore \frac{d^2 V(z)}{dz^2} = -\omega^2 L_L C_L V(z)$$

The  
Wave

$$\therefore \frac{d^2 I(z)}{dz^2} = -\omega^2 L_L C_L I(z)$$

Eq'n's

General sol'n to voltage eq'n is:

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

Check:

$$\frac{dV(z)}{dz} = -j\beta V_+ e^{-j\beta z} + j\beta V_- e^{j\beta z}$$

✗

$$\frac{d^2V(z)}{dz^2} = -\beta^2 V_+ e^{-j\beta z} - \beta^2 V_- e^{j\beta z}$$

$$= -\beta^2 \left[ V_+ e^{-j\beta z} + V_- e^{j\beta z} \right]$$

$\curvearrowright$   
 $V(z)$

$$\therefore \frac{d^2V(z)}{dz^2} = -\beta^2 V(z)$$

This is a solution to the wave eq'n for  $V(z)$  provided

$$\beta^2 = \omega^2 L_\ell C_\ell \Rightarrow \boxed{\beta = \omega \sqrt{L_\ell C_\ell}}$$


Full time-dependent voltage is  $\therefore$ :

$$V(z, t) = V(z) e^{j\omega t}$$

$$= \left[ V_+ e^{-j\beta z} + V_- e^{j\beta z} \right] e^{j\omega t}$$

$$\therefore v(z, t) = V_+ e^{j(\omega t - \beta z)} + V_- e^{j(\omega t + \beta z)}$$

Consider  $\sin(\omega t - \beta z)$

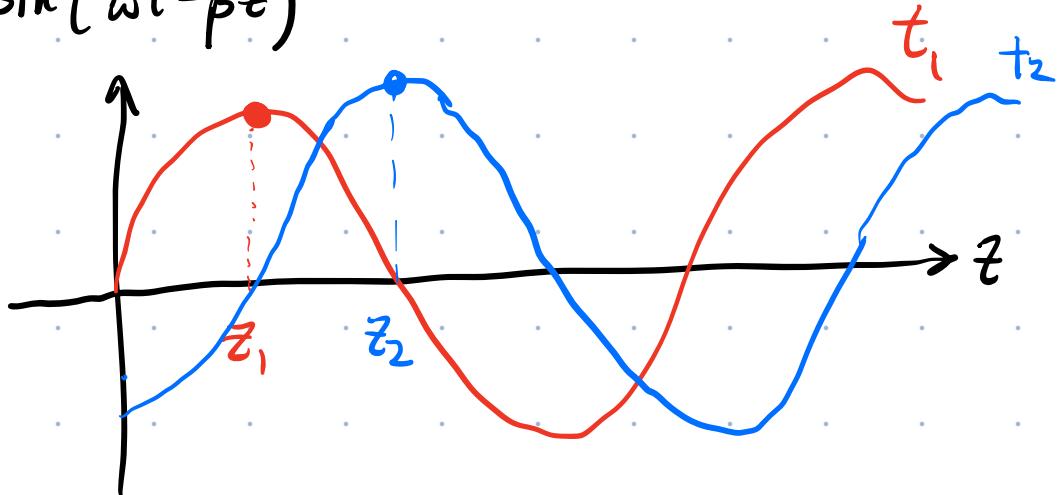

Require:  $\sin(\omega t_1 - \beta z_1) = \sin(\omega t_2 - \beta z_2)$

$$\therefore \omega t_1 - \beta z_1 = \omega t_2 - \beta z_2$$

$$\underbrace{\omega(t_2 - t_1)}_{\Delta t} = \underbrace{\beta(z_2 - z_1)}_{\Delta z}$$

$$\therefore \frac{\omega}{\beta} = \underbrace{\frac{\Delta z}{\Delta t}}_S$$

$S$  the speed of the signal.

$$S = \frac{\omega}{\beta} \quad \text{know } \beta = \omega \sqrt{L_C C_L}$$

$$S = \frac{\omega^1}{\omega \sqrt{L_e C_e}}$$

$$S = \frac{1}{\sqrt{L_e C_e}}$$

Last class, for a parallel pair of conductors of radius  $a$  separated by dist.  $d$ , we had:

$$C_e = \frac{\pi \epsilon_0}{\ln\left(\frac{d}{a}\right)} \quad L_e = \frac{\mu_0}{\pi} \ln\left(\frac{d}{a}\right)$$

$$\therefore L_e C_e = \mu_0 \epsilon_0 = \frac{1}{c^2}$$

$$\therefore S = c$$

$\therefore$  our signal on the transmission line travels at the speed of light.

In general, if our parallel wires were surrounded by a dielectric and/or a material w/ a relative permeability  $\mu_r$ , then  $C_e \rightarrow \epsilon_r C_e$

$$L_e \rightarrow \mu_r L_e$$


Then  $S$  would become

$$S = \frac{C}{\sqrt{\mu_r \epsilon_r}} = \frac{C}{n} \quad \text{where } n \text{ is refractive index.}$$

If we analyzed the  $\omega t + \beta z$  term in  $V(z, t)$  sol'n, we would find the same result for  $S$ , but w/ opposite sign :  $S = -\frac{1}{\sqrt{\mu_r \epsilon_r}} = -c$ .

$V_+ e^{j(\omega t - \beta z)}$  : forward travelling wave.

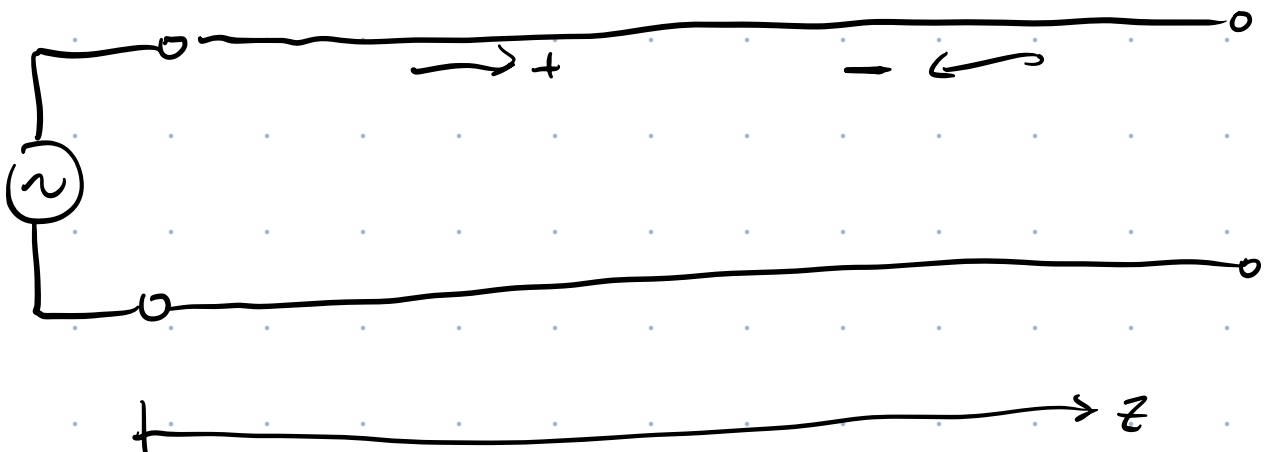$V_- e^{j(\omega t + \beta z)}$  : backwards travelling wave.



Backwards travelling waves are due to reflections from the opposite end of the transmission.

What is the physical interpretation of  $\beta$ ?

$$S = \frac{\omega}{\beta} = \lambda f$$



$$\frac{2\pi f}{\beta} = \lambda f \Rightarrow \beta = \frac{2\pi}{\lambda}$$

Called wave number or propagation constant.

Return to eq'n's # 1. Both expressions for

$$\frac{dV(z)}{dz} \quad \{ \text{ must be equal.}$$

$$-\cancel{j\beta} V_+ e^{-j\beta z} + \cancel{j\beta} V_- e^{j\beta z} = -\cancel{j\omega L_L} I(z)$$

Solve for  $I(z)$ :

$$I(z) \leftarrow \frac{\beta \left[ -V_+ e^{-j\beta z} + V_- e^{j\beta z} \right]}{-\omega L_L}$$

$$\therefore I(z) = \frac{\omega \sqrt{L_c C_d}}{\sqrt{L_d}} \left[ V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

$$\therefore I(z) = \sqrt{\frac{C_d}{L_d}} \left[ V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

↑      ↴      ↴  
 units A      must have      units V  
 units of  $\frac{1}{\Omega}$ .

Define  $\sqrt{\frac{L_d}{C_d}}$  as the "characteristic impedance"  
 of the transmission line.

$$Z_0 \equiv \sqrt{\frac{L_d}{C_d}}$$