

- Assignment #2 is on course website.

Last Time:

For a transmission line driven by a harmonic signal, the voltage & current amplitudes along the length of the line are given by:

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$


$$I(z) = \frac{1}{Z_0} [V_+ e^{-j\beta z} - V_- e^{j\beta z}]$$

$$\beta = \omega \sqrt{L_\ell C_\ell} \quad \text{prop. const. or wave number}$$

$$Z_0 = \sqrt{\frac{L_\ell}{C_\ell}} \quad \text{characteristic impedance}$$

In physics labs, coaxial transmission lines are designed such that $Z_0 = 50 \Omega$.

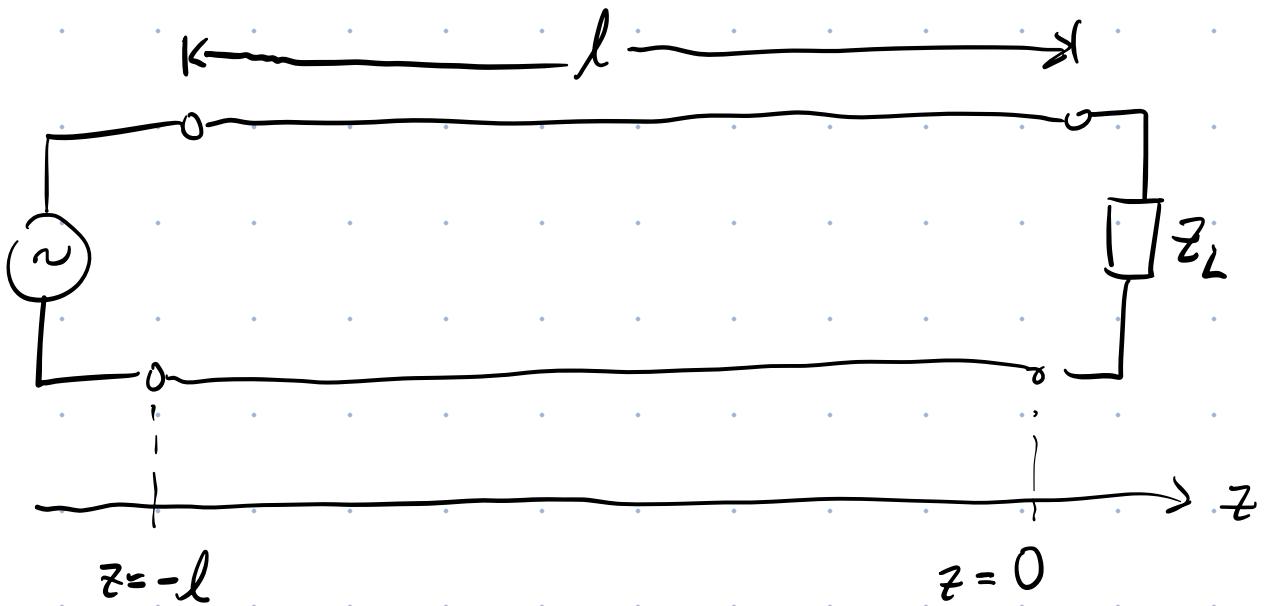Consider a trans. line of length l terminated by a "load" impedance Z_L at its end.



With i 's choice of coord. sys., the voltage & current amplitudes at the position of Z_L ($z=0$) are given by:

$$V(0) = V_+ + V_-$$

$$I(0) = \frac{1}{Z_0} [V_+ - V_-]$$

The ratio $\frac{V(0)}{I(0)}$ must be equal to the load impedance Z_L at $z=0$.

$$\frac{V(0)}{I(0)} = Z_L = Z_0 \left[\frac{V_+ + V_-}{V_+ - V_-} \right]$$

solve for V_- .

reflection coefficient
 Γ

$$\text{Find } V_- = V_+ \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right)$$

amp. of
backwards travelling waves
amp. of forward travelling waves

$$\boxed{\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

$$V_- = \Gamma V_+$$


Special Cases:

① $Z_L = 0$ (short circuit)



$$\Gamma = \frac{0 - Z_0}{0 + Z_0} = -1$$


perfect reflection
($|\Gamma| = 1$), but the reflected signal is inverted relative to incident signal.

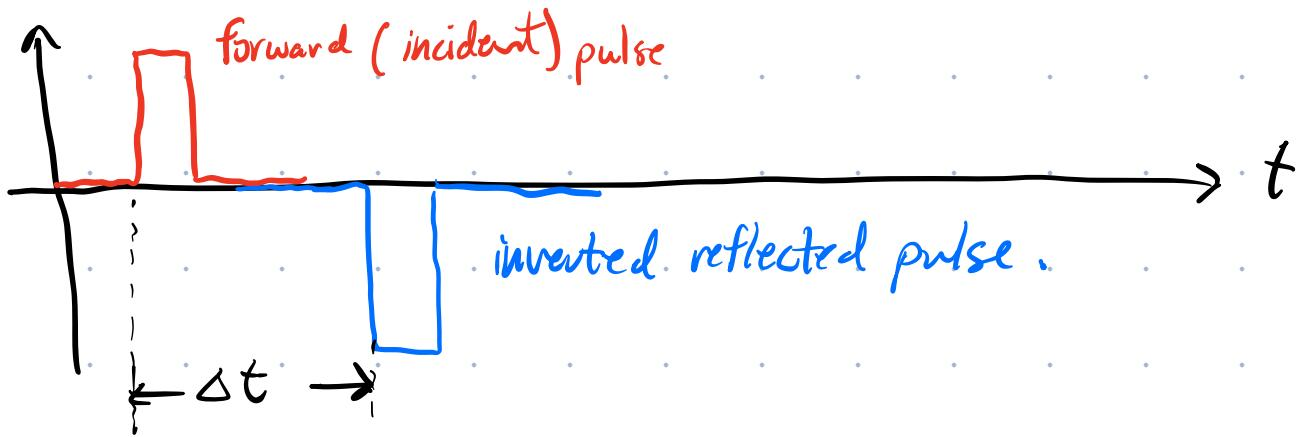


$$\Delta t = \frac{2l}{s} \quad \text{propagation speed.}$$

Time for pulse to travel length of transmission line and back again.

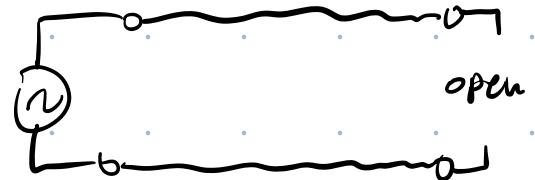(2) $Z_L \rightarrow \infty$ (open circuit)


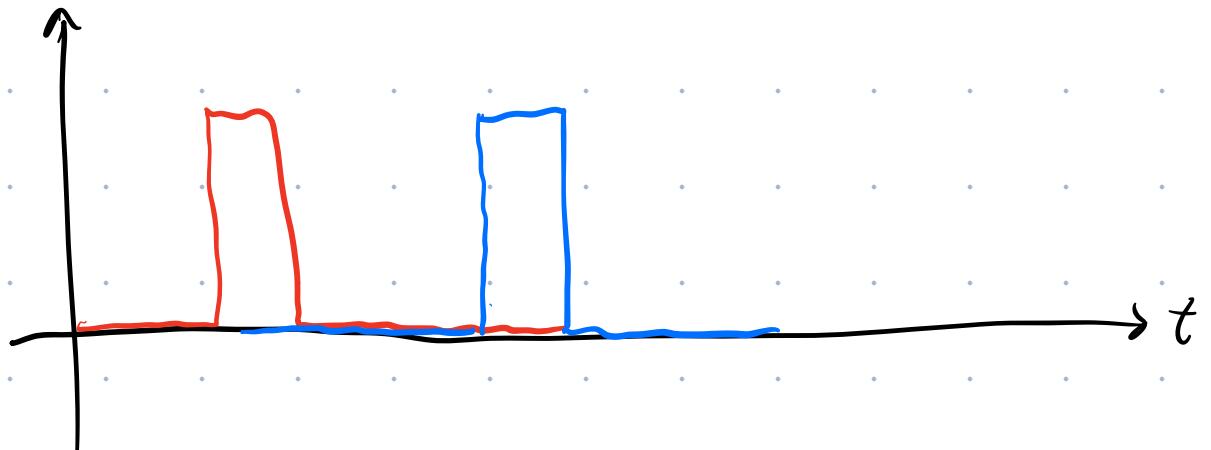
$$R = \frac{\infty - Z_0}{\infty + Z_0} = +1 \quad \begin{matrix} \text{perfect reflection} \\ \text{w/o inversion.} \end{matrix}$$



$$\textcircled{3} \quad Z_L = Z_0 \quad \Gamma = \frac{Z_0 - Z_L}{Z_0 + Z_L} = 0$$

This is called impedance matching.

We usually desire to achieve $Z_L = Z_0$.

no reflection. All incident signal power is absorbed by the load impedance Z_L .

When are transmission line effects important and when can they be ignored?

$$c = \lambda f \quad \therefore \quad \lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{10 \times 10^3 \text{ 1/s}}$$

$$= 3 \times 10^4 \text{ m}$$

$$= 30 \text{ km!}$$

We will find that transmission effects are important when the wavelength of the signal is comparable or shorter than the length l of the trans. line.

$$f = 3 \text{ GHz} \quad \lambda = \frac{3 \times 10^8 \text{ m/s}}{3 \times 10^9 \text{ 1/s}}$$

$$= 0.1 \text{ m} = 10 \text{ cm}$$

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$\beta = \frac{2\pi}{\lambda} = \omega \sqrt{L_\ell C_\ell}$$

The coaxial cables used in the lab are called RG-58 & designed s.t.

$$\left. \begin{array}{l} C_\ell = 80 \text{ pF/m} \\ L_\ell = 0.20 \mu\text{H/m} \end{array} \right\} Z_0 = \sqrt{\frac{L_\ell}{C_\ell}} = 50 \Omega$$

$$\beta = \omega \sqrt{L_\ell C_\ell} \quad \text{let's take as an example } \omega = 2\pi(10 \text{ kHz}) \\ = 2.5 \times 10^{-4} \text{ m}^{-1}$$

If we take $\lambda \approx 1 \text{ m}$

$$\beta z = 2.5 \times 10^{-4} \ll 1$$

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$V(z) \approx V_+ + V_- \quad (\text{const}).$$

likewise, for current, would find $I(z) \approx \frac{1}{Z_0} [V_+ - V_-]$
 (const) .

When $\beta z \ll 1$, current & volt. along transmission are constant and we can safely ignore trans. line effects.

$$\text{Recall } \beta = \frac{2\pi}{\lambda} \Rightarrow \lambda = \frac{2\pi}{\beta}$$

using $\beta = 2.5 \times 10^{-4} \text{ m}^{-1}$, we get $\lambda = 25 \text{ km}!$

When λ much larger than trans. line length l , ignore these effects.

If, on the other hand, we take

$$\omega = 2\pi (3 \text{ GHz})$$

$$\beta = \omega \sqrt{\epsilon \mu \epsilon_0} \approx 75 \text{ m}^{-1}$$

In this case, for $z \approx 1 \text{ m}$, the product βz is not small.

Cannot approx $e^{\pm j\beta z}$ as 1.

$$\text{In fact, } e^{\pm j\beta z} = \cos \beta z \pm j \sin \beta z$$

We will instead find that the voltage & current osc. along the length of transmission line.

Impedance at an arbitrary position z along the transmission line.

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} [V_+ e^{-j\beta z} - V_- e^{j\beta z}]$$

at an arbitrary pos. z , the impedance is given by :

$$\overrightarrow{Z(z)} = \frac{\overrightarrow{V(z)}}{\overrightarrow{I(z)}} = Z_0 \frac{V_+ e^{-j\beta z} + V_- e^{j\beta z}}{V_+ e^{-j\beta z} - V_- e^{j\beta z}}$$

↑ impedance ↑ position

Recall that $V_- = \sqrt{V_+}$

$$Z(z) = Z_0 \frac{\cancel{V_+} (e^{-j\beta z} + \cancel{\sqrt{V_+}} e^{j\beta z})}{\cancel{V_+} (e^{-j\beta z} - \cancel{\sqrt{V_+}} e^{j\beta z})}$$

Red arrows indicate terms that cancel out.

$$\text{Sub in } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{j\beta z}}{e^{-j\beta z} - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{j\beta z}}$$

mult. by $\frac{Z_L + Z_0}{Z_L + Z_0}$

$$= Z_0 \frac{(Z_L + Z_0)e^{-j\beta z} + (Z_L - Z_0)e^{j\beta z}}{(Z_L + Z_0)e^{-j\beta z} - (Z_L - Z_0)e^{j\beta z}}$$

collect like terms of $Z_L \& Z_0$

$$Z(z) = Z_0 \frac{Z_L(e^{-j\beta z} + e^{j\beta z}) + Z_0(e^{-j\beta z} - e^{j\beta z})}{Z_L(e^{-j\beta z} - e^{j\beta z}) + Z_0(e^{-j\beta z} + e^{j\beta z})}$$

use the identities $e^{j\beta z} + e^{-j\beta z} = 2\cos\beta z$

$$e^{j\beta z} - e^{-j\beta z} = 2j\sin\beta z$$


$$\therefore Z(z) = Z_0 \frac{2Z_L \cos\beta z - 2jZ_0 \sin\beta z}{-2jZ_L \sin\beta z + 2Z_0 \cos\beta z}$$

mult. by $\frac{1}{\cos\beta z}$

$$\therefore \bar{Z}(z) = Z_0$$

$$\frac{Z_L - jZ_0 \tan \beta z}{Z_0 - jZ_L \tan \beta z}$$

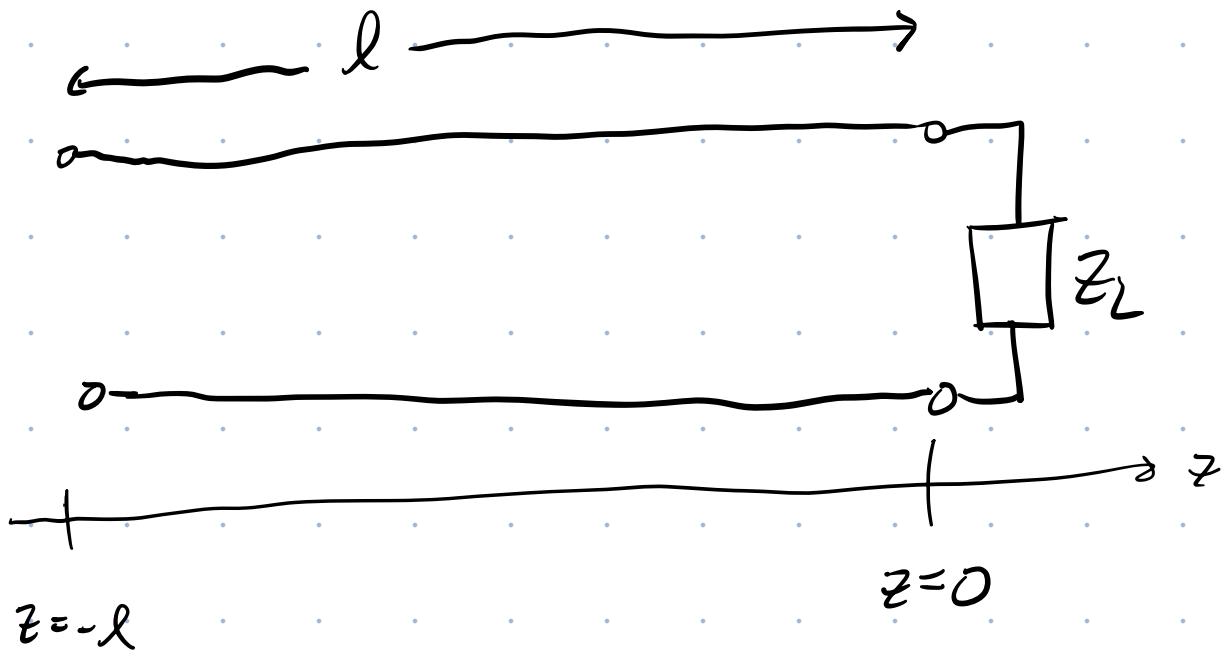Impedance
at any pos.
along trans.
line that has
been terminated
by Z_L .



To find the impedance looking into trans. line
from $z = -l$, sub in $z = -l$.

Recall that $\tan(-x) = -\tan x$

$$\Rightarrow \tan(-\beta l) = -\tan \beta l$$

Transmission line input impedance

$$Z_{in} = Z(-l) = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

Special cases

① $\beta l = n\pi$

Select l s.t. we satisfy

$$\beta l = n\pi \text{ where } n \text{ is integer}$$

$$\therefore \frac{2\pi}{\lambda} l = n\pi \Rightarrow l = n\left(\frac{\lambda}{2}\right)$$

Equivalent to selecting l to be an integer multiple of half wave lengths.

$$\Rightarrow \tan \beta l = \tan n\pi = 0.$$


$$Z_{in} = \cancel{Z_0} \frac{Z_L}{\cancel{Z_0}} = Z_L.$$

As if transmission line is not there

(as if Z_L is connected directly to signal source).

$$\textcircled{2} \quad \beta l = n' \left(\frac{\pi}{2} \right) \text{ where } n' \text{ is an } \underline{\text{odd}} \text{ integer}$$
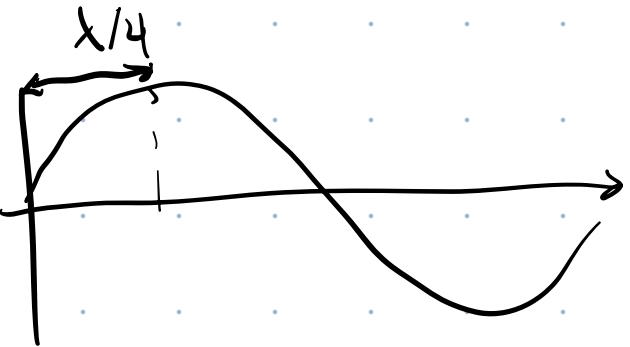
$$\frac{2\pi}{\lambda} l = n' \frac{\pi}{2} \Rightarrow l = n' \left(\frac{\lambda}{4} \right)$$



length is an odd mult. of quarter wavelengths.

$$\tan \beta l = \tan \left(n' \frac{\pi}{2} \right) \rightarrow \pm \infty$$

In this case, $Z_{in} \approx Z_0$

$$\frac{j Z_0 \tan \beta l}{j Z_L \tan \beta l} = \frac{Z_0^2}{Z_L}$$

In effect, we're transforming impedances from Z_L to $\frac{Z_0^2}{Z_L}$.

③ $Z_L = Z_0$ (impedance matching condition).

$$Z_{in} = Z_0$$

$$\frac{Z_0 + jZ_0 \tan \beta l}{Z_0 + jZ_0 \tan \beta l}$$

$$Z_{in} = Z_0$$

As if Z_0 has been connected directly to signal source.
Usually the desired situation.

Note that, in this case, $Z_{in} = Z_0$ regardless of the length l of the trans. line.