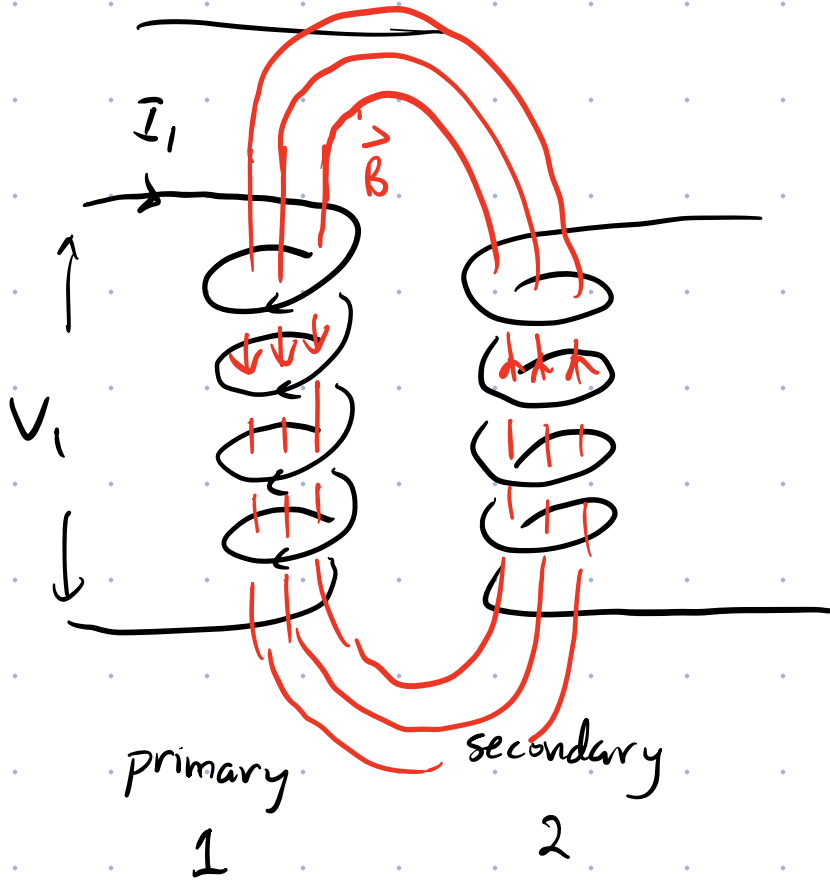


Transformers



Usually trans. windings are wrapped around a magnetic material (like iron).  
 $\Rightarrow$  All  $\vec{B}$  fields that pass through primary also pass through secondary.

$$\Phi_1 = \Phi_2 \quad \text{magnetic flux}$$

$$\equiv \Phi$$

Trans. works only for AC currents/voltages. b/c we need a changing magnetic flux to induce voltage/current in secondary.

Faraday's Law:  $V_1 = -N_1 \frac{d\Phi}{dt}$

$$V_2 = -N_2 \frac{d\Phi}{dt}$$

$N_1$ : no. of windings in primary

$N_2$ : no. of windings in secondary.

$$\therefore \frac{V_2}{V_1} = \frac{+N_2 \cancel{d\Phi/dt}}{+N_1 \cancel{d\Phi/dt}} \Rightarrow \boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1}}$$

$$\therefore V_2 = V_1 \frac{N_2}{N_1}$$

We can use a transformer to easily step up  $\left(\frac{N_2}{N_1} > 1\right)$  or step down  $\left(\frac{N_2}{N_1} < 1\right)$  the voltage @ secondary.

By conservation of energy

$$\left[ \begin{array}{l} V_1 I_1 = V_2 I_2 \\ (P_1 = P_2) \end{array} \right. \rightarrow \frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\Rightarrow \boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1} \quad \frac{I_2}{I_1} = \frac{N_1}{N_2} \quad \frac{P_2}{P_1} = 1}$$

# Impedance

Primary  $Z_1 = \frac{V_1}{I_1}$

Secondary  $Z_2 = \frac{V_2}{I_2}$


$$\frac{Z_2}{Z_1} = \frac{V_2}{I_2} \frac{I_1}{V_1}$$

$$= \left( \frac{V_2}{V_1} \right) \left( \frac{I_1}{I_2} \right) = \left( \frac{N_2}{N_1} \right)^2$$

$$\frac{Z_2}{Z_1} = \left( \frac{N_2}{N_1} \right)^2$$

## Practical Applications

### 1. Impedance Matching.

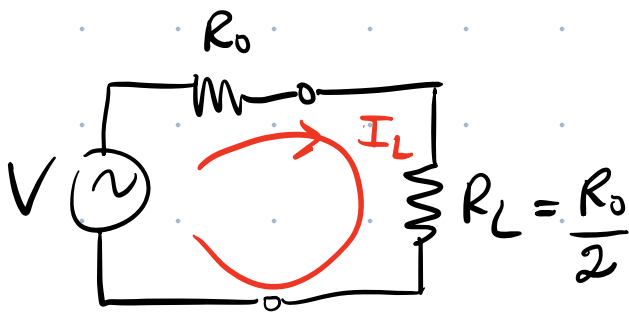

$$I_L = \frac{V}{R_0 + R_L} = \frac{V}{3R_0/2}$$

$$I_L = \frac{2V}{3R_0}$$

$$P_L = I_L^2 R_L = \frac{4 V^2}{9 R_0^2} \left( \frac{R_0}{2} \right) = \frac{2}{9} \frac{V^2}{R_0}$$

Source power  $P_S = VI_L = \frac{2V^2}{3R_0}$


Power Trans.

Efficiency

$$\eta = \frac{P_L}{P_S} = \frac{\frac{2}{9} \frac{V^2}{R_0}}{\frac{2}{3} \frac{V^2}{R_0}} = \frac{2}{9} \frac{3}{2} = \frac{1}{3}$$

In this example  $\frac{1}{3}$  of system power is delivered to  $R_L$  &  $\frac{2}{3}$  is lost to  $R_0$  (output resistance of signal gen.).

Next, consider

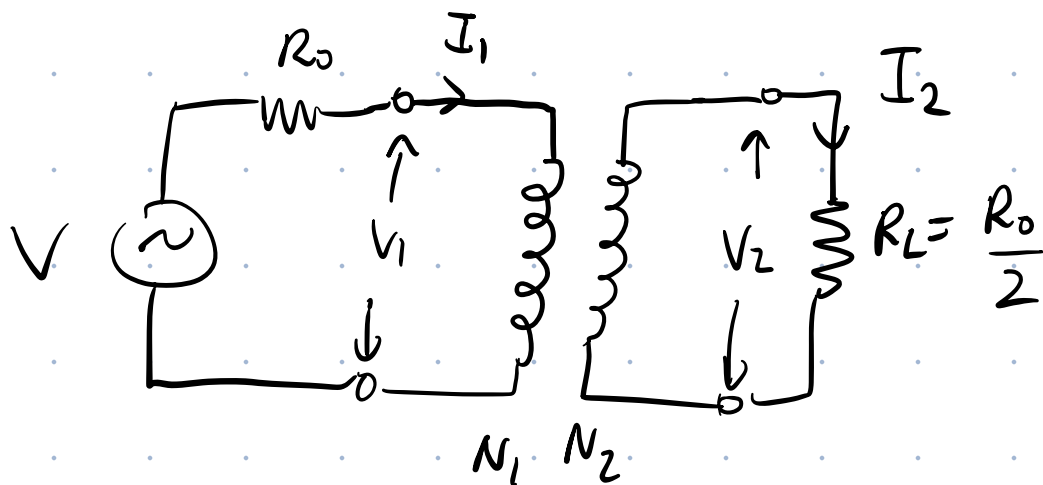

$$\text{choose } \left(\frac{N_2}{N_1}\right)^2 = \frac{1}{2}$$

$$\text{Know: } V_2 = I_2 R_L$$

$$\therefore V_1 \left(\frac{N_2}{N_1}\right) = I_1 \left(\frac{N_1}{N_2}\right) R_L$$

$$\therefore V_1 = I_1 \left(\frac{N_1}{N_2}\right)^2 R_L$$



$$= I_1 \left[ \left(\frac{N_1}{N_2}\right)^2 R_L \right]$$



$$R_{\text{eff}} = 2 \left(\frac{R_0}{2}\right) = R_0$$

We have used the transformer to transform the load resistance  $R_L$  from  $\frac{R_0}{2}$  to  $R_{\text{eff}} = R_0$  (impedance matching).

Equiv. circuit.

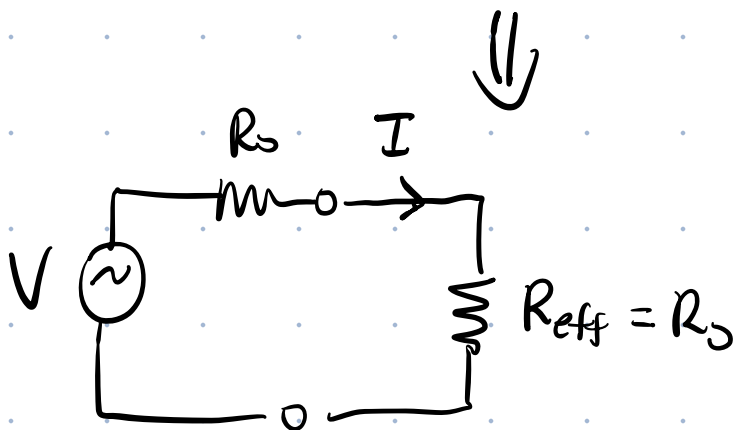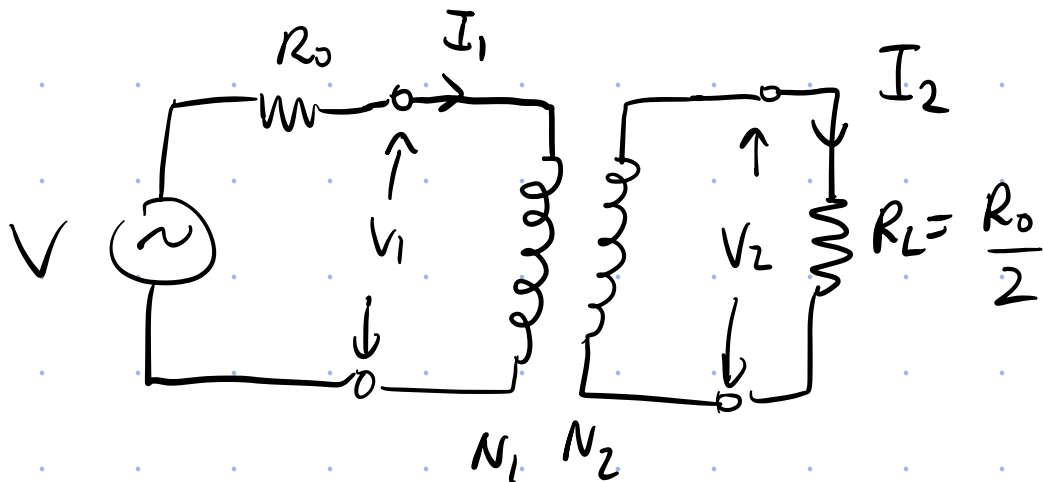

current in equiv. circuit is  $I = \frac{V}{2R_0}$

$$P_S = VI = \frac{V^2}{2R_0}$$

$$P_L = I_2^2 R_L = \left( I_1 \frac{N_1}{N_2} \right)^2 \frac{R_0}{2}$$

same!

Need to find  $I_1$ . Start w/.

$$V - I_1 R_0 = V_1$$

$$V = I_1 R_0 + I_1 \left( \frac{N_1}{N_2} \right)^2 R_L$$

$$\text{Solve for } I_1 = \frac{V}{R_0 + \left( \frac{N_1}{N_2} \right)^2 R_L} = \frac{V}{R_0 + R_0} = \frac{V}{2R_0}$$

$$\begin{aligned} \therefore P_L &= \left( \frac{V}{2R_0} \cdot \frac{N_1}{N_2} \right)^2 \frac{R_0}{2} = \frac{V^2}{4R_0^2} \cdot \frac{R_0}{2} \\ &= \frac{V^2}{4R_0} \end{aligned}$$

$\therefore$  The new power transfer efficiency is:

$$\eta = \frac{P_L}{P_S} = \frac{V^2/4R_0}{V^2/2R_0} = \frac{1}{2} \quad \checkmark$$

Note that we could have analyzed the simpler equiv. circuit to find the same result.

$$P_s = VI = \frac{V^2}{2R_0}$$

$$P_L = I^2 R_{\text{eff}} = \left( \frac{V}{2R_0} \right)^2 R_0 = \frac{V^2}{4R_0}$$

$$\therefore \eta = \frac{P_s}{P_L} = \frac{1}{2} \quad \text{same as before!}$$

For a source w/ output resistance  $R_0$ , get a max.  $\eta$  of  $1/2$  when  $R_L = R_0$ .


Dissipated at least 50% of power in output resistance of signal generator.

---




Question: Why do hydro lines deliver power at high voltage & low current?

Consider the following circuit.

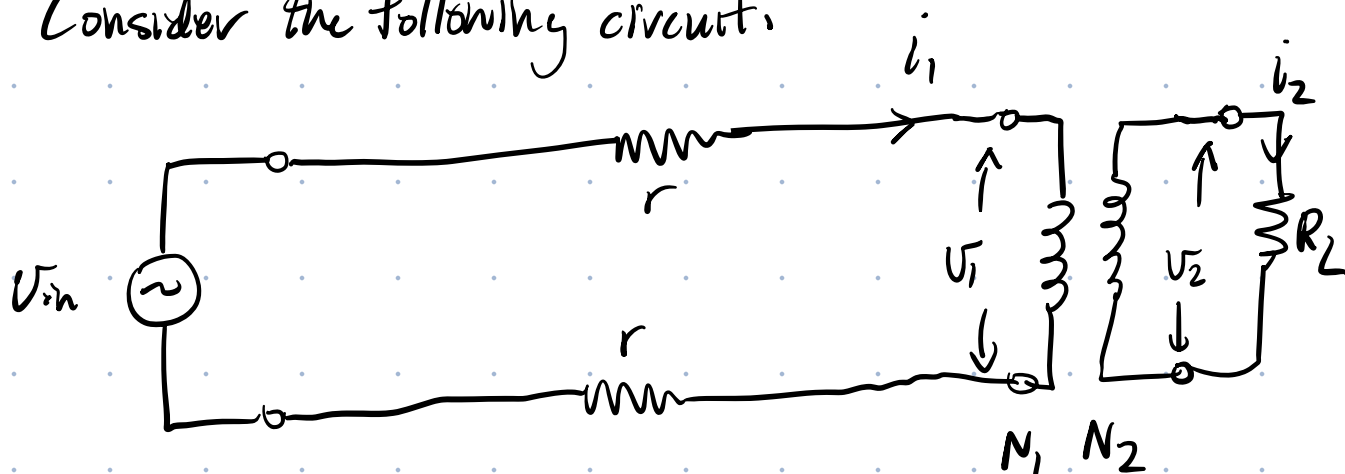

Small resistance assoc. with trans. cables.

equiv. circuit

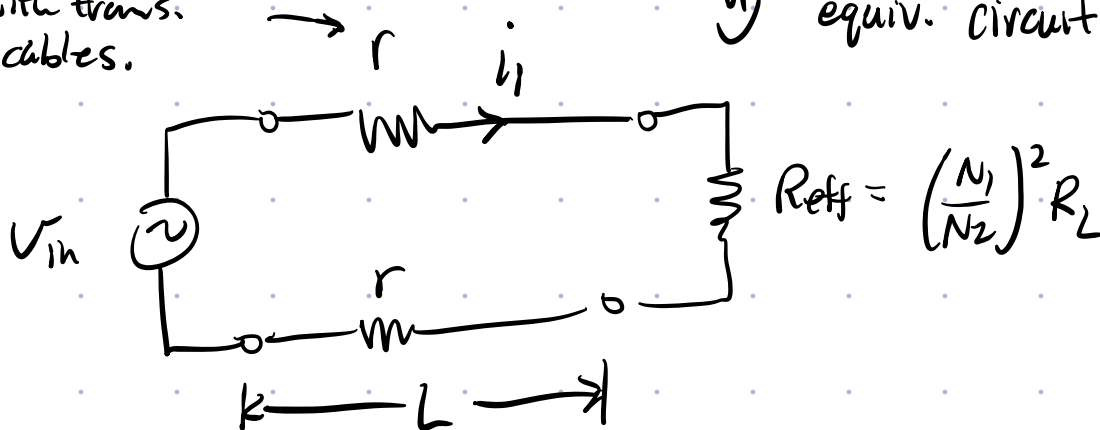

Keep  $r$  &  $R_L$  fixed.

$$r = 0.5 \Omega$$

$$R_L = 9 \Omega$$

Want to deliver power to  $R_L$  while minimizing the power dissipated by trans. line.

What about trans. line effects?

For power delivered to homes  $f = 60 \text{ Hz}$ .

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{60 \text{ 1/s}} = 0.5 \times 10^7 \text{ m} \\ = 5000 \text{ km!}$$

Assume that  $L \ll \lambda$

$$i_1 = \frac{V_{in}}{R_{eff} + 2r} = \frac{V_{in}}{\left(\frac{N_1}{N_2}\right)^2 R_L + 2r}$$

Power Provided  
by sys.

$$P_{sys} = V_{in} i_1 = \frac{V_{in}^2}{\left(\frac{N_1}{N_2}\right)^2 R_L + 2r}$$

Power delivered  
to  $R_L$

$$P_L = i_2^2 R_L = i_1^2 \left(\frac{N_1}{N_2}\right)^2 R_L$$

Power dissipated  
by trans. line

$$P_r = 2 i_1^2 r$$

Plan is to vary  $V_{in} \uparrow \frac{N_1}{N_2}$  while keeping

$$P_{sys} = V_{in} i_1 = \text{const.}$$

Eg.  $V_{in} = 1000V$   $\frac{N_1}{N_2} = 1$

In this case,  $i_1 = \frac{1000V}{(1)^2 9\Omega + 2(0.5\Omega)} = 100A.$

Low volt. (relatively)  $\uparrow$  high current case.

$$P_{sys} = V_{in} i_1 = 100 \text{ kW}$$

$$P_L = (100A)^2 (1)^2 9\Omega = 90 \text{ kW}$$

$$P_r = 2(100A)^2 (0.5\Omega) = 10 \text{ kW}$$

In this case,  $\frac{P_r}{P_{\text{sys}}} = \frac{10}{100} \Rightarrow 10\%$  power loss to dissipation by trans. line.

Let's now consider the high voltage, low current case. Keep  $P_{\text{sys}} = 100 \text{ kW}$ , but set  $V_{\text{in}} = 100 \text{ kV}$

$$\therefore i_1 = \frac{P_{\text{sys}}}{V_{\text{in}}} = \frac{100 \text{ kW}}{100 \text{ kV}} = 1 \text{ A}$$

Figure out  $\frac{N_1}{N_2}$  :  $i_1 = \frac{V_{\text{in}}}{\left(\frac{N_1}{N_2}\right)^2 R_L + 2r}$

$$\therefore \left(\frac{N_1}{N_2}\right) = \sqrt{\frac{\frac{V_{\text{in}}}{i_1} - 2r}{R_L}} = 105.4087, \dots$$

$$P_L = i_1^2 \left( \frac{N_1}{N_2} \right)^2 R_L = 99.999 \text{ kW}$$

$$P_r = 2i_1^2 r = 1 \text{ W} = 0.001 \text{ kW}$$

$$\frac{P_r}{P_{\text{sys}}} = \frac{1}{10^5} \Rightarrow 0.001 \%$$

power dissipated by cables.