

## Review of Complex Nos. & their Physical Meaning

Recall that we can express any complex number in two different ways:

① Mag. & Phase:

$$Z = |Z| e^{j\theta} \quad (j \equiv \sqrt{-1})$$

$$= |Z| (\cos\theta + j \sin\theta)$$

Euler's Eq'n  $e^{\pm j\theta} = \cos\theta \pm j \sin\theta$

② real & imaginary components

$$Z = \underbrace{x}_{\text{real component}} + j \underbrace{y}_{\text{imaginary component}}$$

Can easily switch between the two representations:

$$\underline{x} + j \underline{y} = \underline{|Z|} (\underline{\cos\theta} + j \underline{\sin\theta})$$

Equation real & imaginary components on left & right gives:

$$x = |z| \cos \phi$$

$$y = |z| \sin \phi$$

$$|z| = \sqrt{x^2 + y^2}$$


$$\frac{y}{x} = \tan \phi$$

$$\phi = \tan^{-1} \left( \frac{y}{x} \right)$$

$$\text{If } \operatorname{Im}[z] = 0, \quad y = 0, \quad \tan \phi = 0$$

$$x \neq 0$$

$$\rightarrow \phi = 0$$

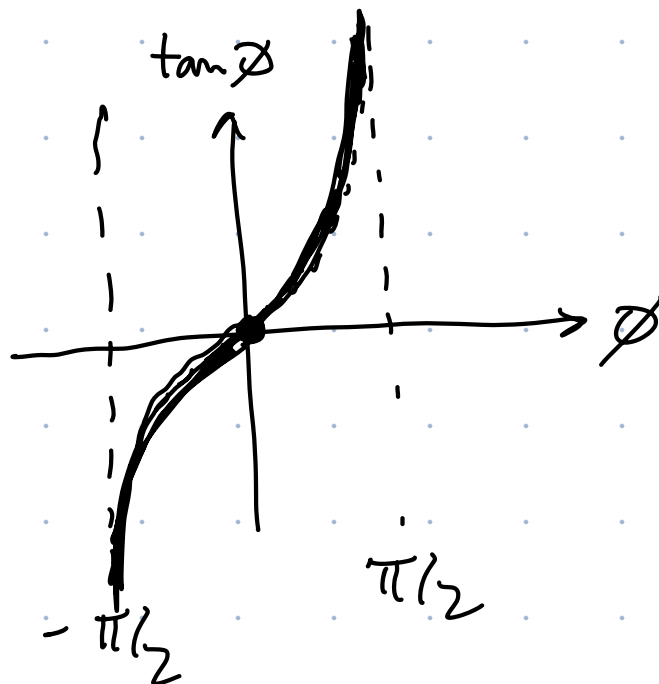

A purely real number w/  $y = \text{Im}[z] = 0$   
has a phase of zero.

If  $y$  is large and  $\frac{y}{x} > 0$  (positive).

then  $\phi \rightarrow +\pi/2$


If  $y$  is large and  $\frac{y}{x} < 0$  (negative)

then  $\phi \rightarrow -\pi/2$

The relative size and sign of  $x, y$  determine the phase  $\phi$ . Real nos, w/  $y = 0$ , have  $\phi = 0$ .


Alternatively, a nonzero imaginary component  $y$  implies a nonzero phase.

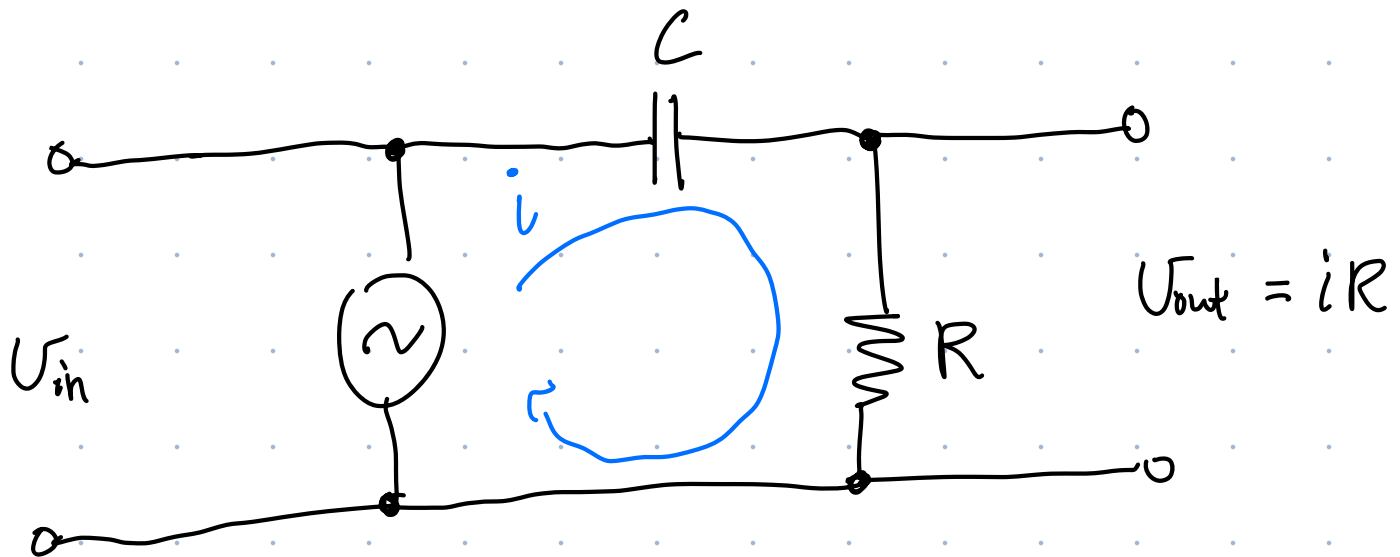Consider an example from electronics.  
RC series circuit.



Write  $V_{in} = V_{in} e^{j\omega t}$        $V_{out} = V_{out} e^{j(\omega t + \phi)}$

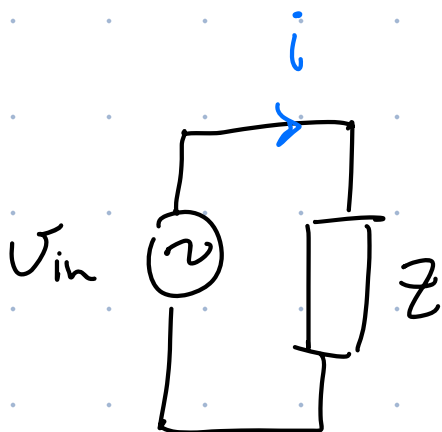To fully determine  $V_{out}$ , need to find the amplitude  $V_{out}$  & phase  $\phi$ .



$$i = \frac{V_{in}}{Z} \quad (1)$$

For our RC circuit

$$Z = \frac{1}{j\omega C} + R$$

$$Z = \frac{1 + j\omega RC}{j\omega C}$$

From (1)  $i = V_{in} \left( \frac{j\omega C}{1 + j\omega RC} \right) \frac{(1 - j\omega RC)}{(1 - j\omega RC)}$

$$= V_{in} \left( \frac{j\omega C + \omega^2 RC^2}{1 + (\omega RC)^2} \right)$$

$$i = \omega C V_{in} \left( \frac{j + \omega RC}{1 + (\omega RC)^2} \right)$$

$$\therefore V_{out} = iR = \omega RC V_{in} \left( \frac{j + \omega RC}{1 + (\omega RC)^2} \right)$$

Recall that

$$V_{in} = V_{in} e^{j\omega t}$$

$$V_{out} = V_{out} e^{j(\omega t + \phi)}$$

$$= V_{out} e^{j\omega t} e^{j\phi}$$

$$V_{out} \cancel{e^{j\omega t}} \underbrace{e^{j\phi}}_{\cos\phi + j\sin\phi \text{ (Euler)}} = V_{in} \cancel{e^{j\omega t}} \frac{\omega RC (j + \omega RC)}{1 + (\omega RC)^2}$$

$$V_{out} (\cos\phi + j\sin\phi) = V_{in} \frac{\omega RC (j + \omega RC)}{1 + (\omega RC)^2}$$

real & imaginary parts on left must equal  
real & imaginary parts on right.

Real:

$$V_{out} \cos\phi = V_{in} \frac{(\omega RC)^2}{1 + (\omega RC)^2} \equiv X$$

Imaginary:

$$V_{out} \sin\phi = V_{in} \frac{\omega RC}{1 + (\omega RC)^2} \equiv Y$$

$X$  is the real component of  $V_{out}$

$Y$  is the imaginary component of  $V_{out}$


Our eventual goal is to see how we can use a lock-in detector to directly meas.  $X$  &  $Y$ .

To find the amplitude of  $V_{out}$ , evaluate  $\sqrt{X^2 + Y^2}$

$$\begin{aligned} V_{out} = \sqrt{X^2 + Y^2} &= \sqrt{\frac{V_{in}^2 (\omega RC)^4}{(1 + (\omega RC)^2)^2} + \frac{V_{in}^2 (\omega RC)^2}{(1 + (\omega RC)^2)^2}} \\ &= \frac{V_{in} \omega RC}{1 + (\omega RC)^2} \sqrt{(\omega RC)^2 + 1} \end{aligned}$$

$$\therefore V_{out} = V_{in} \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

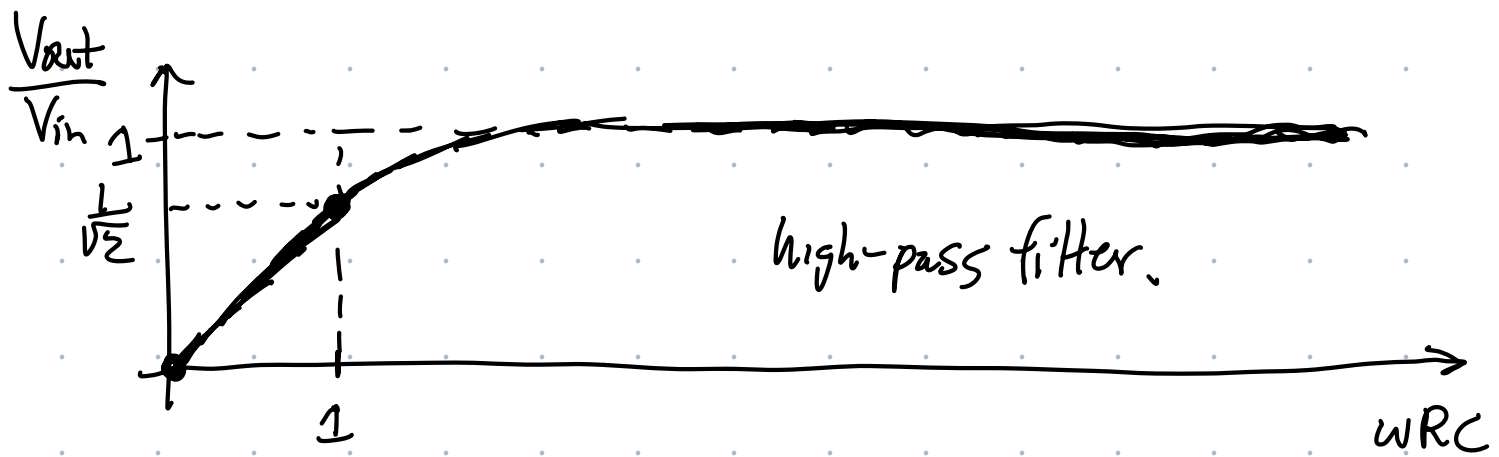Amplitude of  $V_{out}$  in terms of known quantities.







To get the phase, consider  $\frac{Y}{X} = \tan \phi$ .

$$\therefore \tan \phi = \frac{\cancel{V_{in}} \cancel{\omega RC}}{\underbrace{1 + \cancel{(\omega RC)^2}}_Y} \cdot \frac{\cancel{1 + (\omega RC)^2}}{\underbrace{\cancel{V_{in}} (\omega RC)^2}_{\frac{1}{X}}} = \frac{1}{\omega RC}$$

$$\therefore \phi = \tan^{-1} \left( \frac{1}{\omega RC} \right)$$

| $\omega$       | $1/\omega RC$ | $\phi$  |
|----------------|---------------|---------|
| 0              | $\infty$      | $\pi/2$ |
| $\frac{1}{RC}$ | 1             | $\pi/4$ |
| $\infty$       | 0             | 0       |

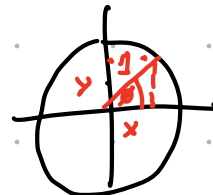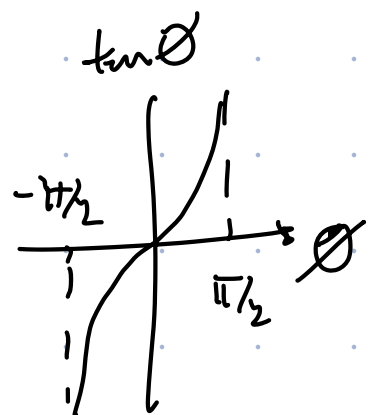


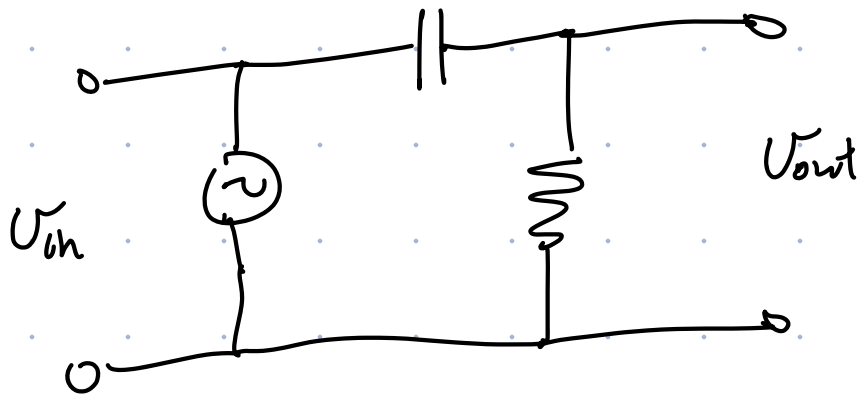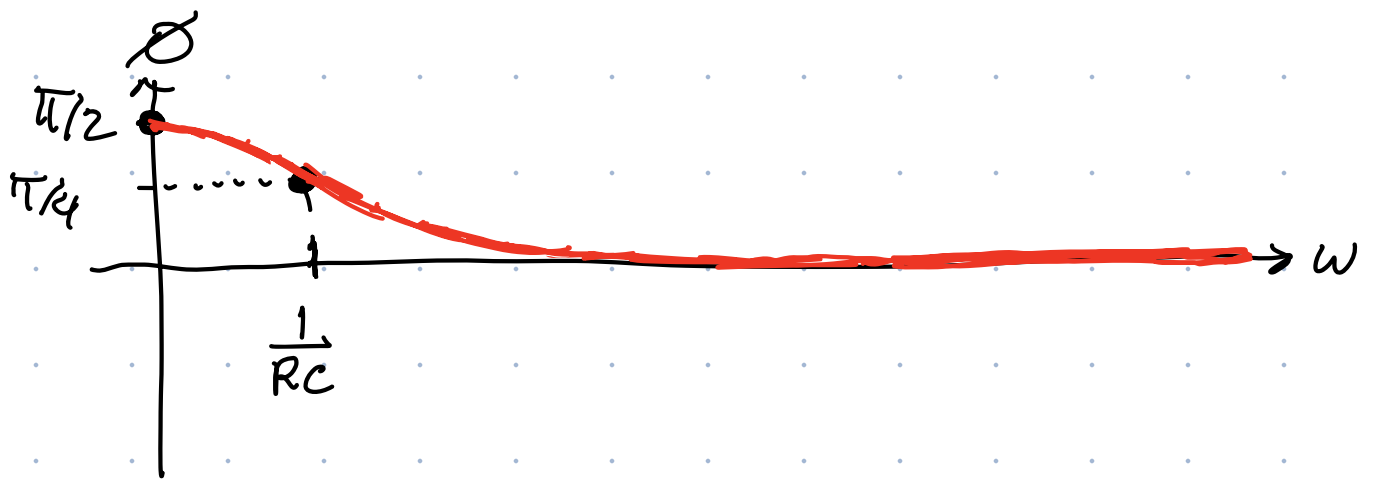

At high freq, no phase ( $\phi = 0$ ) between input and output.

$$Z = \frac{1}{j\omega C} + R$$

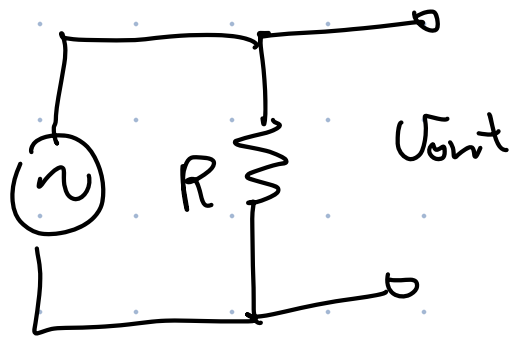At high freq ( $\omega \gg \frac{1}{RC}$ ), the impedance of the cap. vanishes ( $Z_C = \frac{1}{j\omega C}$ ) and the circuit looks like:



At low freq,  $\left( \omega \ll \frac{1}{RC} \right)$  the impedance of the cap. becomes very large  $\left( Z_C = \frac{1}{j\omega C} \right)$  s.t.  $Z_C \gg R$

and  $Z \approx \frac{1}{j\omega C}$

The cap. introduce the phase shift of  $90^\circ$ .

