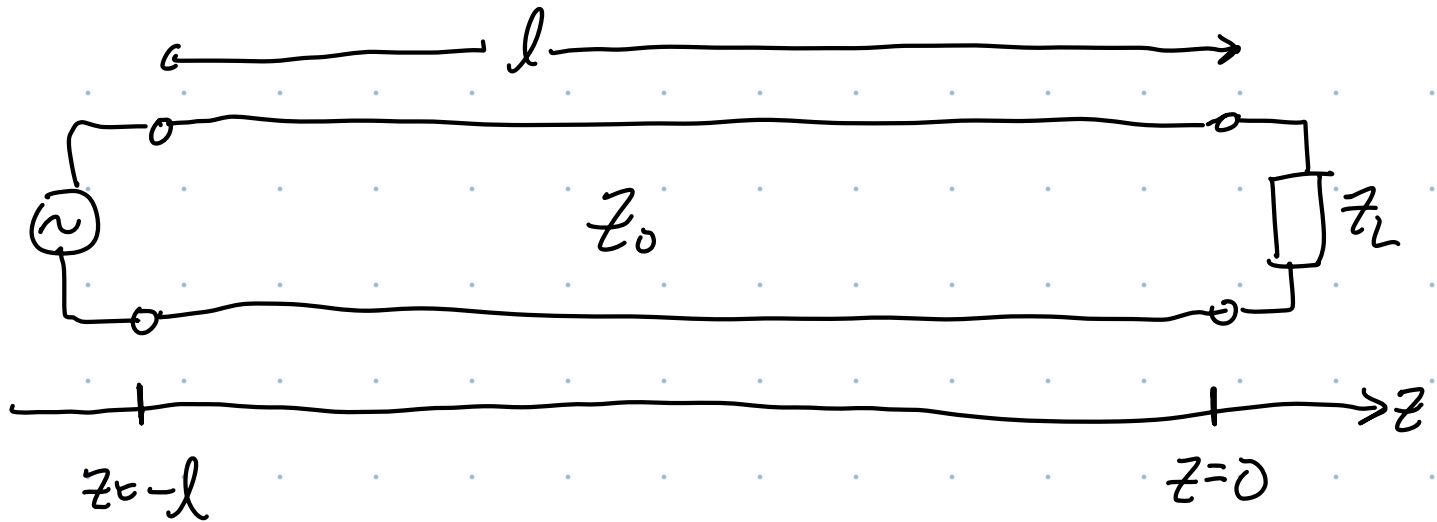


Two weeks ago... Transmission Lines



Summary:

$$V(z, t) = V(z) e^{j\omega t}$$

$$i(z, t) = I(z) e^{j\omega t}$$

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} [V_+ e^{-j\beta z} - V_- e^{j\beta z}]$$

$$\beta = \omega \sqrt{L_0 C_0} = \frac{2\pi}{\lambda}$$

$$S = \frac{1}{\sqrt{L_0 C_0}}$$


$$Z_0 = \sqrt{\frac{L_0}{C_0}}$$

Reflection Coefficient: $\Gamma = \frac{V_-}{V_+} = \frac{Z_L - Z_0}{Z_L + Z_0}$

Today: Special cases of Γ

① $Z_L = 0$ (short circuit)

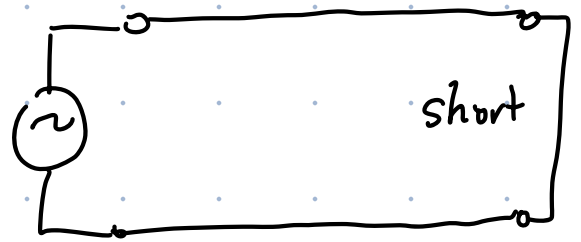
$$\Gamma = \frac{0 - Z_0}{0 + Z_0} = -1$$



reflected wave is inverted.

Corresponds to a perfect 100% reflection

$$|\Gamma| = 1.$$

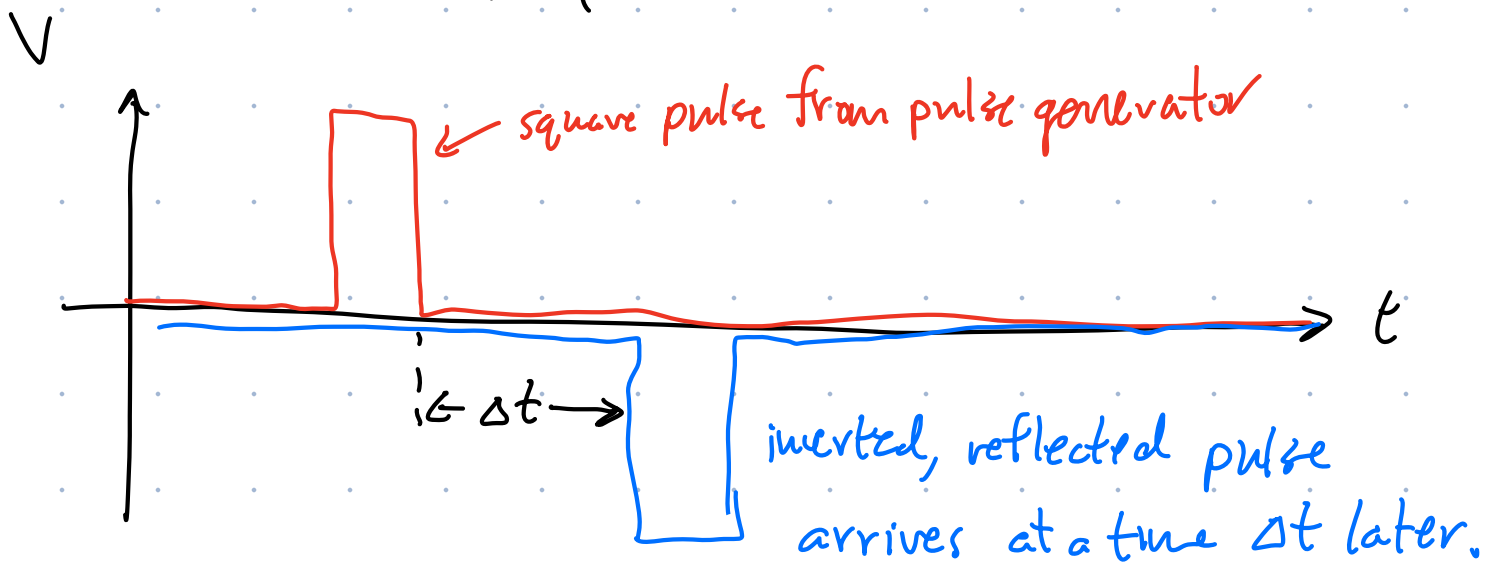


$$\Delta t = \frac{2l}{S}$$

Δt is time for pulse to travel the TL length l , reflect at $Z_L = 0$, and return to input.


② $Z_L \rightarrow \infty$ (open circuit)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad Z_L \gg Z_0$$

$$\approx \frac{Z_L}{Z_L} = +1$$

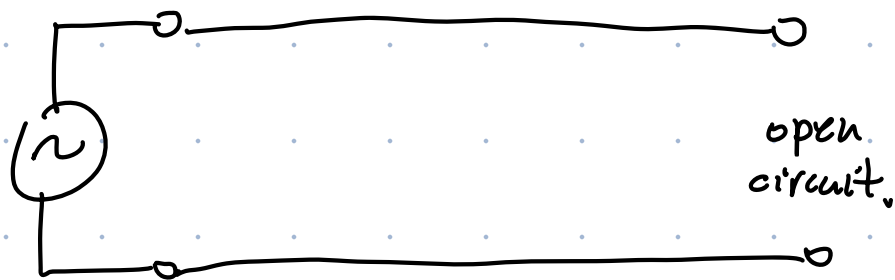

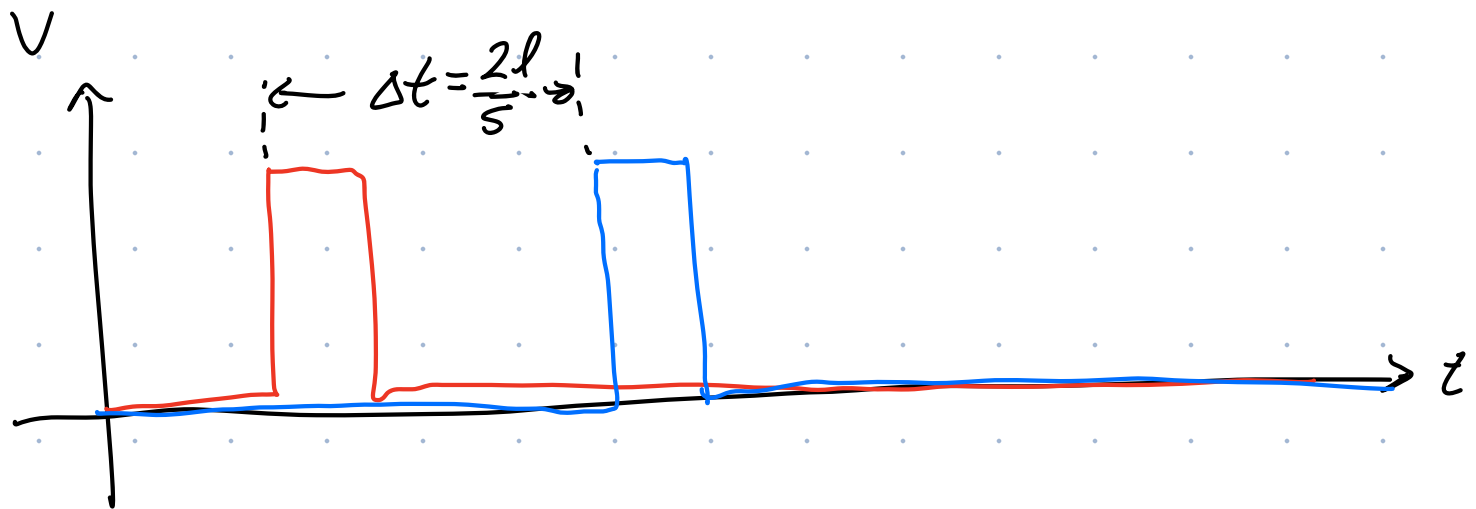Again, get a perfect reflection, but this time w/o an inversion.




③ $Z_L = Z_0$

Set the load impedance Z_L to be equal to the characteristic impedance Z_0 of the TL.



Typically $Z_0 = 50\Omega$ for coaxial cables used in a physics lab.
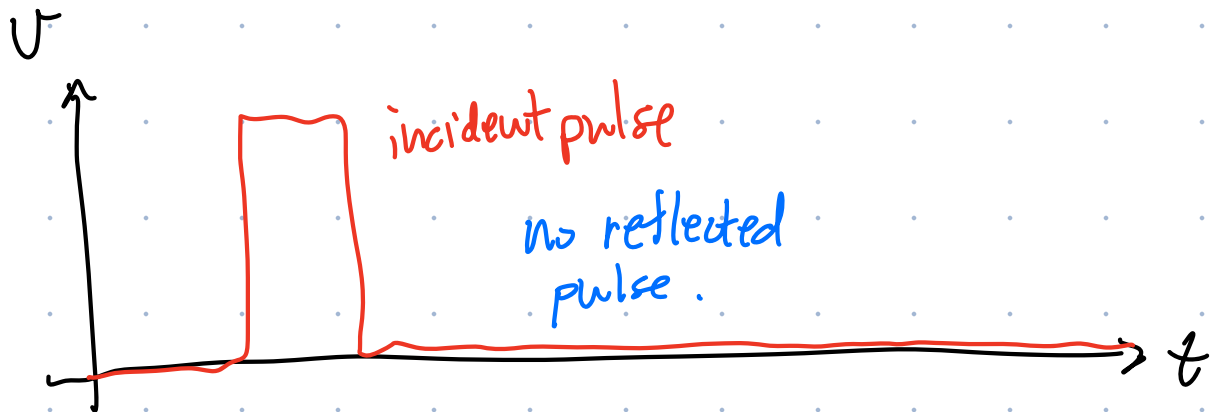
$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0}{2Z_0} = 0 \quad \text{No reflection at all.}$$



This is called impedance matching. We usually desire to achieve $Z_L = Z_0$ to efficiently transfer power from source to some device.

When are TL effects important and when can they be ignored?

$$c = \lambda f \quad \therefore \lambda = \frac{c}{f}$$

take $f = 10 \text{ kHz}$ (typical freq in PHYS 231)

$$\Rightarrow \lambda = \frac{3 \times 10^8 \text{ m/s}}{10 \times 10^3 \text{ /s}} = 3 \times 10^4 \text{ m} = 30 \text{ km!}$$

Here $\lambda \gg$ length of cable.

take $f = 3 \text{ GHz}$ (microwave regime)

$$\lambda = \frac{3 \times 10^8 \text{ m/s}}{3 \times 10^9 \text{ /s}} = 0.1 \text{ m} = 10 \text{ cm}$$

comparable or shorter than typical cable.

We will find that TL effects are important when the wavelength is comparable or shorter than cable lengths.

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z} \quad \text{volt. amp. as a fun of position } z.$$

$$\beta = \frac{2\pi}{\lambda} = \omega \sqrt{L_l C_l}$$

The coaxial cables in the lab are called RG-58 and designed s.t.

$$\left. \begin{array}{l} C_l \approx 80 \text{ pF/m} \\ L_l \approx 0.20 \mu\text{H/m} \end{array} \right\} z_0 = \sqrt{\frac{L_l}{C_l}} \approx 50 \Omega$$

$$\beta = \omega \sqrt{L_l C_l} \quad \text{let's take as a first example}$$

$$\omega = 2\pi (10 \text{ kHz})$$

$$\Rightarrow \beta = 2.5 \times 10^{-4} \text{ m}^{-1}$$

$$\text{If we take } z \approx 1 \text{ m, } \beta z = 2.5 \times 10^{-4} \ll 1$$

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z} = V_+ + V_- = \text{const.}$$

For low freq, our TL voltage (and current) amplitudes are uniform along the TL length.

If, on the other hand, we take $\omega = 2\pi(3\text{GHz})$

$$\beta = \omega \sqrt{LC_0} \approx 75 \text{ m}^{-1}$$

In this case, for $0 < z < 1 \text{ m}$, the product βz is not always small.

Cannot approx $e^{\pm j\beta z}$ as 1.

$$\text{In fact, } e^{\pm j\beta z} = \cos \beta z \pm j \sin \beta z$$

Here, we find that the voltage and current amp. osc. along the length of the TL.

→ Gives rise to all the TL effects.

Impedance at an arbitrary position z along the TL.

$$V(z) = V_+ e^{-j\beta z} + V_- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left[V_+ e^{-j\beta z} - V_- e^{j\beta z} \right]$$

At position z , the impedance is given by:

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_+ e^{-j\beta z} + V_- e^{j\beta z}}{V_+ e^{-j\beta z} - V_- e^{j\beta z}}$$

impedance $\nearrow$
position $\nearrow$

① replace V_- w/ ΓV_+

$$Z(z) = Z_0 \frac{\cancel{V_+} e^{-j\beta z} + \Gamma \cancel{V_+} e^{j\beta z}}{\cancel{V_+} e^{-j\beta z} - \Gamma \cancel{V_+} e^{j\beta z}}$$

② replace $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$Z(z) = Z_0 \frac{e^{-j\beta z} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{j\beta z}}{e^{-j\beta z} - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{j\beta z}} \quad \frac{(Z_L + Z_0)}{(Z_L + Z_0)}$$

③ mult by $1 = \frac{Z_L + Z_0}{Z_L + Z_0}$

$$Z(z) = Z_0 \frac{(\underline{Z_L} + \underline{Z_0}) e^{-j\beta z} + (\underline{Z_L} - \underline{Z_0}) e^{j\beta z}}{(\underline{Z_L} + \underline{Z_0}) e^{-j\beta z} - (\underline{Z_L} - \underline{Z_0}) e^{j\beta z}}$$


④ Collect Z_L , Z_0 factors

$$Z(z) = Z_0 \frac{\overbrace{Z_L \cos \beta z}^{Z_L \cos \beta z} (e^{-j\beta z} + e^{j\beta z}) - \overbrace{Z_0 (e^{j\beta z} - e^{-j\beta z})}^{Z_0 \sin \beta z}}{\underbrace{Z_0 (e^{j\beta z} + e^{-j\beta z})}_{Z_0 \cos \beta z} - \underbrace{Z_L (e^{j\beta z} - e^{-j\beta z})}_{Z_L \sin \beta z}}$$

⑤ mult by $1 = \frac{1}{\cos \beta z}$

$$Z(z) = Z_0 \frac{Z_L - j Z_0 \tan \beta z}{Z_0 - j Z_L \tan \beta z}$$

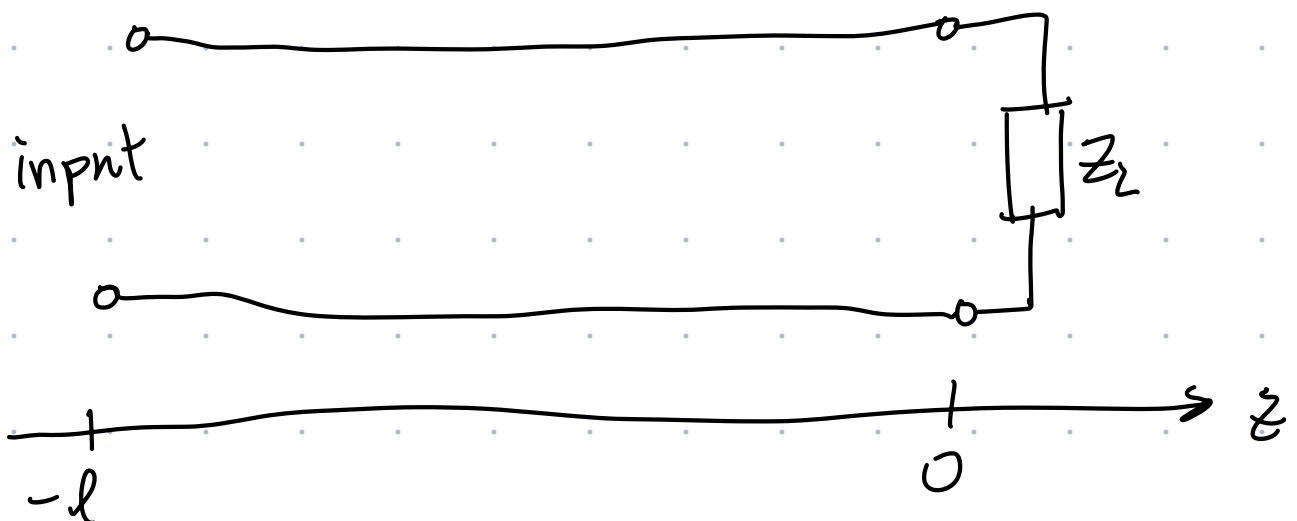Impedance at any position z along the TL terminated by Z_L .



To get the impedance at the TL input, Z_{in} , set $z = -l$ and use $\tan(-x) = -\tan x$

$$Z_{in} \equiv Z(-l) = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

Impedance looking into a TL of length l terminated by impedance Z_L .

Special Cases:

① $\beta l = n\pi$ Select l or ω s.t. we satisfy $\beta l = n\pi$.

$$\frac{\cancel{2\pi}}{\lambda} l = n\cancel{\pi} \Rightarrow l = n \left(\frac{\lambda}{2} \right)$$

Equivalent to setting l to be an integer multiple of half wavelengths.

$$\tan \beta l = \tan(n\pi) = 0$$

$$Z_{in} = \cancel{Z_0} \frac{Z_L}{\cancel{Z_0}} \Rightarrow Z_{in} = Z_L$$

As if the TL is not there. Like we've connected Z_L directly to the source.

② $\beta l = n' \left(\frac{\pi}{2} \right)$ where n' is an odd integer.

$$\frac{2\cancel{\pi}}{\lambda} l = n' \frac{\cancel{\pi}}{2} \Rightarrow l = n' \left(\frac{\lambda}{4} \right)$$

length of TL is an odd
mult. of quarter wavelengths.

$$\tan \beta l = \tan \left(n' \frac{\pi}{2} \right) \rightarrow \pm \infty$$

In this case:

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

$$\approx Z_0 \frac{\cancel{j Z_0 \tan \beta l}}{\cancel{j Z_L \tan \beta l}}$$

$$= \frac{Z_0^2}{Z_L}$$

In effect, we're transforming
impedances from Z_L to
 $\frac{Z_0^2}{Z_L}$.

Eg. If $Z_0 = 50 \Omega$ & $Z_L = 25 \Omega$, then $\frac{Z_0^2}{Z_L} = 1000 \Omega$

transformed from a small Z_L to a larger Z_0^2/Z_L .

③ $Z_L = Z_0$ (impedance matching condition)

$$Z_{in} = Z_0 \frac{\cancel{Z_L} + j \cancel{Z_0} \tan \beta l}{\cancel{Z_0} + j \cancel{Z_L} \tan \beta l}$$

$$\text{If } Z_L = Z_0,$$

$$\text{then } Z_{in} = Z_0$$

Usually desired. Get impedance matching at all freq. $\rightarrow$ Efficient power transfer w/ no reflections.