


Sept. 10, 2025

Transmission Line


Input Impedance Recursion Calculation.

Jake Bobowski

TL Circuit model.

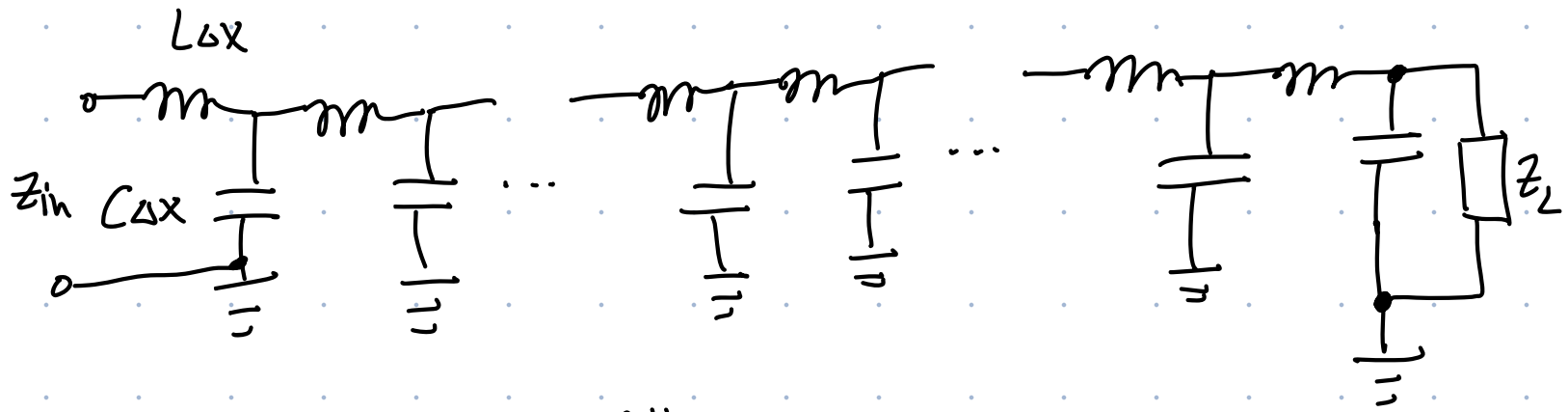

Can redraw in the following way:

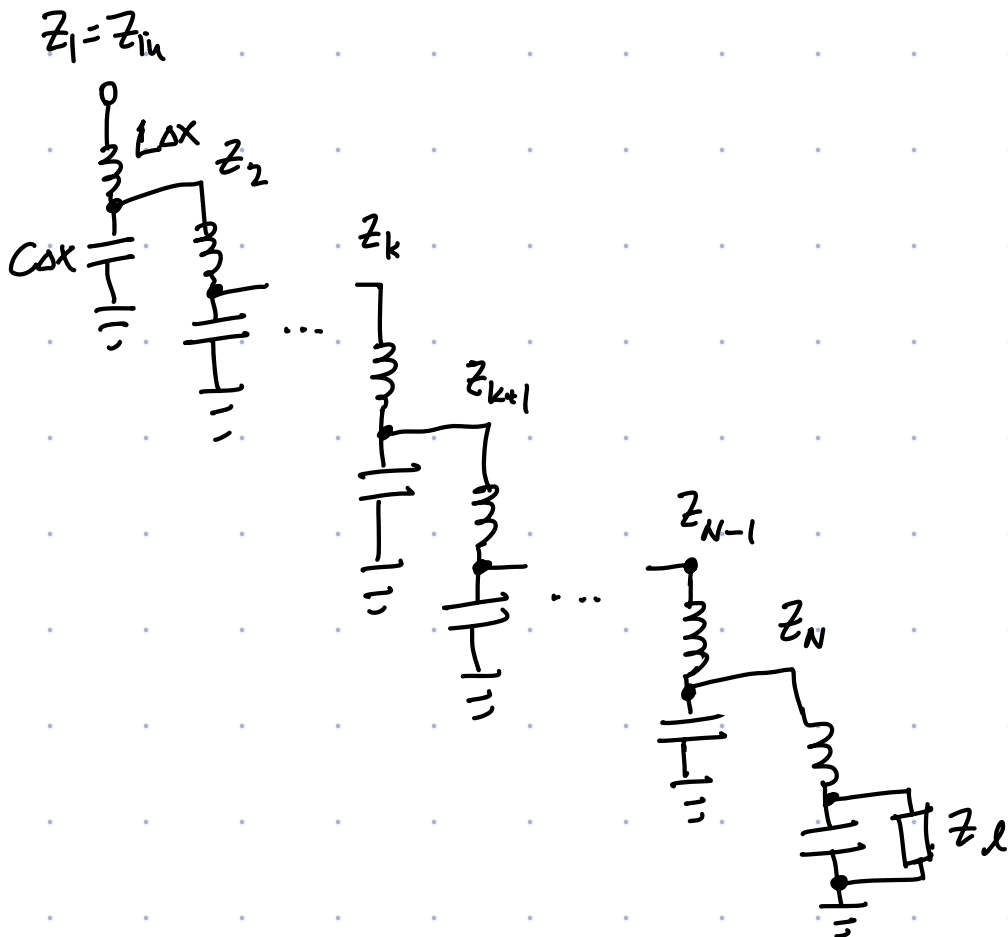

$$Z_N = Z_L + Z_C \parallel Z_L$$

define the load impedance as

$$Z_{N+1} = Z_L$$

$$Z_{N-1} = Z_L + Z_C \parallel Z_N$$

⋮

$$Z_k = Z_L + Z_C \parallel Z_{k+1}$$

Impedance recursion relation.

$$Z_k = j\omega L \Delta x + \left(\frac{\frac{Z_{k+1}}{j\omega C \Delta x}}{\frac{1}{j\omega C \Delta x} + Z_{k+1}} \right)$$

$$\therefore Z_k = j\omega L \Delta x + \frac{Z_{k+1}}{1 + j\omega C \Delta x Z_{k+1}}$$

Note that we can write $Z_k = \frac{V_k}{I_k}$

$$Z_{k+1} = \frac{V_{k+1}}{I_{k+1}}$$

$$\therefore \frac{V_k}{I_k} = j\omega L \Delta x + \frac{V_{k+1}/I_{k+1}}{1 + j\omega C \Delta x \frac{V_{k+1}}{I_{k+1}}}$$

$$= \frac{j\omega L \Delta x \left(1 + j\omega C \Delta x \frac{V_{k+1}}{I_{k+1}} \right) + \frac{V_{k+1}}{I_{k+1}}}{1 + j\omega C \Delta x \frac{V_{k+1}}{I_{k+1}}}$$

$$= \frac{j\omega L \Delta x (I_{k+1} + j\omega C \Delta x V_{k+1}) + V_{k+1}}{I_{k+1} + j\omega C \Delta x V_{k+1}}$$

$$\therefore \frac{V_k}{I_k} = \frac{(1 - \omega^2 LC \Delta x^2) V_{k+1} + j\omega L \Delta x I_{k+1}}{j\omega C \Delta x V_{k+1} + I_{k+1}}$$

We can express this relationship via the following "transfer" matrix:

$$\begin{pmatrix} V_k \\ I_k \end{pmatrix} = \begin{pmatrix} 1 - \omega^2 LC \Delta x^2 & j\omega L \Delta x \\ j\omega C \Delta x & 1 \end{pmatrix} \begin{pmatrix} V_{k+1} \\ I_{k+1} \end{pmatrix}$$

$$\equiv \underline{\underline{T}}$$

$$\begin{pmatrix} V_k \\ I_k \end{pmatrix} = \underline{\underline{T}} \begin{pmatrix} V_{k+1} \\ I_{k+1} \end{pmatrix}$$

The transfer matrix, or its inverse gives us a way to calc the voltage & current amplitudes at each node of the discrete TL.

The strategy is to start at the load where

$$Z_{N+1} = Z_L = \frac{V_L}{I_L}$$

Then, apply T repeatedly in order to work our way back to $Z_{in} = Z_1 = \frac{V_1}{I_1}$.

Need to apply $\underline{\underline{T}}$ N times to go from Z_{N+1} to Z_1 .

$$\therefore \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \underline{\underline{T}}^N \begin{pmatrix} V_L \\ I_L \end{pmatrix}$$

Let's work on $\underline{\underline{T}}^N$

$$\underline{\underline{T}} = \begin{pmatrix} 1 - \omega^2 LC \Delta x^2 & j\omega L \Delta x \\ j\omega C \Delta x & 1 \end{pmatrix}$$

First, in the limit of large N , $\Delta x = \frac{l}{N} \rightarrow 0$.

$\therefore$ we'll neglect Δx^2 .

$$\underline{\underline{T}} \approx \begin{pmatrix} 1 & j\omega L \Delta x \\ j\omega C \Delta x & 1 \end{pmatrix} = \underbrace{\begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}}_{\underline{\underline{I}}} + j\omega \Delta x \underbrace{\begin{pmatrix} 0 & L \\ C & 0 \end{pmatrix}}_{\underline{\underline{A}}}$$

$$\underline{\underline{T}} = \underline{\underline{I}} + j\omega \Delta x \underline{\underline{A}}$$

$$\text{Now, } \underline{\underline{T}}^N = \left(\underline{\underline{I}} + j\omega \Delta x \underline{\underline{A}} \right)^N$$

but, recall, $\Delta x = \frac{l}{N}$ where l is the TL length.

$$\underline{\underline{T}}^N = \left(\underline{\underline{I}} + \frac{j\omega L \underline{\underline{A}}}{N} \right)^N$$

Recall the scalar identity

$$\lim_{N \rightarrow \infty} \left(1 + \frac{x}{N} \right)^N = e^x$$

Can get to this relation via a compound interest calculation $\leadsto$ see Numberphile.

We will apply this identity to our matrix equation w/ $x \rightarrow j\omega L \underline{\underline{A}}$ and $\underline{\underline{A}} = \begin{pmatrix} 0 & L \\ C & 0 \end{pmatrix}$

$$\therefore \underline{\underline{T}}^N = e^{j\omega L \underline{\underline{A}}}$$

To evaluate the exponential of a matrix, we use the series representation of $e^x = 1 + x + \frac{1}{2!}x^2 + \frac{1}{3!}x^3 + \dots$

Before doing so, however, note the following:

$$\underline{\underline{A}}^2 = \begin{pmatrix} 0 & L \\ C & 0 \end{pmatrix} \begin{pmatrix} 0 & L \\ C & 0 \end{pmatrix} = \begin{pmatrix} LC & 0 \\ 0 & LC \end{pmatrix} = LC \underline{\underline{I}}$$

identity matrix

$$\underline{\underline{I}}^N = \underline{\underline{I}} + j\omega l \underline{\underline{A}} + \frac{1}{2!} \underbrace{(j\omega l)^2}_{-(\omega l)^2} \underbrace{\underline{\underline{A}}^2}_{LC \underline{\underline{I}}} + \frac{1}{3!} \underbrace{(j\omega l)^3}_{-j(\omega l)^3} \underbrace{\underline{\underline{A}}^3}_{LCA \underline{\underline{I}}} + \frac{1}{4!} \underbrace{(j\omega l)^4}_{(\omega l)^4} \underbrace{\underline{\underline{A}}^4}_{(LC)^2 \underline{\underline{I}}} + \dots$$

$$= \underline{\underline{I}} \left[1 - \frac{1}{2!} (\omega \sqrt{LC} l)^2 + \frac{1}{4!} (\omega \sqrt{LC} l)^4 - \dots \right]$$

$$j \left(\frac{1}{\sqrt{LC}} \right) \underline{\underline{A}} \left[\omega \sqrt{LC} l - \frac{1}{3!} (\omega \sqrt{LC} l)^3 + \dots \right]$$

$\swarrow \cos \beta l$
 $\nwarrow \sin \beta l$

If we identify $\omega \sqrt{LC} \equiv \beta$, we can write:

$$\underline{\underline{I}}^N = \underline{\underline{I}} \cos \beta l + j \underline{\underline{A}}' \sin \beta l$$

Note that $A' = \frac{1}{\sqrt{LC}} \begin{pmatrix} 0 & L \\ C & 0 \end{pmatrix} = \begin{pmatrix} 0 & \sqrt{\frac{L}{C}} \\ \sqrt{\frac{C}{L}} & 0 \end{pmatrix}$

Now, identify $Z_0 = \sqrt{\frac{L}{C}}$, such that:

$$A' = \begin{pmatrix} 0 & Z_0 \\ Z_0^{-1} & 0 \end{pmatrix}$$

Note that $\beta = \omega \sqrt{LC}$ is the TL prop. constant.

$Z_0 = \sqrt{\frac{L}{C}}$ is the TL's characteristic impedance.

Recall that L and C are the per-unit-length inductance and capacitance respectively.

Finally, we can attempt to calc. Z_{in} .

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \underline{T}^N \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$= \left[\begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} \cos \beta l + j \begin{pmatrix} 0 & Z_0 \\ Z_0^{-1} & 0 \end{pmatrix} \sin \beta l \right] \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$= \begin{pmatrix} V_2 & 0 \\ 0 & I_2 \end{pmatrix} \cos \beta l + j \begin{pmatrix} Z_0 I_2 \\ V_2 / Z_0 \end{pmatrix} \sin \beta l$$

$$\therefore V_1 = V_2 \cos \beta l + j Z_0 I_2 \sin \beta l$$

$$I_1 = I_2 \cos \beta l + j \frac{V_2}{Z_0} \sin \beta l$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{V_2 \cos \beta l + j Z_0 I_2 \sin \beta l}{I_2 \cos \beta l + j \frac{V_2}{Z_0} \sin \beta l}$$

mult. top & btm by $\frac{1}{I_2 \cos \beta l}$

$$Z_{in} = \frac{V_e/I_e + j Z_0 \tan \beta l}{1 + j \frac{V_e/I_e}{Z_0} \tan \beta l}$$

use that $V_e/I_e \equiv Z_L$ and mult. top & btm by Z_0

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

Expected result for the input impedance of a lossless TL of length l .

Let's see if we can determine $V(x)$ & $I(x)$ at any point along a continuous TL.

Start w/

$$\begin{pmatrix} V_k \\ I_k \end{pmatrix} = \underline{T} \begin{pmatrix} V_{k+1} \\ I_{k+1} \end{pmatrix}$$

$\underline{T}$ propagates V & I backwards along the line.

$$\therefore \begin{pmatrix} V_{k+1} \\ I_{k+1} \end{pmatrix} = \underline{\underline{T}}^{-1} \begin{pmatrix} V_k \\ I_k \end{pmatrix} \dots \text{forward propagating}$$

$$\begin{aligned} \underline{\underline{T}}^{-1} &= \left(\underline{\underline{I}} + j\omega \Delta x \underline{\underline{A}} \right)^{-1} \\ &= \begin{pmatrix} 1 & j\omega \Delta x L \\ j\omega \Delta x C & 1 \end{pmatrix}^{-1} \end{aligned}$$

For a 2×2 matrix $\underline{\underline{B}} = \begin{pmatrix} a & b \\ c & d \end{pmatrix}$:

$$\underline{\underline{B}}^{-1} = \frac{1}{\det B} \begin{pmatrix} d & -b \\ -c & a \end{pmatrix} = \frac{1}{ad-bc} \begin{pmatrix} d & -b \\ -c & a \end{pmatrix}$$

$$\therefore \underline{\underline{T}}^{-1} = \frac{1}{1 + \omega^2 \Delta x^2 LC} \begin{pmatrix} 1 & -j\omega \Delta x L \\ -j\omega \Delta x C & 1 \end{pmatrix}$$

ignore Δx^2 term.

$$\therefore \underline{\underline{T}}^{-1} \approx \underline{\underline{I}} - j\omega \Delta x \underline{\underline{A}}$$

$\therefore$ If $x = k \Delta x$ (step k times to a position $x = k \Delta x$) $\Rightarrow \Delta x = \frac{x}{k}$

then

$$\begin{pmatrix} V_k \\ I_k \end{pmatrix} = (\underline{\underline{T}}^{-1})^k \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

$$= \left(\underline{\underline{I}} - j\omega x \frac{\underline{\underline{A}}}{k} \right)^k \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

If we make $\Delta x \rightarrow 0$, then need $k \rightarrow \infty$ steps to get to position x .

$$\therefore \begin{pmatrix} V(x) \\ I(x) \end{pmatrix} = e^{-j\omega x \underline{\underline{A}}} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

Same strategy as before... Write out series expansion of e^x .

$$\text{Recall } \underline{\underline{A}}^2 = LC \underline{\underline{I}}$$

$$\text{and } \beta = \omega \sqrt{LC} \quad Z_0 = \sqrt{\frac{L}{C}}$$

$$e^{-j\omega x \underline{\underline{A}}} = 1 + \underbrace{\left(-j\omega x \underline{\underline{A}}\right)}_{-j\omega x \underline{\underline{A}}} + \frac{1}{2!} \underbrace{\left(-j\omega x \underline{\underline{A}}\right)^2}_{-(\omega x)^2 LC \underline{\underline{I}}}$$

$$+ \frac{1}{3!} \underbrace{\left(-j\omega x \underline{\underline{A}}\right)^3}_{j(\omega x)^3 LC \underline{\underline{A}}} + \frac{1}{4!} \underbrace{\left(-j\omega x \underline{\underline{A}}\right)^4}_{j(\omega x)^4 (LC)^2 \underline{\underline{I}}} + \frac{1}{5!} \underbrace{\left(-j\omega x \underline{\underline{A}}\right)^5}_{-j(\omega x)^5 (LC)^2 \underline{\underline{A}}} + \dots$$

$$\therefore e^{-j\omega x \underline{A}} = \underline{I} \left[1 - \frac{(\beta x)^2}{2!} + \frac{(\beta x)^4}{4!} - \dots \right]$$

$$\underbrace{-j \frac{\underline{A}}{\sqrt{LC}}}_{-j \underline{A}'} \left[\underbrace{\beta x - \frac{(\beta x)^3}{3!} + \frac{(\beta x)^5}{5!} - \dots}_{\sin \beta x} \right]$$

where $\underline{A}' = \begin{pmatrix} 0 & z_0 \\ z_0^{-1} & 0 \end{pmatrix}$

$$\therefore e^{-j\omega x \underline{A}} = \underline{I} \cos \beta x - j \underline{A}' \sin \beta x$$

$$\therefore \begin{pmatrix} V(x) \\ I(x) \end{pmatrix} = \left[\cos \beta x \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} - j \sin \beta x \begin{pmatrix} 0 & z_0 \\ z_0^{-1} & 0 \end{pmatrix} \right] \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

$$\therefore V(x) = V_1 \cos \beta x - j Z_0 I_1 \sin \beta x \quad \textcircled{a}$$


$$I(x) = -j \frac{V_1}{Z_0} \sin \beta x + I_1 \cos \beta x \quad \textcircled{b}$$

This looks different than $V(x) = V_+ e^{-j\beta x} + V_- e^{j\beta x} \quad \textcircled{c}$

$$I(x) = \frac{1}{Z_0} [V_+ e^{-j\beta x} - V_- e^{j\beta x}] \quad \textcircled{d}$$

Let's investigate.

Π geometry:

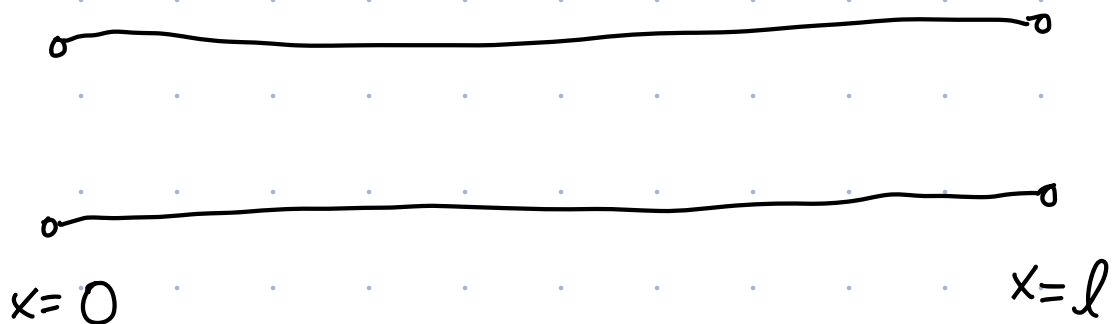

Start by find V_1 & I_1 from $\textcircled{c}$ & $\textcircled{d}$.

$$V_1 = V(0) = V_+ + V_-$$

$$I_1 = I(0) = \frac{1}{Z_0} [V_+ - V_-]$$

$$2V_+ = V_1 + Z_0 I_1$$

$$2V_- = V_1 - Z_0 I_1$$

$$\therefore V_+ = \frac{1}{2} (V_1 + Z_0 I_1)$$

$$V_- = \frac{1}{2} (V_1 - Z_0 I_1)$$

sub into (c) & (d):

$$V(x) = \frac{1}{2} (V_1 + Z_0 I_1) e^{-j\beta x} + \frac{1}{2} (V_1 - Z_0 I_1) e^{j\beta x}$$

$$= \frac{V_1}{2} (e^{-j\beta x} + e^{j\beta x}) + \frac{j Z_0 I_1}{2j} (e^{-j\beta x} - e^{j\beta x})$$

$$= V_1 \cos \beta x - j Z_0 I_1 \sin \beta x \quad \text{same as (a) } \checkmark$$

$$\begin{aligned}
 I(x) &= \frac{1}{Z_0} \left[\frac{1}{2}(V_1 + Z_0 I_1) e^{-j\beta x} - \frac{1}{2}(V_1 - Z_0 I_1) e^{j\beta x} \right] \\
 &= \frac{1}{Z_0} \left[\frac{j V_1}{2j} (e^{-j\beta x} - e^{j\beta x}) + \frac{Z_0 I_0}{2} (e^{-j\beta x} + e^{j\beta x}) \right]
 \end{aligned}$$

$$\therefore I(x) = -j \frac{V_1}{Z_0} \sin \beta x + I_0 \cos \beta x \text{ same as } \textcircled{b} \checkmark$$

The transfer matrix can be used to reproduce the wave equation that we derived in class.

Start from:

$$\begin{pmatrix} V_{k+1} \\ I_{k+1} \end{pmatrix} = \underline{T}^{-1} \begin{pmatrix} V_k \\ I_k \end{pmatrix}$$

and:

$$\underline{T}^{-1} \approx \underline{I} - j\omega \Delta x \underline{A}$$

$$\therefore \begin{pmatrix} V(x+\Delta x) \\ I(x+\Delta x) \end{pmatrix} = \begin{bmatrix} \underline{I} & -j\omega \Delta x \underline{A} \end{bmatrix} \begin{pmatrix} V(x) \\ I(x) \end{pmatrix}$$

$$\therefore \begin{pmatrix} \frac{V(x+\Delta x) - V(x)}{\Delta x} \\ \frac{I(x+\Delta x) - I(x)}{\Delta x} \end{pmatrix} = -j\omega \underline{A} \begin{pmatrix} V(x) \\ I(x) \end{pmatrix}$$

In the limit that $\Delta x \rightarrow 0$

$$\frac{dV}{dx} = -j\omega C I$$

$$\frac{dI}{dx} = -j\omega L V$$

these lead to the familiar wave equations that we saw in class.